

**This homework is due September 26, 2016, at Noon.**

**1. Homework process and study group**

- (a) Who else did you work with on this homework? List names and student ID's. (In case of homework party, you can also just describe the group.)
- (b) How long did you spend working on this homework? How did you approach it?

**2. Ring oscillator**

Figure 1 shows a ring oscillator circuit with three inverters. These inverters are modeled as **non-ideal** op-amps using the general op-amp model we saw earlier in the semester. Remember, **our golden rules don't apply** for the models below. Each op-amp acts as an inverter with gain. The voltage inputs terminals are considered open circuits.  $R_{out} = 10k\Omega$ ,  $C_{o1} = C_{o2} = C_{o3} = 1pF$ , and  $K_1 = K_2 = K_3 = 2$

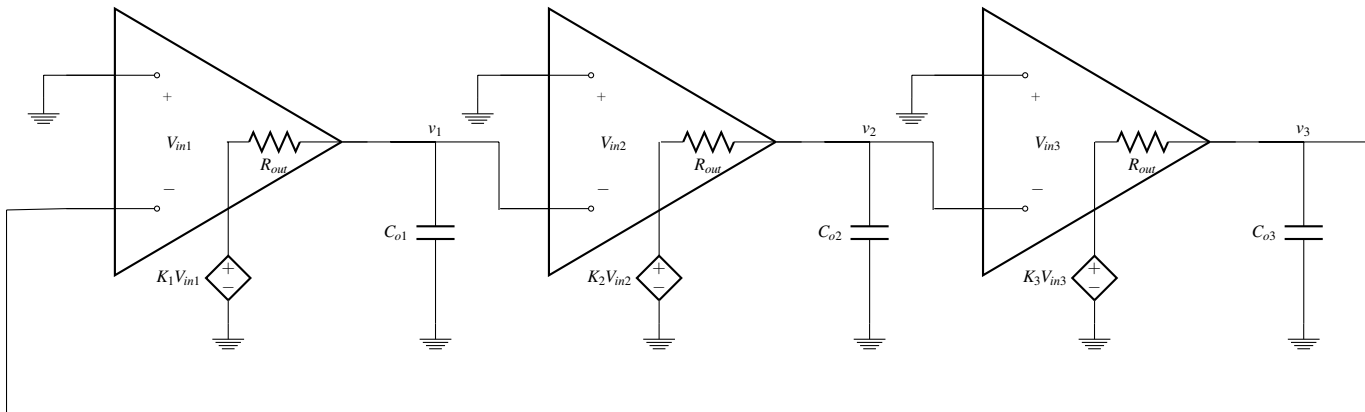


Figure 1: Ring Oscillator Modeled with Non-Ideal Op-Amps

- (a) First, let's look at the first op-amp in the chain. For the circuit in figure 2, find the transfer function for  $\frac{v_1}{v_0}$ .

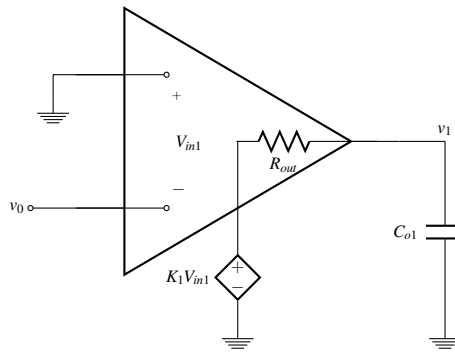


Figure 2: First Op-Amp in Ring Oscillator

- (b) Now, let's look at three of these op-amps cascaded together as seen in figure 3. What is the transfer function for  $\frac{v_3}{v_0}$ ? (Hint: since the input of each op-amp is an open circuit, the overall transfer function can be represented as the individual transfer functions of each amplifier cascaded together.)

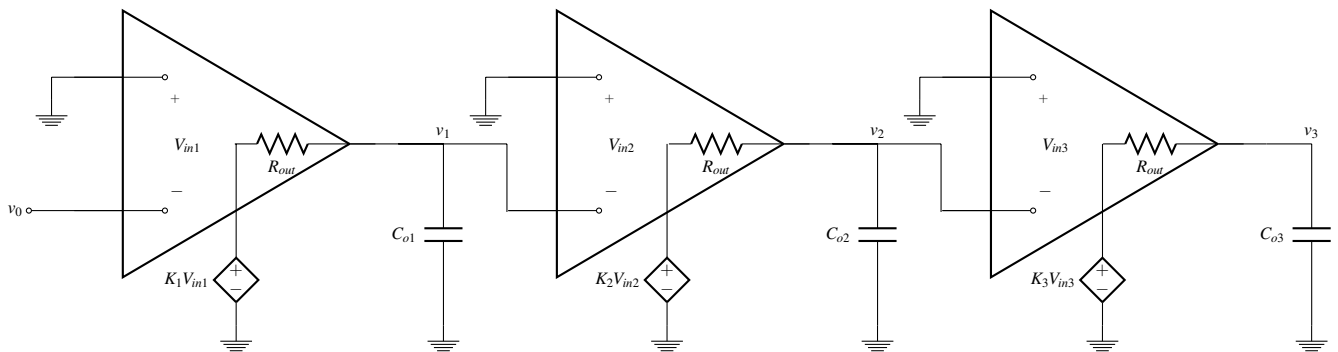


Figure 3: Ring Oscillator without Feedback

- (c) Draw the bode plots for the magnitude and phase of  $\frac{v_3}{v_0}$ .
- (d) At what frequency is the phase of  $\frac{v_3}{v_0}$  equal to  $-\pi$ ? What is the magnitude of  $\frac{v_3}{v_0}$  at that frequency? How does  $v_3$  compare to  $v_0$  at this frequency? An interesting consequence of this result is that this system will have a sustained oscillation when placed in feedback.

### 3. Warm-up: matrix powers

For real numbers, a "power" of that number is computed by recursive multiplication. For example, for a real number  $x$

$$\begin{aligned} x^1 &= x \\ x^2 &= xx^1 = xx \\ x^3 &= xx^2 = xxx \\ &\vdots \end{aligned}$$

Powers of a matrix  $A$  are defined similarly as

$$A^1 = A$$

$$A^{k+1} = AA^k.$$

(a) Compute  $A^2$  and  $A^3$  for the following two matrices

i.

$$A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \end{bmatrix}$$

ii.

$$A = \begin{bmatrix} 1.1 & 1 & 0 \\ 0 & 0.9 & 1 \\ 0 & 0 & 0.8 \end{bmatrix}$$

(b) If  $A$  is diagonalizable as  $A = PDP^{-1}$ , how would you compute a general form for  $A^k$ ?

#### 4. Transistor review

(a) Draw a CMOS circuit (one which employs a pull-up network of PMOS transistors and pull-down network of NMOS transistors) that gives the Boolean formula  $Y = A \oplus B$ . For inputs, you may use  $A$ ,  $B$ ,  $\bar{A}$ , and  $\bar{B}$ .

(b) Write the differential equations of the circuit below in the form  $\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}$ . Model the PMOS as a switch with an on-resistance of  $R_p$  and threshold voltage of  $|V_{th}| = 0.4V$ . The voltage source  $v_p(t)$  behaves as follows:

$$v_p(t) = \begin{cases} 1V & \text{for } t \leq 0 \\ 0V & \text{for } t > 0 \end{cases}$$

(Hint:  $\vec{x}(t)$  should contain  $i_L(t)$  and  $v_C(t)$ .)

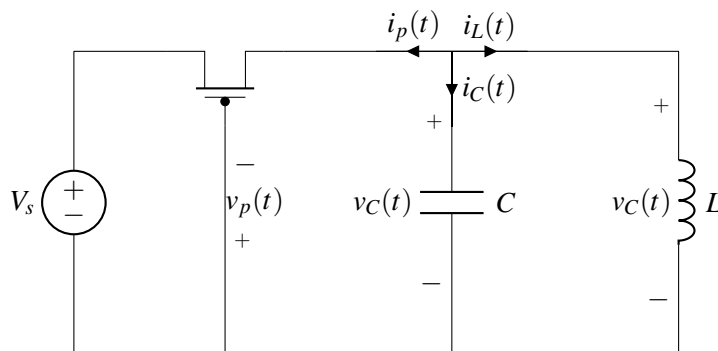


Figure 4: Second-order circuit

#### Contributors:

- Brian Kilberg.
- John Maidens.
- Deborah Soung.