

This homework is due September 5, 2017, at 11:59AM.

1. Fundamental Theorem of Solutions to Differential Equations

In this question, you will discover the power of the fundamental theorem of solutions to differential equations. For convenience, we shall restate the theorem here.

Theorem. Consider a differential equation of the form,

$$\frac{d^n y}{dt^n}(t) + \alpha_{n-1} \frac{d^{n-1} y}{dt^{n-1}}(t) + \dots + \alpha_1 \frac{dy}{dt}(t) + \alpha_0 y(t) = 0$$

Given n initial conditions of the form,

$$y(t_0) = a_0, \frac{dy}{dt}(t_0) = a_1, \dots, \frac{d^{n-1} y}{dt^{n-1}}(t_0) = a_{n-1},$$

there exists a unique solution (say, f).

(a) Consider the following 2 functions.

$$\phi_1(x) = e^x, \phi_2(x) = \sum_{n=0}^{\infty} \frac{x^n}{n!}$$

Prove that $\phi_1(x) = \phi_2(x)$ by showing that both functions satisfy the following differential equation:

$$\frac{df}{dx}(x) = f(x) \text{ with } f(0) = 1$$

Side note: Assume $0^0 = 1$.

(b) Consider the following 2 functions.

$$\phi_1(x) = \cos(x), \phi_2(x) = \cos(-x)$$

Prove that $\phi_1(x) = \phi_2(x)$ by showing that both functions satisfy the following differential equation:


$$\frac{d^2 f}{dx^2}(x) = -f(x) \text{ with } f(0) = 1, \frac{df}{dx}(0) = 0$$

2. Transistors and Boolean Logic

A Boolean formula can be implemented in digital circuitry using nMOS and pMOS transistors. In circuits, the truth value 1 (*true*) is represented by a high voltage, called POWER (V_{DD}). The truth value 0 (*false*) is represented by a low voltage, called GROUND (GND). In this problem, we will only use the truth values in

order to simplify notations. That is, if you see $A = 1$ for a point A , then it means the voltage of A is equal to V_{DD} . Similarly, if $A = 0$, then the voltage of A is equal to GND.

 
An inverter can be implemented with 1 nMOS and 1 pMOS, as shown in the figure below. When the input A is 0, then the nMOS is OFF and the pMOS is ON. Thus, the output Y is pulled up to 1 because it is connected to V_{DD} . Conversely, when A is 1, then the nMOS is ON and the pMOS is OFF, and Y is pulled down to 0. Therefore, the circuit implements the Boolean formula, $Y = \bar{A}$.




In general, a Boolean-formula circuit has an nMOS *pull-down network* to connect the output to 0 (GND) and a pMOS *pull-up network* to connect the output to 1 (V_{DD}). The pull-up and pull-down networks in the inverter example each consist of a single transistor.

In this problem, we will ask you to design pull-up networks when pull-down networks are given.

 
- (a) The pull-down network of the Boolean formula (a 2-input NAND gate), $Y = \overline{(A * B)}$, is given below. Design the pull-up network (the dashed box) with 2 pMOS transistors.



 
- (b) The pull-down network of the Boolean formula (a 2-input NOR gate), $Y = \overline{(A + B)}$, is given below. Design the pull-up network (the dashed box) with 2 pMOS transistors.



 - (c) The pull-down network of the Boolean formula, $Y = \overline{(A * B) + C}$, is given below. Design the pull-up network (the dashed box) with 3 pMOS transistors.



 
- (d) The pull-down network of the Boolean formula, $Y = \overline{(A + B) * C}$, is given below. Design the pull-up network (the dashed box) with 3 pMOS transistors.



(e) You have designed four pull-up networks. What can you conclude about the rules for designing pull-up networks when pull-down networks are given?

 (f) For the circuit below, write the truth table for inputs A and B with output Y. What boolean operation is this?

Note some of the gate voltages are \bar{A} and \bar{B}



3. RC Circuit

Consider the circuit below, assume that when $t \leq 0$, the capacitor has no charge stored ($V_c(t = 0) = 0$). At $t = 0$, the switch closes. Assume $V_s = 15 \text{ V}$, $R = 500\Omega$, and $C = 100\mu\text{F}$.

 



Figure 1: RC Circuit with Voltage Source

- What are the boundary conditions for $I_c(t)$ (i.e. what is $I_c(t = 0)$ and $I_c(t \rightarrow \infty)$)?
- Use KVL and the relationship between charge and current ($q = \int I dt$) to find the first order differential equation in terms of the current through the capacitor, I_c . Assume $\frac{dV_s}{dt} = 0$ (Hint: you will need to take a derivative with respect to time to get the equation)
- What is the eigenvalue λ of this equation?
- Using the eigenvalue and boundary conditions found in previous parts, find an expression for $I_c(t)$ in terms of V_s , R and C
- What order of magnitude of time (nanoseconds, milliseconds, 10's of seconds, etc.) does this circuit settle (I_c is $<5\%$ of it's initial value)?
- Give 2 ways to reduce the settling time of the circuit if we are allowed to change one component in the circuit.
- Sketch the current vs time plot of $I_c(t)$ Make sure to label $I_c(t)$ at $t = 0$, $t = \tau$, $t = 2\tau$, and $t = 3\tau$

 4. From Transistors to Inverter

The following circuit is an inverter built with one pMOS and one nMOS transistor. We assume V_{out} is connected to the input of another identical inverter (not shown). We also assume there is a capacitance connected between V_{out} and GND. In real transistors, this capacitance arises from a combination of capacitances contributed by the transistors of both the inverter in question and any inverters connected to the output. For the moment, we'll just call this capacitance C_L (for load). The resistances associated with the pMOS and nMOS are R_{onP} and R_{onN} , respectively. Let the threshold voltage of the pMOS be V_{tp} , while that for the nMOS be V_{tn} . We will now model the action of the inverter as an RC circuit with two switches controlled by V_{in} as what we did in lectures.


- For starters, what are the on-off conditions of the two switches? Please draw the RC circuit modeling this inverter.



- (b) Assume $V_{in} = V_{DD}$ for $t < 0$, and $V_{in} = 0$ for $t \geq 0$. In other words, we are assuming the input to our inverter can switch states infinitely fast (this is not true in real life, but gives us a good lower bound on how fast an inverter can switch). How much energy does it take to fully charge C_L ?
- (c) Given the same condition as in (b), write down the differential equation that describes $V_{out}(t)$ for $t \geq 0$.
- (d) What is the solution to this differential equation? Plot $V_{out}(t)$ for $t > 0$.
- (e) The term *propagation delay* is used to describe the amount of time it takes between when the input reaches $\frac{V_{DD}}{2}$ and when the output reaches $\frac{V_{DD}}{2}$. Calculate the propagation delay for our inverter above (keep in mind that the input to our inverter changes instantly). Is propagation delay a function of V_{DD} ?
- (f) Now consider a serial chain of inverters, each driving the one before it. If we assume that $|V_{in}| = |V_{tp}| = \frac{V_{DD}}{2}$ what is the propagation delay for one of these inverters, given (d) and (e)? (If you like, ignore the first inverter and assume it is driven by an input as in (a)). Here we let $R_{onP} = R_{onN} = R$.
- (g) Now let's consider the following scenario: there are N inverters on the chip in your cell phone. It takes E Joules of energy to charge all of the inverters at once (from zero to V_{DD}). What is the value of C_L ?
- (h) Here we interpret a voltage V as logic "1" when $V > \frac{V_{DD}}{2}$, and logic "0" when $V < \frac{V_{DD}}{2}$. Let's assume the maximum frequency, f , at which an inverter can switch back and forth between logic "0" and logic "1" at the output is the inverse of the propagation delay (i.e. we can only switch as fast as one propagation delay). Find an expression that links f , C_L , and R .

 5. Digital-analog converter

A digital-analog converter (DAC) is a circuit for converting a digital representation of a number (binary) into a corresponding analog voltage. In this problem, we will consider a DAC made out of resistors only (resistive DAC) called the R-2R ladder. Here is the circuit for a 3-bit resistive DAC.



Let $b_0, b_1, b_2 = \{0, 1\}$ (that is, either 1 or 0), and let the voltage sources $V_0 = b_0 V_{DD}$, $V_1 = b_1 V_{DD}$, $V_2 = b_2 V_{DD}$, where V_{DD} is the supply voltage.

As you may have noticed, (b_2, b_1, b_0) represents a 3-bit binary (unsigned) number where each of b_i is a binary bit. We will now analyze how this converter functions.

- (a) If $b_2, b_1, b_0 = 0, 0, 1$, what is V_{out} ? Express your answer in terms of V_{DD} .
- (b) If $b_2, b_1, b_0 = 0, 1, 0$, what is V_{out} ? Express your answer in terms of V_{DD} .
- (c) If $b_2, b_1, b_0 = 1, 1, 1$, what is V_{out} ? Express your answer in terms of V_{DD} .
- (d) If $b_2, b_1, b_0 = 1, 0, 0$, what is V_{out} ? Express your answer in terms of V_{DD} .
- (e) Finally, solve for V_{out} in terms of V_{DD} and the binary bits b_2, b_1, b_0 .
- (f) Explain how your results above show that the resistive DAC converts the 3-bit binary number (b_2, b_1, b_0) to the output analog voltage V_{out} .

Contributors:

- Siddharth Iyer.
- Yen-Sheng Ho.
- Kyle Tanghe.
- Yu-Yun Dai.
- Edward Wang.