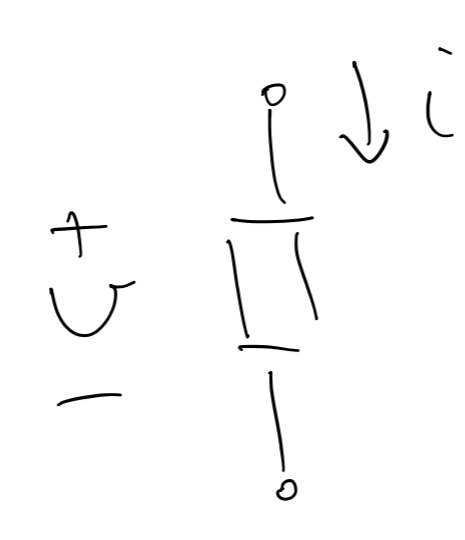



Element




$i = \text{Amps}$   
 $U = \text{Volts}$

$U \cdot i = \text{power into element}$



Resistor

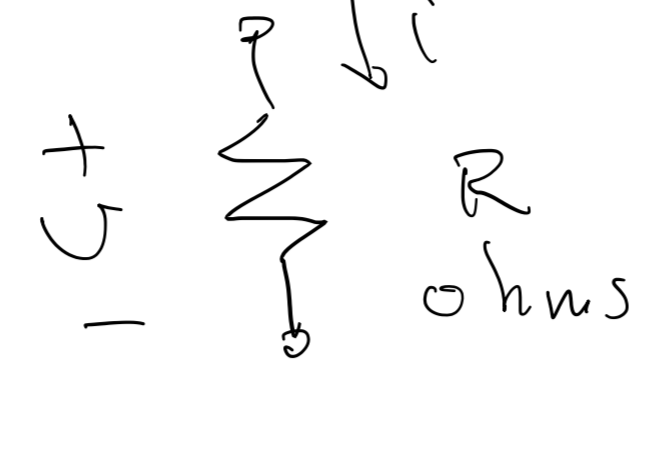


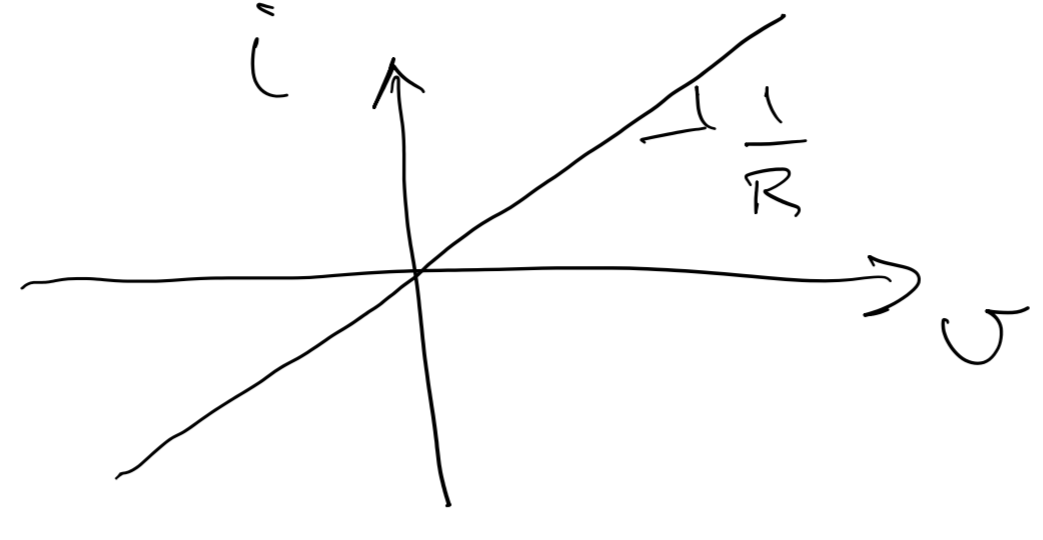
$U = Ri$   
 $i = \frac{1}{R} U = \frac{GV}{\text{ohms}}$







Volt. Source

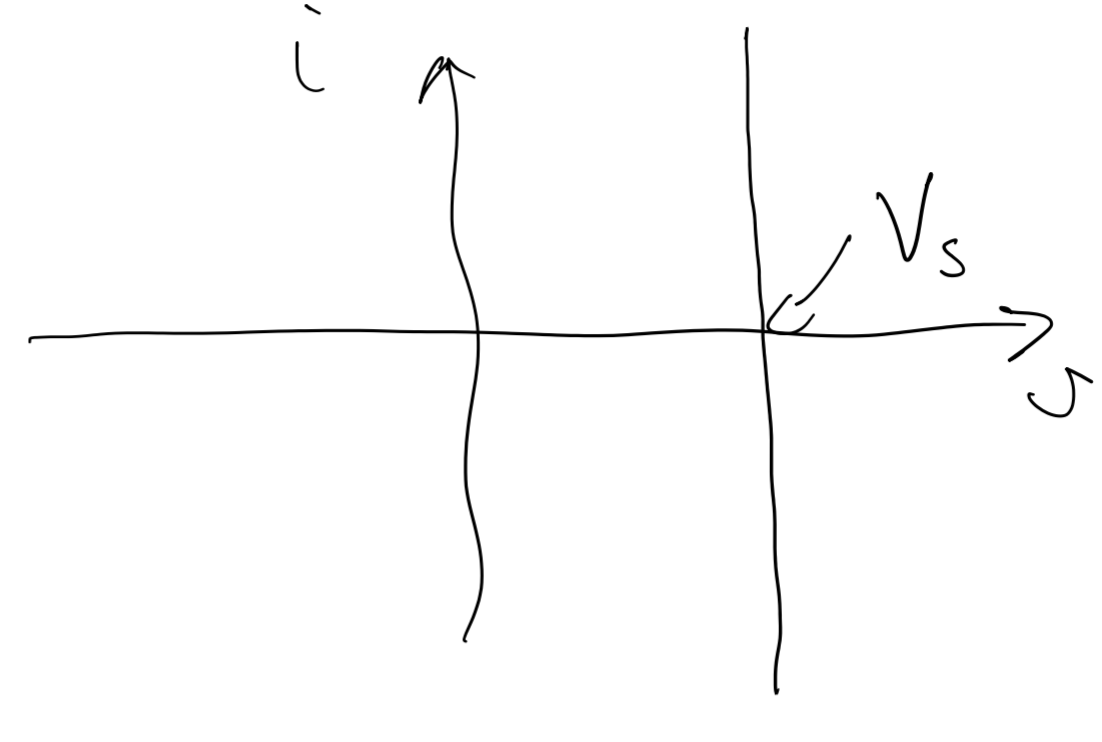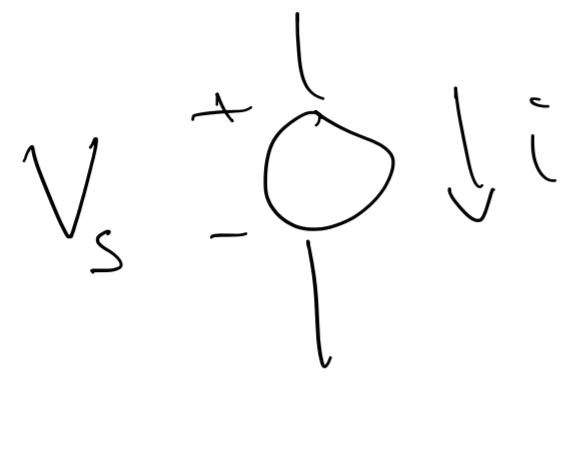

Current Source

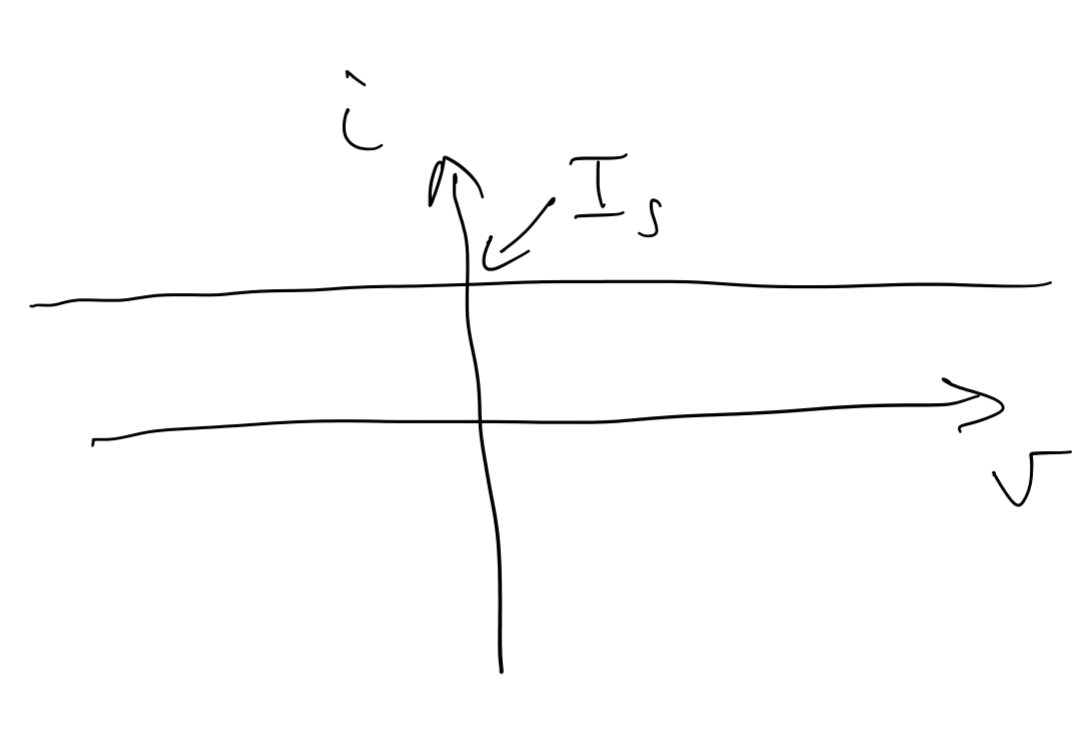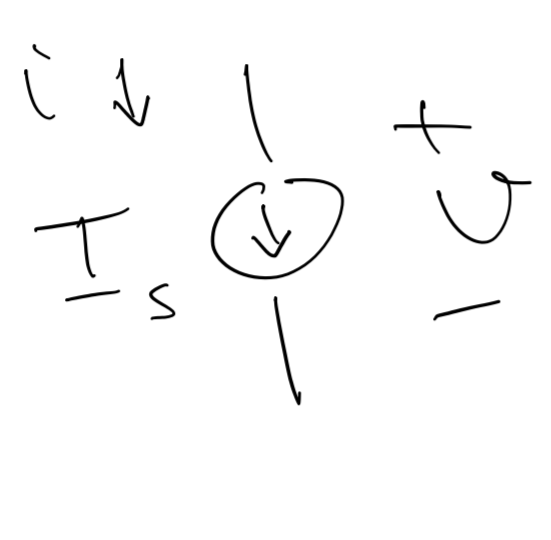

Parallel R's

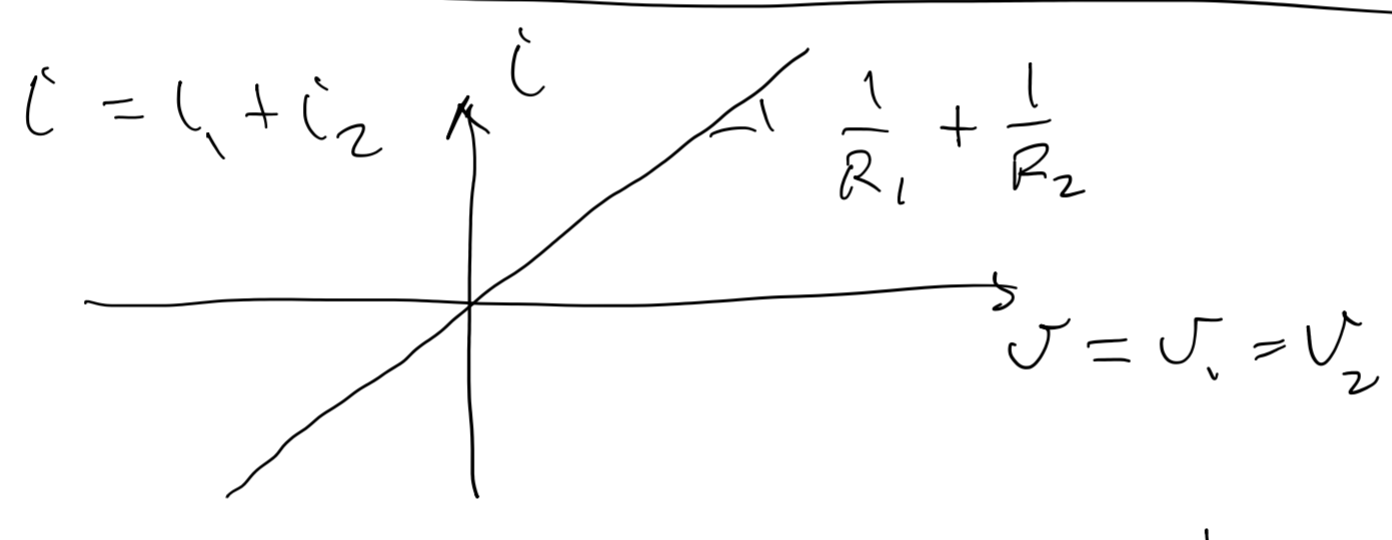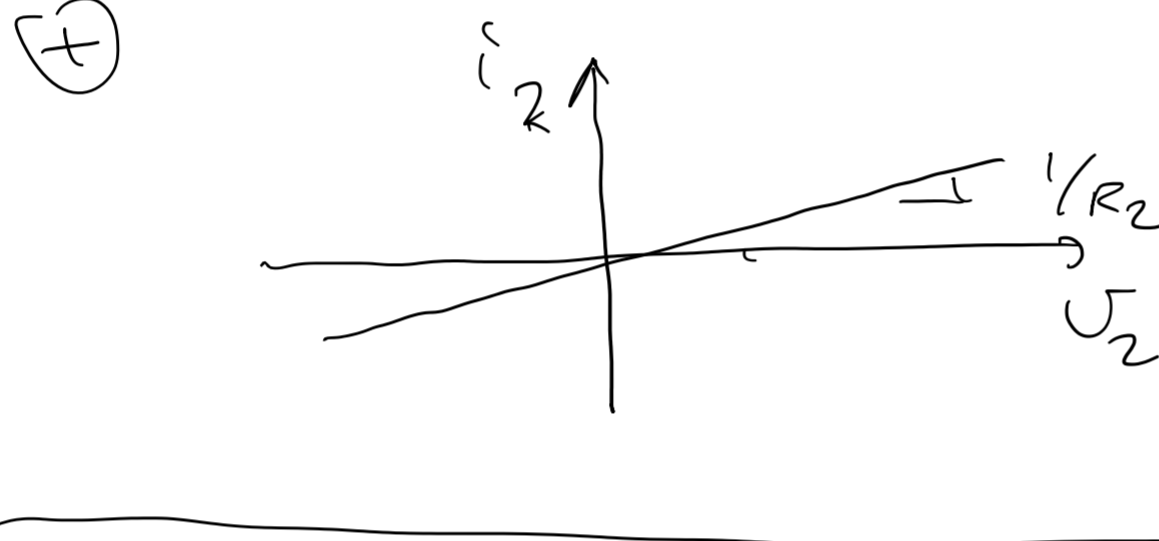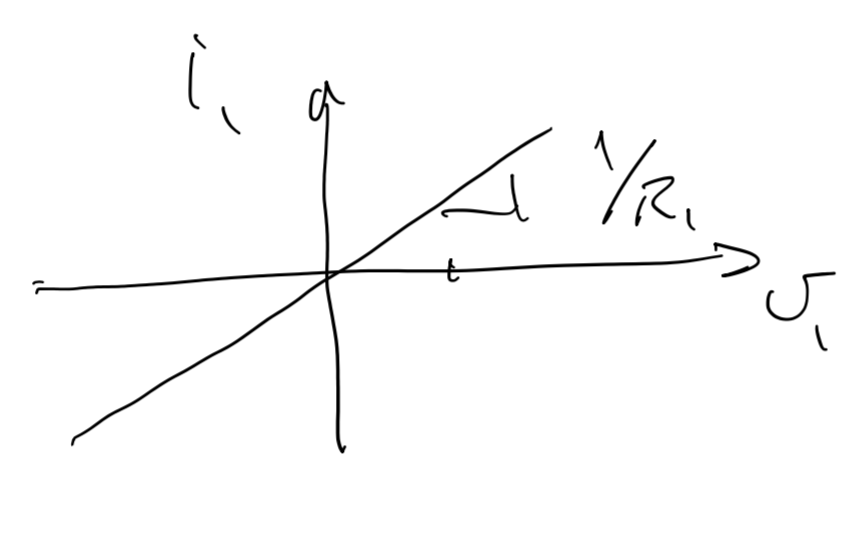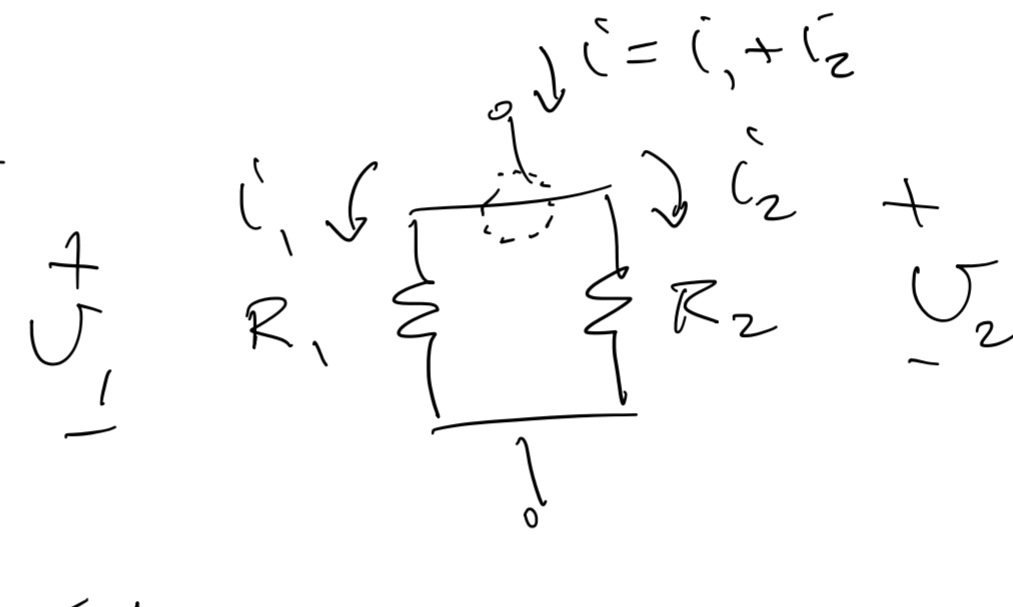


$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

Ckt Analysis

- KVL
- KCL

Nodal Analysis

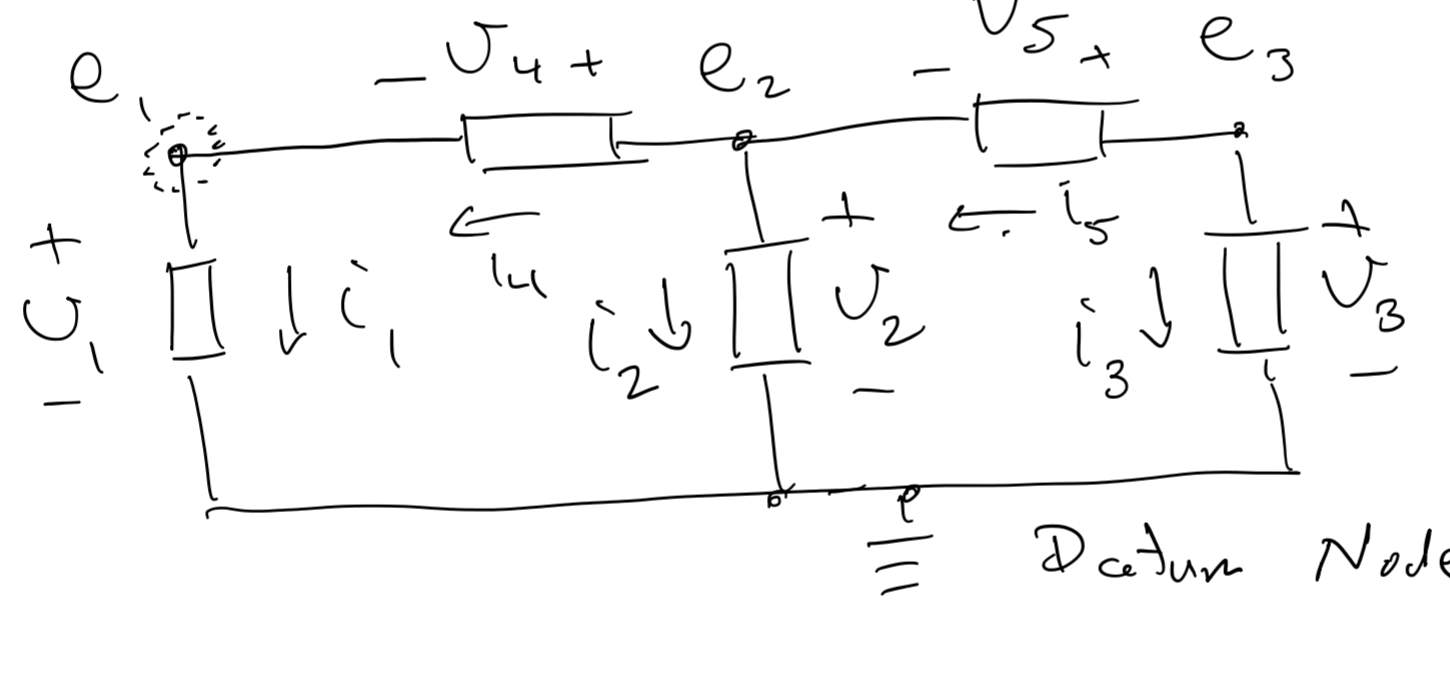

• If we know  $e_1, e_2, e_3 \Rightarrow$  know all branch voltages  
 $U_4 = e_2 - e_1$

• Would like to bring in KCL constraints to help solve. With nodal analysis, bring in constitutive relations to expedite form of node eqns.

Nodes

- ①  $i_1 - i_4 = 0$
- ②  $i_2 + i_4 - i_5 = 0$
- ③  $i_3 + i_5 = 0$





How to analyze?

1) Already know this is a voltage divider


$U_o = \frac{R_2}{R_1 + R_2} V_s$

2) Thevenin/Norton Eq. Ckts

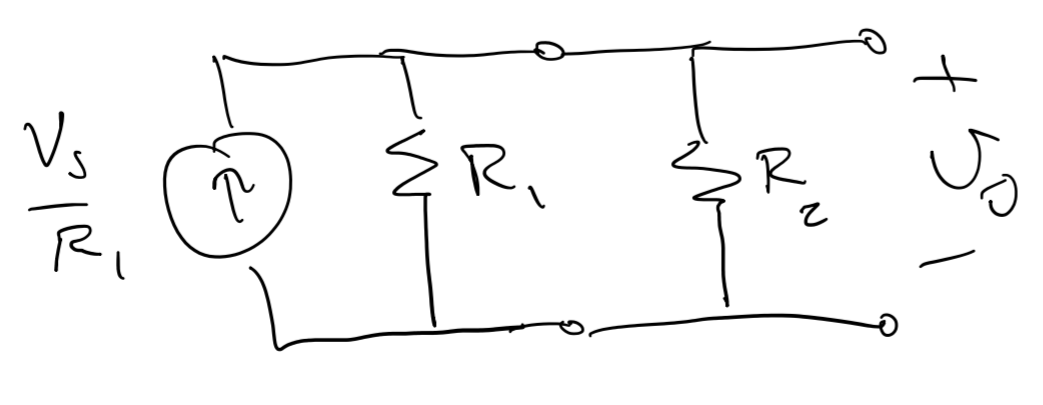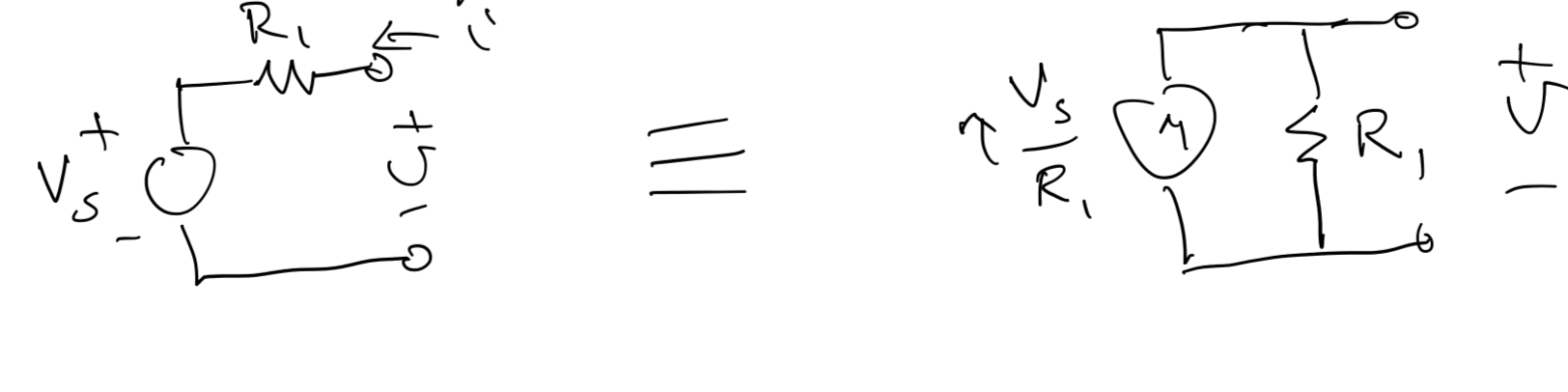

$U_o = \frac{V_s}{R_1} \cdot \frac{R_1 R_2}{R_1 + R_2} = V_s \frac{R_2}{R_1 + R_2}$

③ Node Analysis

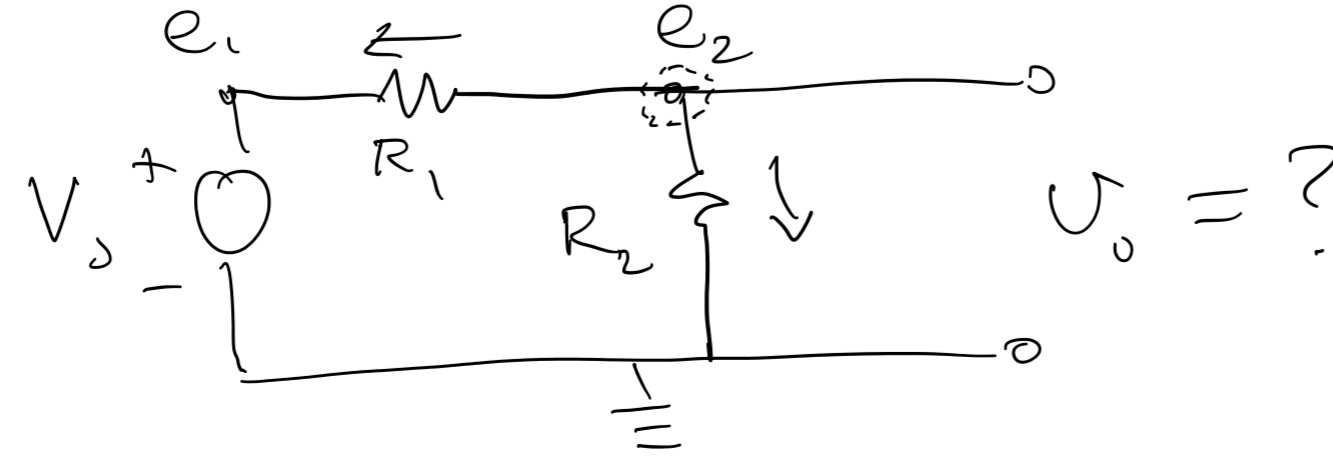

cheat: know  $e_1 = V_s$

Node ②:  $\frac{e_2}{R_2} + \frac{e_2 - V_s}{R_1} = 0$

solve  $\Rightarrow e_2 = U_o$