

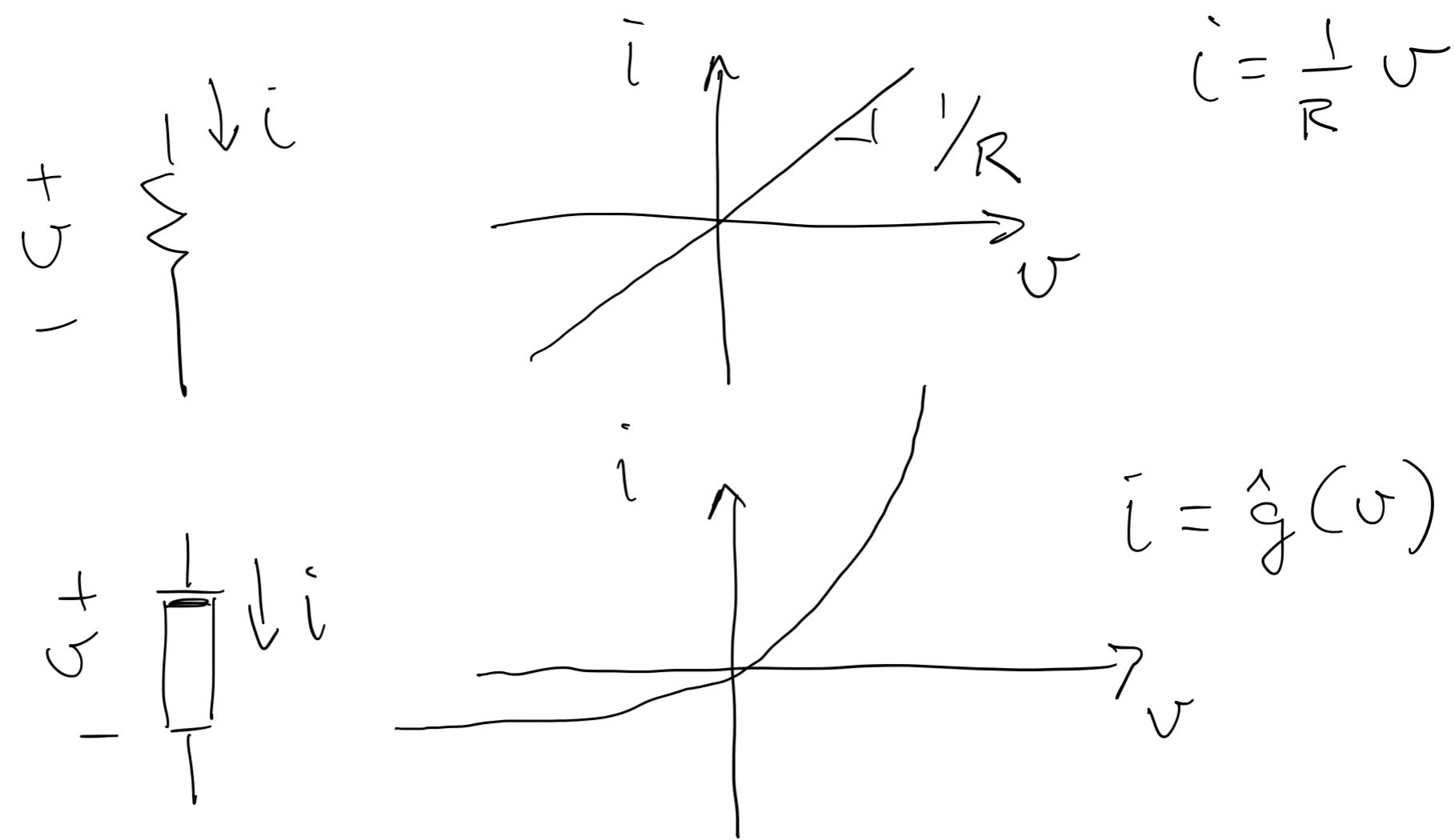


MOSFET = Metal Oxide Semiconductor Field Effect Transistor

• New device: transistor

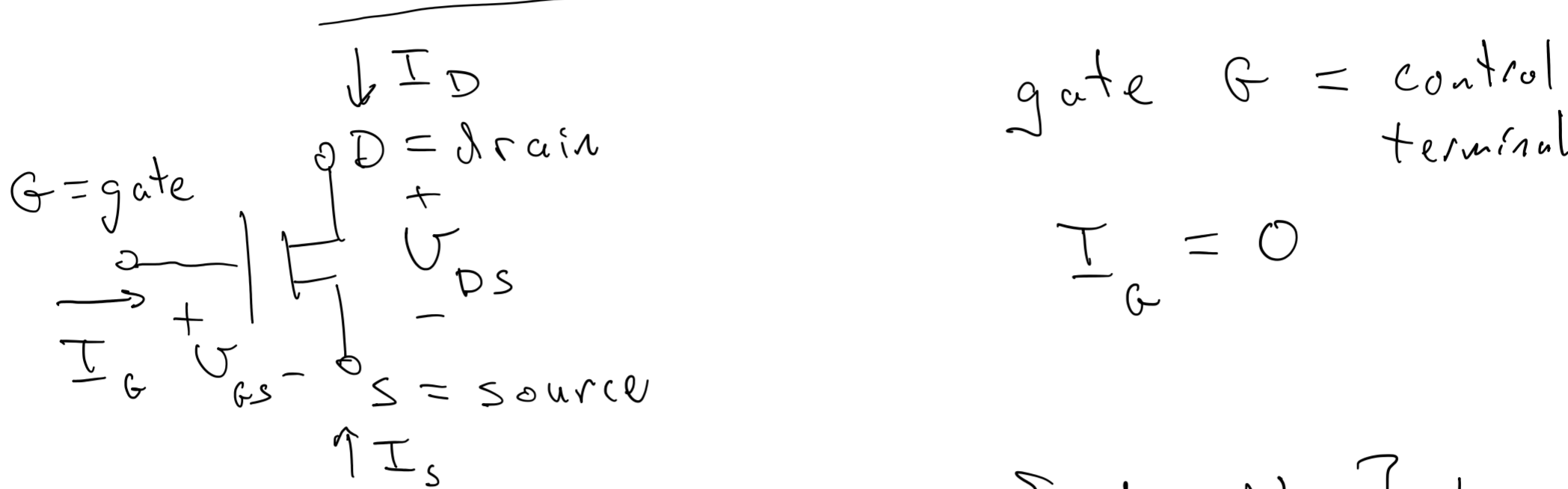

MOSFET

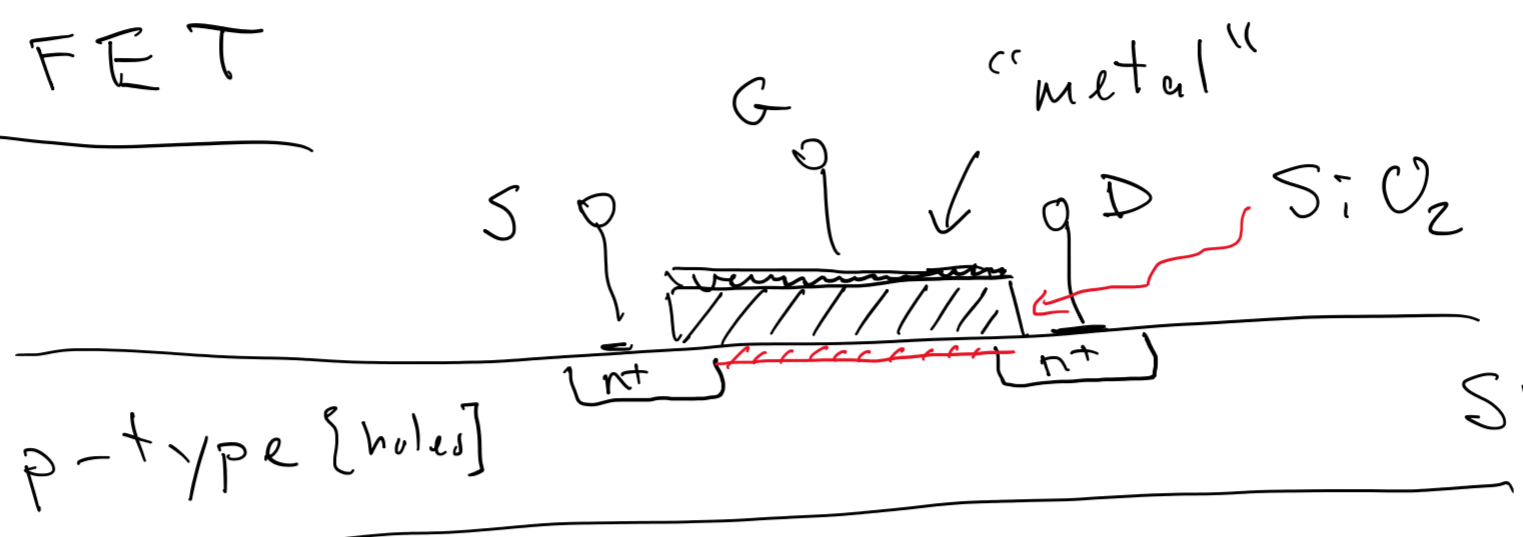

* I think these 2 voltages $[V_{DS}, V_{GS}]$ to characterize all branch voltages.

$$V_{DC} = V_{DS} - V_{GS} \quad \{KVL\}$$


* How many terminal currents to char. behavior?

typically we use I_D and $I_G = 0$

[If we labeled I_S , would have $I_S + I_D + I_G = 0$ {KCL}]

$$I_G = 0 \Rightarrow I_S = -I_D$$

* Variables:

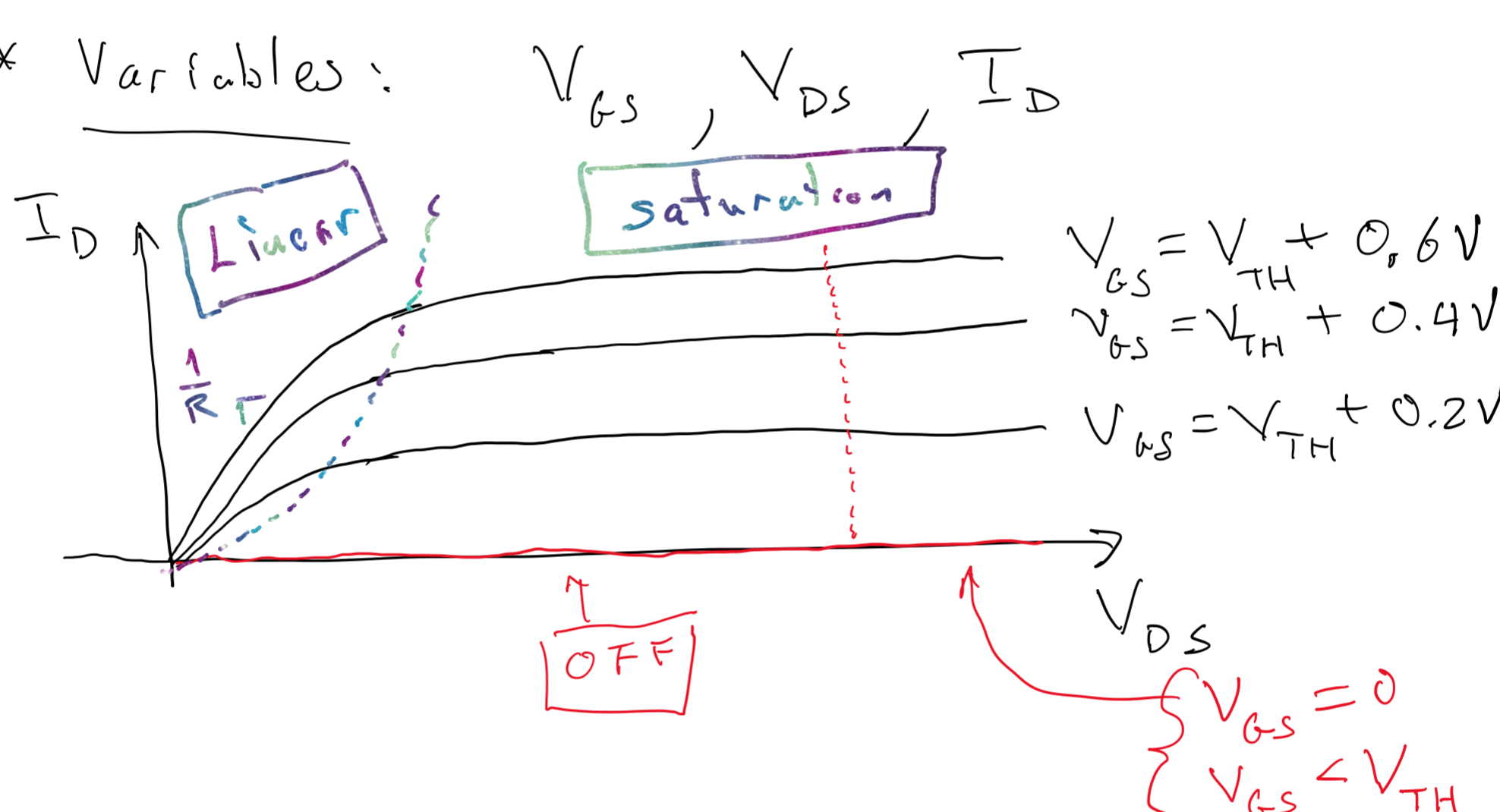

MOSFET: multiple regions of operation

- (0) OFF $V_{GS} < V_{TH}$
- (1) ON in "linear region" near origin $V_{GS} > V_{TH}; V_{DS}$ small
- (2) ON in "saturation" $V_{GS} > V_{TH}, V_{DS}$ somewhat larger

Behaviors

- (0) OFF is OFF
- (1) linear \leftrightarrow ON state of switch but with resistance
- (2) saturation $V_{DS} > 0$ constant
 nice "analog" function; more V_{GS} gives more I_D
 \Rightarrow like voltage-controlled current source

V_{TH} = Threshold Voltage, $\approx 0.2 - 0.3$ V

$$V_{GS} < V_{TH} \Rightarrow \text{OFF}$$

$V_{GS} > V_{TH} \Rightarrow$ ON \rightarrow linear; low V_{DS}
 \rightarrow saturation; more V_{DS}

[EE 130 - other electr. classes to become fluent]

First MOSFET called NMOS
 \uparrow electrons conducting carriers

Second MOSFET called PMOS
 \uparrow holes [absence of an electron] conducting carriers

n & p material reversed:

