 


You are given the following circuit:



Which of the following statements are true? [Note: Positive power dissipation indicates that the element is dissipating power while negative power dissipation indicates that the element is generating power.]

1. The power dissipated by all elements must sum to 0.
2. According to Ohm's law, the power dissipated by the resistors must be non-negative.
3. The power dissipated by the voltage source must be less than 0.

[courses.berkeley.edu/courses/1491216/quizzes/2307332/take?preview=1](https://courses.berkeley.edu/courses/1491216/quizzes/2307332/take?preview=1)

Quiz: Final A

4. The power dissipated by the current source  $P_I$  may be found by shorting the voltage source, finding  $V_I$ , and then calculating  $P_I = V_I I_s$ .

- 1 and 2 only.
- 1, 2, and 3 only.
- 1, 2, 3, and 4.
- 2, 3, and 4 only.
- 1, 3, and 4 only.

# SP2020 FINAL A QUESTION 10

1. "The power dissipated by all elements must sum to 0."

→ Law of Conservation of Energy - energy

can neither be created nor destroyed

\*\* if power dissipated  $> 0$ , it implies energy was destroyed

\*\* if power dissipated  $< 0$ , it implies energy was created

2. Power dissipated by resistors must be nonnegative.

$$\rightarrow P = VI = (IR)I = I^2R$$

$I^2$  is always positive,  $R$  is always positive

$\therefore P$  dissipated by resistor is always positive

3. Power dissipated by the voltage source must be less than 0.

→  $P = VI$  ... just need one of  $V_s$  or  $I_s$  to be negative in this case

→ It's okay for voltage source to dissipate

rate power... there is a current source to compensate by generating

4. The power dissipated by current source may be found by shorting the voltage source, finding  $V_I$ , and calculating  $P_I = V_I I_S$ .

→ **Superposition** doesn't work like that!  
Need to also remove current source and do circuit analysis to find final  $V_I$  value.






# SP2020 FINAL B QUESTION 8

- goal: advantage of CMOS inverter over NMOS in context of power consumption and output voltage


\* assume transistors don't have internal resistance or capacitance

→ draw it out for better intuition

when M2 is open ( $V_{in} \leq V_{th}$ )

 

CMOS inverter

 


NMOS inverter

$V_o = V_{DD}$   
 $P = \frac{V_{DD}^2}{R_2} = \frac{V^2}{R}$


→ voltage divider  
 $V_o = \left( \frac{R_2}{R_2 + R_p} \right) V_{DD}$   
 $P = \frac{V_{DD}^2}{(R_2 + R_p)} = \frac{V^2}{R}$

\* we can surely conclude the maximum output voltage of CMOS is higher than that of NMOS

when M2 is closed ( $V_{in} > V_{th}$ )

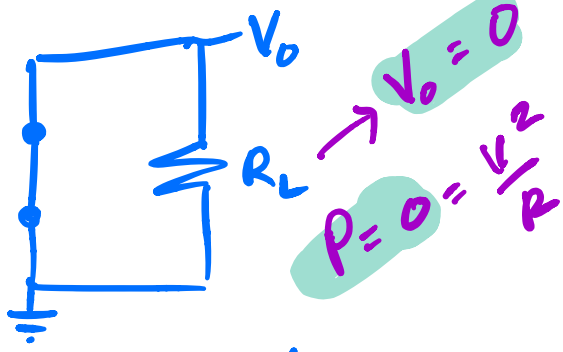

CMOS inverter

 


NMOS inverter

\* if M2 stays closed (no switching), power consumption of CMOS is lower than that of NMOS

\*\* ILLUSTRATED BOTH CASES PROVING ONLY II AND III

# FA2019 MIDTERM 1 QUESTION 3

(exam on TBP site)

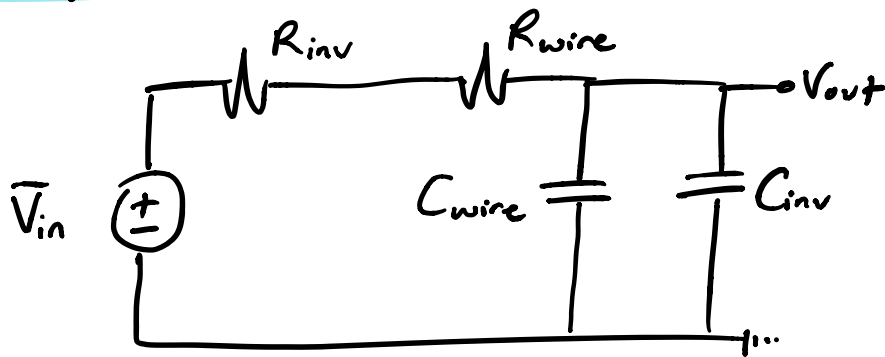


(a) since  $\bar{V}_{in} = 0V$  for all  $t < 0$ , at  $t = 0$ , ckt is in steady state


\*\* mathematically:  $\frac{d}{dt} V_{C_{wire}} = 0$ ;  $\frac{d}{dt} V_{C_{inv}} = 0$

$$I_{C_{wire}}(t) = C_{wire} \frac{d}{dt} V_{C_{wire}}(t) = 0 @ t=0$$
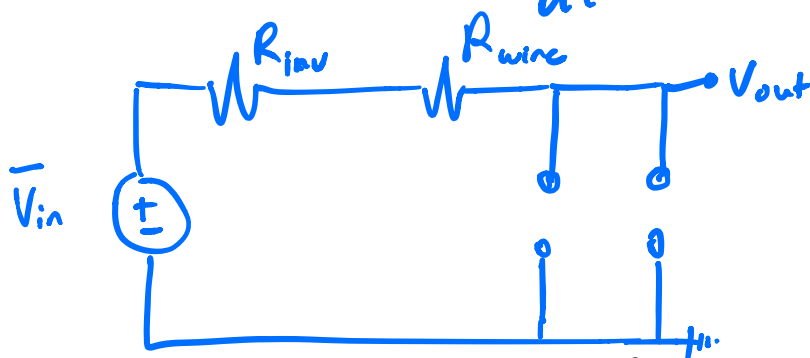
$$I_{C_{inv}}(t) = C_{inv} \frac{d}{dt} V_{C_{inv}}(t) = 0 @ t=0$$



 → no current  
 $\therefore V_{out} = \bar{V}_{in} = 0$   
 @  $t = 0$



$$Q = CV; \frac{d}{dt} Q(t) = C \frac{d}{dt} V(t) = I$$

$$I_{C_{wire}} = C_{wire} \frac{d}{dt} V_{C_{wire}}(t) = C_{wire} \frac{d}{dt} V_{out}(t) \quad I_{C_{inv}} = C_{inv} \frac{d}{dt} V_{C_{inv}}(t) = C_{inv} \frac{d}{dt} V_{out}(t)$$

$$V_{out}(t) = \bar{V}_{in}(t) - (R_{inv} + R_{wire}) (I_{C_{wire}} + I_{C_{inv}}) \\ = \bar{V}_{in}(t) - (R_{inv} + R_{wire}) \left( \frac{d}{dt} V_{out}(t) \right) (C_{wire} + C_{inv})$$

$$\frac{d}{dt} V_{out}(t) = \frac{\bar{V}_{in}(t) - V_{out}(t)}{(R_{inv} + R_{wire})(C_{wire} + C_{inv})}$$

$$(c) \quad \tilde{V}(t) = \bar{V}_{in}(t) - V_{out}(t) \quad ; \quad \frac{d}{dt} \tilde{V}(t) = - \frac{d}{dt} V_{out}(t)$$

$$\frac{d}{dt} \tilde{V}(t) = \frac{-\tilde{V}(t)}{(R_{inv} + R_{wire})(C_{wire} + C_{inv})} \quad \lambda = 10^{-7} \quad \tau = 10^7$$

$$\lambda = (R_{inv} + R_{wire})(C_{wire} + C_{inv}) \quad ; \quad \tau = \frac{1}{\lambda}$$


$$\frac{d}{dt} \tilde{V}(t) = -\tau \tilde{V}(t) \rightarrow \tilde{V}(t) = A e^{-\tau t}$$

$$\frac{d}{dt} \tilde{V}(t) = -\tau (A e^{-\tau t}) = -\tau \tilde{V}(t)$$

$$\tilde{V}(0) = A e^{-\tau(0)} = A = \bar{V}_{in}(0) - V_{out}(0) = 1 \text{ V} \quad \rightarrow \text{Given} \quad \rightarrow \text{part a}$$

$$\tilde{V}(t) = e^{-10^7 t} \rightarrow \bar{V}_{in}(t) - V_{out}(t) = e^{-10^7 t}$$

$$V_{out}(t) = 1 - e^{-10^7 t}$$

 


$$V_{out}(t)_{t \rightarrow \infty} = 1 - e^{-\infty} = 1$$

$$V_{out}(t) \Big|_{t=RC} = 1 - e^{-10^7(10^{-7})}$$
$$= 1 - e^{-10^0} = 1 - e^{-1}$$

You are given the inverter circuit shown below. You would like to reduce the power supplied by the power supply by a factor of 2.

 You are given that  $C_L = 1 \text{ pF}$ ,  $f_s = 1 \text{ GHz}$  (the clock rate),  $R_{on,p} = R_{on,n} = 10\Omega$ , and  $V_{dd} = 1 \text{ V}$ . You are only allowed to adjust the circuit as described below. Which of the following could you do?



- 
- Add another PMOS transistor in series with M1 and another NMOS transistor in series with M2.
- 

es.berkeley.edu/courses/1491216/quizzes/2309167/take?preview=1

Quiz: Final B

- None of the other choices.
- 
- Double  $C_L$ .
- 
- Double  $V_{dd}$ .
- 
- Add another PMOS transistor in parallel with M1 and another NMOS transistor in parallel with M2.



# SP 2020 FINAL B QUESTION 9

• goal: reduce power supplied by a factor of 2  $\rightarrow P = VI$

$\rightarrow$  so either reduce voltage or current  
 \* we can surely eliminate "Double  $V_{DD}$ "

$\rightarrow$  draw it out for better intuition

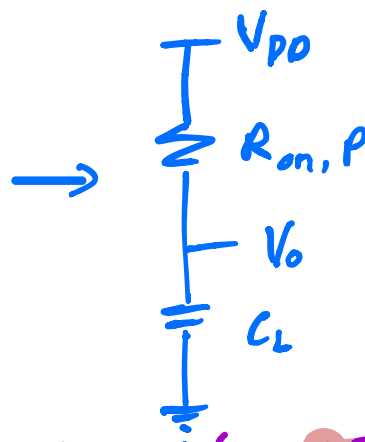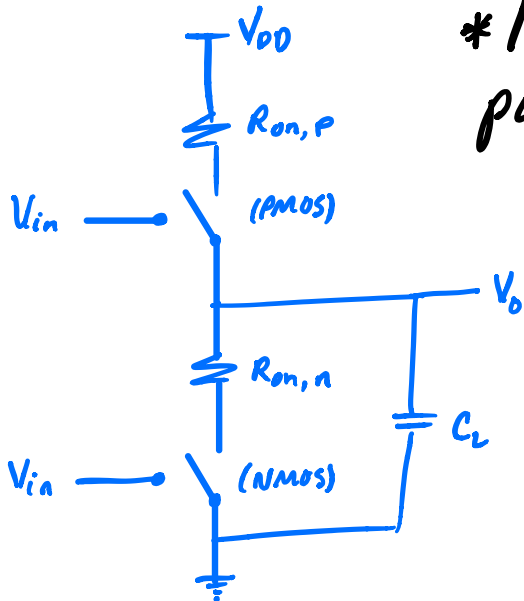\* look at circuit from POV that power is being supplied



$$I = C_L \frac{d}{dt} V_o(t)$$

$$= (V_{DD} - V_o) / R_{on,p}$$



$$P = VI = V_{DD} C_L \frac{d}{dt} V_o(t)$$

\* we can surely eliminate "Double  $C_L$ "  
 pattern for voltage of a charging capacitor when input voltage is 1V in an RC circuit (based on Fall 2019 MT1):

$$V_c(t) = 1 - e^{-t/RC}$$

$$P = V_{DD} I = \frac{V_{DD} (V_{DD} - V_c)}{R_{on,p}} =$$
 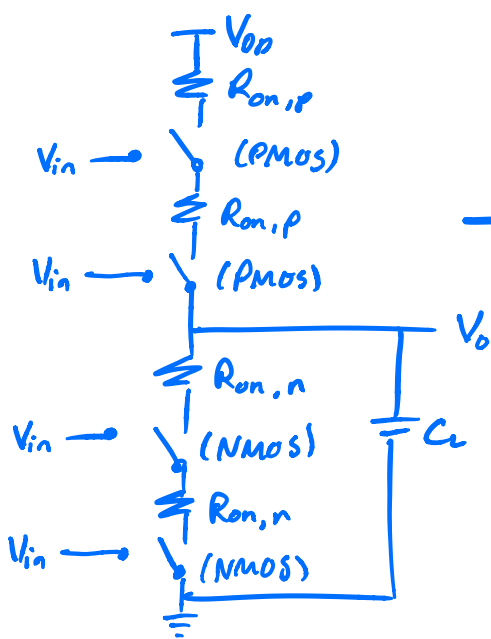
$$= \frac{V_{DD} (1 - 1 + e^{-t/RC})}{R_{on,p}} = \frac{V_{DD} e^{-t/(R_{on,p} C)}}{R_{on,p}}$$




effective R is  
 $2 R_{on,p}$

$$P = \frac{V_{DD} e^{-t/2R_{on,p}C}}{2R_{on,p}}$$

\* not perfect factor of 2  
 due to exponent

\* we can surely eliminate "Add another PMOS transistor in series..."

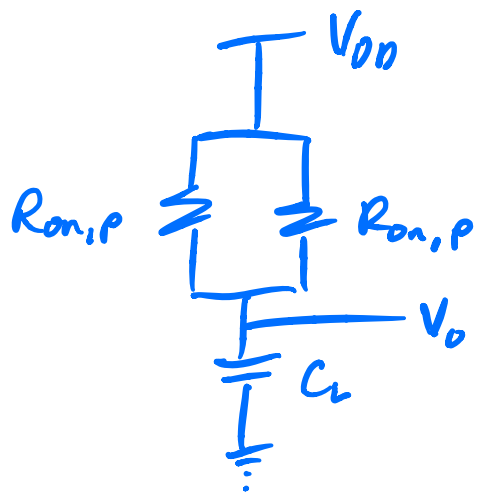(can draw out if you want but you can also realize by inspection)



effective R is  $0.5 R_{on,p}$

$$P = \frac{V_{DD} e^{-t/0.5R_{on,p}C}}{0.5 R_{on,p}}$$

\* not even reduced

\* we can surely eliminate "Add another PMOS transistor in parallel..."

\*\* LEAVING "None of the other choices"




# SP2020 MIDTERM 1 QUESTION 3 (exam on TBP site)

$e^{j\theta} = j \sin \theta + \cos \theta \rightarrow$  Euler's Formula

a) i. magnitude =  $\sqrt{2}$   
 $\hookrightarrow \sqrt{1^2 + 1^2} = |1+j|$

angle =  $45^\circ = \pi/4$   
 $\hookrightarrow \arctan(1/1)$

$1+j = \sqrt{2}e^{j\pi/4}$

 

ii.  $\sqrt{j} = j^{1/2}$       $j = e^{j\pi/2}$

$\sqrt{j} = (e^{j\pi/2})^{1/2} = e^{j\pi/4}$

b) i.  $3e^{j\pi/3}$       $3e^{j\pi/3} = 3(j \sin \frac{\pi}{3} + \cos \frac{\pi}{3}) =$

$3(j \frac{\sqrt{3}}{2} + \frac{1}{2}) = \frac{3\sqrt{3}}{2}j + \frac{3}{2}$

ii.  $-\sqrt{7}e^{\pi j}$       $-\sqrt{7}e^{\pi j} = -\sqrt{7}(j \sin \pi + \cos \pi) =$

method 1:  $-\sqrt{7}(j(0) + (-1)) = \sqrt{7}$

method 2:  $e^{\pi j} = -1$       $(-\sqrt{7})(-1) = \sqrt{7}$

c) i.  $\frac{1}{j} = -j$  ①      $\frac{1}{j} \times j = -j \times j$

②  $\frac{j}{j} = -(j^2)$

③  $1 = -(-1)$

④  $1 = 1 \checkmark$  Q.E.D.

ii.  $\sin(2x) = 2\cos x \sin x$

①  $e^{j\theta} = j\sin\theta + \cos\theta$

②  $e^{-j\theta} = j\sin(-\theta) + \cos(-\theta) = -j\sin\theta + \cos\theta$

positive trig mapping ③a  $e^{j\theta} + e^{-j\theta} = j\sin\theta + \cos\theta + (-j\sin\theta + \cos\theta) = 2\cos\theta$

Sin	All
Tan	Cos

④a  $\cos\theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$

③b  $e^{j\theta} - e^{-j\theta} = j\sin\theta + \cos\theta - (-j\sin\theta + \cos\theta) = 2j\sin\theta$

④b  $\sin\theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$

①  $\sin(2x) = \frac{e^{j(2x)} - e^{-j(2x)}}{2j}$

②  $\cos x \sin x = 2 \left( \frac{e^{jx} + e^{-jx}}{2} \right) \left( \frac{e^{jx} - e^{-jx}}{2j} \right) =$

$\frac{(e^{jx})^2 - (e^{-jx})^2}{2j} = \frac{e^{j2x} - e^{-j2x}}{2j}$

Q.E.D.

