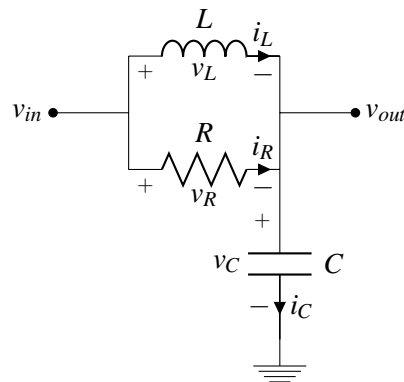


### 1. An RLC example



For the RLC filter above, with component values  $R = 1\text{ k}\Omega$ ,  $C = 10\text{ nF}$ , and  $L = 1\text{ }\mu\text{H}$ ,

- Find the transfer function. The easiest way is probably to treat it as a voltage divider.
- Create a Bode plot of that transfer function. Please do it step by step and use the Bode plot table in the next page.
- (Optional) Connect a DC voltage  $V_s$  source to  $v_{in}$ , derive the differential equations to describe the changes of  $i_L$  and  $v_C$ .

$$\begin{pmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{pmatrix} = A \begin{pmatrix} i_L \\ v_C \end{pmatrix} + B \quad (1)$$