## EECS 16B Designing Information Devices and Systems II Spring 2016 Anant Sahai and Michel Maharbiz Discussion 7B

1. RLC circuit In this problem, we study the differential equations governing a series RLC circuit, which we solve to get the transient behavior. We consider the simple RLC circuit below. Suppose that the switch is closed at time t = 0.



- (a) Write the voltages  $v_C$ ,  $v_R$ ,  $v_L$  in terms of the current *i*, with respect to time *t*.
- (b) Write down a second order differential equation for the current in the circuit with respect to time, in terms of the constants R, L, C.
- (c) Rewrite your second order differential equation in the form

$$\begin{pmatrix} \frac{di}{dt} \\ \frac{dv_L}{dt} \end{pmatrix} = A \begin{pmatrix} i \\ v_L \end{pmatrix}$$
(1)

where A is a  $2 \times 2$  matrix with coefficients that depend only on R, L, C.

- (d) Find the eigenvalues and corresponding eigenvectors of your matrix A from the previous part.
- (e) For the case where the two eigenvalues are real, we claim that the solution to this system of differential equations is of the form

$$\binom{i}{v_L} = c_0 e^{\lambda_0 t} \vec{v}_0 + c_1 e^{\lambda_1 t} \vec{v}_1 \,,$$

where  $c_0, c_1$  are constants, and  $\lambda_0, \lambda_1$  are the eigenvalues of A with eigenvectors  $\vec{v}_0, \vec{v}_1$  respectively. Solve for the constants  $c_0, c_1$ , with the initial conditions  $i = 0, v_L = 1$  at t = 0. Write your solution for *i* as a function of *t*.

(f) For the case where the eigenvalues are complex, the solution to the system has the same form as in the previous part. Find *i* as a function of *t* in this case.

## 2. RLC circuit in AC

We study a simple RLC circuit with an AC voltage source given by

$$v_s = B\cos(\omega t - \phi)$$



- (a) Write out the phasor representation of  $v_s, R, C, L$ .
- (b) Use Kirchhoff's laws to write down a loop equation relating the phasors in the previous part.
- (c) Solve the equation in the previous step for the current *I*. What is the polar form of *I*?
- (d) Compute the polar form of  $V_R, V_L, V_C$ .

## **Contributors:**

• Lynn Chua.