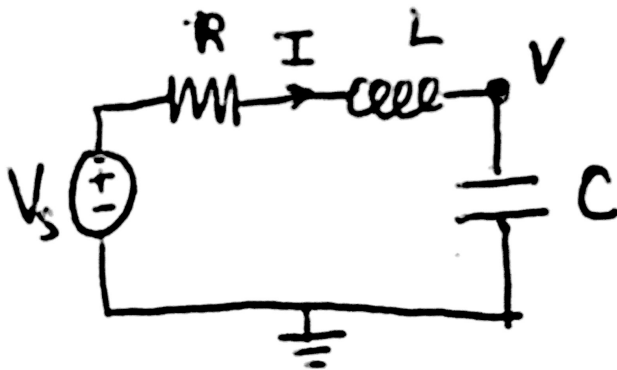


RLC Circuit

Recall the circuit from last lecture:



What would happen in a transient behavior like below:

$V_s = 1$ for a long time then at time $t=0$, V_s becomes 0 and stays at zero.

Unlike capacitors where we got two real eigenvalues, in this setup depending on the values of R , L and C , we can get complex values.

Especially, if $R = 0$, we are just left with L and C and it will be purely imaginary numbers and these imaginary eigenvalues will in general correspond to oscillations especially between the inductor and the capacitor.

Recall that we always end up with equation as follows: $\frac{d}{dt}(x(t)) = s * x(t)$ $X(0) = X_0$ And it gets solved by $x(t) = Ke^{st}$ where $K = X_0$. This is one solution.

How do we prove that this is the only solution?

Suppose there exists $y(t)$ that solves the equation as well.

Consider $\frac{y(t)}{e^{st}} = y(t)e^{-st}$.

Check at $t=0$: $\frac{y(0)}{e^0} = X_0$ (from the condition " $X(0) = X_0$ ")

If we want to show that the value doesn't change over time, take derivative and see if it's zero:

Compute $\frac{d}{dt}(y(t)e^{-st}) = \frac{d}{dt}(y(t))e^{-st} + y(t)\frac{d}{dt}(e^{-st}) = s * y(t)e^{-st} - s * y(t)e^{-st} = 0$.

Thus, we know that this is the unique solution.

Going back to the RLC problem, writing equations (through KVL and KCL), we get:

$$I(t) = C \frac{dV}{dt}$$

$$\text{Knowing } V_s = 0, 0 - IR - V = L \frac{dI}{dt}$$

$$\text{Writing these equations into a matrix form, } \frac{d}{dt} \begin{bmatrix} I(t) \\ V(t) \end{bmatrix} = \begin{bmatrix} \frac{R}{L} & \frac{-1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} I(t) \\ V(t) \end{bmatrix} = A \begin{bmatrix} I(t) \\ V(t) \end{bmatrix}$$

Initial conditions are:

$$V(0) = 1$$

$$I(0) = 0$$

TRICK: Usually, voltage through capacitor and current through inductor.

Next step is to diagonalize this matrix by eigenvalues and eigenvectors: $\det(A - \lambda I) = 0$

$$\text{We get: } \lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0$$

Solve for λ :

$$\lambda = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Eigenvectors we choose to be: $\begin{bmatrix} 1 \\ \frac{1}{C\lambda} \end{bmatrix}$

Try: $R=0$ and for simplicity, $L=1, C=1 \rightarrow \lambda_+ = \sqrt{-1} = +j$ and $\lambda_- = -\sqrt{-1} = -j$

Then for this example (after some algebra),

$$I(t) = K_1 e^{jt} + K_2 e^{-jt} = -\sin(t)$$

$$V(t) = \cos(t)$$

Take note that if eigenvalues are purely imaginary, solutions in time domain are going to be sinusoids.

Try another example: $R = 2, L=1, C=0.5 \rightarrow \lambda = -1 \pm \sqrt{1-2} = -1 \pm j$

Then for this example (after some algebra),

$I(t) = K_1 e^{(-1+j)t} + K_2 e^{(-1-j)t} = e^{-t}(K_1 e^{jt} + K_2 e^{-jt})$ [phase shifted cosine, "damped oscillation" - looks like below graph]

