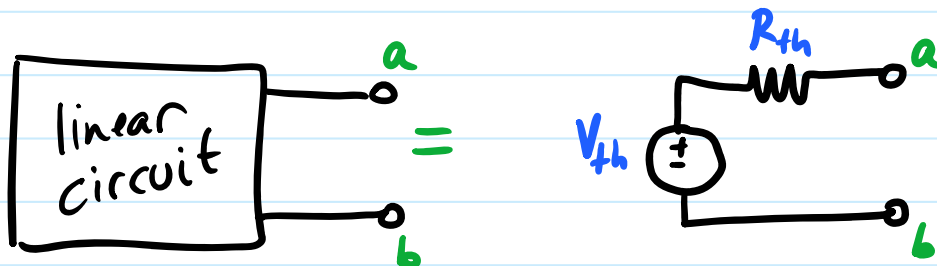


# Thevenin / Norton Equivalent Circuits and Source Transformation


Wednesday, February 1, 2017 12:30 PM

## I. Thevenin equivalent circuits



a. There are three methods to find  $V_{th}$  and  $R_{th}$ .

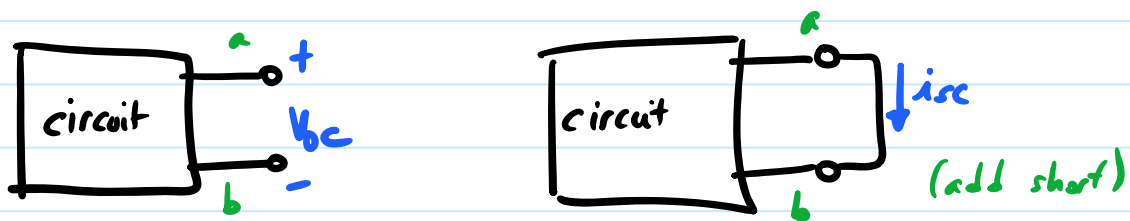
i) Find  $V_{oc}$  (open circuit voltage) and  $i_{sc}$  (short circuit current).




$$\text{then, } V_{th} = V_{oc} \quad \text{and} \quad R_{th} = \frac{V_{oc}}{i_{sc}}$$

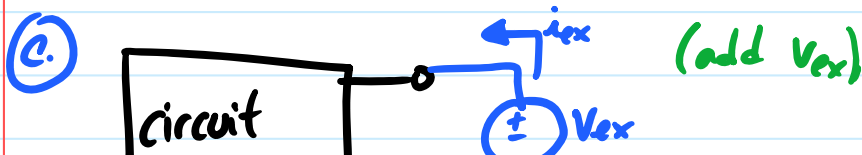b. Find either  $V_{oc}$  and  $i_{sc}$  as above (whichever is easier).

Then, deactivate all independent sources (i.e. set them to 0). Then, simplify circuit to find the equivalent resistance. This is  $R_{th}$ . (This method only works if there are no dependent sources in circuit).



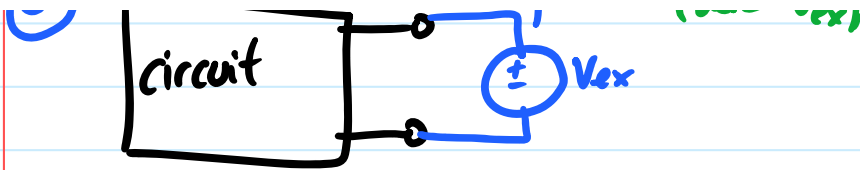

Add a fictitious  $V_{ex}$  as above.


Solve for  $i_{ex}$ .

$$R_{th} = \frac{V_{ex}}{i_{ex}}$$

$V_{oc}$  or  $i_{sc}$  can be solved as above.
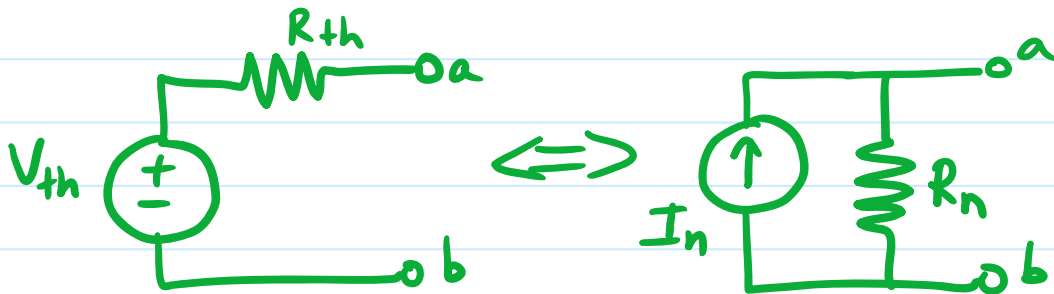
## II. Source transformations

If a circuit can be represented by a voltage source and a resistor, it stands to reason that it should also be similarly represented by a current source and a resistor.



$$I_n = I_{th}$$

$$I_n = \frac{V_{th}}{R_{th}}$$