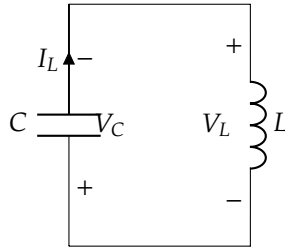


## 1 LC Tank: Diagonalization with complex eigenvalues

Consider the following circuit like you saw in lecture:



This is sometimes called an *LC* tank and we will derive its response in this problem. Assume at  $t = 0$  we have  $V_C(0) = V_S = 1$  V and  $\frac{dV_C}{dt}(t = 0) = 0$ .

- a) **Write the system of differential equations in terms of state variables  $x_1(t) = I_L(t)$  and  $x_2(t) = V_C(t)$  that describes this circuit for  $t \geq 0$ . Leave the system symbolic in terms of  $V_S$ ,  $L$ , and  $C$ .**

- b) **Write the system of equations in vector/matrix form with the vector state variable  $\vec{x}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$ . This should be in the form  $\frac{d}{dt}\vec{x}(t) = A\vec{x}(t)$  with a  $2 \times 2$  matrix  $A$ .**

**Find the initial conditions  $\vec{x}(0)$ .**

c) Find the eigenvalues of the  $A$  matrix symbolically.

d) What are the eigenvectors associated with these eigenvalues?

e) Use the eigenvalues and eigenvectors found above to diagonalize  $A$  as  $A = V\Lambda V^{-1}$  where  $\Lambda$  is a diagonal matrix. Suppose  $L = 9 \text{ nH}$  and  $C = 1 \text{ nF}$ .

f) Use a change of basis for the state variable  $\vec{x}(t)$  into  $\vec{z}(t)$  such that  $\frac{d}{dt}\vec{z}(t) = \Lambda\vec{z}(t)$ , and express the initial conditions  $\vec{z}(0)$

**Solve the differential equations in  $\vec{z}(t)$**

- g) **Convert your solutions back to  $\vec{x}(t)$ . Plot  $V_C(t)$  and  $I_L(t)$ .** What do you notice about the solutions? Are they complex functions? HINT: Remember  $e^{j\theta} = \cos(\theta) + j \sin(\theta)$ .

## 2 Complex Matrix Inverse

Consider a complex matrix

$$M = M_r + jM_i$$

and its inverse

$$N = N_r + jN_i$$

- a) **Show that the inverse of  $\overline{M} = M_r - jM_i$  (the complex conjugate of  $M$ ) is equal to  $\overline{N} = N_r - jN_i$  (the complex conjugate of  $N$ ).**