

This homework is designed as a practice for midterm 1. Solutions are published with the homework. Problems 1-3 are designed for midterm practice and problem 4-5 are related to filter and transfer function, materials covered in the class most recently.

There is no self-grade and grading deadline.

1 Matrix Differential Equations

In this problem, we consider ordinary differential equations which can be written in the following form

$$\begin{bmatrix} x'(t) \\ y'(t) \end{bmatrix} = A \begin{bmatrix} x(t) \\ y(t) \end{bmatrix}, \quad (1)$$

where x, y are variables depending on t , $x' = \frac{dx}{dt}$, $y' = \frac{dy}{dt}$, and A is a 2×2 matrix with constant coefficients. We call (1) a matrix differential equation.

- a) Suppose we have a system of ordinary differential equations

$$x' = 8x + 7y \quad (2)$$

$$y' = -4x - 3y \quad (3)$$

Write this in the form of (1).

- b) Compute the eigenvalues of the matrix A from the previous part.
 c) We claim that the solution for $x(t), y(t)$ is of the form

$$\begin{bmatrix} x(t) \\ y(t) \end{bmatrix} = \begin{bmatrix} c_0 e^{\lambda_0 t} + c_1 e^{\lambda_1 t} \\ c_2 e^{\lambda_0 t} + c_3 e^{\lambda_1 t} \end{bmatrix},$$

where c_0, c_1, c_2, c_3 are constants, and λ_0, λ_1 are the eigenvalues of A . Suppose that the initial conditions are $x(0) = 1, y(0) = 1$. Solve for the constants c_0, c_1, c_2, c_3 .

- d) Verify that the solution for $x(t), y(t)$ found in the previous part satisfies the original system of differential equations (2), (3).
 e) We now apply the method above to solve another second-order ordinary differential equation. Suppose we have the system


$$z''(t) - 5z'(t) + 6z(t) = 0, \quad (4)$$

where $z' = \frac{dz}{dt}$ and $z'' = \frac{d^2z}{dt^2}$. Write this in the form of (1), by choosing your state variables to be $x(t) = z(t), y(t) = z'(t)$.

- f) Solve the system in (4) with the initial conditions $z(0) = 1, z'(0) = 1$, using the method developed in parts (b) and (c).

2 RL Circuit

Consider the circuit below

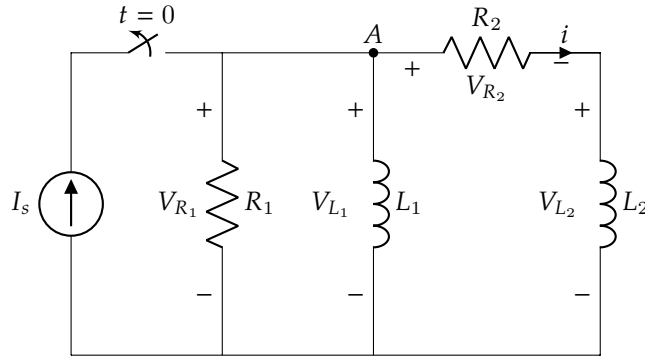

a) What is $i(0)$.

Hint: What is the current flowing through L_1 before the switch opens? Consequently what is the current flowing through L_2 ?

b) What is $\frac{di}{dt}(0)$?

c) What is the relationship between the voltages across L_1 and R_1 ?

d) Use KCL on node A and the relationship derived above to arrive at a differential equation of the form

$$\frac{d^2i}{dt^2}(t) + a_1 \frac{di}{dt}(t) + a_0 i(t) = 0$$

where $i(t)$ is the current going through L_2 .

e) Let $R_1 = R_2 = R$ and $L_1 = L_2 = L$. Recall that the above differential equation can be reshaped into the following linear algebra problem:

$$\begin{bmatrix} \frac{di}{dt} \\ \frac{d^2i}{dt^2} \end{bmatrix} = A \begin{bmatrix} i \\ \frac{di}{dt} \end{bmatrix}$$

What is the A matrix and what are its eigenvalues?

f) Will this circuit exhibit any oscillations?

g) Now, consider the case when the switch is open for time $t < 0$, and the switch closes at $t = 0$. What is V_{R_1} ?


3 Transfer Functions and Filters

- a) Identify each of the Bode Plots, circuits, and transfer functions as either a lowpass or highpass filter. Indicate your answer by filling in the appropriate bubble.



Table 1: Table to be filled in for your answers. Fill in bubbles.

	Lowpass	Highpass
Bode Plot A	<input type="radio"/>	<input type="radio"/>
Bode Plot B	<input type="radio"/>	<input type="radio"/>
Circuit C	<input type="radio"/>	<input type="radio"/>
Circuit D	<input type="radio"/>	<input type="radio"/>
Transfer Fn E	<input type="radio"/>	<input type="radio"/>
Transfer Fn F	<input type="radio"/>	<input type="radio"/>


Bode Plot A ($\omega_c = 10^6$)

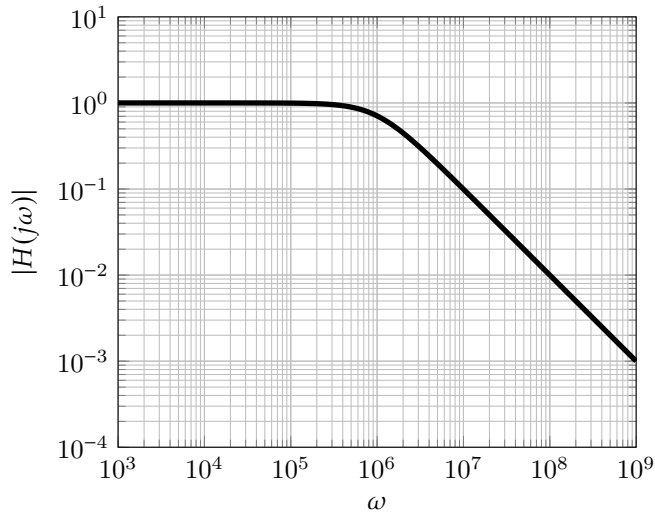

Bode Plot B ($\omega_c = 10^6$)

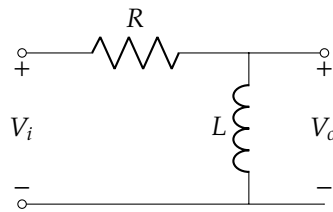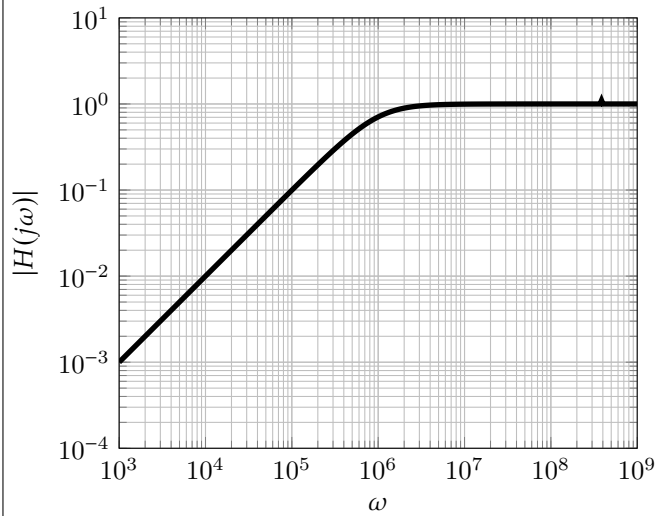

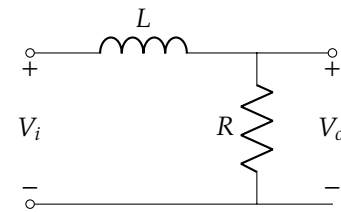Circuit C: $H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_i}$



Circuit D: $H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_i}$

$$\text{Transfer function E: } H_E(j\omega) = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}} \quad | \quad \text{Transfer function F: } H_F(j\omega) = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$

b) Consider the three filters in cascade below, with unity-gain op-amp buffers in between them:

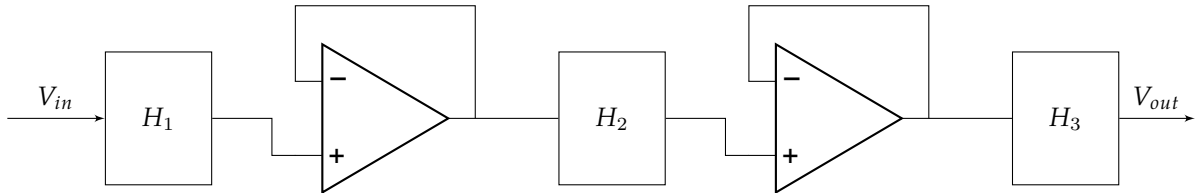


Figure 2: Three filters cascaded via unity-gain op-amp buffers

Suppose that at some frequency ω_0 radians/sec we know that:

$$H_1(j\omega_0) = 3e^{j\frac{\pi}{4}} \quad H_2(j\omega_0) = \frac{1}{2}e^{-j\frac{\pi}{3}} \quad H_3(j\omega_0) = 4e^{j\frac{5\pi}{6}}$$

If $V_{in}(t) = 2 \sin\left(\omega_0 t + \frac{\pi}{2}\right)$:

What is the phasor for the input voltage: \widetilde{V}_{in} ?

What is the phasor for the output voltage: \widetilde{V}_{out} ?

What is $V_{out}(t)$?

4 Bandpass Filter: Lowpass and Highpass Cascade

In lecture, you heard about how you can go through the design of a bandpass filter by cascading lowpass and highpass filters via buffers (Op-Amps in unity-gain negative feedback to prevent loading effects). In this problem, you will do this for yourself.

Consider an input signal that is composed of the superposition of:


- 20mV level pure tone at 60Hz corresponding to power line noise.
- 1mV level pure tone at 600Hz corresponding to a voice signal.
- 10mV level pure tone at 60kHz corresponding to fluorescent light noise.

This is the signal that you want to filter.

- a) We would like to keep the 600Hz tone, which could correspond to a voice signal, for example.
Ignoring any phase offset for each signal (i.e. set the phases to zero), **write the $V_{in}(t)$ that describes the above input in time domain.**
- b) **What are the radian/sec frequencies ω s involved and the phasors associated with each tone?**
- c) To achieve your goal of keeping the voice tone but rejecting the noise from the power-lines and fluorescent lights, **at what frequency do you want to have the knee or cutoff-frequency for the lowpass filters?**
- d) To achieve your goal of keeping the voice tone but rejecting the noise from the power-lines and fluorescent lights, **at what frequency do you want to have the knee or cutoff-frequency for the highpass filters?**
- e) Suppose that you only had $1\mu\text{F}$ capacitors to use. **What resistance values would you choose for your highpass and lowpass filters so that they have the desired cutoff frequencies?**

5 Transfer functions and why loading is annoying

Consider the circuit below.

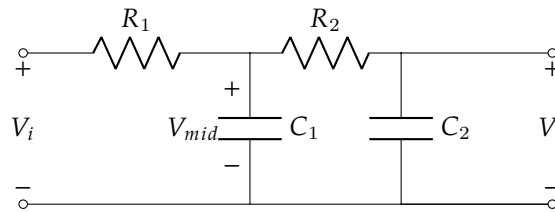

The circuit has an input phasor voltage \tilde{V}_i at frequency ω rad/sec applied at the input terminals shown in the illustration above, causing an output phasor voltage \tilde{V}_o at output terminals.

- a) We are going to construct the transfer function $H(\omega) = \frac{\tilde{V}_o}{\tilde{V}_i}$ in two steps.
We will compute two intermediate transfer functions, $H_1(\omega) = \frac{\tilde{V}_{mid}}{\tilde{V}_i}$ and $H_2(\omega) = \frac{\tilde{V}_o}{\tilde{V}_{mid}}$. Then, we will find the overall transfer function as the product of these two intermediate transfer functions, i.e. $H(\omega) = \frac{\tilde{V}_o}{\tilde{V}_i} = H_1(\omega)H_2(\omega)$.
This approach is valid since the \tilde{V}_{mid} cancel.
For the first step, **find the intermediate transfer function $H_2(\omega) = \frac{\tilde{V}_o}{\tilde{V}_{mid}}$.** Have your expression be in terms of Z_{R_2} and Z_{C_2} , that is the impedances of R_2 and C_2 .

b) Now, **compute the other intermediate transfer function** $H_1(\omega) = \frac{\tilde{V}_{mid}}{\tilde{V}_i}$. Have your expression be in terms of Z_{R1} , Z_{R2} , Z_{C1} , and Z_{C2} . (i.e. Don't forget to consider the impact of loading by R_2 and C_2 in this transfer function.) *hint: Applying KCL at the V_{mid} node would be a good place to start. You should try to find an expression for H_1 that has factors that H_2 can cancel out.*

c) Then, **use these two intermediate transfer functions to calculate the overall transfer function** as $H(\omega) = \frac{\tilde{V}_o}{\tilde{V}_i} = H_1(\omega)H_2(\omega)$.

d) Sometimes it is useful to collect all the frequency dependence into one place and to figure out how to think about what scale might be somewhat natural for the frequency. **Obtain an expression for $H(\omega) = \tilde{V}_o/\tilde{V}_i$ in the form**

$$H(\omega) = \frac{V_o}{V_i} = \frac{1}{1 + 2\xi \frac{j\omega}{\omega_c} + \frac{(j\omega)^2}{\omega_c^2}},$$

given that $R_1 = 2\Omega$, $R_2 = 4\Omega$, $C_1 = \frac{9}{2}\text{F}$, and $C_2 = 1\text{F}$. What are the values of ξ and ω_c ?

e) **For the previous case, what is the magnitude of the transfer function at the $\omega = \omega_c$ you calculated?**

This is here so that you can see that just because we called it ω_c doesn't mean that the amplitude here is $\frac{1}{\sqrt{2}}$.

f) We can express the transfer function $H(\omega)$ in the polar form. That is,

$$H(\omega) = M(\omega)e^{j\phi(\omega)}$$

The functions $M(\omega)$ and $\phi(\omega)$ are the magnitude and the phase angle of $H(\omega)$, respectively. **Write down $M(\omega)$ and $\phi(\omega)$ using the transfer function you derived in part (b).**

g) Use a computer and then **draw Bode Plots of $|H(\omega)|$ and $\angle H(\omega)$.**