
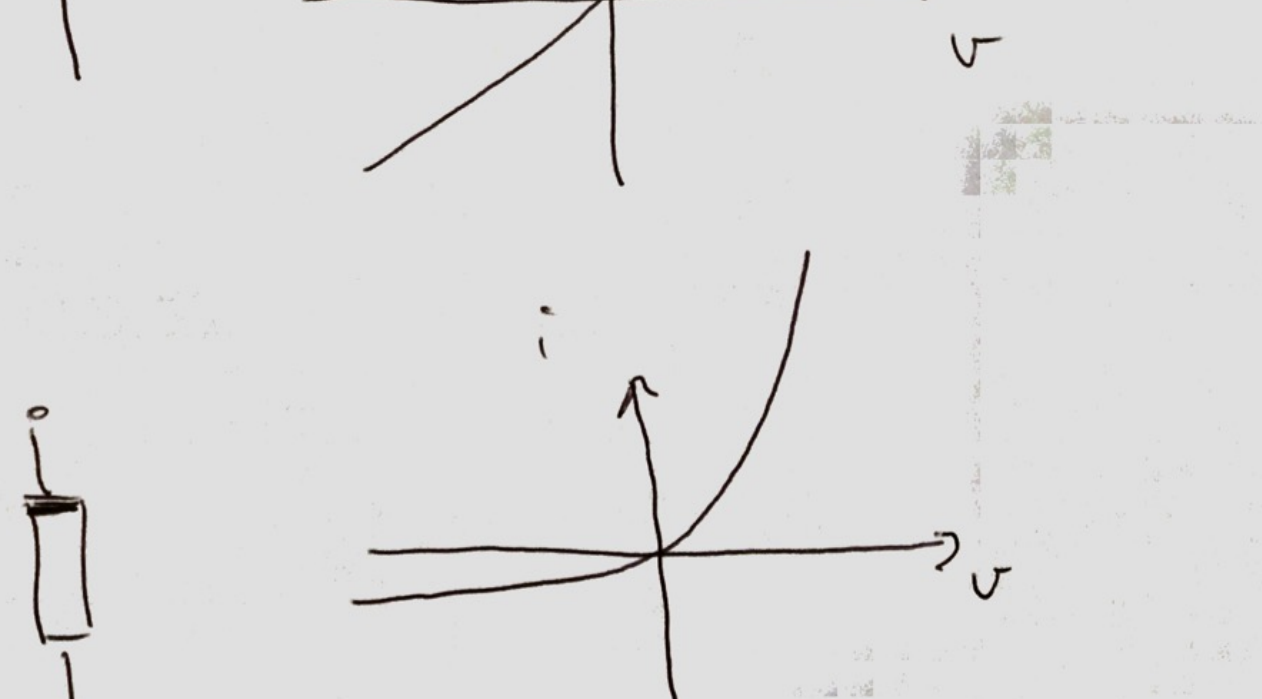


ECS 16B Jan 23 2020

New device Transistor

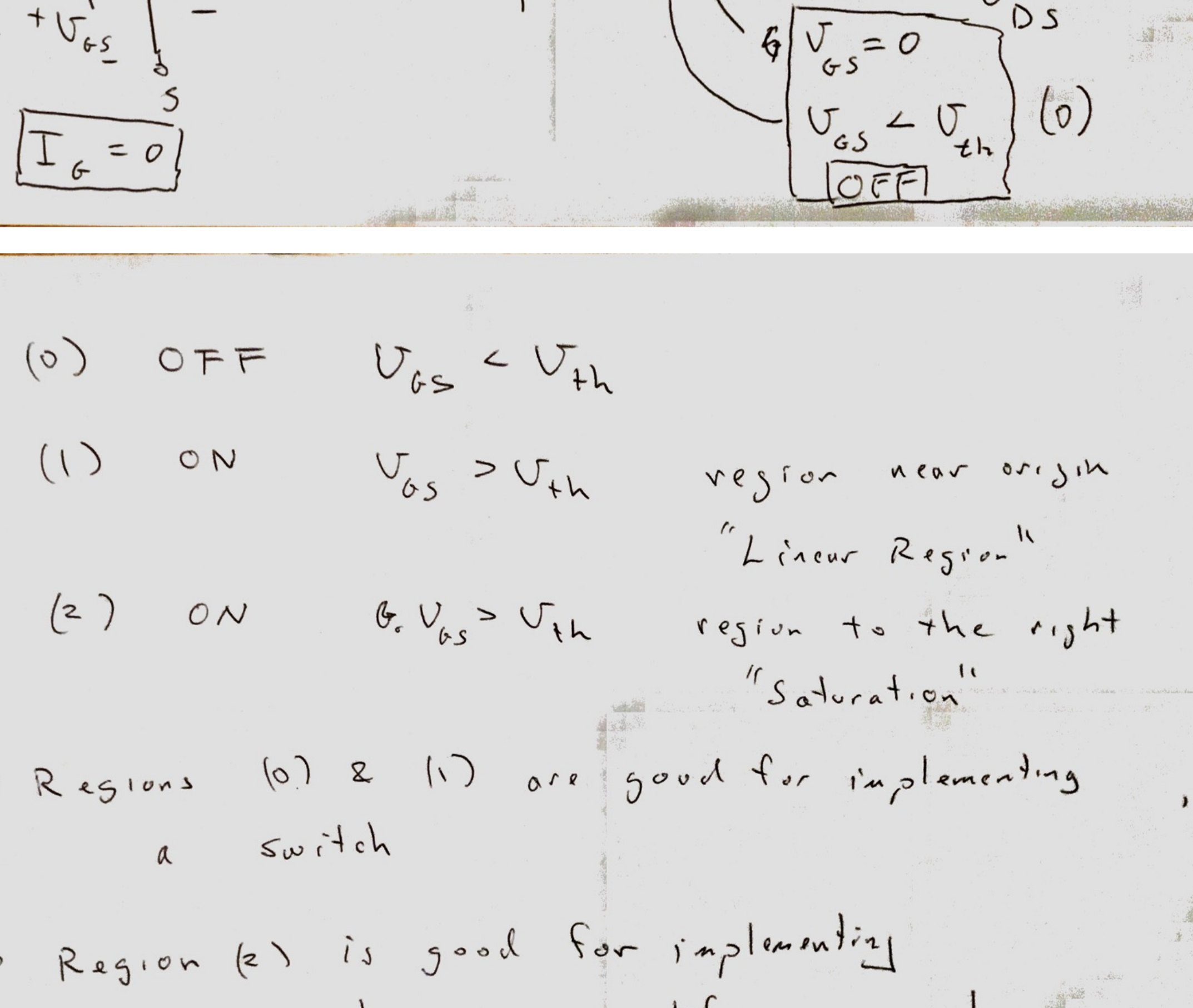


① MOSFET \triangleq Metal Oxide Semiconductor Field Effect Transistor




Regions (0) & (1) are good for implementing a switch
 Region (2) is good for implementing current source, amplifier, ..., analog

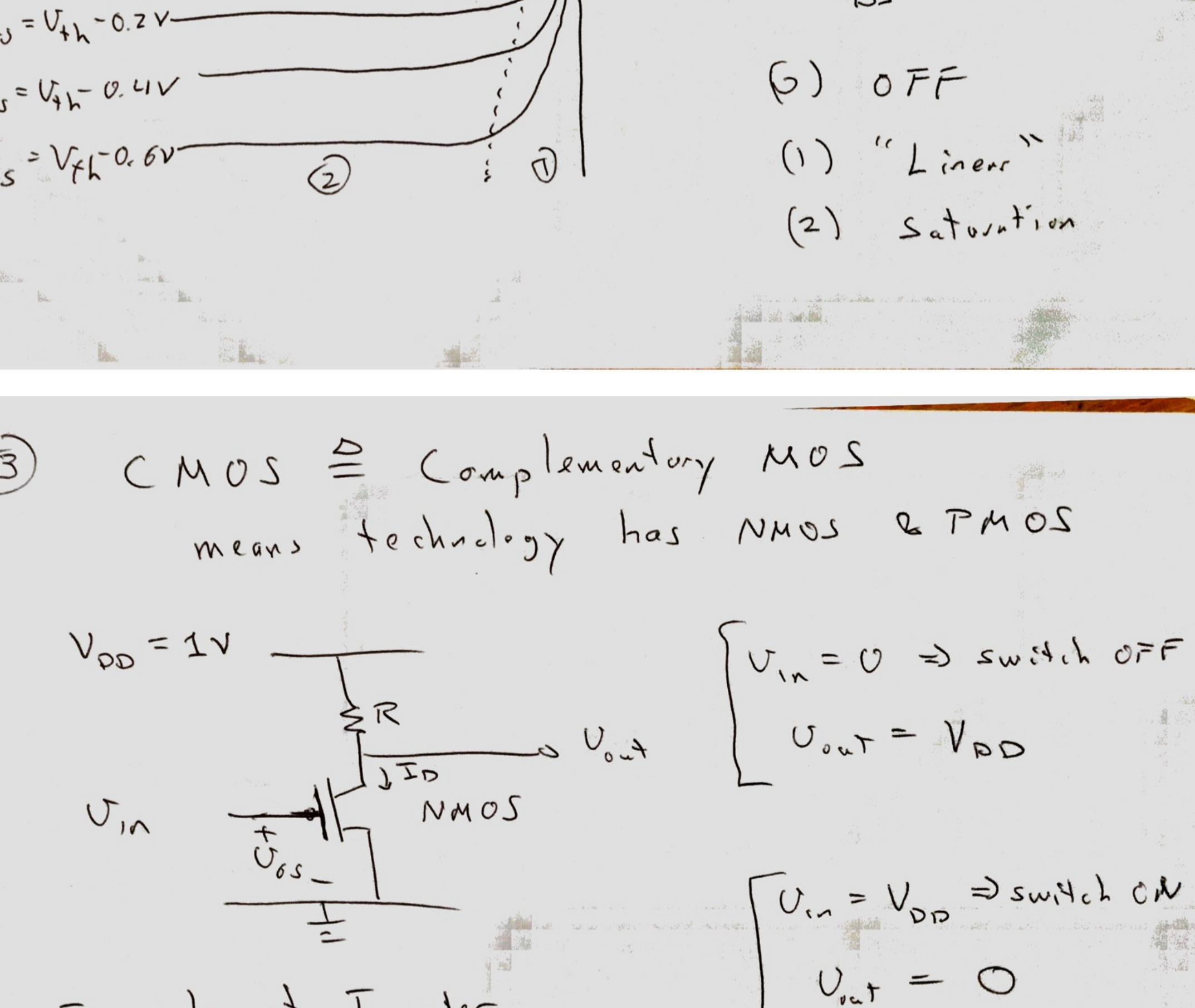
② 1st MOSFET called "NMOS"
 2nd MOSFET "PMOS"



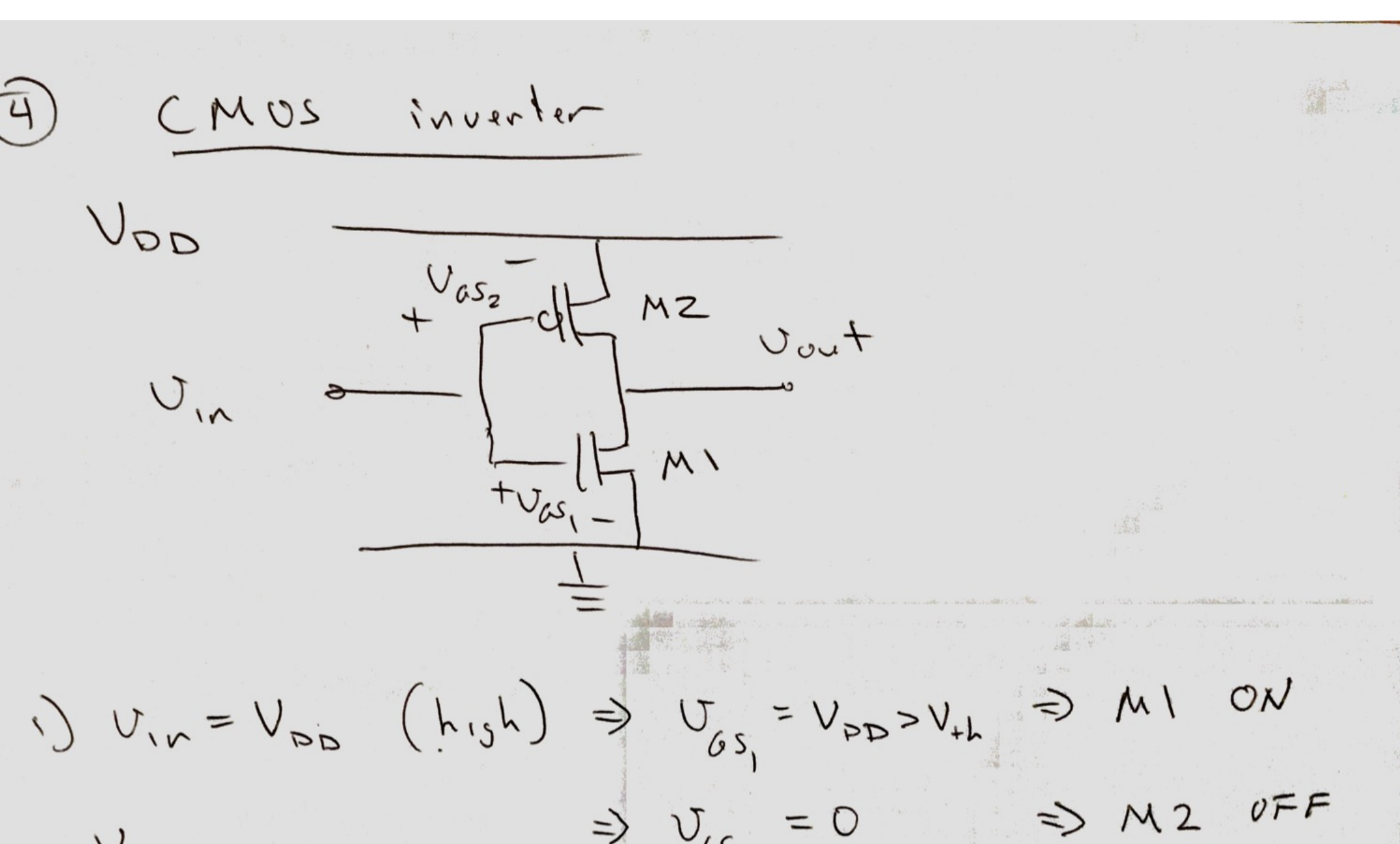
③ CMOS \triangleq Complementary MOS means technology has NMOS & PMOS




④ CMOS inverter

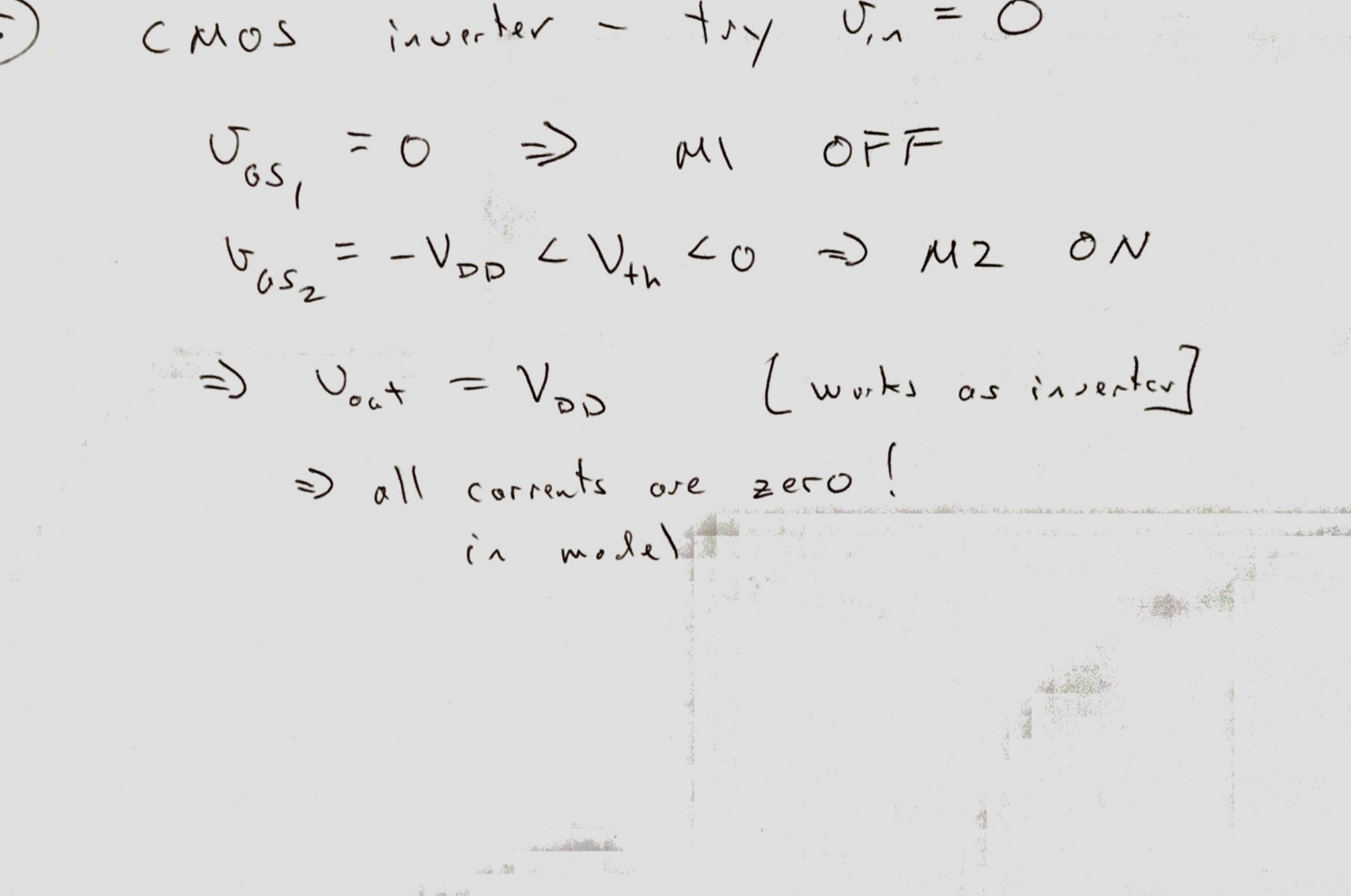


⑤ CMOS inverter - try $V_{in} = 0$

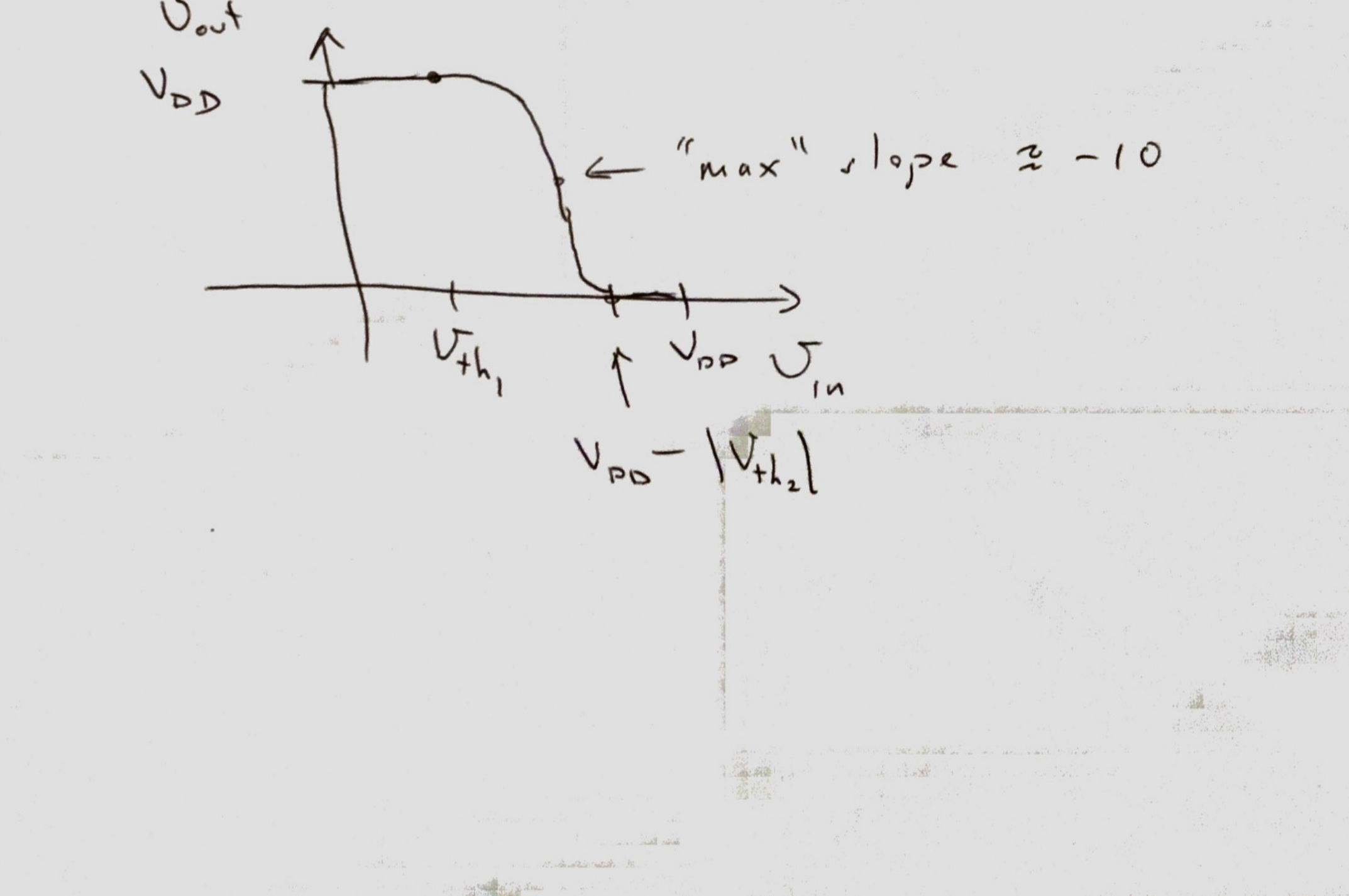


⑥ Overall input-output char.

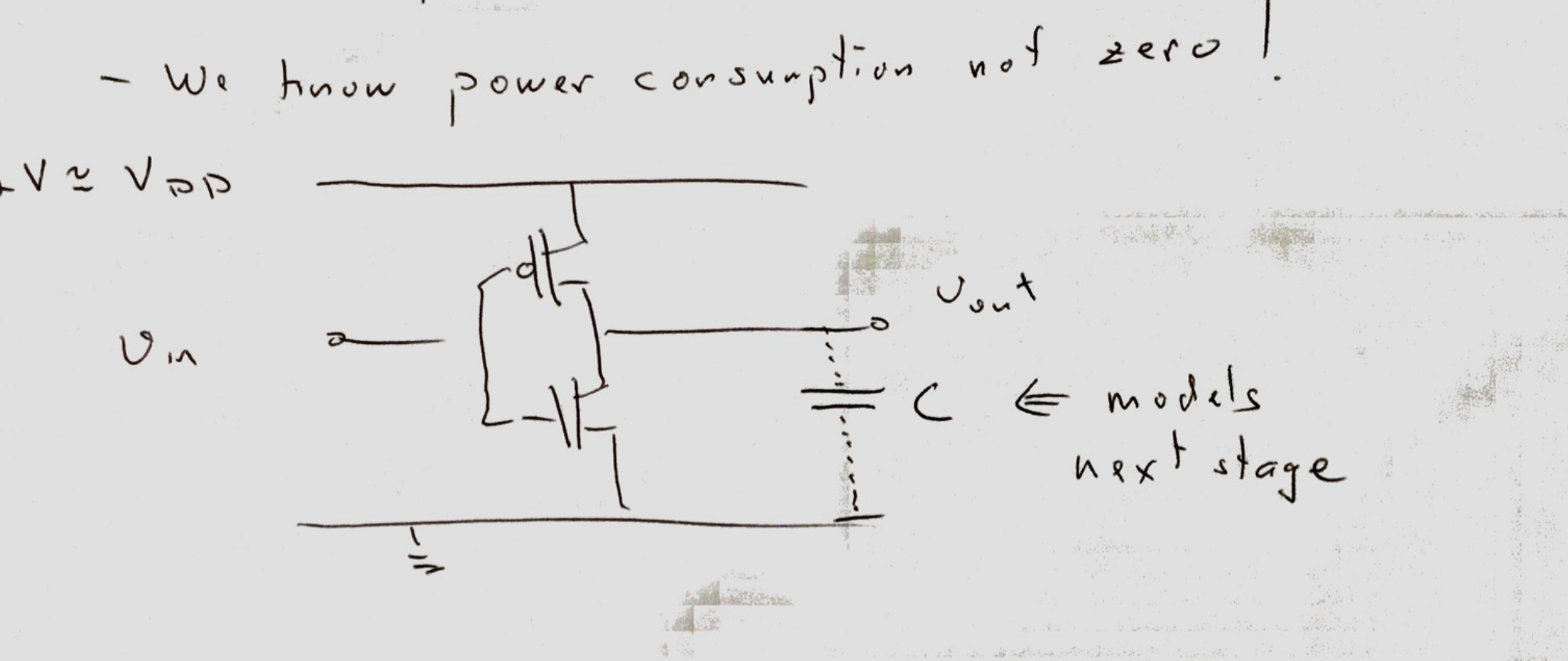

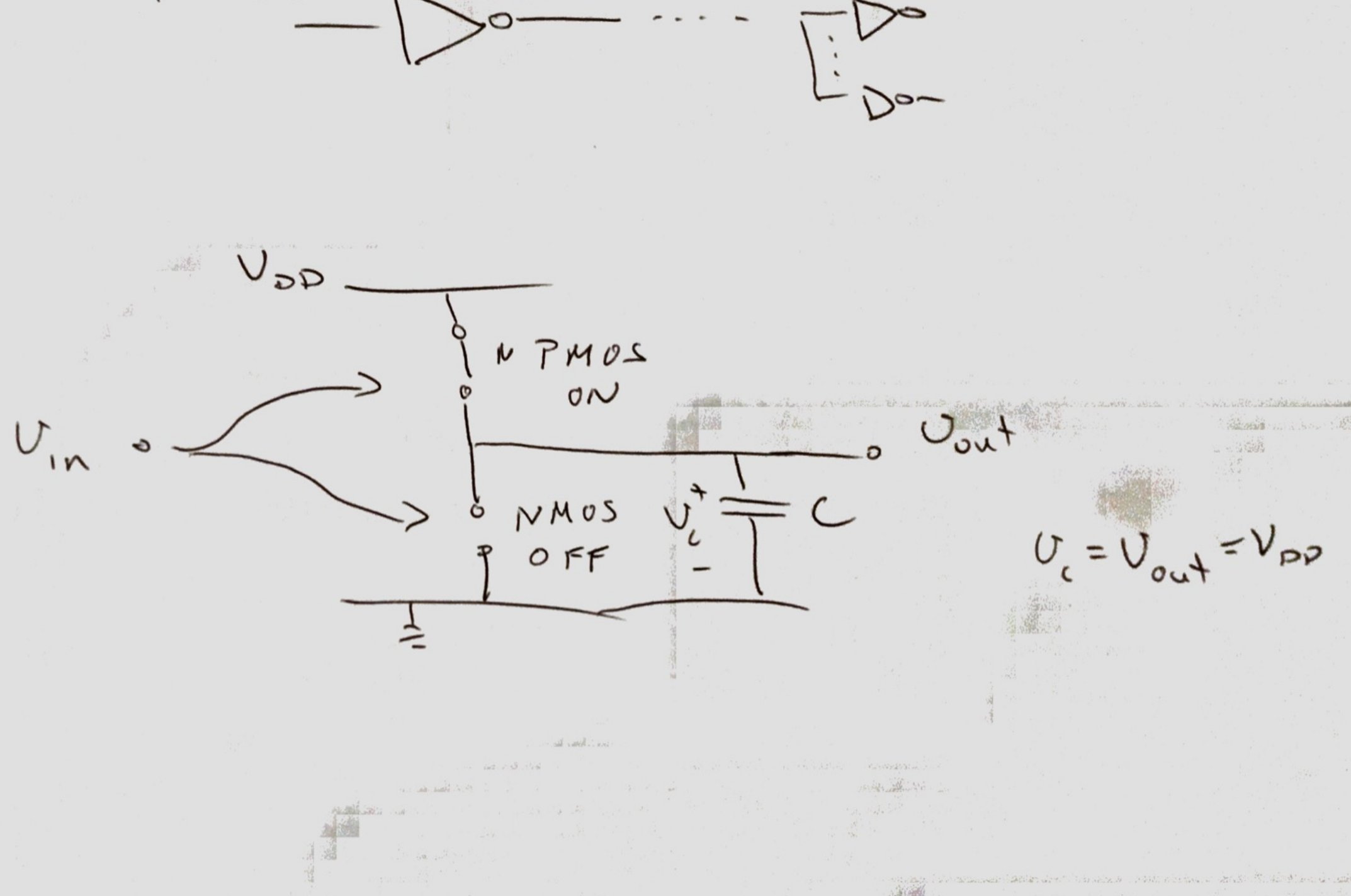
⑦ Inverter: Perfect Model \Rightarrow zero current in CMOS inverter



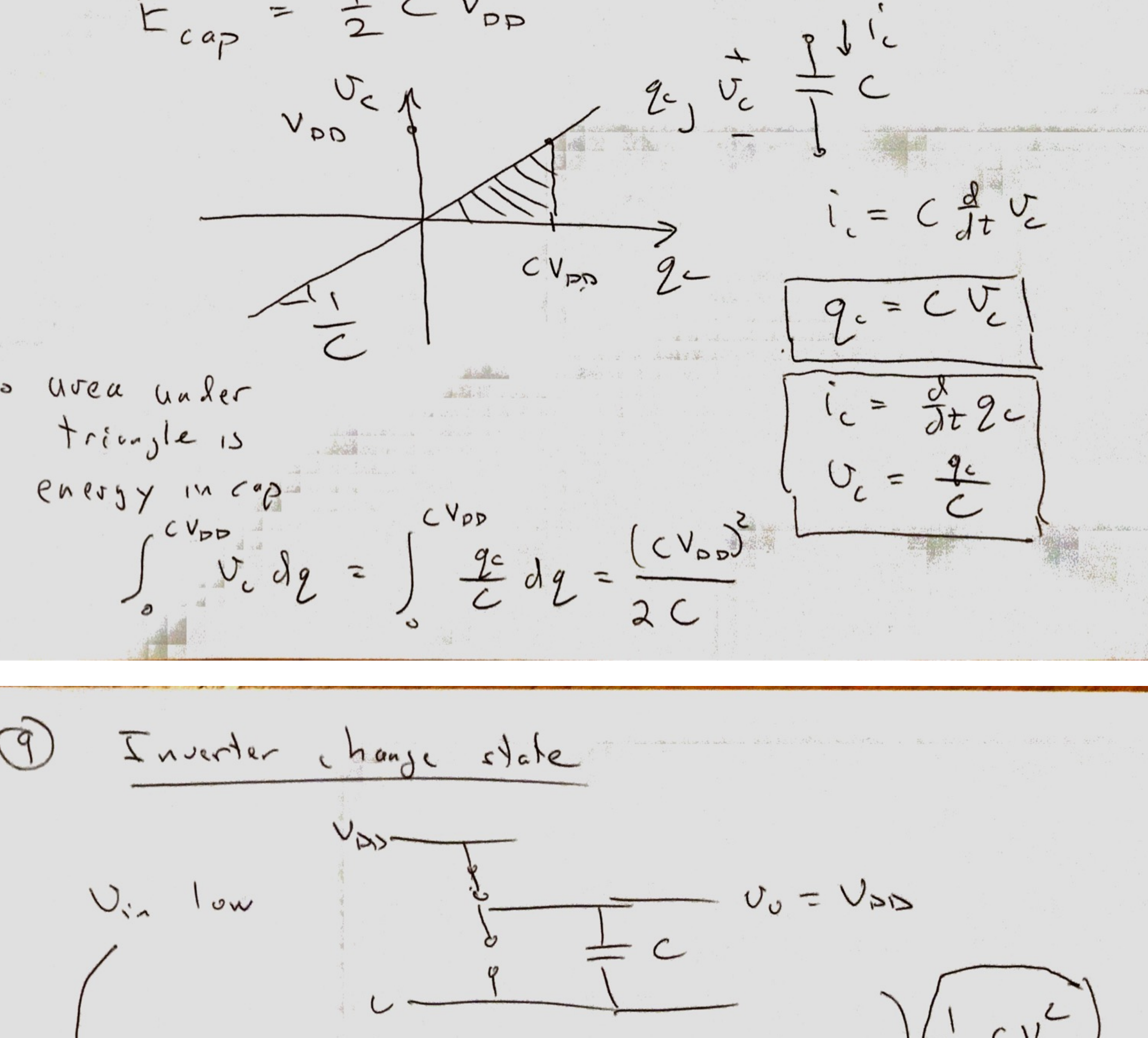
⑧ what is energy in cap if $V_c = V_{DD}$?



⑨ Inverter charge state

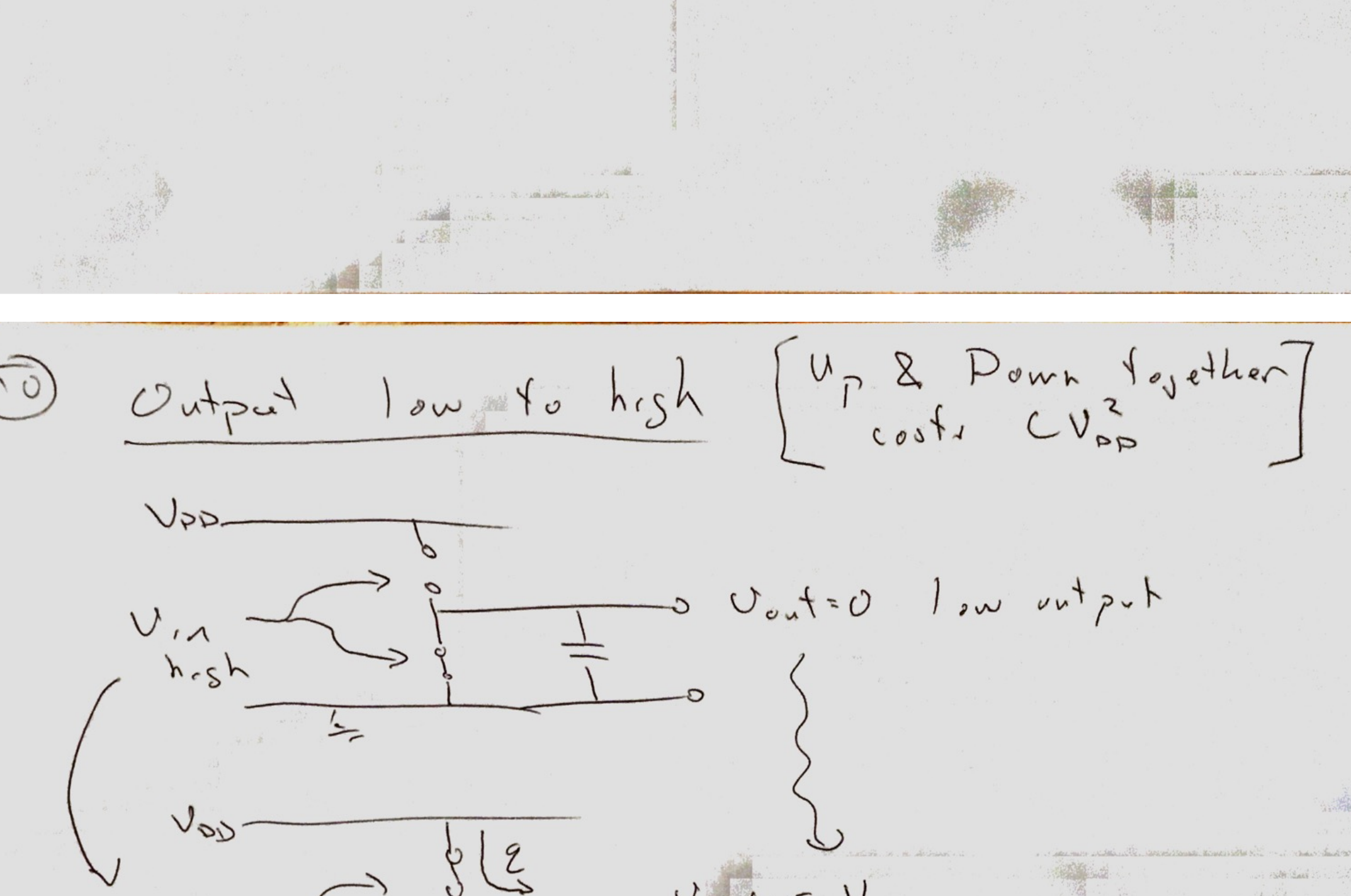

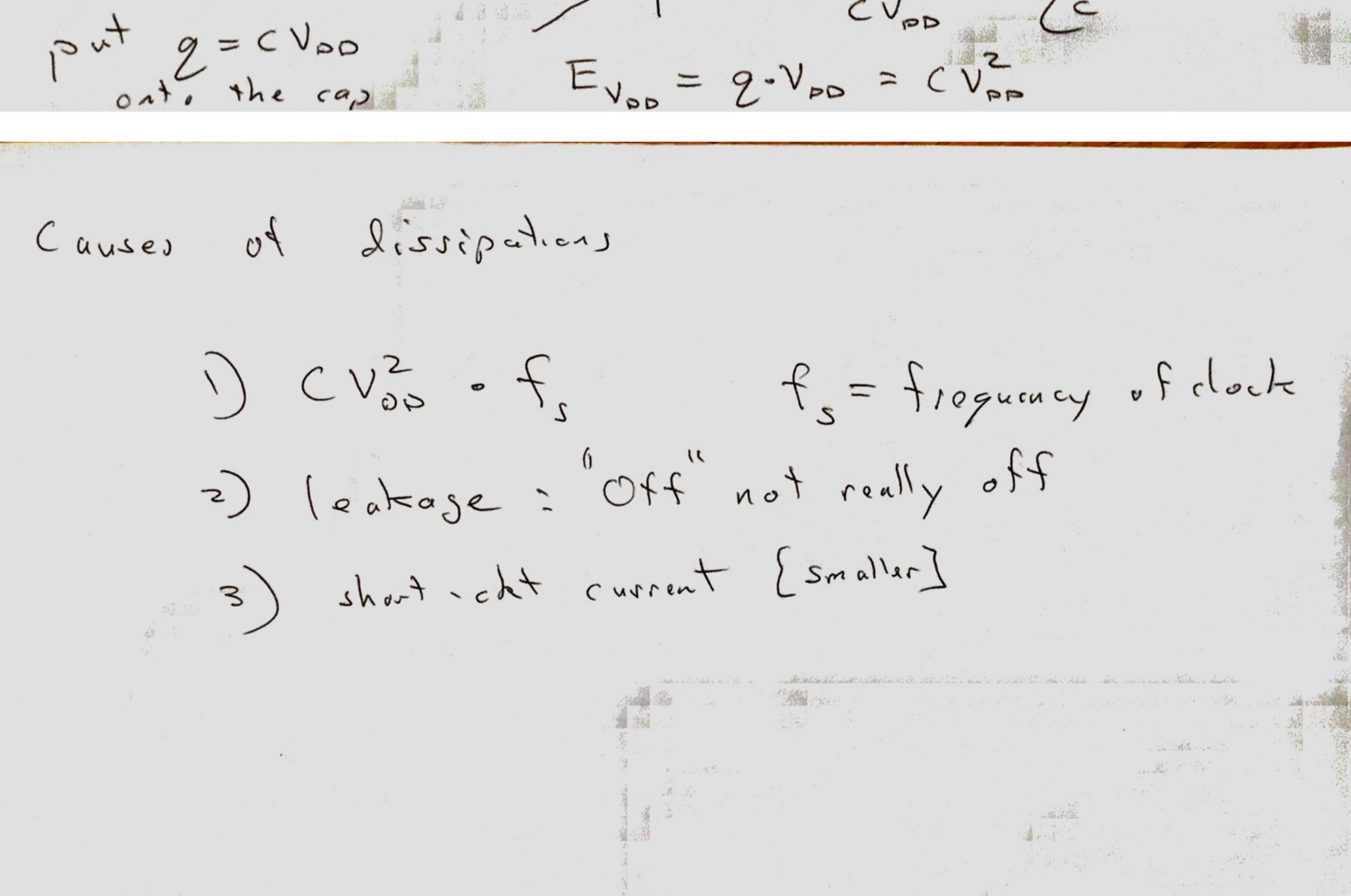⑩ Output low to high [Up & Down together] costs $C V_{DD}^2$



Causes of dissipation

- $C V_{DD}^2 \cdot f_s$ f_s = frequency of clock
- leakage = "Off" not really off
- short-circuit current [smaller]