

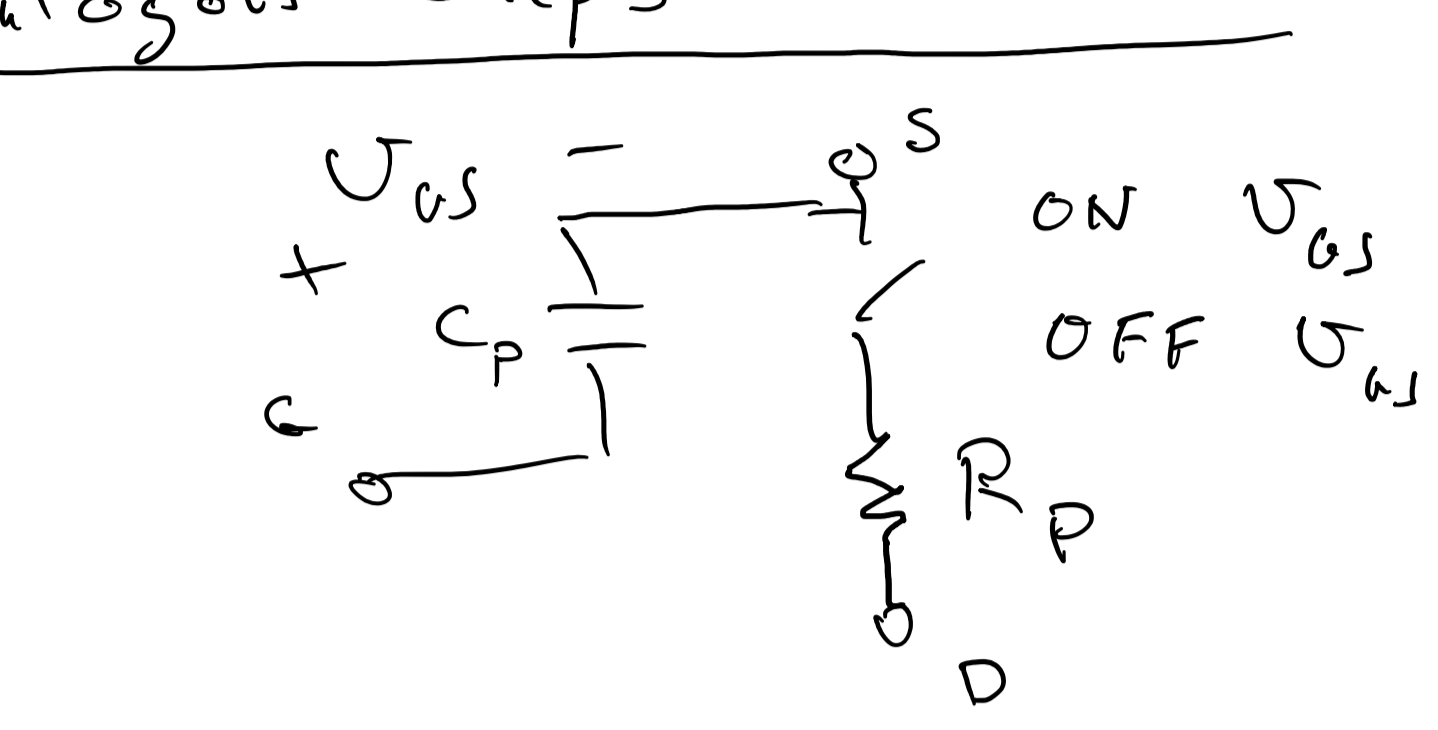
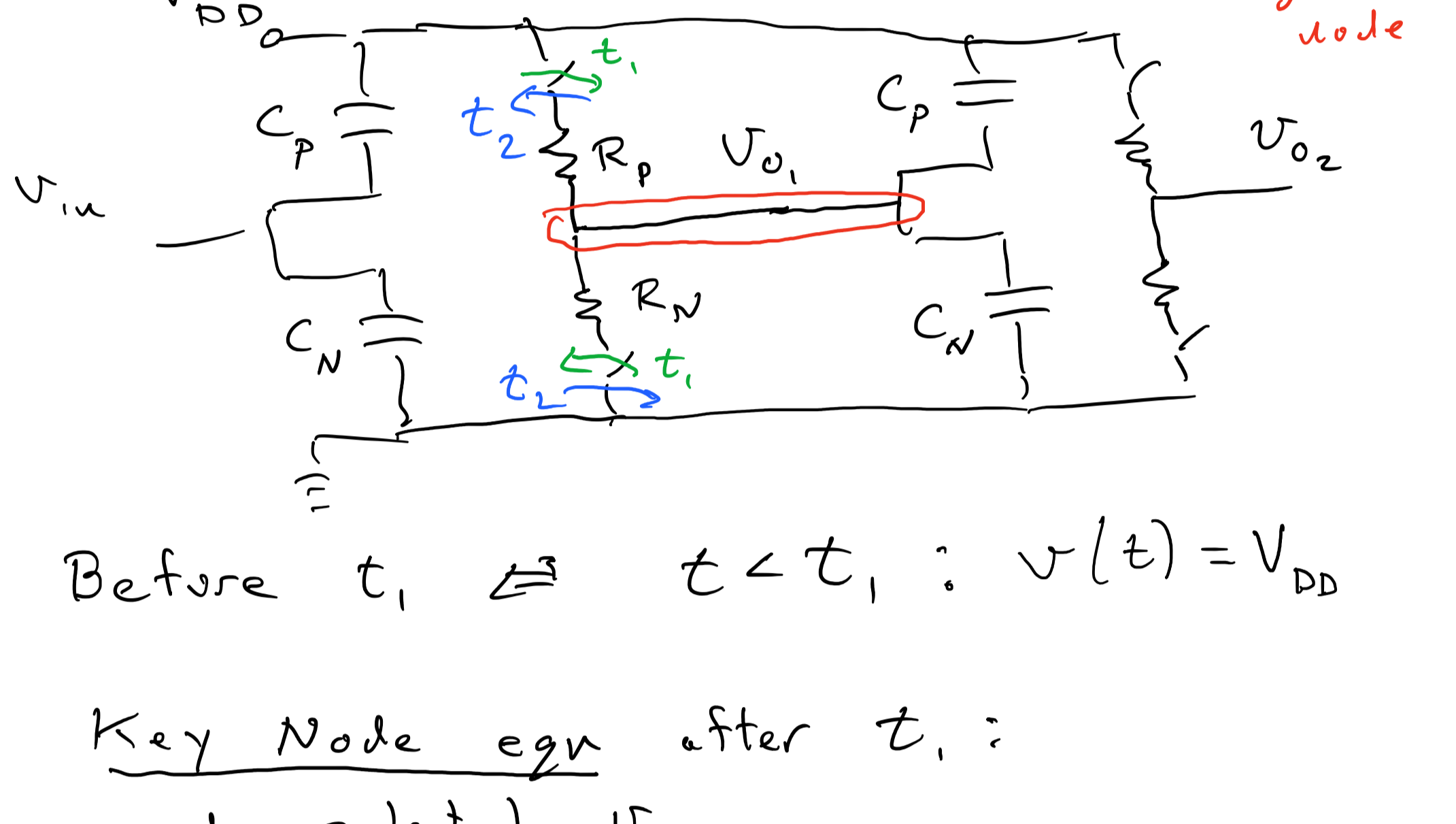


Today: model transitions between ON & OFF as occurring at $V_{GS} = \frac{1}{2} V_{DD}$

Suggests simplified model for NMOS

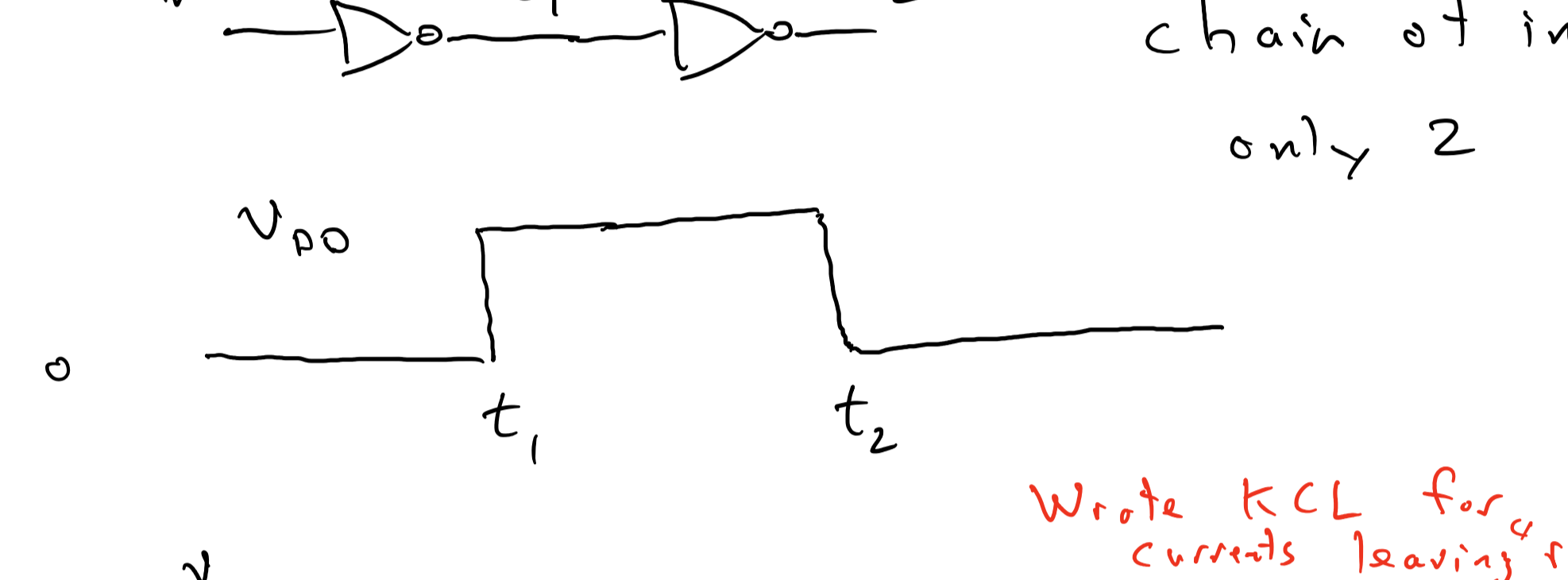

Analogous steps for PMOS

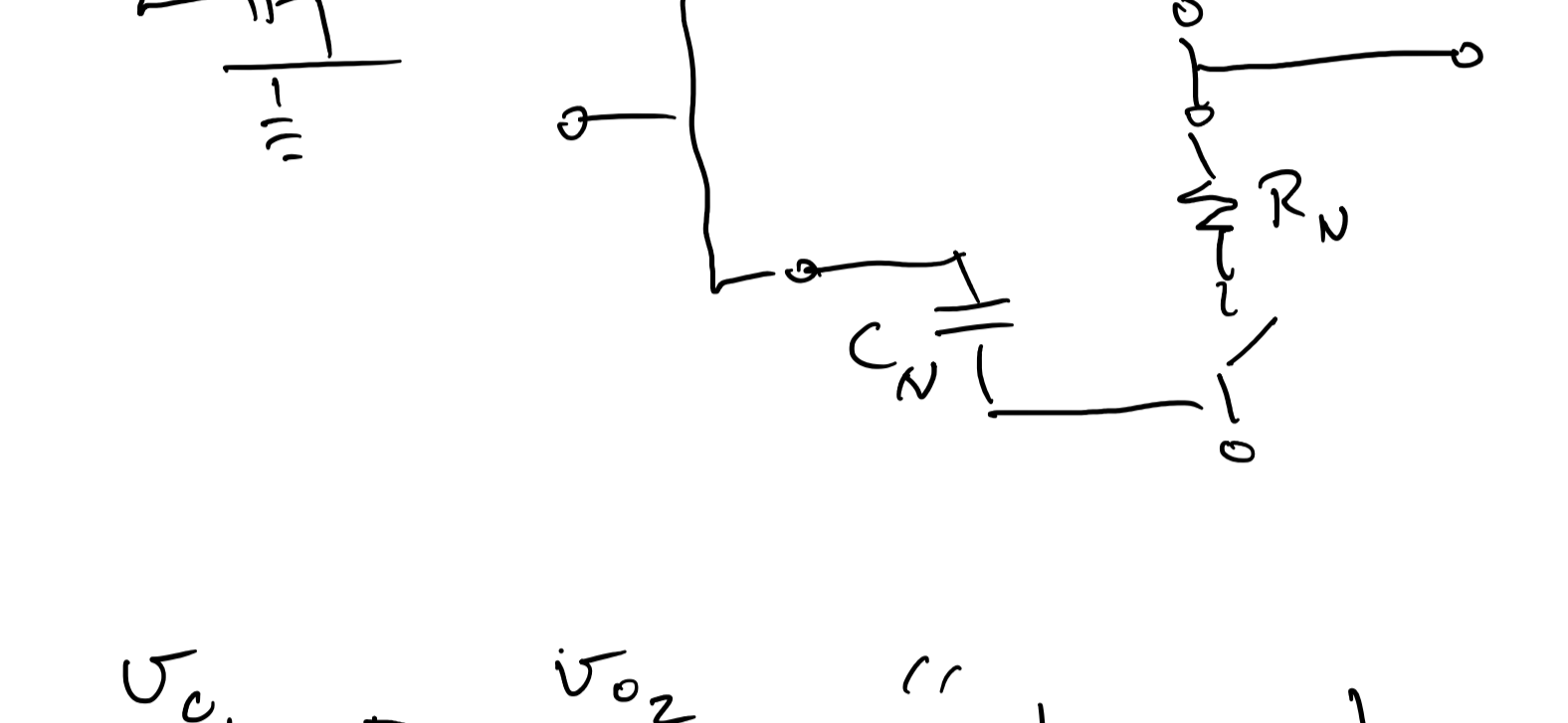

Before $t_1 \Leftrightarrow t < t_1 : v(t) = V_{DD}$

Key Node eqn after t_1 :
 node potential V_{o1}

$$(x) \frac{V_{o1}}{R_N} + C_N \frac{d}{dt} V_{o1} + C_P \frac{d}{dt} (V_{o1} - V_{DD}) = 0$$

$$\frac{d}{dt} V_{o1} + \frac{1}{R_N(C_N + C_P)} V_{o1} = 0$$

$$V_{o1}(t_1) = V_{DD}$$

$$R_N(C_N + C_P) \approx \text{time constant} = \tau$$

$$10^6 \Omega \cdot 10^{-15} F = 10^{-9} s = nS$$

state of art time constant $\approx 10 ps$

$$\frac{d}{dt} V_{o1} = -\frac{1}{\tau} V_{o1} ; V_{o1}(t_1) = V_{DD}$$

$$-\frac{1}{\tau} = \lambda \text{ "lambda"}$$

$$\boxed{\frac{d}{dt} V_{o1} = \lambda V_{o1}} ; \boxed{V_{o1}(t_1) = V_{DD}}$$

separation of variables

$$\int \frac{dV_{o1}}{V_{o1}} = \int \lambda dt \quad \text{det. integral}$$

$$V_{o1} = e^{\lambda t} \quad \checkmark$$

$$\frac{d}{dt} V_{o1} = \lambda e^{\lambda t} = \lambda V_{o1}$$

Need $V_{o1}(t_1) = V_{DD}$

$$V_{o1} = A e^{\lambda t}$$

$$\frac{d}{dt} V_{o1} = \lambda A e^{\lambda t} = \lambda V_{o1} \quad \checkmark$$

$$A = ? \Leftrightarrow V_{o1}(t_1) = V_{DD}$$

$$A e^{\lambda t_1} = A e^{\lambda t_1} = V_{DD}$$

$$A = V_{DD} e^{-\lambda t_1}$$

$$V_{o1} = V_{DD} e^{-\lambda t} \cdot e^{\lambda t_1}$$

Just solved a differential eqn

- universal and ubiquitous in science & engineering

Broad theorem [rule] says a big class of diff eqns has unique solution

$$\frac{d}{dt} x = f(x, t)$$

- (1) $\left\{ \begin{array}{l} \text{say } f(x, t) \text{ is differentiable w.r.t } x \\ \text{and } \left| \frac{\partial f}{\partial x} \right| < M \end{array} \right.$ (real #)
- (2) $\left\{ \begin{array}{l} f(x, t) \text{ has only finite \# of discontinuities} \\ \text{in } t \text{ in any unit interval } [t, t+1] \end{array} \right.$

If (1) and (2) hold, then our diff eqn has unique solution

$$\frac{d}{dt} V_{o1} = \lambda V_{o1} = f(x) \quad x = V_{o1}$$

$$\frac{\partial f}{\partial x} = \lambda$$

Structure of solution

Determined that solution was: $V_{o1} = V_{DD} e^{-\lambda(t-t_1)}$

$$\lambda = -\frac{1}{\tau} \quad \tau = R_N(C_P + C_N)$$

$$V_{o1} = V_{DD} e^{-\frac{(t-t_1)}{\tau}}$$

sketching exponentials

$$e^{-\frac{t}{\tau}}$$

$$\frac{d}{dt} e^{-\frac{t}{\tau}} = -\frac{1}{\tau} e^{-\frac{t}{\tau}}$$

$e^{\lambda t} \equiv$ eigenfunction

extend to $t=t_2$ and beyond

$$V_{o1}(t_2) = V_{DD} e^{-\frac{(t_2-t_1)}{\tau}}$$

What is relevant diff eqn for $t > t_2$

$$\frac{V_{o1} - V_{DD}}{R_P} + (C_P + C_N) \frac{d}{dt} V_{o1} = 0$$

$$\frac{d}{dt} V_{o1} + \frac{1}{R_P(C_P + C_N)} V_{o1} = \frac{V_{DD}}{R_P(C_P + C_N)}$$

time constant: " τ_p " = $R_P(C_P + C_N)$

Solution 2

$$V_{o1} = V_{DD} + (V_{o1}(t_2) - V_{DD}) e^{-\frac{(t-t_2)}{\tau_p}}$$