


$t < t_1$ and $t > t_2$

$$\frac{d}{dt} v_{o1} = -\frac{1}{R_p(C_n+C_p)} v_{o1} + \frac{V_{DD}}{R_p(C_n+C_p)}$$

$t_1 < t < t_2$

$$\frac{d}{dt} v_{o1} = -\frac{1}{R_n(C_p+C_n)} v_{o1}$$

Oscilloscope

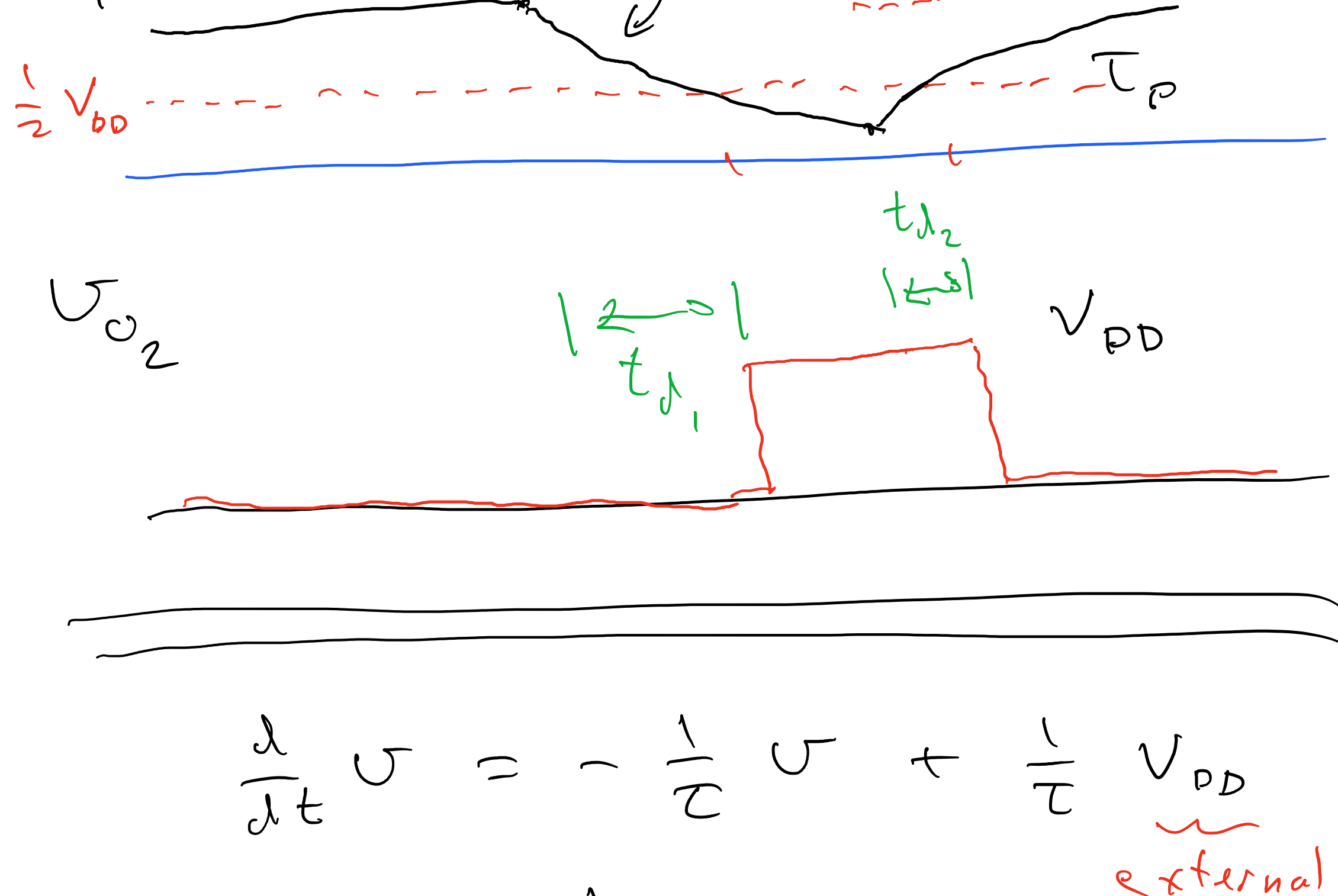

$$\frac{d}{dt} v = -\frac{1}{\tau} v + \frac{1}{\tau} V_{DD}$$

$\lambda = -\frac{1}{\tau}$ external input

Rule:

- 1st order - only variable in play, and only 1st derivative
- RHS has external input that is const.


$v(t_0) = \text{defined}$

$$v = v_{\infty} + (v(t_0) - v_{\infty}) e^{-\frac{t-t_0}{\tau}}$$

evaluate: $t = t_0$

$$v(t_0) = v_{\infty} + [v(t_0) - v_{\infty}] \cdot 1$$

Audio:

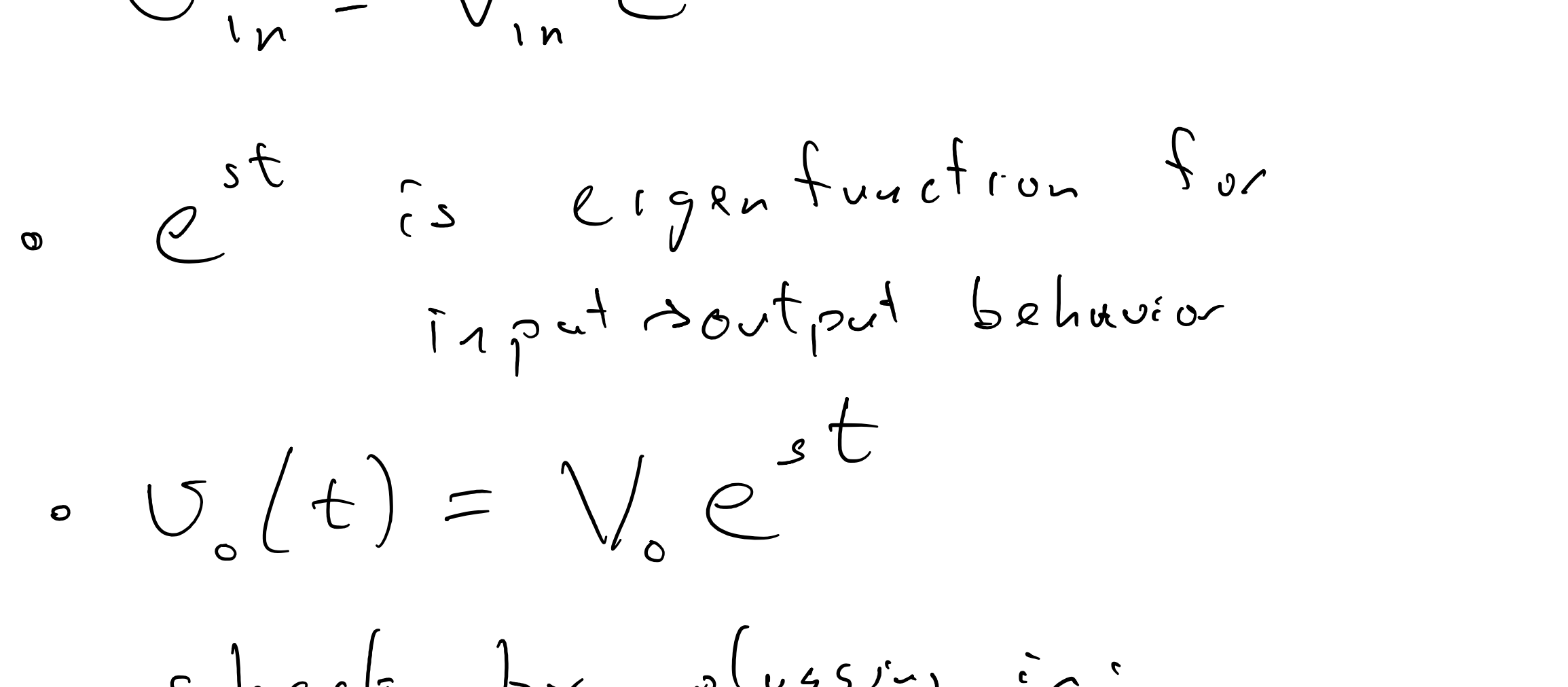

$$\frac{d}{dt} v_o = -\frac{1}{RC} v_o + \frac{1}{RC} v_{in}(t)$$

$$v_{in} = V_{in} e^{st}$$

- e^{st} is eigenfunction for input/output behavior
- $v_o(t) = V_o e^{st}$

check by plugging in:

LHS: $\frac{d}{dt} v_o = \frac{d}{dt} V_o e^{st} = s V_o e^{st}$

$$s V_o e^{st} = -\frac{1}{RC} V_o e^{st} + \frac{1}{RC} V_{in} e^{st}$$

$$s V_o + \frac{1}{RC} V_o = \frac{1}{RC} V_{in}$$

$$V_o = \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}} \cdot V_{in}$$

$$\lambda = -\frac{1}{RC} \text{ (plus in)}$$

$$V_o = \frac{1}{1 - \frac{s}{\lambda}} V_{in}$$

$$v_o(t) = V_o e^{st} = \frac{1}{1 - \frac{s}{\lambda}} V_{in} e^{st}$$

Solution for initial condition at time $t=0$

$$v_o \Big|_{t=0} = V_i$$

Total actual solution

$$v_o(t) = A e^{-\frac{t}{RC}} + \frac{1}{RC} \frac{V_{in} e^{st}}{s + \frac{1}{RC}}$$

re-evaluate at $t=0$

$$V_i = A + \frac{1}{RC} \frac{V_{in}}{s + \frac{1}{RC}}$$

$$A = V_i - \frac{1}{RC} \frac{V_{in}}{s + \frac{1}{RC}}$$

General Structure of Solution to Diff Eqns.

$$v(t) = v_{homogeneous}(t) + v_{particular}(t)$$

For exponential input, particular solution is also exponential with same e^{st}

"Most General" $u(t)$

$$\frac{d}{dt} x(t) = \lambda x(t) + u(t); \quad x(t_0) = x_0$$

Solution "guess"

$$x(t) = e^{\lambda(t-t_0)} x_0 + \int_{t_0}^t e^{\lambda(t-\tau)} u(\tau) d\tau$$

Check: At $t=t_0$, what is value

1st term $\Rightarrow x_0$

2nd term $\Rightarrow 0$

$$\frac{d}{dt} x(t) = \lambda e^{\lambda(t-t_0)} x_0 + \int_{t_0}^t \lambda e^{\lambda(t-\tau)} u(\tau) d\tau$$

b.c. of integral $\lambda x(t)$

$$v_{in}(t) = V_{in} \cos(\omega t)$$

$$v_o = V_o \cos(\omega t + \phi)$$