

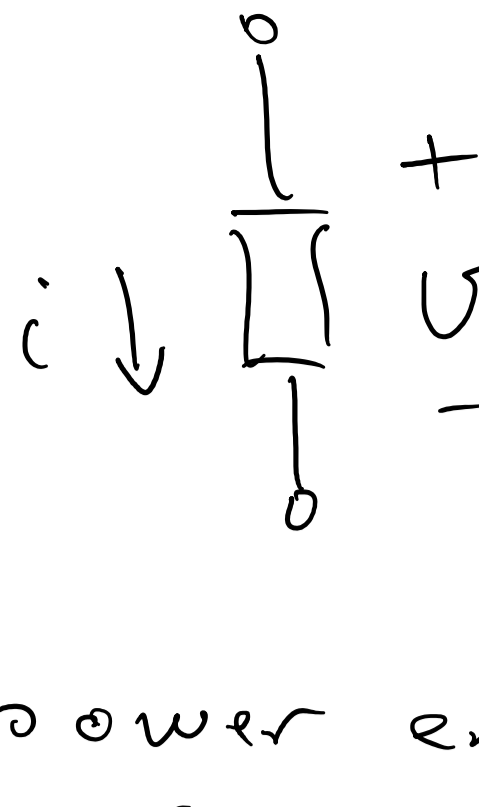


Element

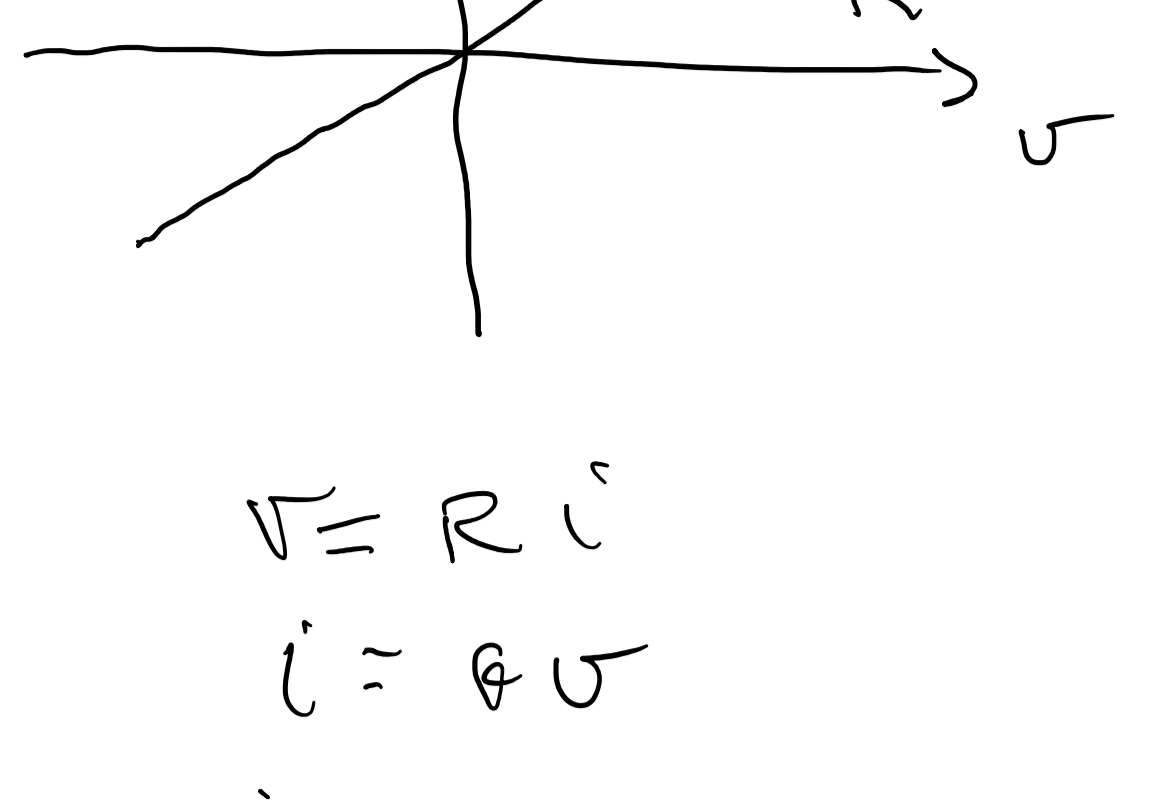



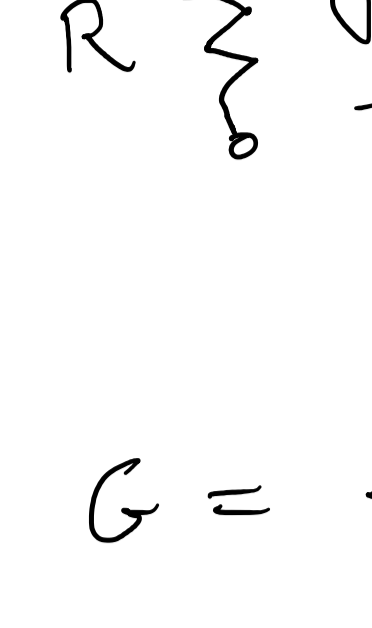
$v \cdot i = \text{power entering device}$







$G = \frac{1}{R}$

$v = Ri$


$i = \frac{1}{R}v$

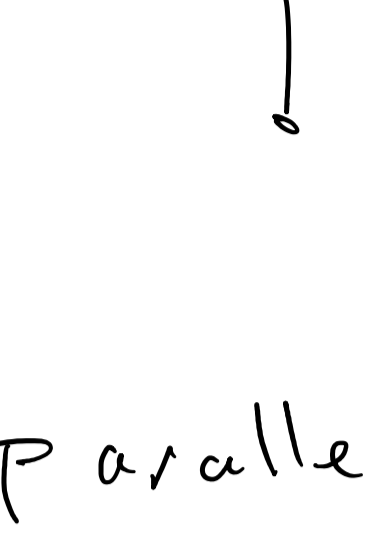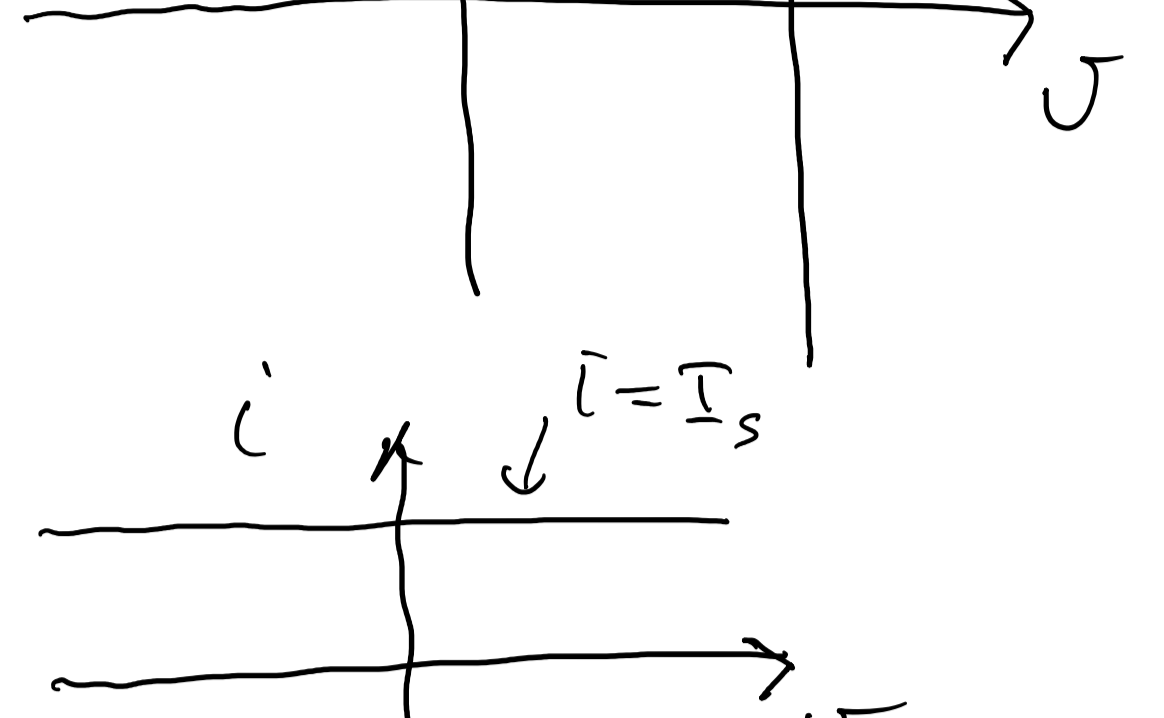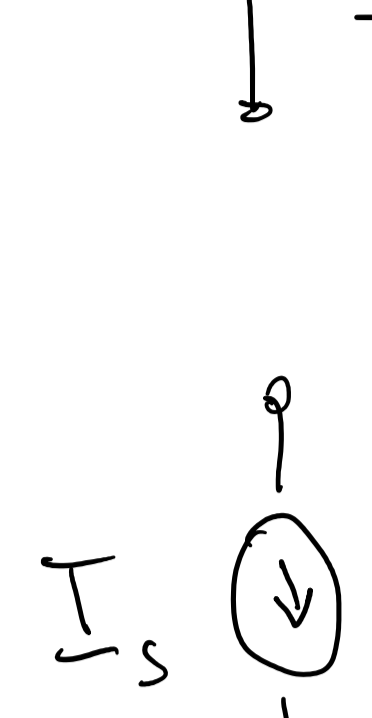

Parallel elements

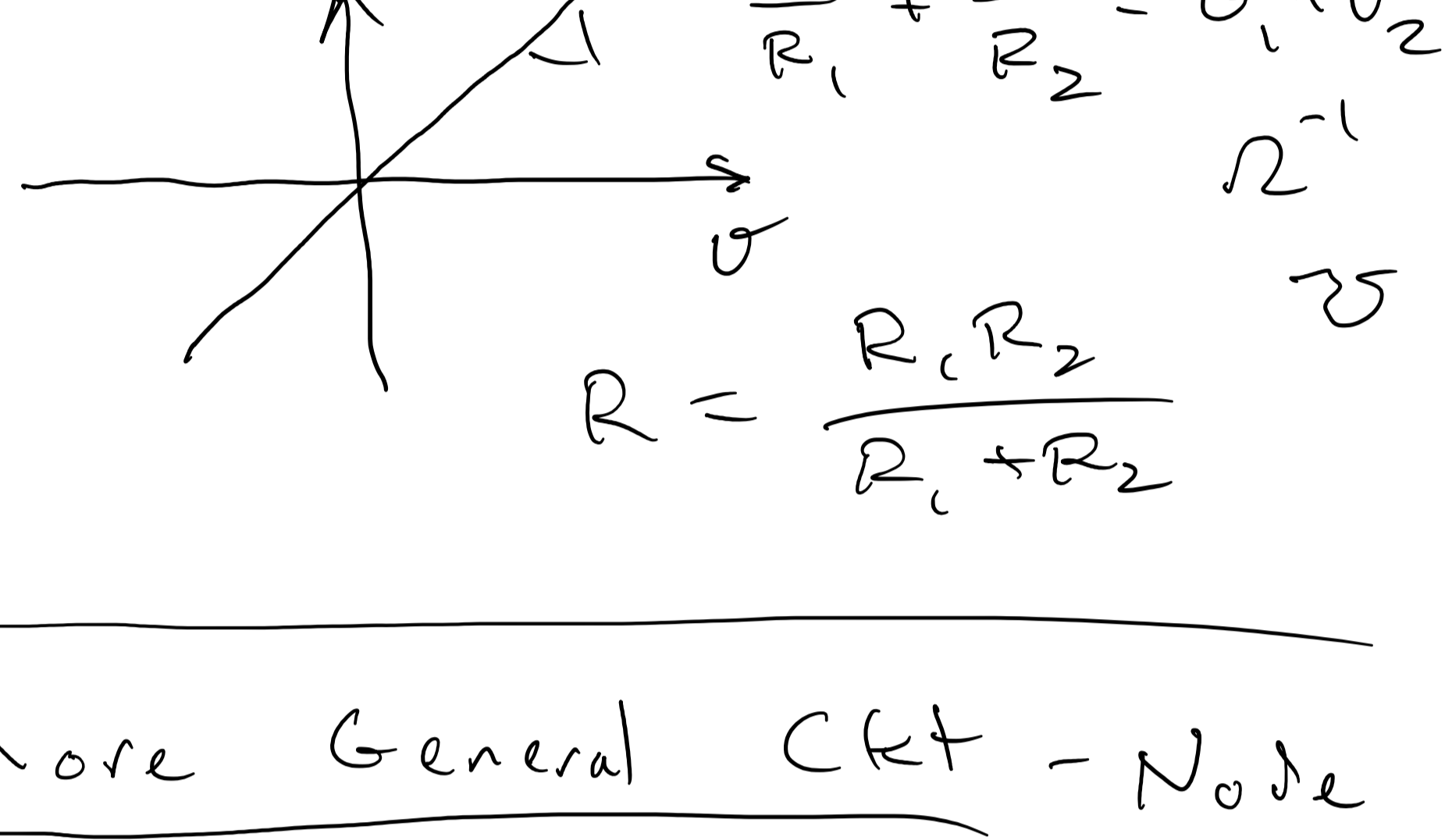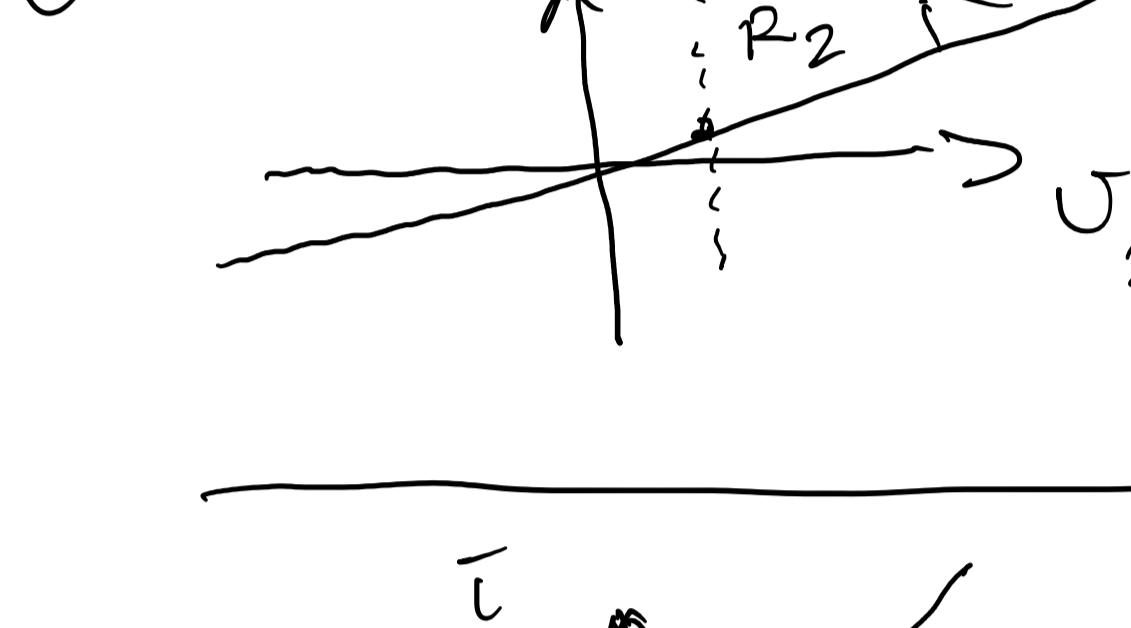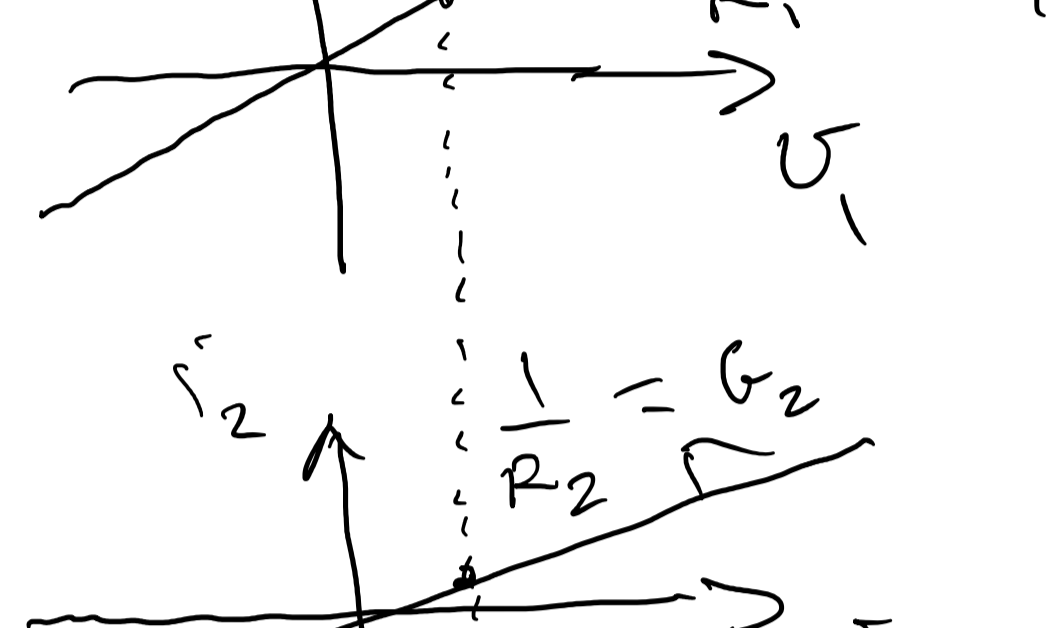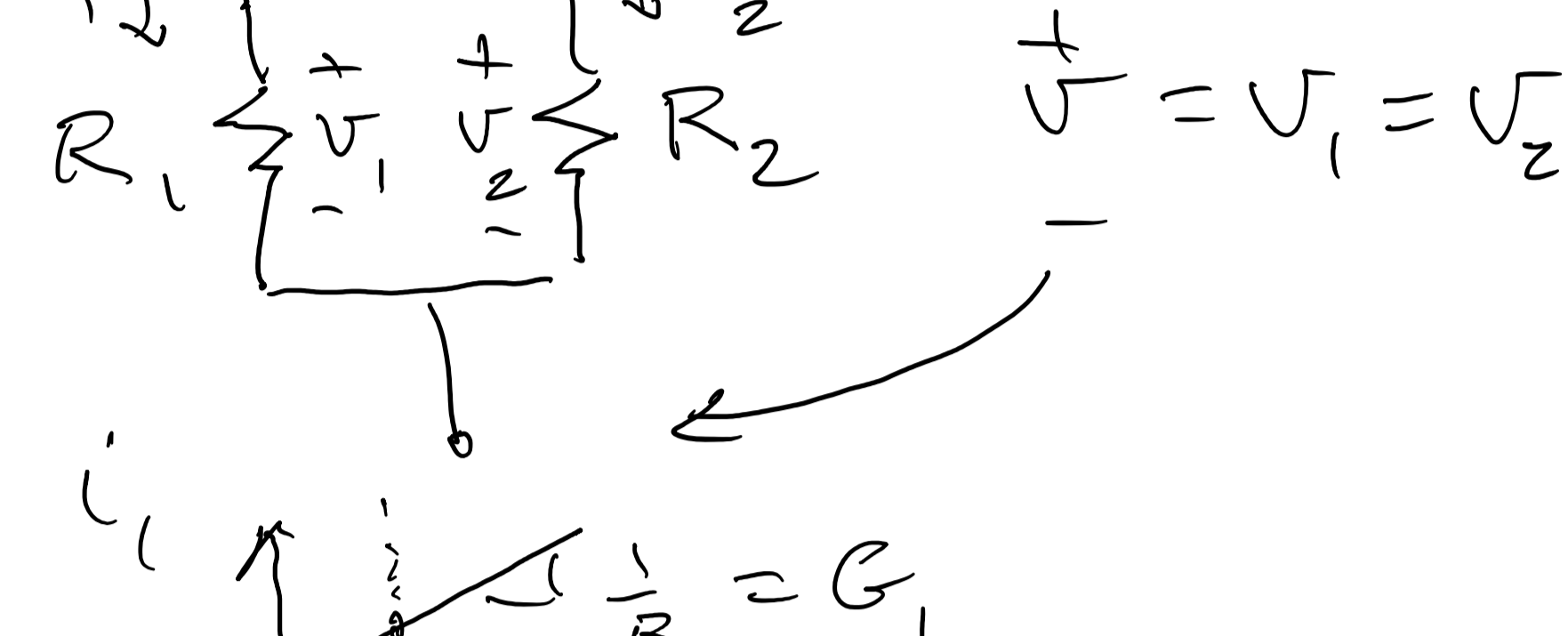

More General CKT - Node Analysis

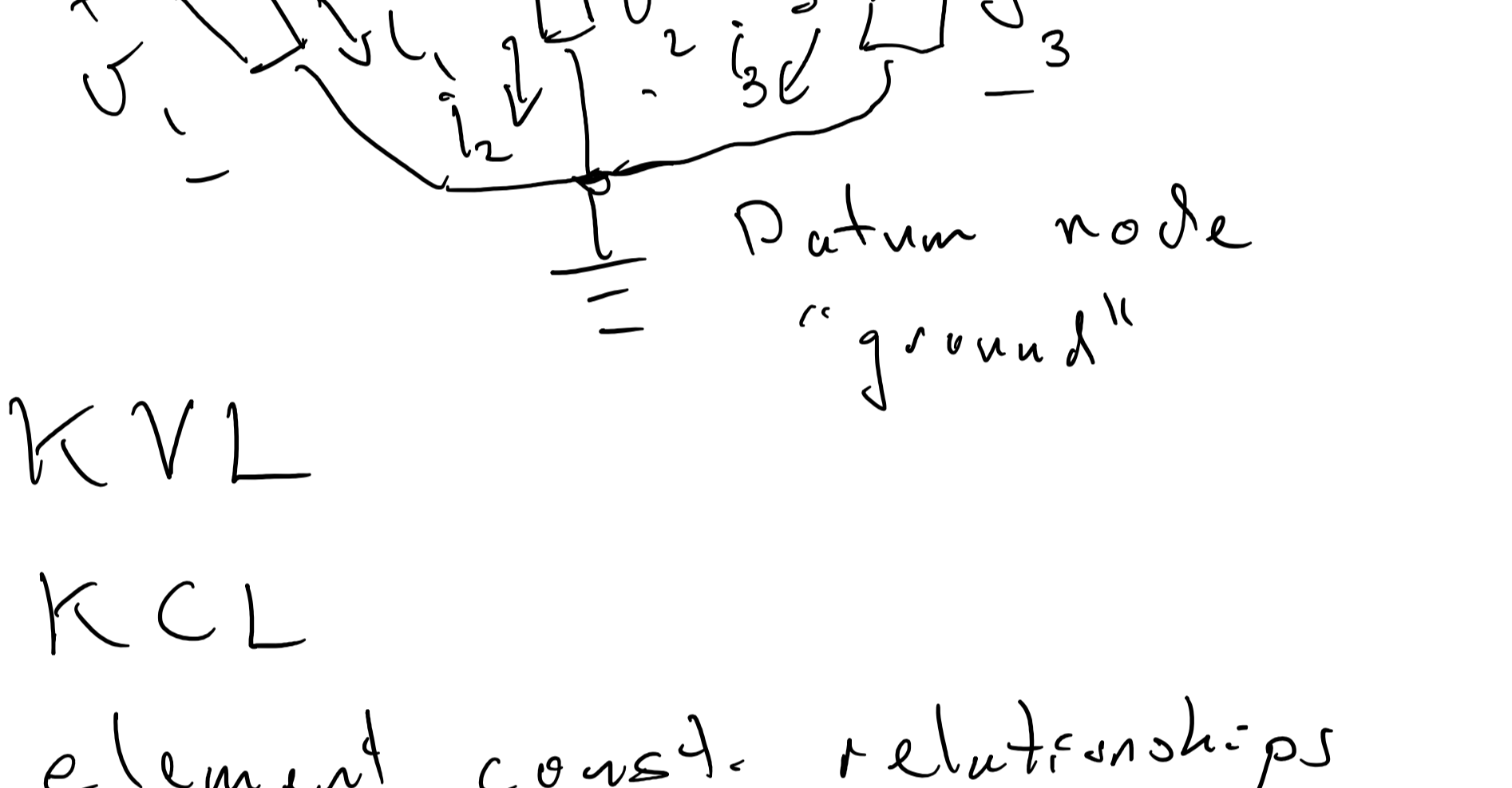

KVL

KCL

element const. relationships


Know  $e_1, e_2, e_3 \Rightarrow$  know all br voltages

Node eq's  $\Leftrightarrow$  KCL

Write sum of currents leaving each node

- ①  $i_1 - i_4 = 0$
- ②  $i_2 + i_4 - i_5 = 0$
- ③  $i_3 + i_5 = 0$
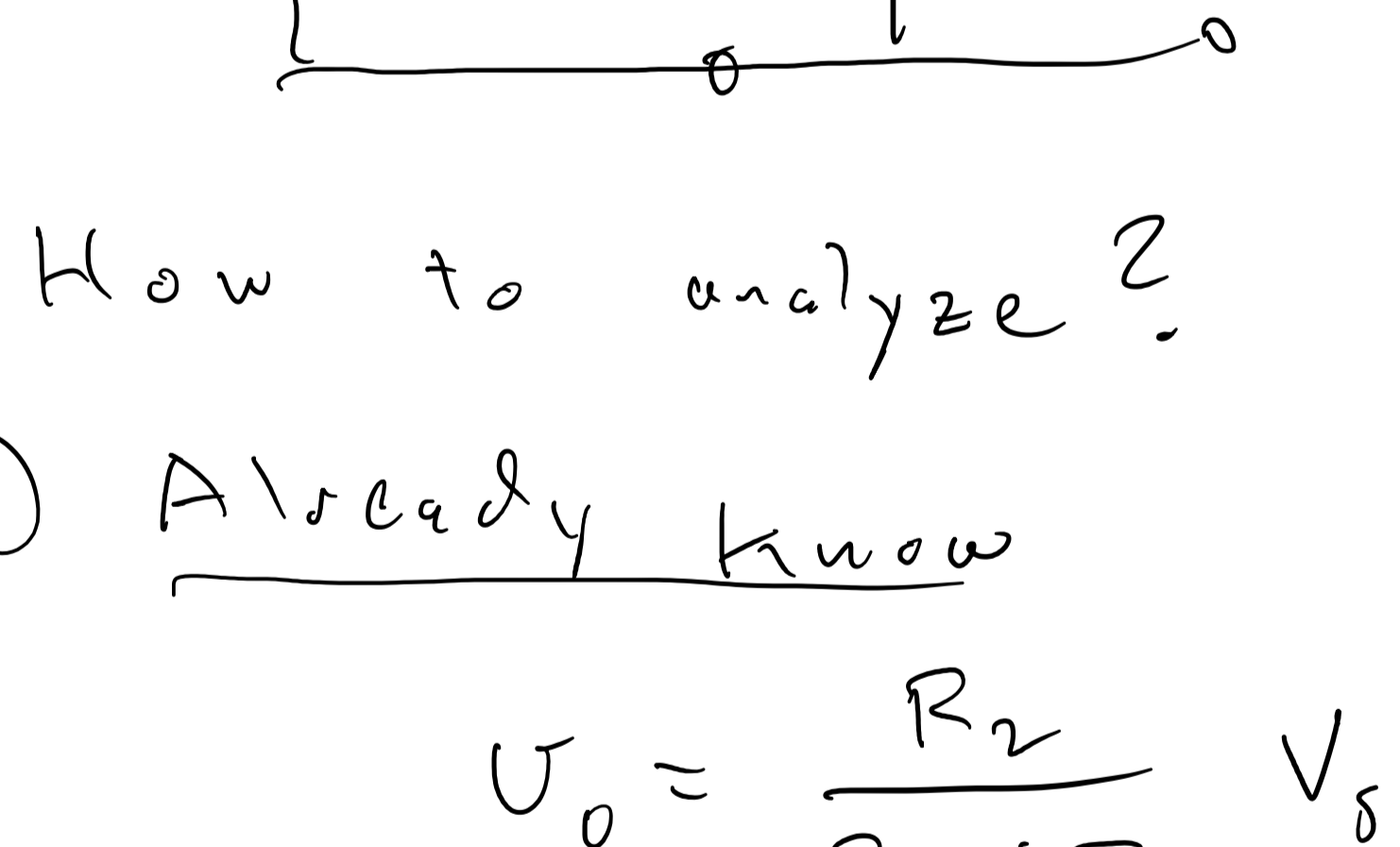
$$\begin{bmatrix} \dots \\ \dots \\ \dots \end{bmatrix} \begin{bmatrix} \dots \\ \dots \\ \dots \end{bmatrix} = 0$$




How to analyze?

① Already know

$$v_0 = \frac{R_2}{R_1 + R_2} v_s$$

② Norton / Thev eq.

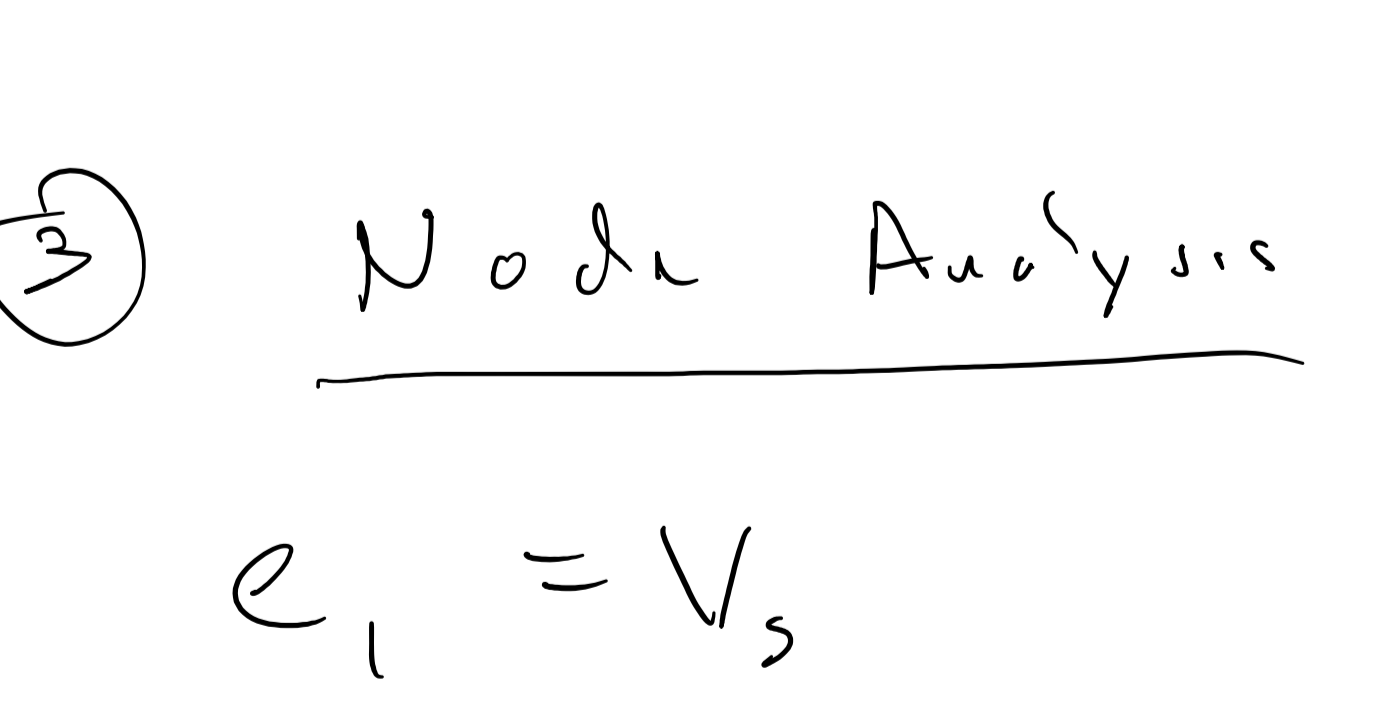

$$v_0 = \frac{v_s}{R_1} \cdot \frac{R_1 R_2}{R_1 + R_2} = \dots$$

③ Node Analysis

$e_1 = v_s$

1 node eqn:

$$\frac{e_2}{R_2} + \frac{-v_s + e_2}{R_1} = 0$$

$e_2 = \dots$  ✓

$v_0 = e_2$

Eigenvalues:  $\leftarrow$  eigenwert / self-value

"self"

$A\vec{v} = \lambda\vec{v} \Rightarrow A\vec{v} - \lambda\vec{v} = 0$

$(A - \lambda I)\vec{v} = 0$

For  $\lambda$  to be an evector  $A - \lambda I$  must have a nontrivial null space, i.e.,  $\det(A - \lambda I) = 0$

$A = \begin{bmatrix} 2 & 1 \\ 0 & 3 \end{bmatrix}$   $\lambda_1 = 2, \lambda_2 = 3$

Show this and find  $\vec{v}_1$  and  $\vec{v}_2$ .