

Lecture 1

- Today:
- * EECS 16B intro
 - * Logistics
 - + Zoom proctoring all exams
 - + Lecture zoom organization (chat and Q&A)
 - + website: eeecs16b.org
 - + STEM Program, DSP
 - * EECS 16A review
 - * Thevenin & Norton Equivalents
 - * Intro to transistors

Key circuit elements:

① Wire

$$\begin{array}{c} + \\ \downarrow I_{el} \\ \text{Vel} \\ - \end{array}$$

$$\text{Vel} = 0$$

$$I_{el} = ?$$

set by ext. ckt

② Resistor

$$\begin{array}{c} + \\ \downarrow I_{el} \\ \text{Vel} \\ - \end{array} \quad R$$

$$\text{Vel} = R \cdot I_{el}$$

(Ohm's law)

③ "Open" circuit


$$\begin{array}{c} + \\ \downarrow I_{el} \\ \text{Vel} \\ - \end{array}$$

$$I_{el} = 0$$

$$\text{Vel} = ?$$


set by the ext. ckt

④ Capacitor

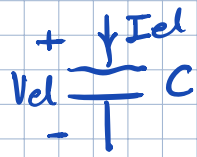


$$Q_{el} = C \cdot V_{el}$$

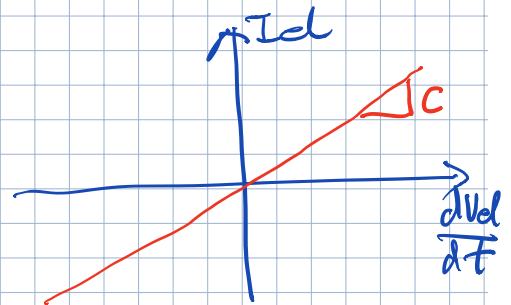know: $I_{el} = \frac{dQ_{el}}{dt} = \int C \frac{dV_{el}}{dt}$
 $C = \text{const in time}$



⑤ Voltage source

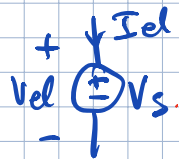


$$V_{el} = V_s$$

$I_{el} = ?$
 set by ext. circ.




⑥ Current source

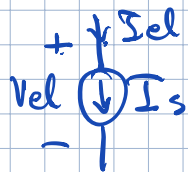


$$I_{el} = I_s$$

$$V_{el} = ?$$

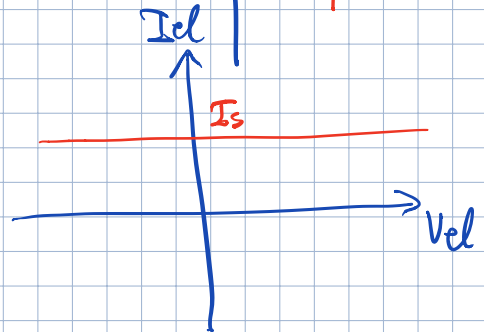

Passive sign convention:

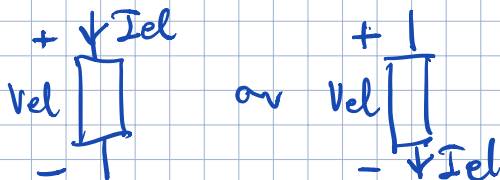


KCL:



$$I_{el1} + I_{el2} - I_{el3} = 0$$

$$I_{el1} + I_{el2} = I_{el3}$$

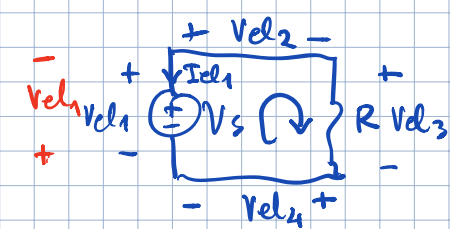KVL: Sum of voltages around the loop is 0.



$$V_{el1} - V_{el2} - V_{el3} - V_{el4} = 0$$


$$V_{el1} = V_{el3}$$

$$-V_{el1} - V_{el2} - V_{el3} - V_{el4} = 0$$



$$-V_{el1} = V_{el3}$$

Op-amp element:

Symbol:

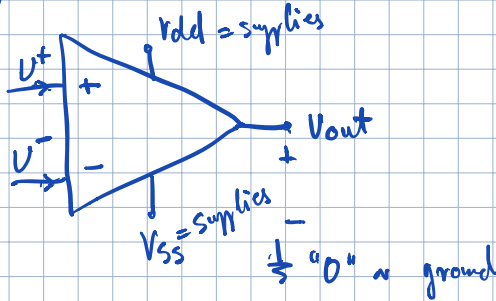

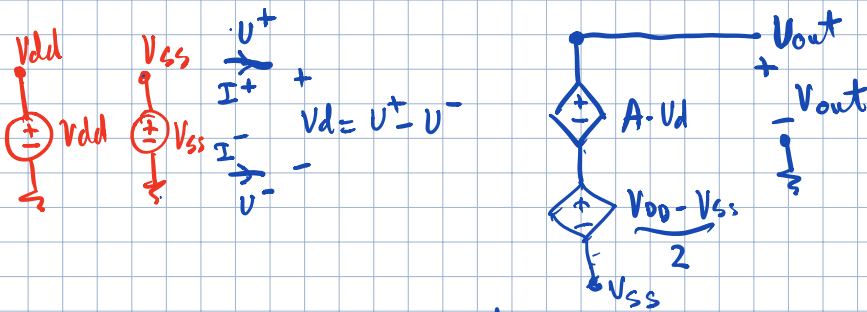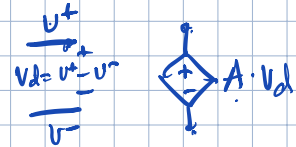New element:
voltage-controlled
voltage source




$$V_{out} = \begin{cases} V_{ss} + \frac{V_{dd} - V_{ss}}{2} + A \cdot V_d & , V_{ss} \leq V^* \leq V_{dd} \\ V_{ss} & , V^* < V_{ss} \\ V_{dd} & , V^* > V_{dd} \end{cases}$$

Negative feedback:


Golden rules:

GR1: $I^+ = I^- = 0$

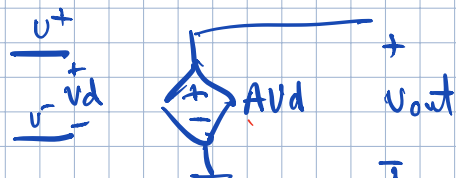


GR2: $V^+ = V^-$ (only when NFB & $A \rightarrow \infty$) \Rightarrow

NFB example: Inverting amplifier

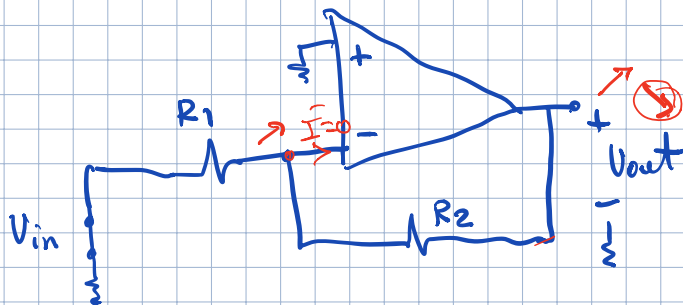

Test NFB:

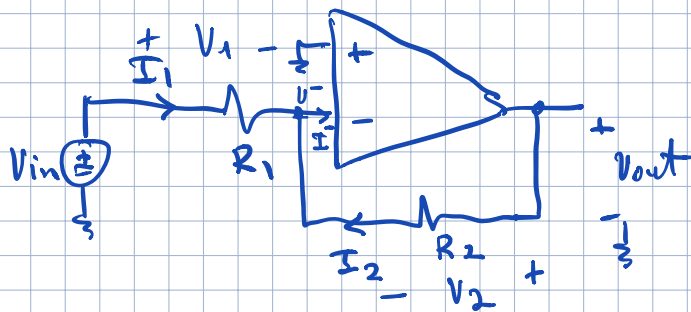- ① Null indep. sources
- ② Apply a change at the output
- ③ Trace the feedback back to the output & verify that the change is cancelled



$$V_{out} = f(V_{in}) = ?$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

KCL: $I_1 + I_2 - I^- = 0$

GR1: $I^- = 0$

$$I_1 + I_2 = 0$$

NFB \rightarrow GR2: $V^+ = V^-$

$$V^+ = 0 \Rightarrow V^- = 0$$



Ohm's Law: $I_1 = \frac{V_1}{R_1} = \frac{V_{in} - 0}{R_1} = \frac{V_{in}}{R_1}$

$$I_2 = \frac{V_2}{R_2} = \frac{V_{out} - 0}{R_2} = \frac{V_{out}}{R_2}$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$



Equivalence:

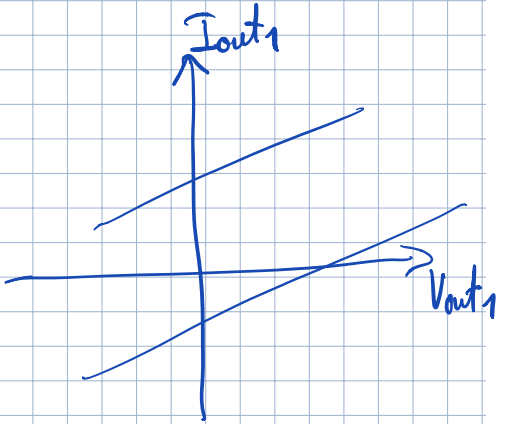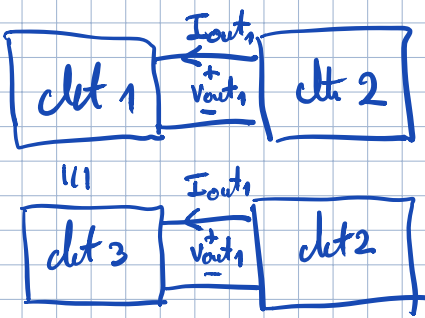

In ccts, two elements are equivalent if they have the same I-V characteristics.

Need a min of two elements (a resistor and a source) to create any I-V line.


Thevenin equivalent:

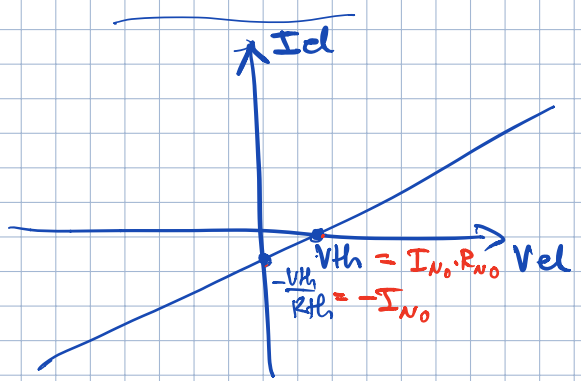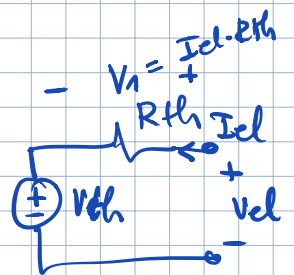

$$V_{in} = V_{th} + I_{in} \cdot R_{th}$$

$$I_{in} = \frac{V_{in} - V_{th}}{R_{th}}$$

Norton equivalent:

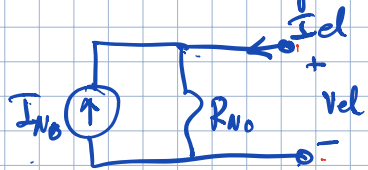

To find V_{th} :

"Connect" an "open-circuit" across terminals and measure $V_{open-circuit} = V_{th}$.

To find R_{th} :

zero-out ("null") indep. sources, and then apply V_{test} and measure I_{test} or apply I_{test} and measure V_{test}

$$R_{th} = \frac{V_{test}}{I_{test}}$$