

EECS 16A Review

Spm Mon

Prof. Renshaw


Lecture 4

EECS 16B


* Recap

* Filter response to cas wt

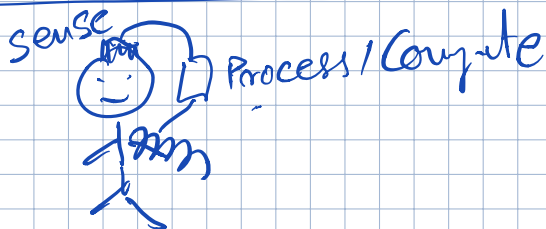* Start 2nd order diff eqns (z-c filters)







Computing: Simple model (Cascade of inv)

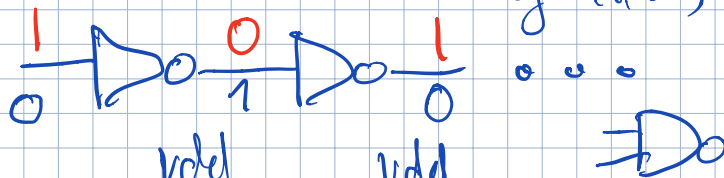


"1" = V_{dd}

"0" = 0V

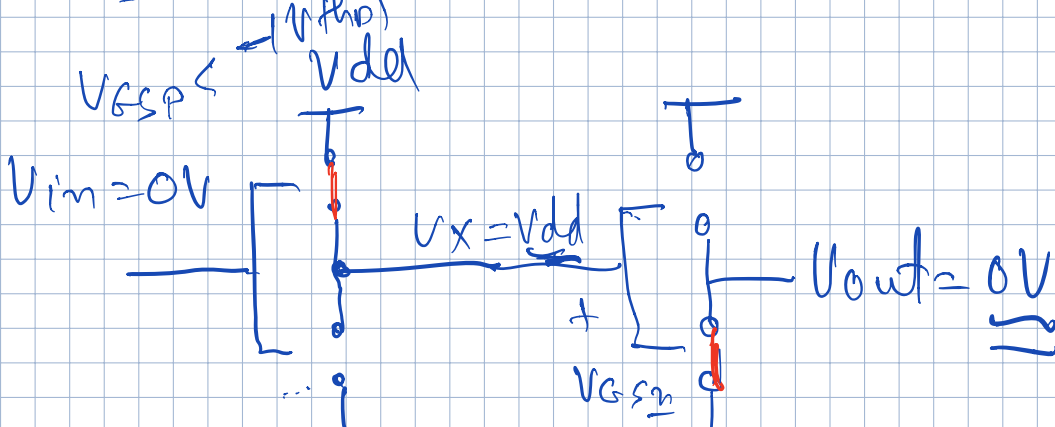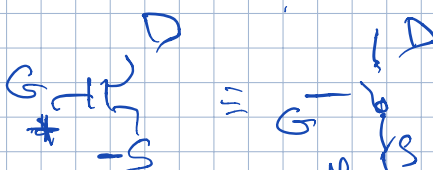
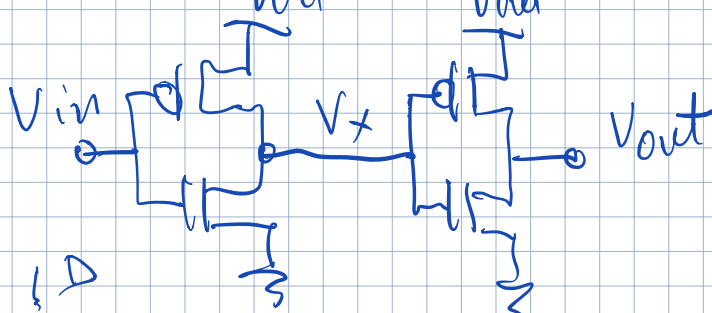


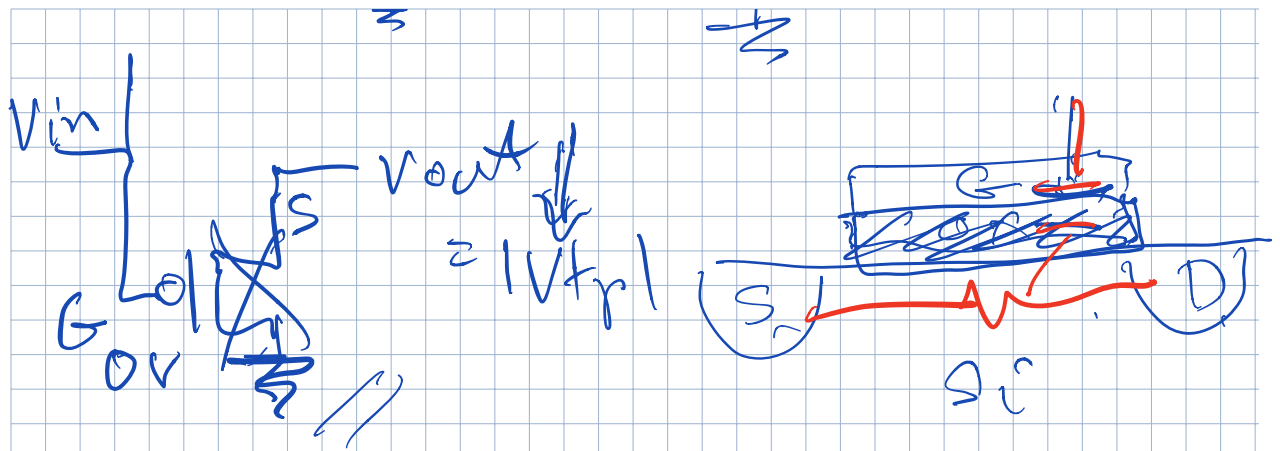


$$V_{GSp} \leq -|V_{Tp1}|$$

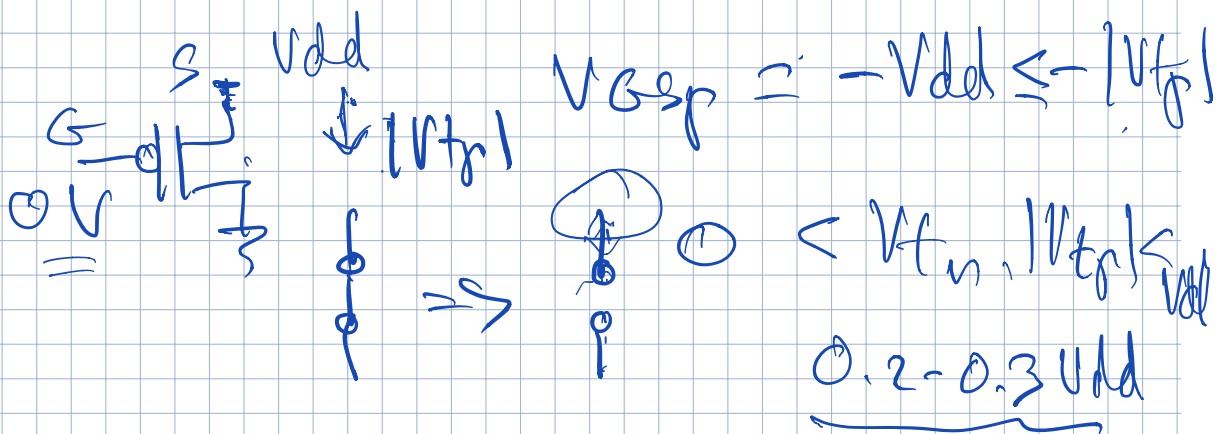

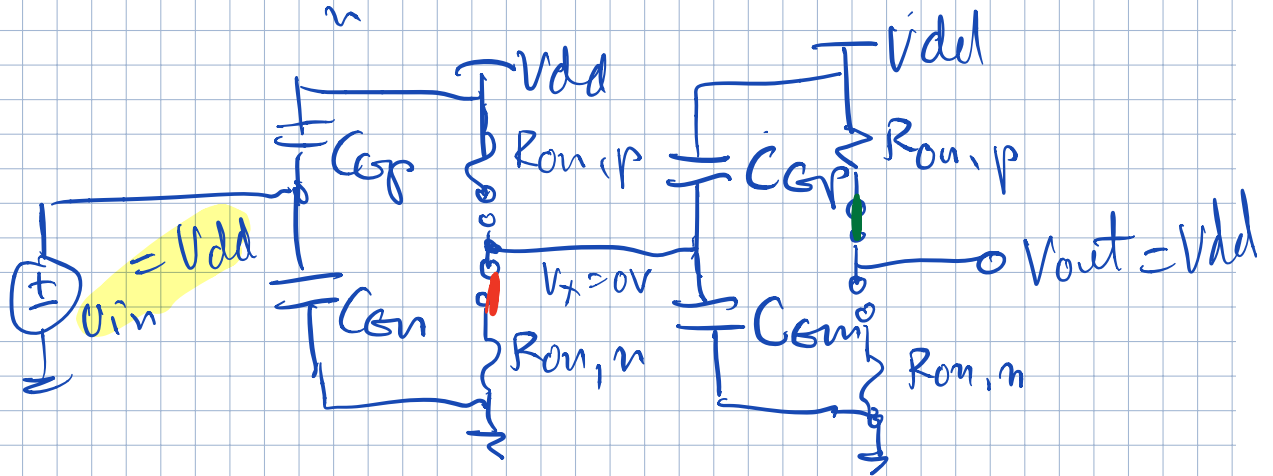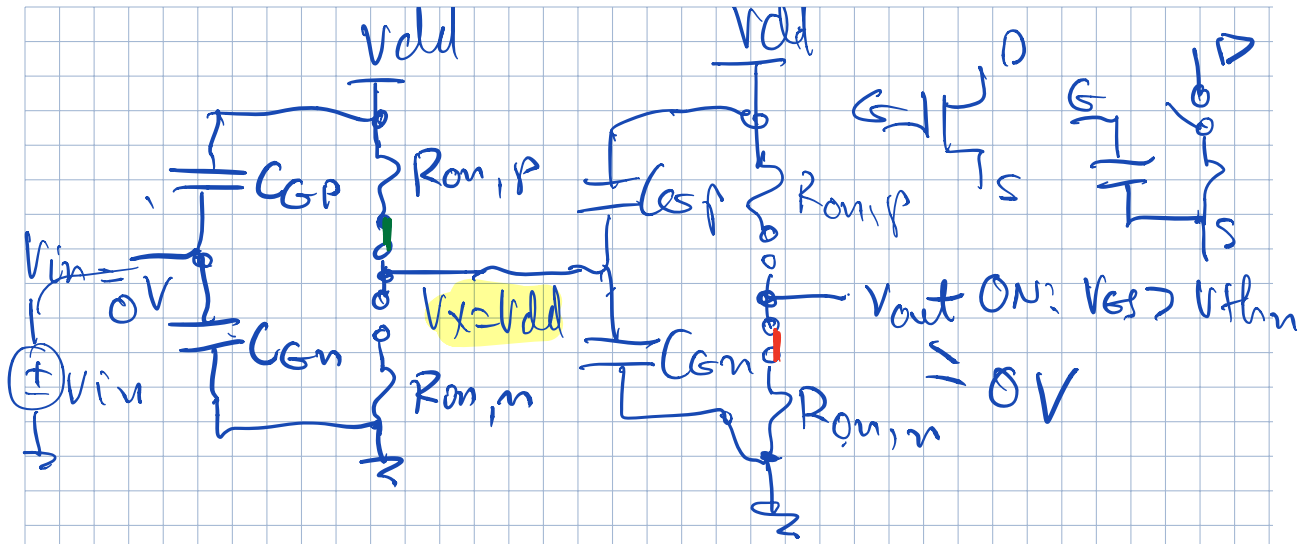How fast can compute work?
 Need a better model.



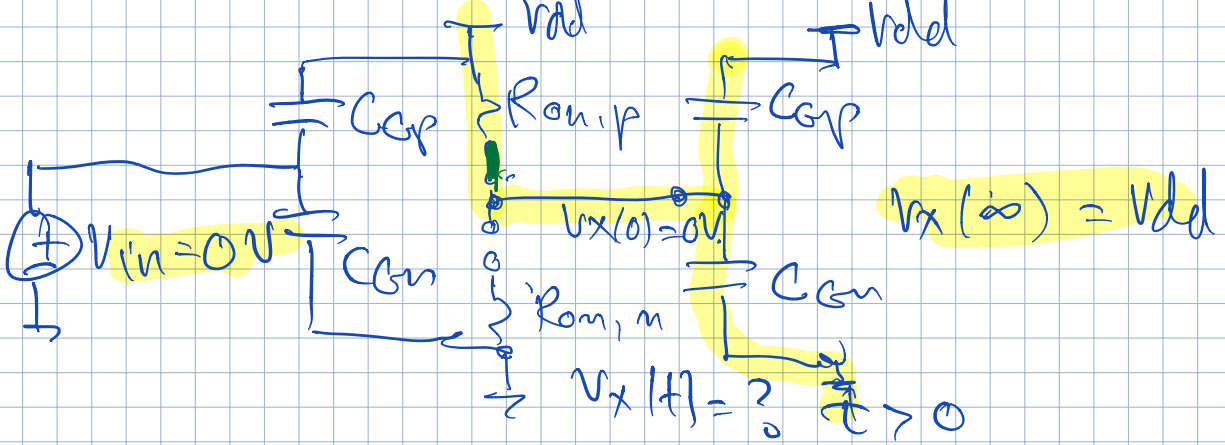$t = 0 \quad V_{in} = V_{dd} \rightarrow 0V$




solve to get $V(x)$

Saw:
$$\frac{dV_x^c}{dt} = -\frac{V_x}{R_{on,p}(C_{ent} + C_{op})} + \frac{v_{dd}}{R_{on,p}(C_{ent} + C_{op})}$$

used a change of variables to

solve:
$$\tilde{V}_x = V_x - v_{dd} \quad (v_{dd} \frac{d}{dt} v_{dd} = 0)$$
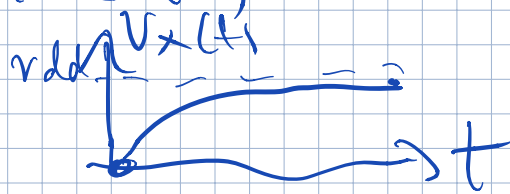
$$V_x(t) = v_{dd} (1 - e^{-\frac{t}{\tau}})$$




Any RC circuit

can be solved like this -

not just logic.



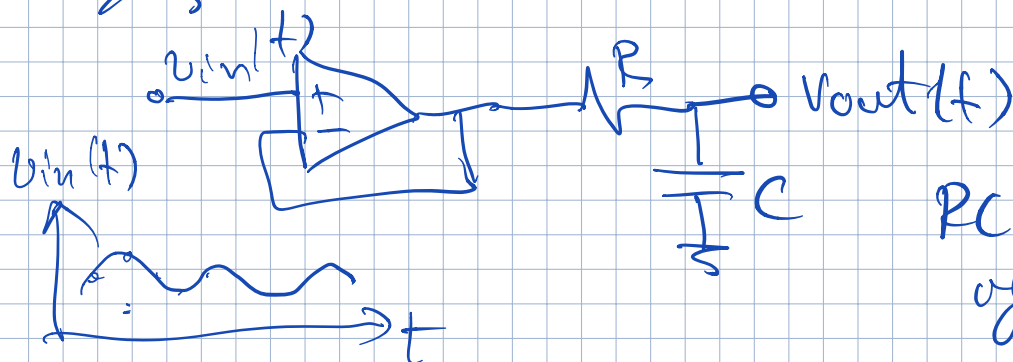
want to design a ckt's filter to remove unwanted signals.



RC circuit again!

solving:
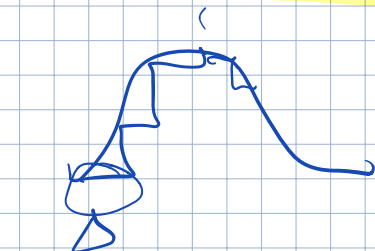
$$\frac{d}{dt} V_{out}(t) = -\frac{V_{out}(t)}{RC} + \frac{V_{in}(t)}{RC}$$



solution:

$$V_{out}(t) = \underbrace{V_{in}(0) \cdot e^{-\frac{t}{RC}}}_{\text{homogeneous (response to init. condition)}} + \underbrace{\frac{1}{RC} \int_0^t V_{in}(\theta) \cdot e^{-\frac{t-\theta}{RC}} d\theta}_{\text{response to input}}$$

↑
contin.

Let's see how this responds to different input signals:

e.g. $V_{in}(t) = RC \cos(\omega t)$?

To simplify:

$$\frac{d}{dt} x(t) = \lambda x(t) + u(t)$$

$$u(t) = \cos \omega t$$

Why pick a cos art?

AC power, RF (cell-phere) $\sim \underline{\underline{\cos \omega t}}$

$$x(t) = x(0) \cdot e^{\lambda t} + \int_0^t \underbrace{\cos(\omega \theta)}_{u(\theta)} \cdot e^{\lambda(t-\theta)} d\theta$$

$$= x(0) e^{\lambda t} + e^{\lambda t} \cdot \int_0^t \cos(\omega \theta) \cdot e^{-\lambda \theta} d\theta$$

$$\int \cos bx e^{ax} dx = \frac{e^{ax}}{a^2 + b^2} (b \sin bx + a \cos bx)$$

$$x(t) = x(0) \cdot e^{\lambda t} + \frac{\lambda e^{\lambda t}}{\lambda^2 + \omega^2} + \frac{\omega \sin(\omega t) - \lambda \cos(\omega t)}{\lambda^2 + \omega^2}$$

$t \rightarrow \infty$ (steady-state)

① $\rightarrow 0$ b/c $\lambda = -\frac{1}{RC}$

② $\rightarrow 0$ — u —

$$\textcircled{3} \quad \frac{\omega \sin(\omega t) - \lambda \cos(\omega t)}{\lambda^2 + \omega^2}$$

$$\lambda = -\frac{1}{RC}$$

$$x(t) = \frac{\omega \sin(\omega t) + \frac{1}{RC} \cos(\omega t)}{\left(\frac{1}{RC}\right)^2 + \omega^2} =$$

$$= \frac{RC (RC \omega \sin(\omega t) + \cos(\omega t))}{1 + (RC)^2 \omega^2}$$

$$\textcircled{1} \quad \omega \gg \frac{1}{RC} \Rightarrow \omega RC \gg 1$$

$$x(t) \approx 0$$

$$\textcircled{2} \quad \omega \ll \frac{1}{RC} \Rightarrow \omega RC \ll 1$$

$$x(t) \approx RC \cos(\omega t + \theta)$$


$$\theta = -\tan^{-1}(\omega RC)$$

From (1) and (2)

we see that the circuit is
a "low-pass" filter

since it passes frequencies
lower than $\frac{1}{RC}$.

Simplest two-capacitor example:

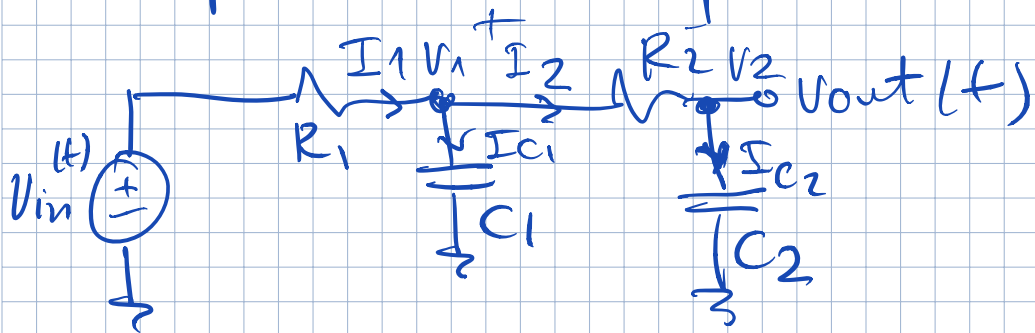

$$\rightarrow v_{out} = v_1 - I_2 \cdot R_2$$

$$I_{C2} = C \frac{dv_2}{dt} \quad , \quad I_2 = I_{C2}$$

$$I_1 = I_2 + I_{C1} = C_2 \frac{dv_2}{dt} + C_1 \frac{dv_1}{dt}$$

$$v_{in} - I_1 R_1 = v_1$$

$$\textcircled{1} \quad \frac{v_{in} - v_1}{R_1} = C_2 \frac{dv_2}{dt} + C_1 \frac{dv_1}{dt}$$

$$\textcircled{2} \quad \frac{v_1 - v_2}{R_2} = C_2 \frac{dv_2}{dt} \Rightarrow$$

$$\Rightarrow v_1 = v_2 + R_2 C_2 \frac{dv_2}{dt}$$

$$R_1 C_1 R_2 C_2 \frac{d^2 v_2}{dt^2} + (R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{dv_2}{dt}$$

$$+ v_2 - v_{in} = 0$$

(2nd order diff. eqn).

$$\frac{v_{in} - v_1}{R_1} = C_1 \frac{dv_1}{dt} + \frac{v_1 - v_2}{R_2}$$

$$\frac{v_1 - v_2}{R_2} = C_2 \frac{dv_2}{dt}$$

$$\frac{dv_1}{dt} = - \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} \right) v_1 + \frac{v_2}{R_2 C_1} + \frac{v_{in}}{R_1 C_1}$$

$$\frac{dv_2}{dt} = \frac{1}{R_2 C_2} v_1 - \frac{1}{R_2 C_2} v_2$$