

Lecture 7

EECS 16B

- * Intro to inductors
- * 2nd order systems with complex eigenvalues

Lab-life sections - just like HW party!
 Join us and be done with the lab in 3 hrs!

Capacitor

$$C \frac{V}{I} \begin{matrix} + \\ - \end{matrix} V$$

$$I(t) = C \frac{d}{dt} V(t)$$

capacitor "ignites the change in voltage"

stores energy in electric field

$$E = \frac{1}{2} C V^2 \quad \text{Farad [F]}$$

at DC: acts as an open-circuit

Inductor

$$L \begin{matrix} + \\ - \end{matrix} \begin{matrix} I \\ V \end{matrix}$$


$$V(t) = L \frac{d}{dt} I(t)$$


"ignites the change in current"

stores energy in magnetic field:

$$E = \frac{1}{2} L I^2$$

short-circuit at constant current

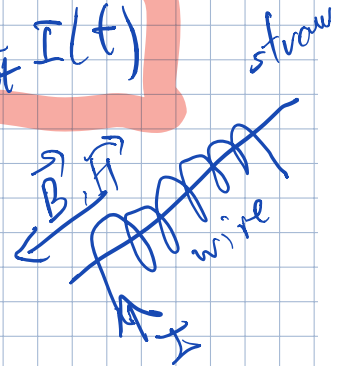


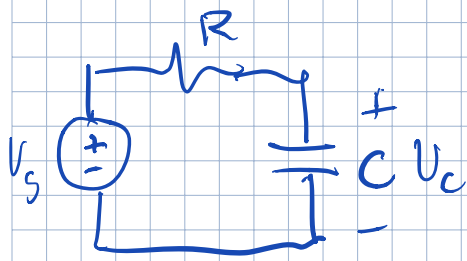

$$V_C \sim e^{-\frac{t}{RC}}$$

$$RC = \tau$$

time constant

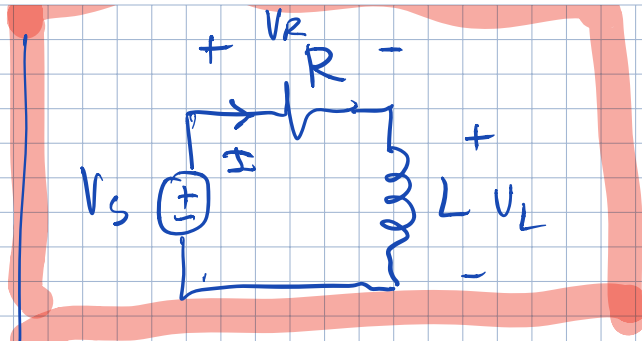

Time constant $\tau = ?$

Decaying exp: $e^{-\frac{t}{\tau}}$

$$V_s(t) = 1V, \quad t \leq 0$$

$$V_s(t) = 0V, \quad t > 0$$

$1V \downarrow 0V$

At the beginning $V_R(0) = V_s(0) - V_L(0)$

$$I(0) = \frac{V_R(0)}{R} = \frac{1V}{R} = 1V$$

$$V_L(t) = L \frac{d}{dt} I(t)$$

$$V_R(t) = R \cdot I(t)$$

$$V_s(t) = V_L(t) + V_R(t)$$

$$V_L(t) = -V_R(t), \quad V_s(t) = 0, \quad t > 0$$


$$L \frac{d}{dt} I(t) = -R I(t)$$

$$\frac{d}{dt} I(t) = -\frac{R}{L} I(t)$$

$$I(t) = I(0) \cdot e^{-\frac{R}{L}t} = I(0) \cdot e^{-\frac{t}{\tau}}$$


time constant $\rightarrow \tau = \frac{L}{R}$

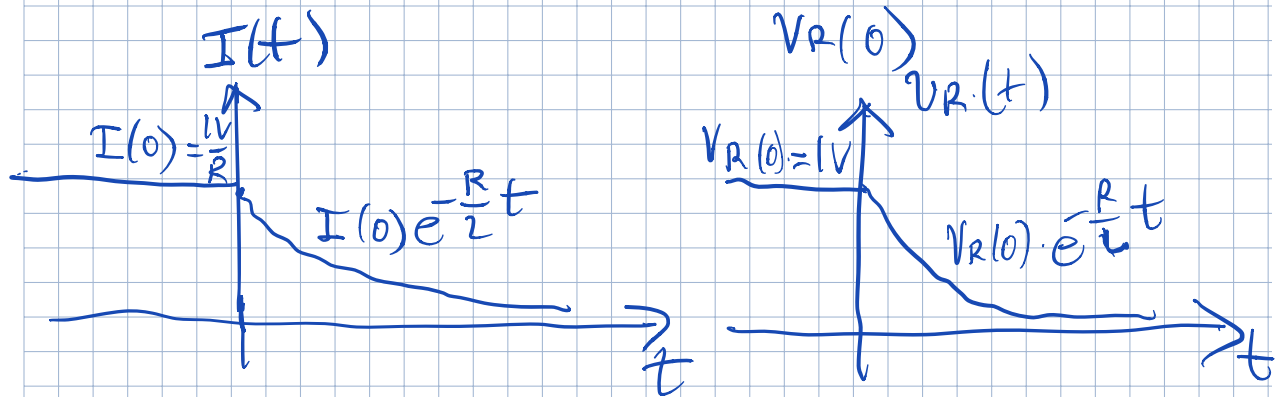
$$V_R(t) = R I(t) = R I(0) e^{-\frac{t}{\tau}}$$



$$V_L(t) = V_S(t) - V_R(t)$$

$$V_L(t) = -V_R(t), \quad t \geq 0$$

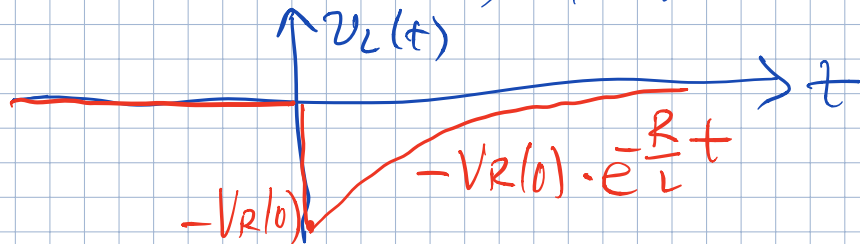

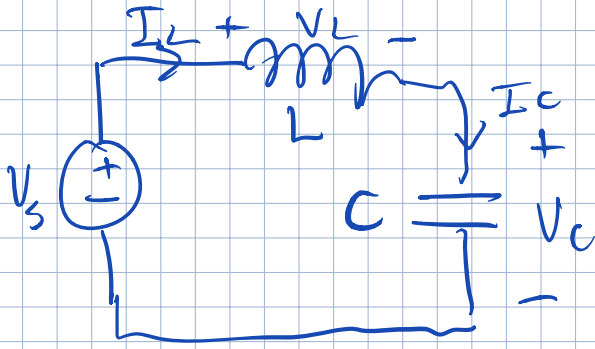

$$I_C(t) = C \frac{d}{dt} V_C(t)$$

$$V_L(t) = L \frac{d}{dt} I_L(t)$$

$$I_L(t) = I_C(t) \quad (\text{KCL})$$

$$V_s(t < 0) = 1V$$

$$V_s(t > 0) = 0V$$

$$V_C(0) = 1V$$

$$I_L(0) = 0A$$

$$V_s(t) = V_C(t) + V_L(t) \quad (\text{KVL})$$

$$t > 0, V_s(t) = 0$$

$$V_L(t) = -V_C(t)$$

$$V_L(t) = L \frac{d}{dt} I_L(t) = -V_C(t) \Rightarrow \frac{d}{dt} I_L(t) = -\frac{1}{L} V_C(t)$$

$$I_L(t) = I_C(t) = C \frac{d}{dt} V_C(t) \Rightarrow \frac{d}{dt} V_C(t) = \frac{1}{C} I_L(t)$$

$$\frac{d}{dt} \begin{bmatrix} I_L(t) \\ V_C(t) \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} I_L(t) \\ V_C(t) \end{bmatrix}$$

A

diagonalize A
to solve

$$\frac{d}{dt} \vec{x}(t) = A \vec{x}(t)$$

$$\vec{x}(t) = \begin{bmatrix} I_L(t) \\ V_C(t) \end{bmatrix}$$

Calculate eigenvalues of A & eigen vectors of A .

$$\det(\lambda I - A) = \det \begin{pmatrix} \lambda & \frac{1}{L} \\ -\frac{1}{C} & \lambda \end{pmatrix} = \lambda^2 + \frac{1}{LC} = 0$$

$$\lambda^2 = -\frac{1}{LC}$$

$$\lambda_{1,2} = \pm j \sqrt{\frac{1}{LC}} \quad \text{where } j = \sqrt{-1}$$

Have the form: $\frac{d}{dt} \vec{x}(t) = A \vec{x}(t)$ where

$$\vec{x}(t) = \begin{bmatrix} I_L(t) \\ v_C(t) \end{bmatrix}, \quad A = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix}$$

Assume: $L = 1H$, $C = 1F$ (really large values)

$$\Rightarrow A = \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \Rightarrow \lambda_{1,2} = \pm j$$

want to find \vec{v}_1, \vec{v}_2 s.t.

$$A \vec{v}_1 = \lambda_1 \vec{v}_1 \quad \& \quad A \vec{v}_2 = \lambda_2 \vec{v}_2$$

Nullspace style

$$\lambda_1 = j$$

$$(A - \lambda_1 I) \cdot \vec{v}_1 = \vec{0}$$

$$\begin{bmatrix} -j & -1 \\ 1 & -j \end{bmatrix} \cdot \begin{bmatrix} 1 \\ -j \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\vec{v}_1 = \begin{bmatrix} 1 \\ -j \end{bmatrix}$$

Ad-hoc style

$\lambda_2 = -j$ any multiple of eigenvector is an eigenvector from eigenspace
 $A k \vec{v}_2 = \lambda_2 k \vec{v}_2$

$$\vec{v}_2 = \begin{bmatrix} 1 \\ ? \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ x \end{bmatrix} = -j \begin{bmatrix} 1 \\ x \end{bmatrix}$$

$$-x = -j \Rightarrow x = j$$

$$\vec{v}_2 = \begin{bmatrix} 1 \\ j \\ 0 \end{bmatrix}$$

$$V = [\vec{v}_1 \quad \vec{v}_2] = \begin{bmatrix} 1 & 1 \\ -j & j \end{bmatrix}$$


$$V^{-1} = \begin{bmatrix} \frac{1}{2} & \frac{j}{2} \\ \frac{1}{2} & -\frac{j}{2} \end{bmatrix}$$

$$\frac{d}{dt} \vec{x}(t) = \underbrace{\begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix}}_A \vec{x}(t)$$

$$\vec{x}(t) = V \vec{\tilde{x}}(t)$$

$$\vec{\tilde{x}}(t) = V^{-1} \vec{x}(t)$$
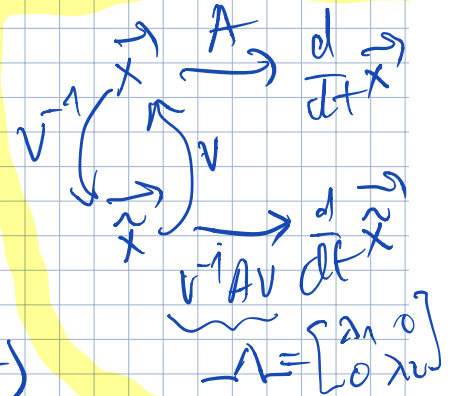
$$\frac{d}{dt} \vec{\tilde{x}}(t) = \underbrace{\begin{bmatrix} j & 0 \\ 0 & -j \end{bmatrix}}_{\Lambda = V^{-1} A V} \vec{\tilde{x}}(t)$$



$$\tilde{x}_1(t) = \tilde{x}_1(0) e^{jt}$$

$$\tilde{x}_2(t) = \tilde{x}_2(0) e^{-jt}$$

$$\vec{\tilde{x}}(0) = V^{-1} \vec{x}(0) = \begin{bmatrix} \frac{1}{2} & \frac{j}{2} \\ \frac{1}{2} & \frac{j}{2} \end{bmatrix} \cdot \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} \frac{j}{2} \\ -\frac{j}{2} \end{bmatrix}$$

$$\vec{\tilde{x}}(t) = \begin{bmatrix} \frac{j}{2} e^{jt} \\ -\frac{j}{2} e^{-jt} \end{bmatrix}$$

$$I_2(0) = 0A$$

$$u_c(0) = 1V$$

$$\vec{x}(t) = V \cdot \vec{\tilde{x}}(t) = \begin{bmatrix} 1 & 1 \\ j & j \end{bmatrix} \cdot \begin{bmatrix} \frac{j}{2} e^{jt} \\ -\frac{j}{2} e^{-jt} \end{bmatrix} = \begin{bmatrix} \frac{j e^{jt} - j e^{-jt}}{2} \\ \frac{e^{jt} + e^{-jt}}{2} \end{bmatrix}$$


Use Euler formula (or from Taylor exp):

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\begin{aligned} & \frac{1}{2} (j(\cos t + j\sin t) - j(\cos(-t) + j\sin(-t))) \\ &= \frac{1}{2} (\cancel{j\cos t} - \sin t - \cancel{j\cos t} + j^2 \sin t) \\ &= -\frac{2\sin t}{2} = -\sin t \end{aligned}$$

$$\frac{e^{jt} + e^{-jt}}{2} = \cos t$$
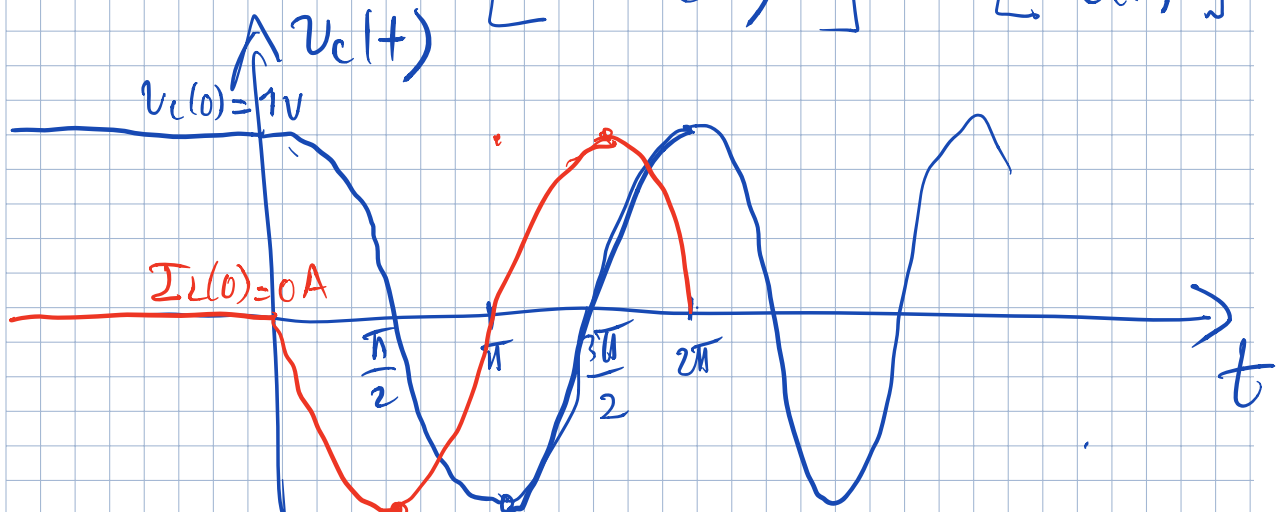
$$\Rightarrow \vec{x}(t) = \begin{bmatrix} -\sin t \\ \cos t \end{bmatrix} = \begin{bmatrix} I_L(t) \\ U_C(t) \end{bmatrix}$$



Note: $\lambda_{1,2} = \pm j \sqrt{\frac{1}{LC}}$

For the general case:

$$\vec{x}(t) = \begin{bmatrix} -\sin\left(\sqrt{\frac{1}{LC}} t\right) \\ \cos\left(\sqrt{\frac{1}{LC}} t\right) \end{bmatrix}$$

