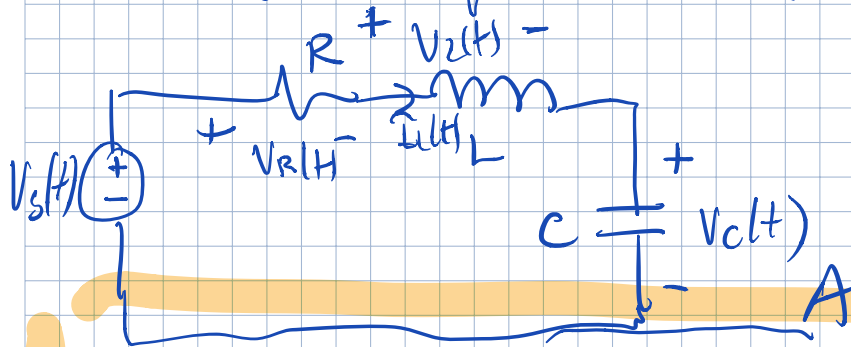


* RLC circuits

* Solving systems of diff. eqns.
with Phasors

A note on homework:



$$\frac{d}{dt} \begin{bmatrix} I_L(t) \\ V_C(t) \end{bmatrix} = \begin{bmatrix} -\frac{R}{L} & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} I_L(t) \\ V_C(t) \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_s(t)$$

$$V_L(t) = V_s(t) - V_R(t) - V_C(t) \quad \text{: KVL}$$

$$L \frac{d}{dt} I_L(t) = V_s(t) - I_L(t) \cdot R - V_C(t)$$

$$\frac{d}{dt} I_L(t) = -\frac{R}{L} I_L(t) - \frac{1}{L} V_C(t) + \frac{1}{L} V_s(t)$$

How to solve:

1) Find eigenvalues & eigenvectors of A

2) Change the coordinates to $\vec{\tilde{x}}(t)$ in the eigenbasis of A .

3) Solve a simpler problem $\vec{\tilde{x}}(t) = \vec{0}$

- use $\vec{\tilde{x}}(0) = V^{-1} \vec{x}(0)$ ($\hat{A} = V^{-1} A V$ would

$\vec{\tilde{x}}(t) = \begin{bmatrix} x_1(0) e^{\lambda_1 t} \\ \vdots \\ x_n(0) e^{\lambda_n t} \end{bmatrix}$ be diagonal or upper triangular)

4) Change the coordinates back:

$$\vec{x}(t) = V \cdot \vec{\tilde{x}}(t)$$

Reminder :

For $\frac{d}{dt} x(t) = \lambda x(t) + u(t)$

when: $u(t) = k \cdot e^{st}$ when $s \neq \lambda$

$$x(t) = \underbrace{\left(x(0) - \frac{k}{s-\lambda}\right) e^{\lambda t}}_{\text{Annoying (comes from initial conditions)}} + \underbrace{\frac{k}{s-\lambda} \cdot e^{st}}_{\text{Nice (same form as input, steady-state solution)}}$$

When can we ignore?

When does $e^{\lambda t} \rightarrow 0$?

$e^{\lambda t} \rightarrow 0$ as $t \rightarrow \infty$ iff $\lambda < 0$

What about complex λ 's?

$$e^{\lambda t} = e^{(\lambda_r + j\lambda_i)t} = e^{\lambda_r t} \cdot e^{j\lambda_i t} = e^{\lambda_r t} (\cos \lambda_i t + j \sin \lambda_i t)$$

$\rightarrow 0$ iff $\lambda_r < 0$ does not go away in t

Let's consider that inputs are of the form $\sim e^{st}$ and assert that all other quantities (solutions) are $\sim e^{st}$, valid if $s \neq \lambda$ and $\text{Re}(\lambda) = \lambda_r < 0$.

Let's try: $\frac{d}{dt} \vec{x}(t) = A \vec{x}(t) + \vec{u}(t)$

when $\vec{u}(t) = \vec{\tilde{u}} e^{st}$ $\vec{\tilde{u}}$ vector of constants

Assert: $\vec{x}(t) = \vec{\tilde{x}} \cdot e^{st}$: $\vec{\tilde{x}}$ vector of constants

$$\begin{aligned} \frac{d}{dt} \vec{x}(t) &= \frac{d}{dt} (\vec{\tilde{x}} e^{st}) = \vec{\tilde{x}} \cdot \frac{d}{dt} e^{st} = \vec{\tilde{x}} \cdot s e^{st} = \\ &= s \vec{\tilde{x}} e^{st} = A \vec{\tilde{x}} e^{st} + \vec{\tilde{u}} e^{st} \end{aligned}$$

$$s \vec{\tilde{x}} e^{st} = A \vec{\tilde{x}} e^{st} + \vec{\tilde{u}} e^{st}$$

$$s \vec{\tilde{x}} = A \vec{\tilde{x}} + \vec{\tilde{u}}$$

$$(sI - A) \vec{x} = \vec{u}$$

System of linear eqns.

$$\vec{x} = (sI - A)^{-1} \vec{u}$$

$$\vec{x}(t) = \vec{x} e^{st}$$


$$\vec{x}(t) = (sI - A)^{-1} \vec{u} e^{st}$$

Remember
 $s \neq \lambda$ so
 $sI - A$ has
no nullspace &
is therefore
invertible.

We solved system of differential equations
by solving a system of linear equations.



Can we use this for clts directly?

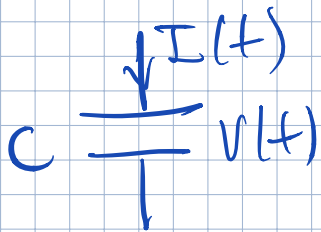

$$I(t) = C \frac{d}{dt} V(t)$$

$$I(t) = \tilde{I} e^{st}$$

$$V(t) = \tilde{V} e^{st}$$


$$\frac{V(t)}{I(t)} = \frac{\hat{V}}{\hat{I}}$$

$$I(t) = \tilde{I} e^{st} = C \frac{d}{dt} (\tilde{V} e^{st}) = C \tilde{V} \underbrace{\frac{d}{dt} e^{st}}_{s e^{st}}$$

$$\cancel{\tilde{I} e^{st}} = sC \cancel{\tilde{V} e^{st}}$$

$$\frac{\hat{V}}{\hat{I}} = \frac{1}{sC}$$

capacitor
s-impedance

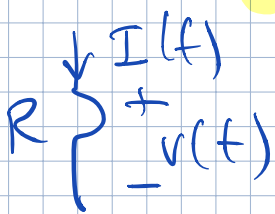


$$V(t) = \tilde{V} e^{st}$$

$$I(t) = \tilde{I} e^{st}$$

$$\underbrace{\tilde{V} e^{st}}_{V(t)} = \underbrace{\tilde{I} e^{st}}_{I(t)} \cdot R$$

$$\frac{\hat{V}}{\hat{I}} = R$$

resistor
s-impedance

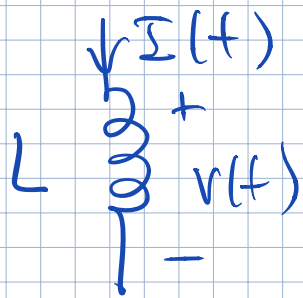

$$v(t) = L \frac{d}{dt} I(t)$$


$$\begin{aligned} \hat{v}(t) &= \hat{v} e^{st} \\ \hat{I}(t) &= \hat{I} e^{st} \end{aligned}$$

$$\hat{v} e^{st} = L \frac{d}{dt} (\hat{I} e^{st}) = L \hat{I} \frac{d}{dt} e^{st}$$

$$\hat{v} e^{st} = s L \hat{I} e^{st}$$

$$\hat{v} / \hat{I} = sL$$

inducta
s-impedance

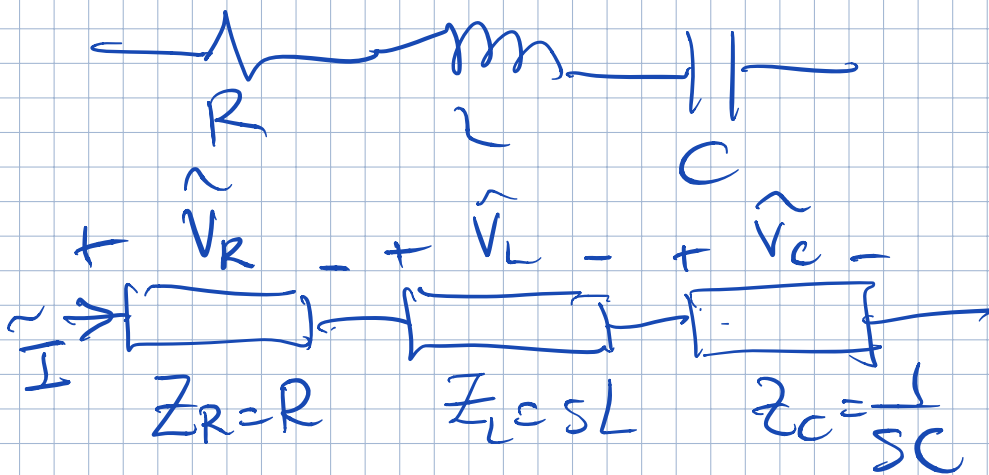

$$\hat{v}, \hat{I}$$

$$\hat{v}_R = \hat{I} \cdot Z_R$$

$$\hat{v}_C = \hat{I} \cdot Z_C$$

$$\hat{v}_L = \hat{I} \cdot Z_L$$

Summary:

sys.
diff.
eqns.

$$\frac{d}{dt} \vec{x}(t) = A \vec{x}(t) + \vec{u}(t)$$

$$\& \quad \vec{u}(t) = \vec{\tilde{u}} e^{st}, \quad s \neq \lambda$$

we have: $\vec{x}(t) = \vec{\tilde{x}} e^{st}$

get

$$s \vec{\tilde{x}} = A \vec{\tilde{x}} + \vec{\tilde{u}}$$

system
of lin
equations.

$$\vec{\tilde{x}} = (sI - A)^{-1} \vec{\tilde{u}}$$

(steady-state
solution)

solutions to:

$$\frac{d}{dt} \vec{x}(t) - A \vec{x}(t) = 0 \quad \text{can always}$$

be added to steady-state solution.

~ of the form $\vec{x}_h(t) = \vec{x}(0) e^{\lambda t}$

when λ is eigenvalue of A .
(these come from init. conditions)

To ignore: $\operatorname{Re} \lambda < 0$ can focus
only on steady-state solution.

For sinusoidal inputs:

$$u(t) = U \cos(\omega t + \phi) = U \cdot \frac{e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)}}{2}$$

$$u(t) = \underbrace{\frac{U \cdot e^{j\phi}}{2}}_{\tilde{u}} \cdot \underbrace{e^{j\omega t}}_{e^{s_1 t}} + \underbrace{\frac{U \cdot e^{-j\phi}}{2}}_{\tilde{u}^-} \cdot \underbrace{e^{-j\omega t}}_{e^{s_2 t}}$$

$s_1 = j\omega$ $s_2 = -j\omega$

always complex conjugates

$$u(t) = \tilde{u} e^{j\omega t} + \tilde{u}^- e^{-j\omega t}$$

Use superposition to solve for ckt v's & i's:

For $s_1 = j\omega$

$$M = s_1 I - A$$

Topology of Re det elements solve:

$$M \begin{bmatrix} \vec{I} \\ \vec{V} \end{bmatrix} = \vec{u} \leftarrow \text{indep sources}$$

$$\begin{bmatrix} \vec{I} \\ \vec{V} \end{bmatrix} = M^{-1} \vec{u}$$

$$s_2 = -j\omega$$

get:

$$\bar{M} = s_2 I - A \\ = -j\omega I - A$$

since:

$$\bar{M} \bar{x} = \bar{M} \cdot \bar{x}$$

$$\bar{M} \begin{bmatrix} \vec{v} \\ \vec{i} \end{bmatrix} = \vec{u}$$

$$\begin{bmatrix} \vec{v} \\ \vec{i} \end{bmatrix} = \begin{bmatrix} \vec{v} \\ \vec{i} \end{bmatrix} = \bar{M}^{-1} \cdot \vec{u} \\ = \bar{M}^{-1} \vec{u}$$

all solutions:

$$\vec{v}(t) = \vec{v} e^{j\omega t} + \vec{v} \cdot e^{-j\omega t}$$


$$\vec{i}(t) = \vec{i} e^{j\omega t} + \vec{i} \cdot e^{-j\omega t}$$

$$s = j\omega:$$

\vec{v} & \vec{i} are phasors (functions of ω)

s-impedances are called impedances (functions of ω)

Phasors reduce IGB to IGA problem!

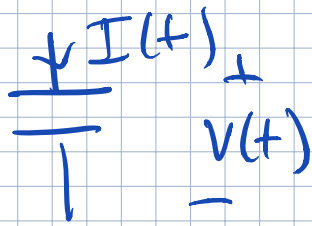

$$v(t) = V_0 \cos(\omega t + \phi)$$

$$v(t) = \underbrace{\frac{V_0}{2} e^{j\phi}}_{\hat{v}} \cdot e^{j\omega t} + \underbrace{\frac{V_0}{2} e^{-j\phi}}_{\hat{v}^*} e^{-j\omega t}$$

$$I(t) = C \frac{d}{dt} v(t) =$$

$$= C \frac{d}{dt} (\hat{v} e^{j\omega t} + \hat{v}^* e^{-j\omega t})$$

$$= \underbrace{j\omega C \hat{v} e^{j\omega t}}_{\hat{I}} - \underbrace{j\omega C \hat{v}^* e^{-j\omega t}}_{\hat{I}^*}$$

$$I(t) = \hat{I} e^{j\omega t} + \hat{I}^* e^{-j\omega t}$$

$$\hat{I} = j\omega C \hat{v} \Rightarrow Z_C = \frac{\hat{v}}{\hat{I}} = \boxed{j\omega}$$