

PRINT your name and student ID: _____

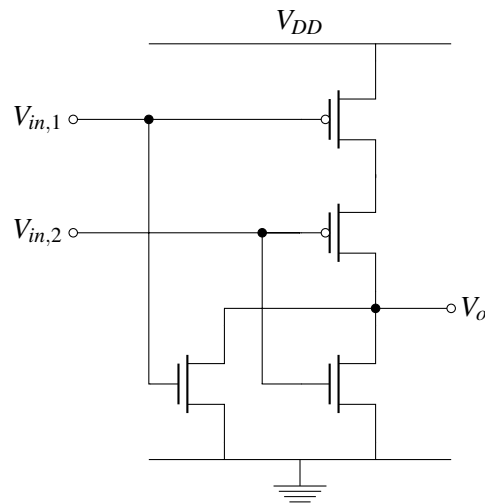
1. CMOS Circuits (40 pts)

Figure 1: CMOS circuit

Consider the CMOS circuit of Figure 1. For each of the sets of $V_{in,1}$ and $V_{in,2}$ in the table below, fill in the corresponding voltage of the output V_o . You may assume that the threshold voltages for the transistors are $0 < V_{tn} < V_{DD}$ and $0 < |V_{tp}| < V_{DD}$.

$V_{in,1}$	$V_{in,2}$	V_o
0V	0V	
V_{DD}	0V	
0V	V_{DD}	
V_{DD}	V_{DD}	

PRINT your name and student ID: _____

2. Differential equations (40 pts)

Consider a certain radioactive isotope sample with an initial mass, M_0 . It is observed that the mass of radioactive sample decays with time. The rate of mass decay at time t is proportional to the mass $M(t)$ at that moment. The constant of proportionality is the decay rate constant, $r > 0$. The rate of mass decay is given by

$$\frac{dM(t)}{dt} = -rM(t). \quad (1)$$

- (a) (20 pts) **Solve the differential equation (1) to determine the mass of the sample at a given time.**

$$M(t) =$$

- (b) (20 pts) **Find the half life $t_{\frac{1}{2}}$ of the sample as a function of r . Note that half life is the time when half of the initial mass has decayed.**

$$t_{\frac{1}{2}} =$$

PRINT your name and student ID: _____

3. Complex Numbers (60 pts)

(a) (20 pts) **Write the following numbers in polar form.** That is, write the numbers as $Ae^{j\theta}$ for some real numbers A and θ with $A \geq 0$ and $-\pi \leq \theta \leq \pi$.

i. $1 + j$

$$1 + j =$$

ii. \sqrt{j}

$$\sqrt{j} =$$

(b) (20 pts) **Write the following numbers in rectangular form.** That is, write each number as $a + bj$ where a and b are real numbers. HINT: $e^{j\theta} = \cos \theta + j \sin \theta$.

i. $3e^{j\frac{\pi}{3}}$

$$3e^{j\frac{\pi}{3}} =$$

ii. $-\sqrt{7}e^{\pi j}$

$$-\sqrt{7}e^{\pi j} =$$

PRINT your name and student ID: _____

(c) (20 pts) **Prove the following identities.**

i. $\frac{1}{j} = -j$

ii. $\sin(2x) = 2 \cos x \sin x.$

PRINT your name and student ID: _____

4. Vector differential equations (60 pts)For this problem, x satisfies the following differential equation:

$$\frac{d}{dt} \vec{x} = A\vec{x}; \quad A = \begin{bmatrix} \alpha & -\omega \\ \omega & \alpha \end{bmatrix},$$

where α and ω are real. Take initial condition $\vec{x}(0) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$.(a) (30 pts) Using the following two eigenvectors of A :

$$v_1 = \begin{bmatrix} j \\ 1 \end{bmatrix}, \quad v_2 = \begin{bmatrix} -j \\ 1 \end{bmatrix},$$

determine a matrix T and a diagonal matrix D such that

$$\frac{d}{dt} \vec{z} = D\vec{z}, \quad \text{where } \vec{z} = T\vec{x}.$$

You may use the fact that $\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$.

Write your answers in the boxes below.

$T =$
$D =$

PRINT your name and student ID: _____
(extra space for (a))

(b) (15 pts) Solve for \vec{z} as a function of t . Your solution may not include unknowns other than α and ω .

PRINT your name and student ID: _____

- (c) (15 pts) Solve for x_1 , the first component of \vec{x} , as a function of t . If possible, state your solution without complex numbers.

PRINT your name and student ID: _____

5. Transient identification (40 pts)

For each of following scalar functions of time,

- If the function may describe a voltage transient response in one of the following circuit types we studied in class: RC, RL, RCRC, overdamped RLC, underdamped RLC; write all that apply.
- Otherwise, write “None.”

Assume $V_0 \neq 0$, $V_1 \neq 0$, $V_2 \neq 0$ and $\omega > 0$.

(a) (10 pts) $v(t) = V_0 e^{\lambda t}$, $\lambda < 0$

(b) (10 pts) $v(t) = V_0 e^{jt}$







(c) (10 pts) $v(t) = V_0 e^{\alpha t} \cos \omega t$, $\alpha < 0$

(d) (10 pts) $v(t) = V_1 e^{\alpha t} + V_2 e^{\beta t}$, $\alpha < 0$, $\beta < 0$

PRINT your name and student ID: _____

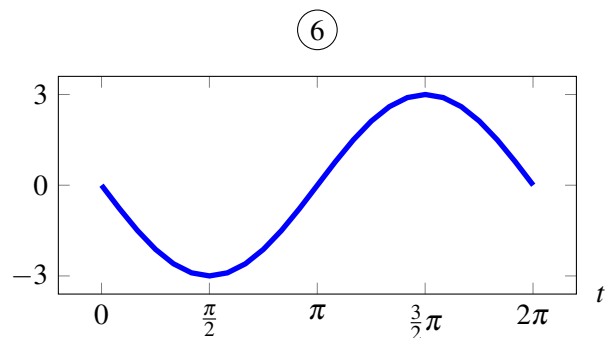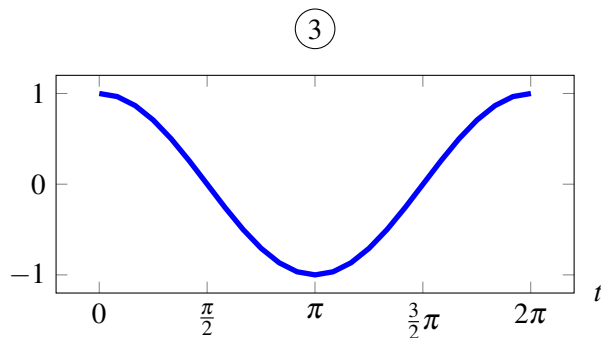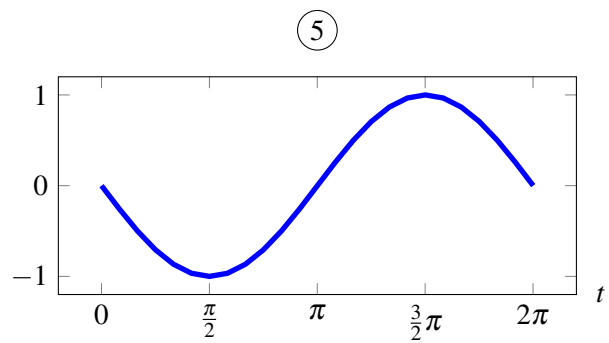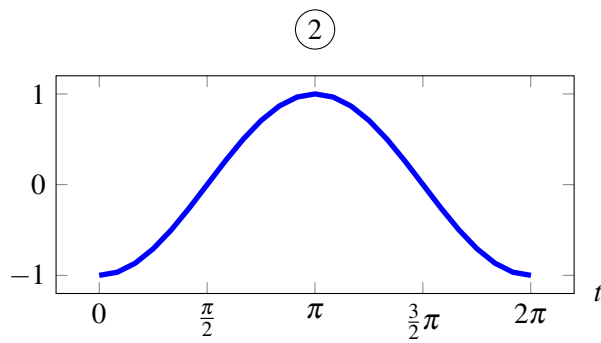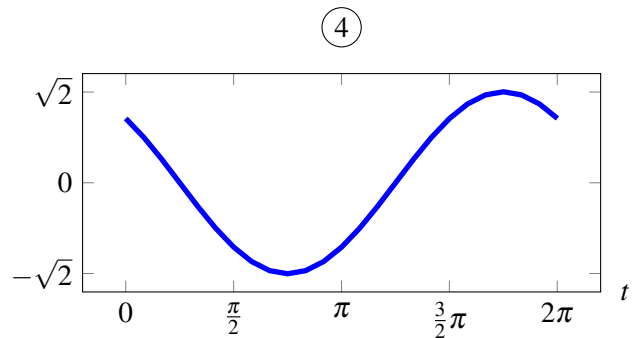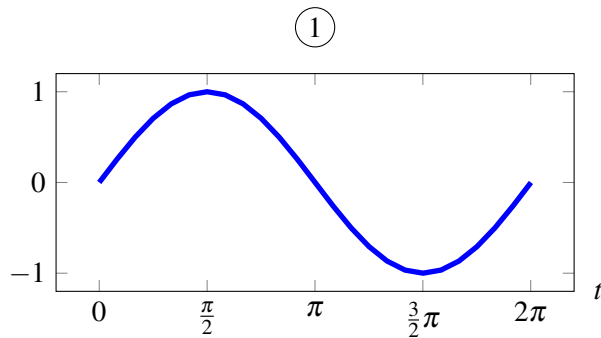6. Phasors (60 pts)



Match each phasor with its corresponding time domain waveform that is shown below. For this problem $\omega = 1$.



	Phasor	Waveform
(a)	$e^{j\frac{\pi}{2}}$	
(b)	$3e^{j\frac{\pi}{2}}$	
(c)	1	
(d)	$e^{-j\frac{\pi}{2}}$	
(e)	$e^{-j\pi}$	
(f)	$e^{j0} + e^{j\frac{\pi}{2}}$	


PRINT your name and student ID: _____

7. Energy (60 pts)

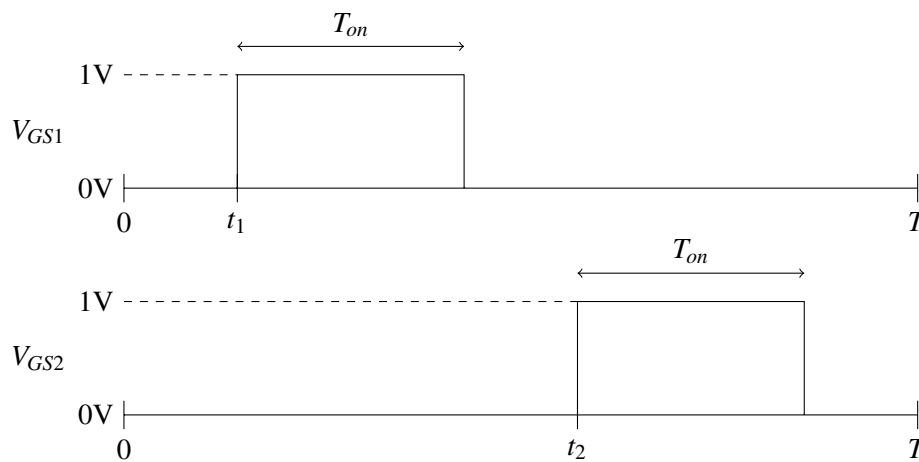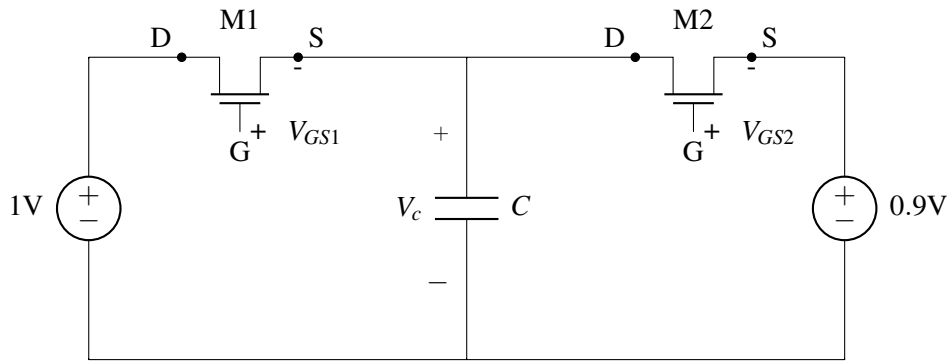

In the figure above, NMOS devices M1 and M2 have threshold voltages of 0.2V, negligible gate-source capacitances, and ON state resistances of value R . Capacitor C has capacitance such that $RC \ll T_{on}$. The associated timing diagram shows that V_{GS1} rises at t_1 , and V_{GS2} rises at t_2 .

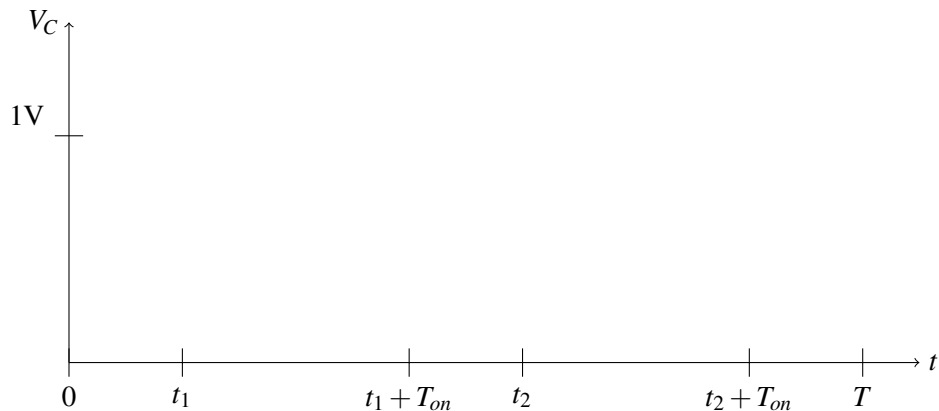- (a) (20 pts) Take $V_C(0) = 0.9V$. On the axes below, sketch the waveform corresponding to $V_C(t)$ for $0 < t < T$. You may make approximations as informed by learnings in class to date.



PRINT your name and student ID: _____

- (b) (20 pts) Determine how much charge flows out of the 1.0V source over the period from 0 to T . You may make reasonable approximations to simplify the analysis, as done in the making of the sketch of part (a).

- (c) (20 pts) Determine how much energy is dissipated in the circuit over the period from 0 to T . Again, you may make reasonable approximations to simplify your analysis.

PRINT your name and student ID: _____

[Extra page. If you want the work on this page to be graded, make sure you tell us on the problem's main page.]

PRINT your name and student ID: _____

[Doodle page! Draw us something if you want or give us suggestions or complaints. You can also use this page to report anything suspicious that you might have noticed.]