

WELCOME TO EECS16B!

Disc. Time : M/W 9-10 AM  
10-11 AM  
1-2 PM  
7-8 PM [Online]

Email: nareaphol.liu@berkeley.edu

↳ Admin Qs direct to Divija / Ali

Name : Gavin

To do : Introduction + 16A Review

ASE : Ben

- ① Self intro + Course Intro + Teaching Style + Zoom
- ② Course Logistics
- ③ 16A Circuits Review (Q2)
- ④ Discussion Q1.4 (3 if time)



### Intro

- Course Intro : Motivating goal :
  - ↳ Module 1 : More Circuits from 16A (Filters, Phasors, SP)
  - ↳ Module 2 : Controls & Linearization
  - ↳ Module 3 : SVD + Applications to ML
- Quick note on teaching style
- Quick note on Zoom + Zoom Participation.

Course Logistics → All information on Website : [eecs16b.org](http://eecs16b.org)

### 16A Review

① Resistor



Passive Sign Convention :  
when labeling currents, label from the "+" to "-"

Equivalent! → What does  $V_R$  mean?




$$V_R = \text{---} - \text{---}$$


Series:  
→ same current going through the elements



$$i_{R1} = i_{R2}$$

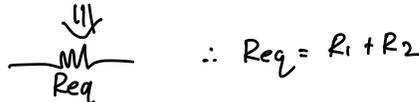

$$\therefore R_{eq} = R_1 + R_2$$

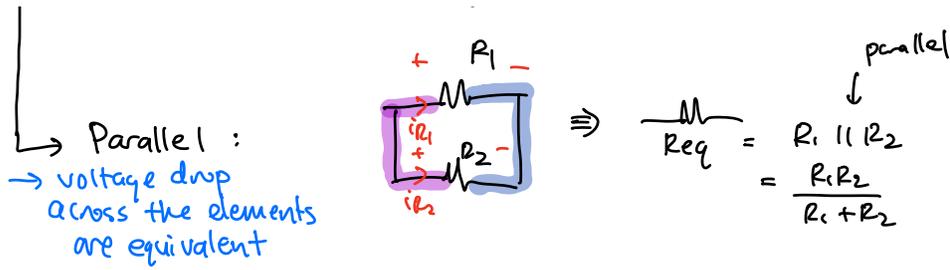

② Capacitors   
 $i_c = C \frac{dV_c}{dt}$



$$i_c = C \cdot \frac{dV_c}{dt}$$

• Series  $\frac{1}{C_1} \frac{1}{C_2} \Rightarrow \frac{1}{C_{eq}} = \frac{C_1 C_2}{C_1 + C_2}$

• Parallel  $\frac{C_1}{C_2} \Rightarrow C_{eq} = C_1 + C_2$

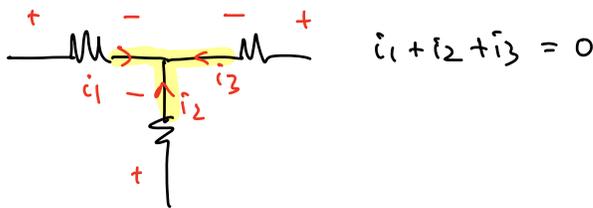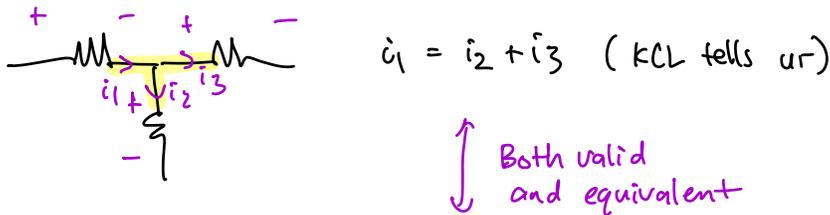
### Tools

① KCL:  $\sum$  currents going into a node =  $\sum$  currents leaving a node




② Nodal Analysis (simplified & better & faster than 16A)

[Dirac Q2]

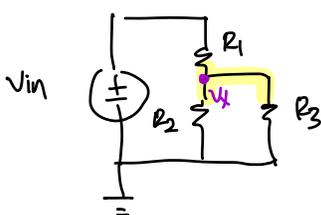


**Step 1:** Pick a node to perform KCL on. Pick a node that has the most # of elements connected to it + what we're interested in

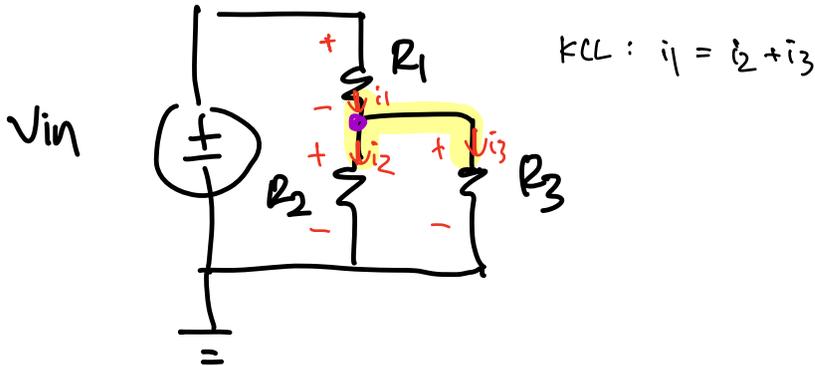
Step 2: Label the currents going through the elements on the node you chose.  
Then perform KCL on the node




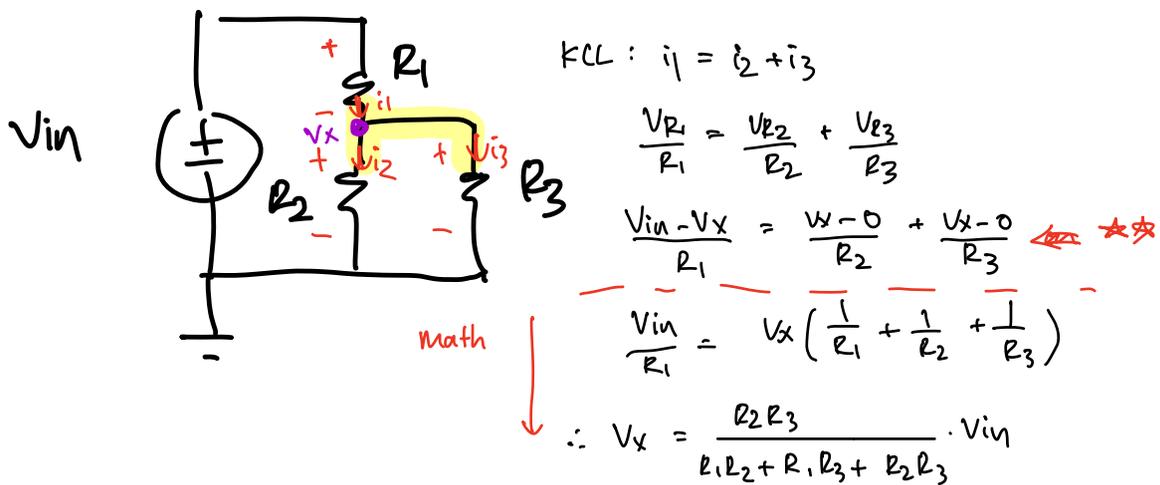Step 3: Convert your KCL equation into V-R relationships or capacitor relationships, etc.  $V = IR$ ,  $i_C = C \frac{dV_C}{dt}$



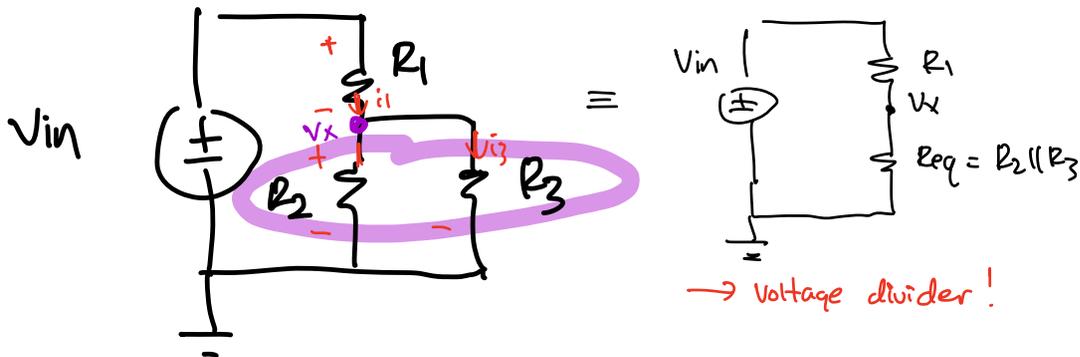(b) Alternatively, you can realize that  $R_2 \parallel R_3$



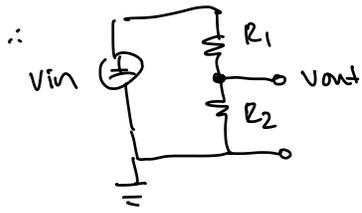


$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$


↓

$$V_x = \frac{R_{eq}}{R_{eq} + R_1} \cdot V_{in}$$

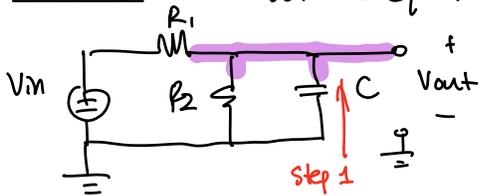Practice : Write out the equation to solve for  $V_{out}$



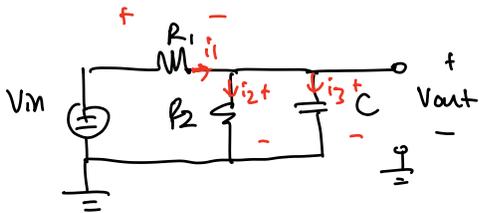Hint : Pick a node to make your life easy



step 2

$$KCL: i_1 = i_2 + i_3$$


Step 3 :  $V = IR$ ,  $i_C = C \frac{dV_C}{dt}$

$$i_1 = i_2 + i_3$$

$$\frac{V_{R1}}{R_1} = \frac{V_{R2}}{R_2} + i_3$$


$$\frac{V_{in} - V_{out}}{R_1} = \frac{V_{out} - 0}{R_2} + C \frac{dV_C}{dt}$$
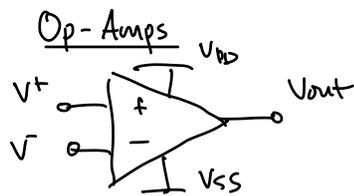
$$\frac{V_{in} - V_{out}}{R_1} = \frac{V_{out}}{R_2} + C \frac{dV_{out}}{dt} \quad (\text{done!})$$



Golden Rules of Op-Amps

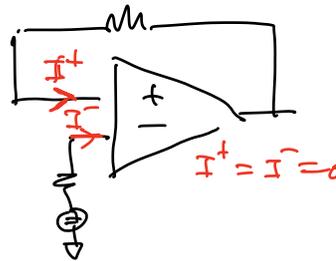①  $I^+ = I^- = 0$   
for an ideal op-amps




② If in negative feedback (NFB), then

$$V^+ = V^-$$

↳ part of the output is fed back into the "-" input


e.g. Buffer

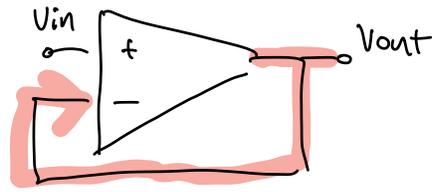

$$V^+ = V^-$$

$$V_{in} = V_{out}$$

Disc Q4 [3-5 min]

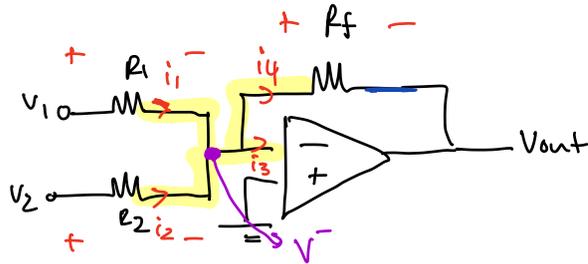

$$\text{KCL: } i_1 + i_2 = i_3 + i_4$$

$$\frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2} = 0 + \frac{V_{Rf}}{R_f}$$

$$\frac{V_1 - V^-}{R_1} + \frac{V_2 - V^-}{R_2} = \frac{V^- - V_{out}}{R_f}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_{out}}{R_f}$$

$$\therefore V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\because \text{op-amp in NFB, } \therefore V^+ = V^-$$

$$0 = V^-$$