




To do : Transistors & RC Models

Email: nareanphol.lin@

- ① PMOS, NMOS, & Transistors
- ② Introduction to RC circuits and Differential equations

Transistor - PMOS / NMOS

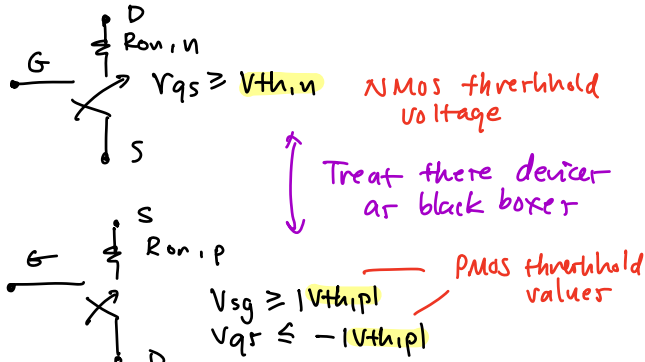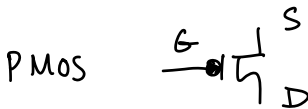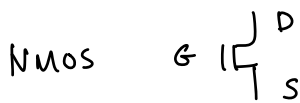
Motivating Q: Why can't our computers go any faster?



★ It is possible for both the PMOS and NMOS to turn on at the same time, or be off at the same time


★ 16B Assumption  $0 \leq V_{th,p}, V_{th,n} \leq V_{DD}$

Inverter

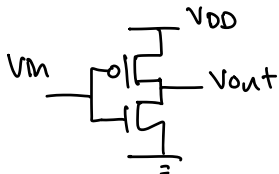

if  $V_{in} = V_{DD}$ ,  $V_{out} = 0V$   
 if  $V_{in} = 0V$ ,  $V_{out} = V_{DD}$


→ Lets check the conditions:

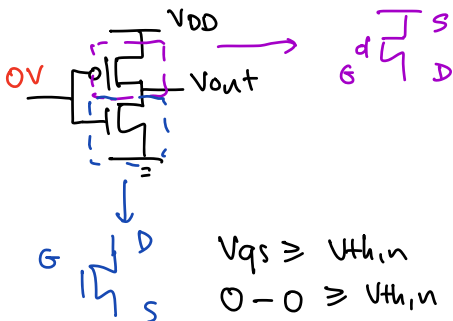

$V_{gs} \leq -|V_{th,p}|$   
 $0 - V_{DD} \leq -|V_{th,p}|$   
 $-V_{DD} \leq -|V_{th,p}|$  ✓ Yes!  
 ∴ condition is satisfied, the PMOS turns "on"

$V_{qs} \geq V_{th,n}$   
 $0 - 0 \geq V_{th,n}$  ✗ No!

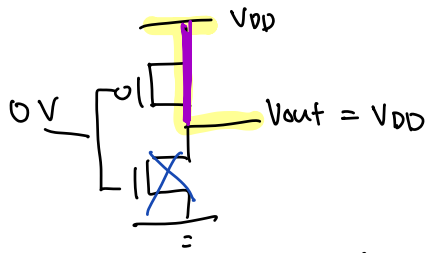∴ condition is NOT satisfied, the NMOS turns "off"




(Vout) in

Trick: To solve for NMOS/PMOS circuits quickly, just remember the inverter. It only works if we know our inputs are high/low (VDD/0)

input low  $\rightarrow$  output high [PMOS on, NMOS off]

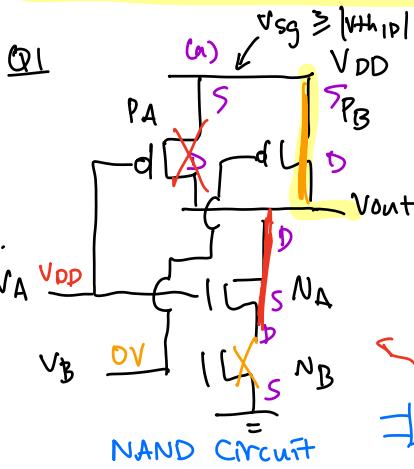input high  $\rightarrow$  output low [PMOS off, NMOS on]



$$V_{DD} - V_{DD} \geq |V_{thp}| \times$$

(b)  $V_A = V_{DD}, V_B = V_{DD}, V_{out} = 0V$

(c)  $V_A = V_{DD}, V_B = 0V, V_{out} = V_{DD}$



(d)  $V_A = 0V, V_B = V_{DD}, V_{out} = V_{DD}$



(e)  $V_A = 0V, V_B = 0V, V_{out} = V_{DD}$

(f)


$V_A$	$V_B$	$V_{out}$
0	0	$V_{DD}$
0	$V_{DD}$	$V_{DD}$
$V_{DD}$	0	$V_{DD}$
$V_{DD}$	$V_{DD}$	0

RC Model

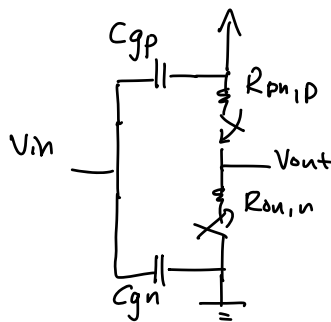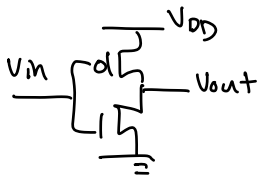


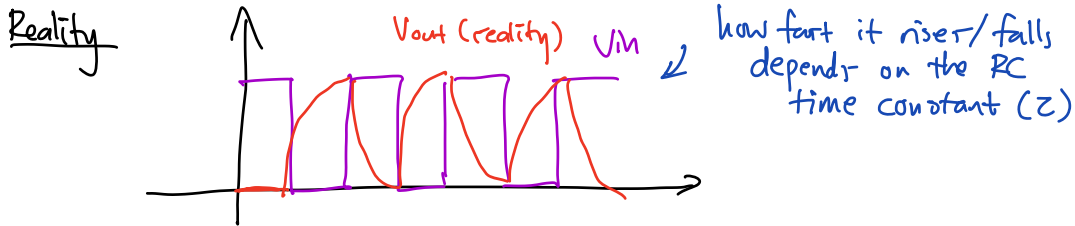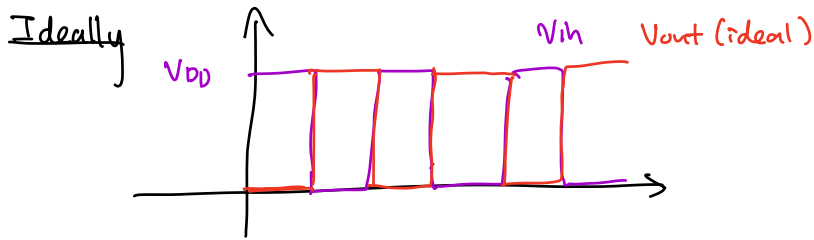

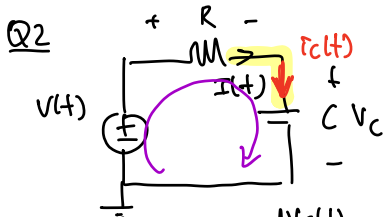To answer our motivating question: Because we are limited by capacitors!



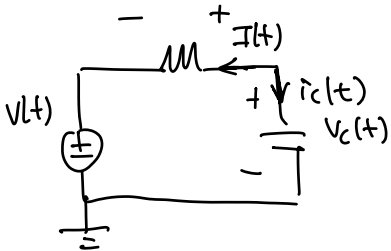(a)  $I_C(t) = C \frac{dv_C(t)}{dt}$   
 $I(t) = C \frac{dv_C(t)}{dt}$



KVL:  $v(t) - v_R(t) - v_C(t) = 0$   
 $v(t) - i(t) \cdot R - v_C(t) = 0$   
 $v(t) - C \frac{dv_C(t)}{dt} \cdot R - v_C(t) = 0$

(b), (c)

KCL:  $I(t) = i_C(t)$

$\frac{v_R(t)}{R} = C \frac{dv_C(t)}{dt}$

$\frac{v(t) - v_C(t)}{R} = C \frac{dv_C(t)}{dt}$

$\therefore \frac{dv_C(t)}{dt} = \frac{v(t) - v_C(t)}{CR}$

KCL:  $0 = I(t) + i_C(t)$

$= I(t) + C \frac{dv_C}{dt}$

$= \frac{v_R(t)}{R}$

$= \frac{v_C(t) - v(t)}{R} + C \frac{dv_C}{dt}$

$\frac{v(t) - v_C(t)}{R} = C \frac{dv_C}{dt}$