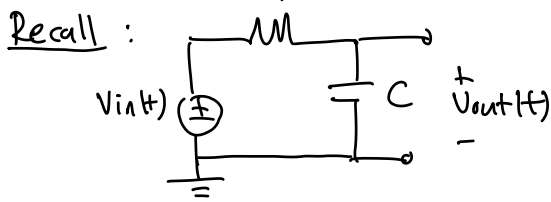


To do : Filters and Transfer Functions

- ① Recap Phasors
- ② Transfer Functions
- ③ Filters

Time Domain



$$V_{in}(t) = 12 \sin(\omega t - \frac{\pi}{4})$$

↓


$$V_{in}(t) = V_0 \cos(\omega t + \phi) \text{ [general form]}$$

$$V_{out}(t) = |H(j\omega)| \cdot V_0 \cos(\omega t + \phi + \angle H(j\omega))$$

↓
scaled by
($|H(j\omega)|$)

↓
shift
by $\angle H(j\omega)$

Phasor Domain

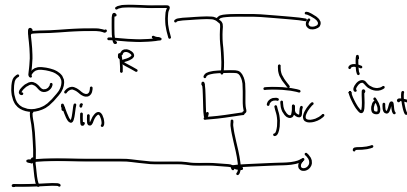

$$\tilde{V}_{out} = \frac{1}{j\omega C + R} \cdot \tilde{V}_{in}$$

①

$$\tilde{V}_{in} = \frac{V_0}{2} e^{j\phi}$$

Transfer Function
 $H(j\omega)$ (the gain
of the circuit)

$$\tilde{V}_{out} = \frac{1}{1 + j\omega RC} \cdot \tilde{V}_{in}$$

express it in
polar form

$$\tilde{V}_{out} = H(j\omega) \cdot \tilde{V}_{in}$$




$$= |H(j\omega)| e^{j\angle H(j\omega)} \cdot \tilde{V}_{in} \frac{V_0}{2} e^{j\phi}$$

$$= |H(j\omega)| \cdot \frac{V_0}{2} e^{j(\phi + \angle H(j\omega))}$$

$$H(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}}$$

from example above : $H(j\omega) = \frac{1}{1 + j\omega RC}$

- $\omega = 0, |H(j\omega)| = 1$ } at low freqs → output gets "preserved"
 - $\omega \rightarrow \infty, |H(j\omega)| \rightarrow 0$ } at high freqs → output dies (becomes 0)
- Low-Pass Filter : low frequencies pass through

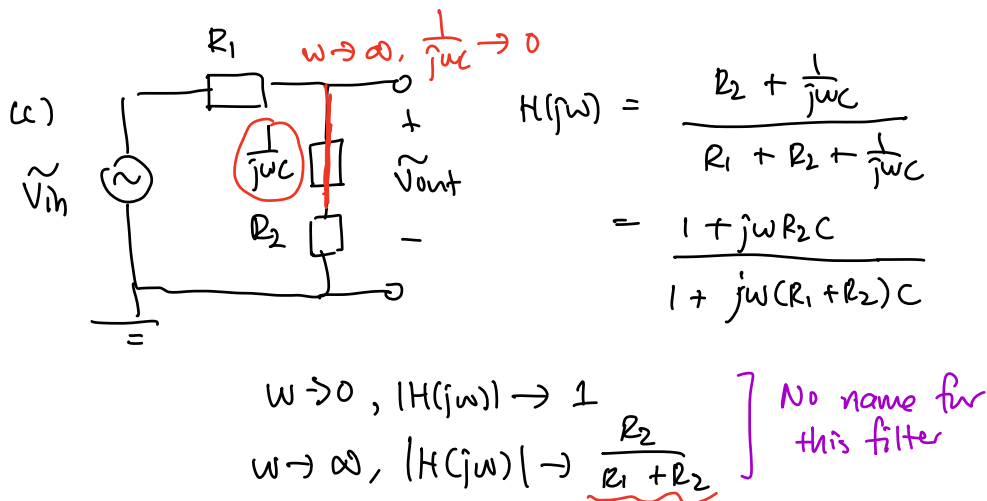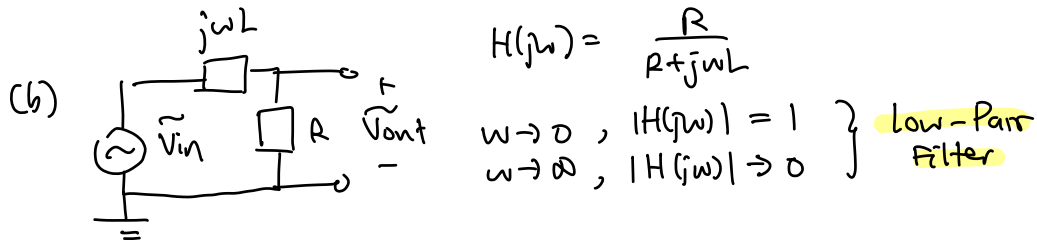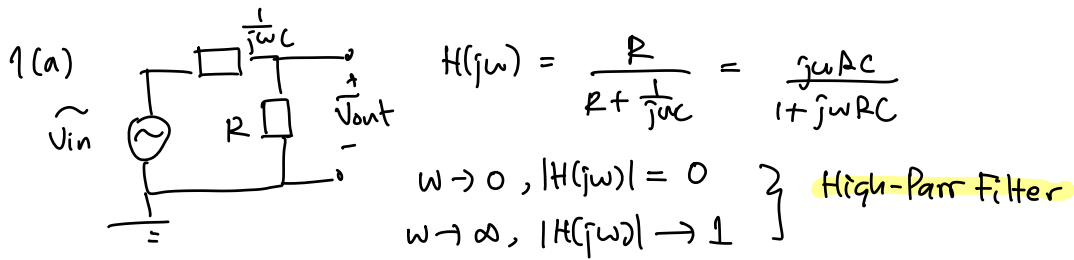

(d) $V_{in}(t) = 12 \sin(100t)$, $H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$

\downarrow
 $V_{oc} \cos(\omega t + \phi) \Leftrightarrow \frac{V_0}{2} e^{j\phi}$
 $\tilde{V}_{out} = H(j\omega) \tilde{V}_{in} \rightarrow V_{out}(t) = |H(j\omega)| \cdot V_0 \cos(\omega t + \phi + \angle H(j\omega))$

\downarrow scaled by $|H(j\omega)|$
 \downarrow shifted by $\angle H(j\omega)$

$V_{in}(t) = 12 \sin(100t) = 12 \cos(100t - \frac{\pi}{2})$
 \downarrow
 $\tilde{V}_{in} = 6e^{j\frac{-\pi}{2}}$


$\sin(\theta) = \cos(\theta - \frac{\pi}{2})$

$$\therefore \tilde{V}_{out} = \frac{j\omega RC}{1+j\omega RC} \cdot 6e^{j\frac{\pi}{2}} = \frac{j}{1+j} \cdot 6e^{j\frac{\pi}{2}}$$

(1+j) *Not in polar*

$$\cdot \left| \frac{j}{1+j} \right| = \frac{|j|}{|1+j|} = \frac{1}{\sqrt{1^2+1^2}} = \frac{1}{\sqrt{2}}$$
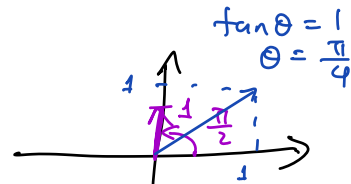
$$\cdot \angle \left(\frac{j}{1+j} \right) = \angle j - \angle(1+j) \\ = \frac{\pi}{2} - \frac{\pi}{4} = \frac{\pi}{4}$$



$$V_o \cos(\omega t + \phi) \Leftrightarrow \frac{V_o}{2} e^{j\phi}$$

$$\therefore \tilde{V}_{out} = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}} \cdot 6e^{j\frac{\pi}{2}} = \frac{6}{\sqrt{2}} e^{j\frac{3\pi}{4}} \quad \left[0, \frac{\pi}{6}, \frac{\pi}{4}, \frac{\pi}{3}, \frac{\pi}{2} \right]$$

$$\downarrow \\ V_{out}(t) = 2 \cdot \frac{6}{\sqrt{2}} \cos(100t - \frac{\pi}{4}) = \frac{12}{\sqrt{2}} \cos(100t - \frac{\pi}{4})$$

$$V_m(t) = 12 \cos(100t - \frac{\pi}{4})$$


$$V_{out}(t) = |H(j\omega)| \cdot V_o \cos(\omega t + \phi + \angle H(j\omega))$$

scaled by
 $|H(j\omega)|$


shifted by
 $\angle H(j\omega)$


conceptually all you need is the transfer function

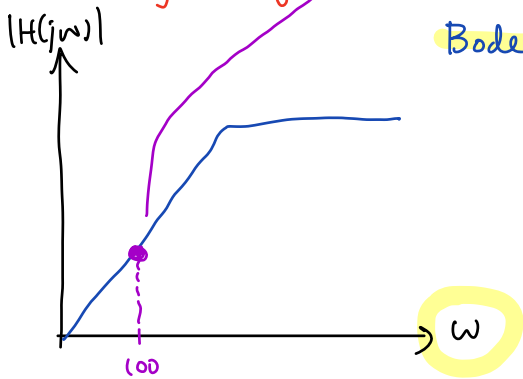$H(j\omega)$
 $\angle H(j\omega)$
at a given ω



Bode Plot $\angle H(j\omega)$

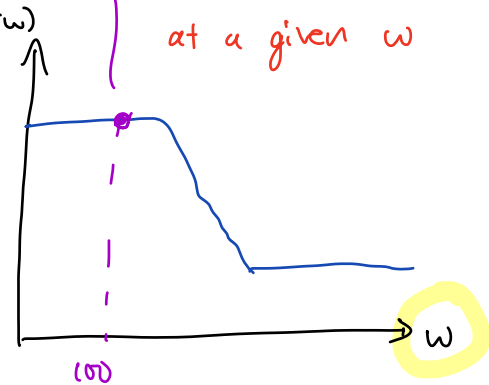

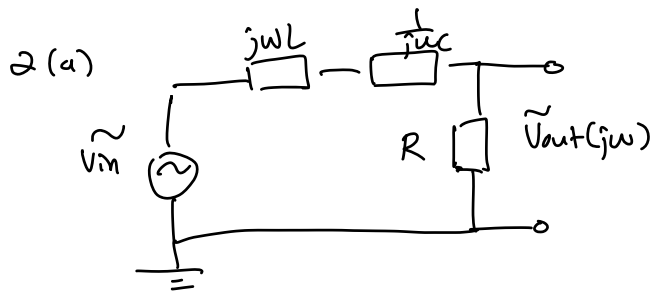

$$H(j\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$\begin{aligned} \text{(b) } Z_{RLC} &= Z_C + Z_L + Z_R \\ &= R + j\omega L + \frac{1}{j\omega C} = \underbrace{R}_{A(\omega)} + j \underbrace{(\omega L - \frac{1}{\omega C})}_{X(\omega)} \end{aligned}$$

$$X(\omega_n) = 0 \quad \rightarrow \quad \therefore \omega L - \frac{1}{\omega C} = 0$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1$$

$$\omega = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{LC}}$$

$$\therefore \omega_n = \frac{1}{\sqrt{LC}}$$