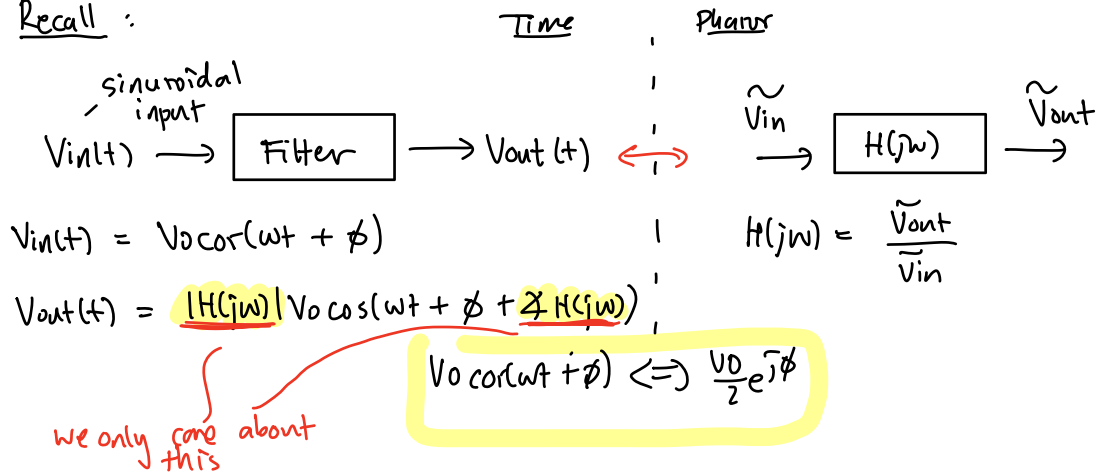


To do : Bode Plots

- ① Transfer Function Review
- ② Cutoff Freq
- ③ Bode Plot

Recall :



Bode Plot :



Cutoff Frequency : Frequency in which the magnitude is attenuated by $\frac{1}{\sqrt{2}}$


$$|H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

• Inspection : $H(j\omega) = \frac{k}{1 + j\frac{\omega}{\omega_c}}$ e.g. $H(j\omega) = \frac{1}{1 + j\omega RC}$

constant value (pointing to k)

$\omega_c = \frac{1}{RC}$


Q1(a)

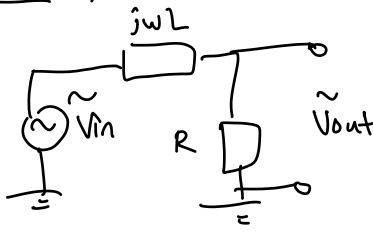

$$H(j\omega) = \frac{R}{R + j\omega L}$$

$$|H(j\omega)| = \left| \frac{R}{R + j\omega L} \right| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$
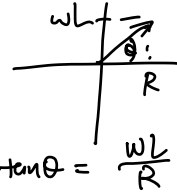
$$\begin{aligned} \angle H(j\omega) &= \angle R - \angle(R + j\omega L) \\ &= 0 - \text{atan2}(\omega L, R) \end{aligned}$$



$$\tan \theta = \frac{\omega L}{R}$$

(b) $H(j\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + \frac{j\omega L}{R}}$

$$\begin{aligned} \theta &= \arctan\left(\frac{\omega L}{R}\right) \\ &= \text{atan2}(\omega L, R) \end{aligned}$$


$\therefore \omega_c = \frac{R}{L}$ cutoff freq. for RL circuit

(c) $H(j\omega) = \frac{R}{R + j\omega L}$

$$|H(j\omega)| = \left| \frac{R}{R + j\omega L} \right| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$\begin{aligned} \angle H(j\omega) &= \angle R - \angle(R + j\omega L) \\ &= 0 - \text{atan2}(\omega L, R) \end{aligned}$$



Magnitude : $\omega = 0, |H(j\omega)| = 1$
 $\omega \rightarrow \infty, |H(j\omega)| \rightarrow 0$

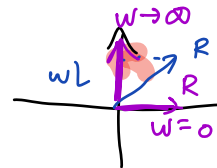



Phase : $\omega = 0, \angle H(j\omega) = -\text{atan2}(\omega L, R) = -0 = 0$

$\omega \rightarrow \infty, \angle H(j\omega) \rightarrow -\frac{\pi}{2}$

(c)

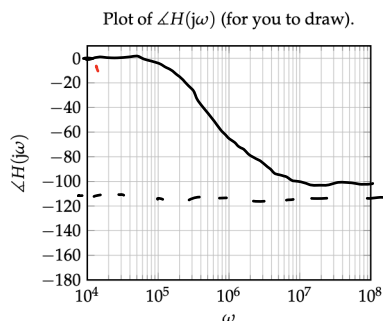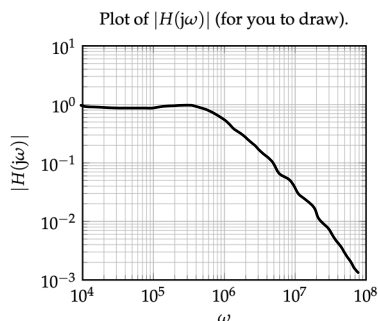

Cascading Filters

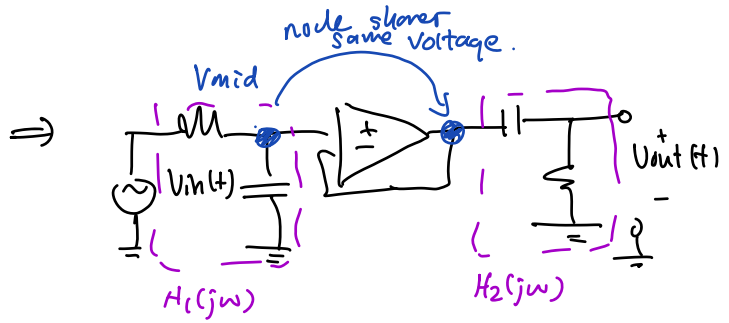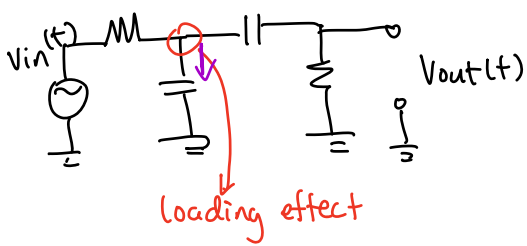

$$\begin{aligned} \tilde{V}_{mid} &= H_1(j\omega) \cdot \tilde{V}_{in} \text{ [at first filter]} \\ \tilde{V}_{out} &= H_2(j\omega) \cdot \tilde{V}_{mid} \text{ [at second filter]} \end{aligned} \quad \left. \vphantom{\begin{aligned} \tilde{V}_{mid} \\ \tilde{V}_{out} \end{aligned}} \right\} \tilde{V}_{out} = \underline{H_1(j\omega) \cdot H_2(j\omega)} \cdot \tilde{V}_{in}$$



cascading filter multiplier transfer functions

$$\begin{aligned} \tilde{V}_{out} &= |H_1(j\omega)| e^{j\phi_{H1}} \cdot |H_2(j\omega)| e^{j\phi_{H2}} \cdot \tilde{V}_{in} \\ &= \underline{|H_1(j\omega)| \cdot |H_2(j\omega)|} \cdot e^{j(\phi_{H1} + \phi_{H2})} \cdot \tilde{V}_{in} \end{aligned}$$

$$V_0 \cos(\omega t + \phi) \Leftrightarrow \frac{V_0}{2} e^{j\phi}$$


$$V_{out}(t) = \underline{|H_1(j\omega)| \cdot |H_2(j\omega)|} V_0 \cos(\omega t + \phi + \phi_{H1} + \phi_{H2})$$

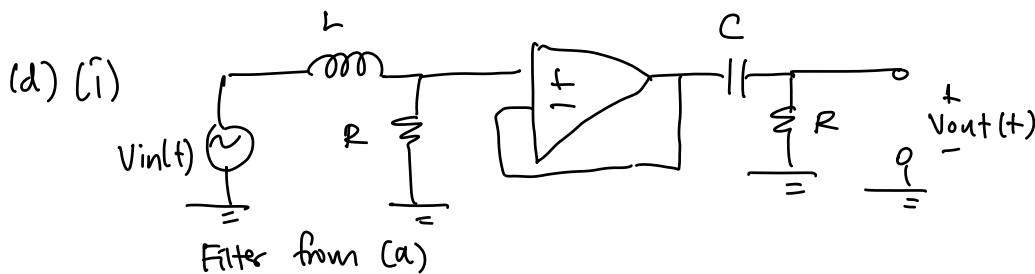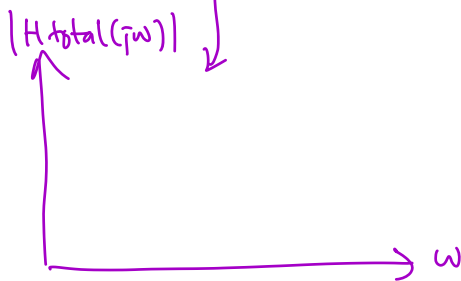What is the bode plot of $H_1(j\omega) \cdot H_2(j\omega)$ [combined filter]




$$V_{out}(t) = \underline{|H_1(j\omega)| \cdot |H_2(j\omega)|} V_0 \cos(\omega t + \phi + \phi_{H1} + \phi_{H2})$$



(ii)

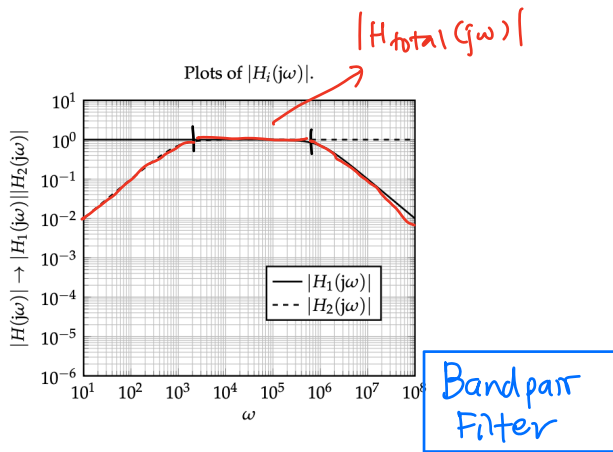

(iii)

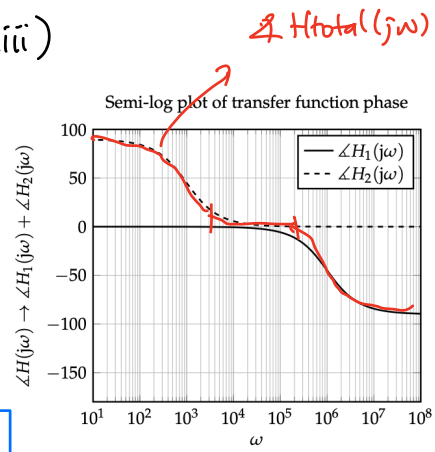

2(a)

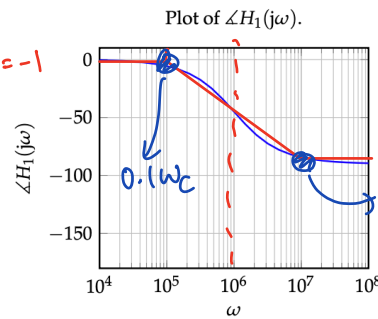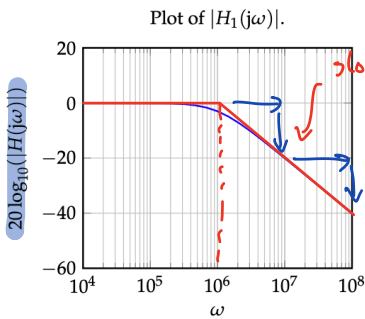



$\omega_c = \frac{R}{L} = 10^6$ [filter from (a)]

$|H(j\omega)| \rightarrow 20 \log_{10}(|H(j\omega)|)$ [decibel dB]

Straight Line Approximation



$\omega_c = \frac{1}{RC} = 10^3$

(b)





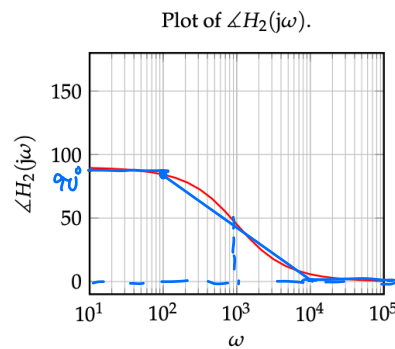
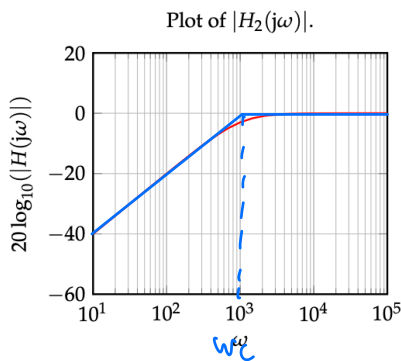


... R-HPF


(c)

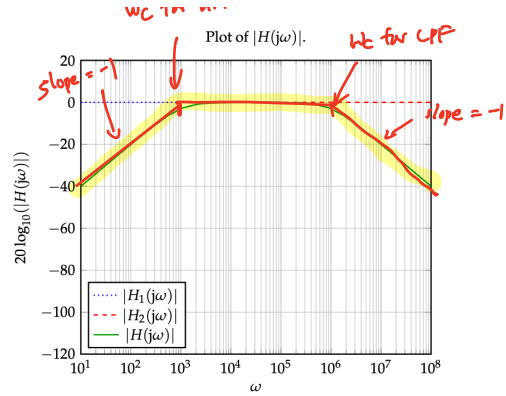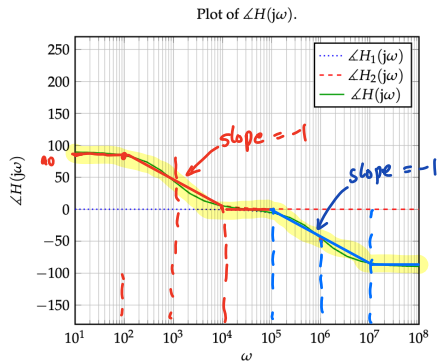

Not every filter has a slope of -1 :

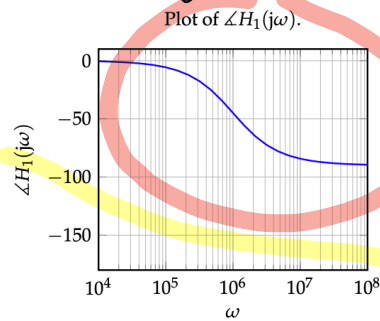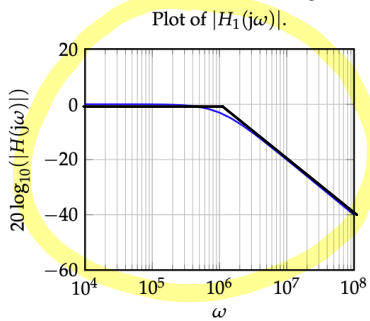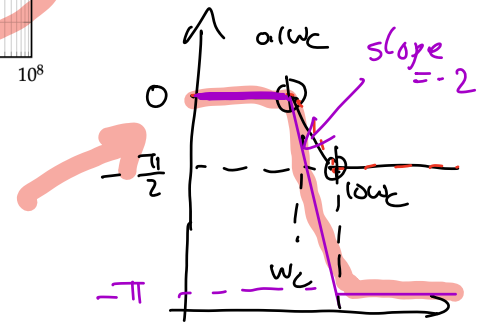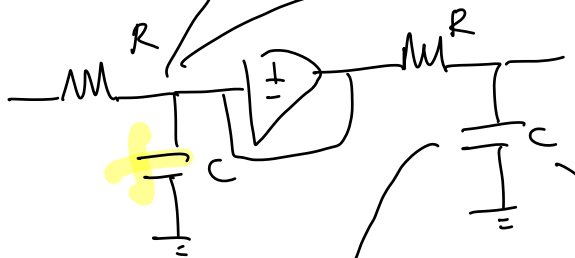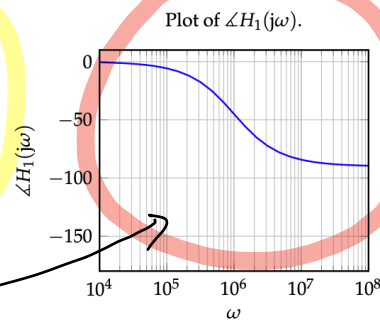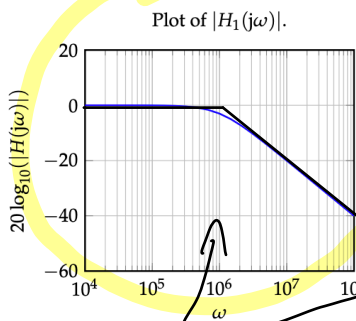


Overall transfer function $|H_{total}(j\omega)| =$

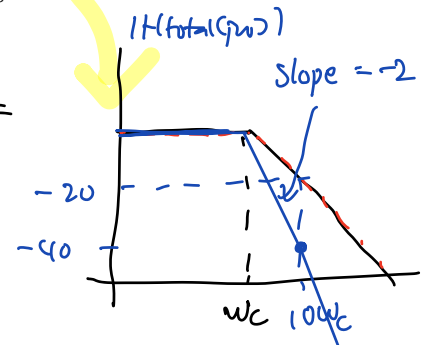


$$5 \cos(10^7 t)$$

$V_{in}(t)$

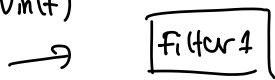


Plot of $|H_1(j\omega)|$.

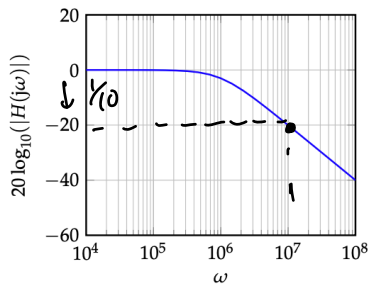


Falq m71
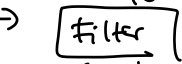
$$V_{out}(t) = 5 \times \frac{1}{10} \cos(10^7 t - \frac{\pi}{2})$$



Plot of $\angle H_1(j\omega)$.

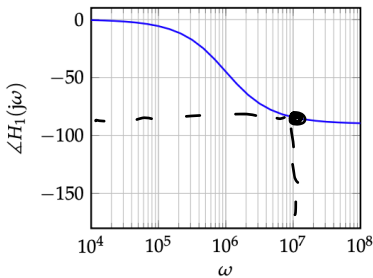

$$V_{out_2}(t) = \frac{5}{10} \times \frac{1}{10} \cos(10^7 t - \pi)$$

$$= \frac{5}{100} \cos(10^7 t - \pi)$$