

Lecture 2

- * Computing: Transistors & Logic
 - * Transistor RC model
 - * Solving RC circuits
 - * RC transients
-



MOSFET (metal-oxide semiconductor field effect transistor)
invented in 1959-60
by Atalia & Kaling

NMOS = n-channel MOSFET

PMOS = p-channel MOSFET


In the past and some present:

Planar devices

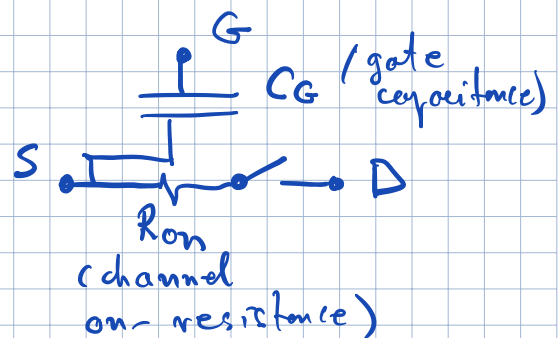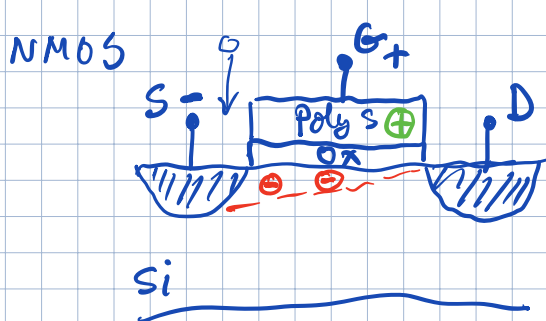

$$V_{GS} \geq V_{thn} \Rightarrow ON$$


$$V_{GS} < V_{thn} \Rightarrow OFF$$

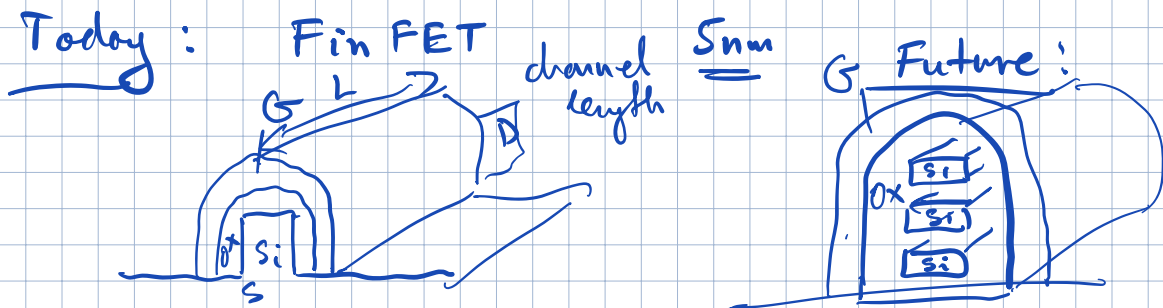

For more details take 105, 151, 130

To analyse this RC model we need to understand RC circuits.

Solving RC circuits:

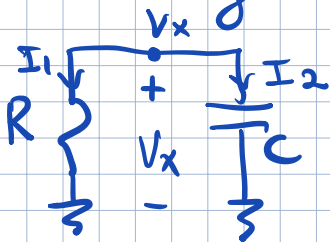

Elements:

$$I_2 = C \cdot \frac{dV_x}{dt}$$

$$V_x = I_1 \cdot R$$

KCL:

$$I_1 + I_2 = 0$$

Want to find $V_x(t)$ for $t \geq 0$.

$$I_1 = \frac{V_x}{R} \quad \text{KCL} \Rightarrow \frac{V_x}{R} + C \frac{dV_x}{dt} = 0$$

$$I_2 = C \frac{dV_x}{dt}$$

$$\boxed{\frac{dV_x}{dt} = -\frac{V_x}{RC}}$$

first order differential equation

① Guess: $V_x(t) = a \cdot e^{bt}$

(educated guess based on the properties of the derivative)

Initial condition:

$$t=0: V_x(0) = a \cdot e^{b \cdot 0} = a$$


$$\frac{d}{dt} V_x(t) = \frac{d}{dt} (a \cdot e^{bt}) = a \cdot b \cdot e^{bt} = b \cdot V_x(t)$$

since $\frac{dV_x}{dt} = -\frac{V_x}{RC} \Rightarrow b = -\frac{1}{RC}$

$V_x(t) = V_x(0) e^{-\frac{t}{RC}}$ is a solution to

$$\frac{dV_x}{dt} = -\frac{V_x}{RC}$$

$$\left. \frac{dV_x}{dt} \right|_{t=0} = -\frac{V_x(0)}{RC}$$

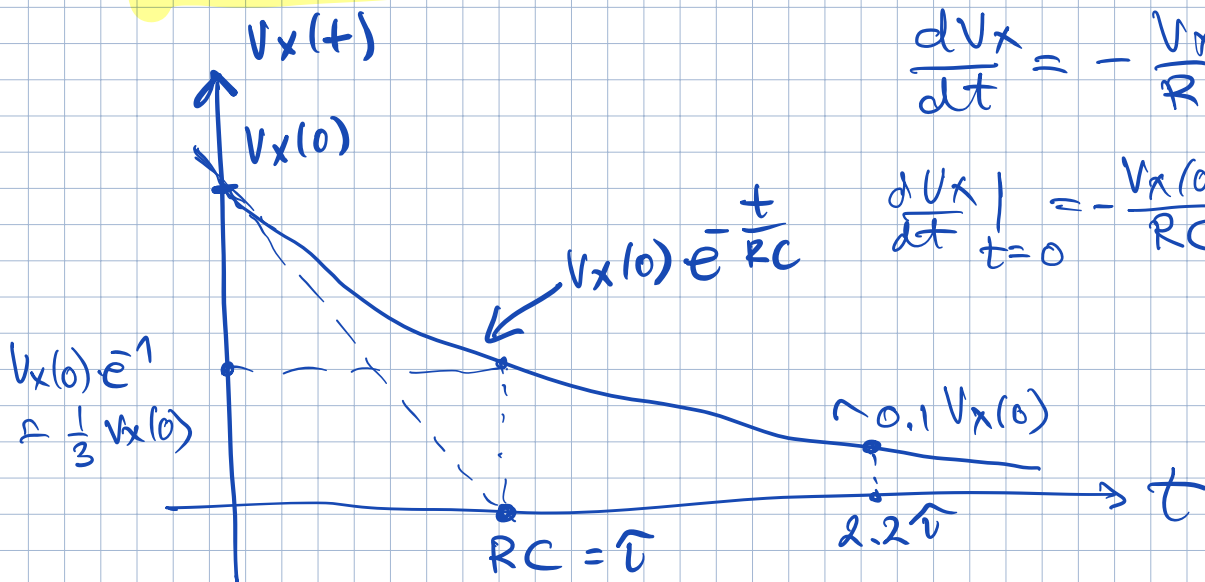

τ - time constant of the RC circuit

② check for uniqueness of the guess:

Suppose $y(t)$ which also solves D.E.

$$x(0) = x_0 \quad (1) \quad V_x(t) = x(t)$$

Shorter notation: $\frac{d}{dt} x(t) = \lambda x(t) \quad (2) \quad \lambda = -\frac{1}{RC}$

In ① we guessed & checked that

$$x_d(t) = x_0 \cdot e^{\lambda t} \quad t \geq 0$$

i.e. satisfies (1) & (2)

In ② need to prove $y(t) = x_d(t)$

- i.e. the solution
is unique

Either prove $\frac{y(t)}{x_d(t)} = 1$ or $y(t) - x_d(t) = 0$.

$$\frac{y(t)}{x_d(t)} = \frac{y(t)}{x_0 e^{\lambda t}}$$

Since $y(t)$ is a solution:
from (2) $\frac{d}{dt} y(t) = \lambda y(t)$ *

$$\frac{d}{dt} \left(\frac{y(t)}{x_d(t)} \right) = \frac{d}{dt} \left(\frac{y(t)}{x_0 e^{\lambda t}} \right) = \frac{1}{x_0} \frac{d}{dt} (y(t) \cdot e^{-\lambda t}) =$$

$$= \frac{1}{x_0} \left(\frac{d}{dt} y(t) \cdot e^{-\lambda t} + y(t) (-\lambda) \cdot e^{-\lambda t} \right) =$$

$$\stackrel{*}{=} \frac{1}{x_0} \left(\lambda y(t) e^{-\lambda t} - \lambda y(t) e^{-\lambda t} \right)$$

$$= 0 \quad \Rightarrow \quad \frac{y(t)}{x_d(t)} = a \quad (\text{constant}) \quad t \geq 0$$

From (1) $x(0) = x_0$




$y(0) = x_0$ since $y(t)$ is also
a solution

$$\frac{y(0)}{x_d(0)} = \frac{x_0}{x_0 e^{\lambda_0}} = \frac{x_0}{x_0} = 1 = a$$



$$\Rightarrow \frac{y(t)}{x_d(t)} = a = 1 \Rightarrow y(t) = x_d(t)$$

so the solution
 $x_d(t) = x_0 e^{\lambda t}$
is unique.

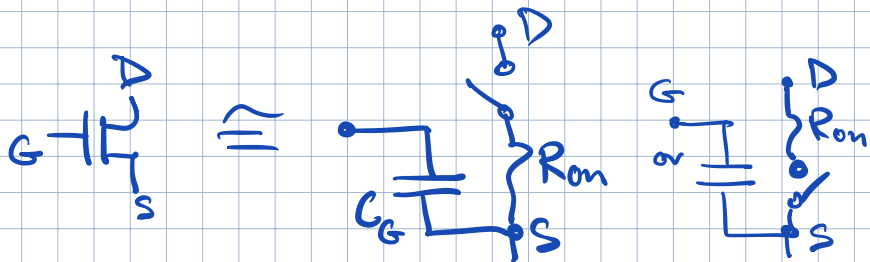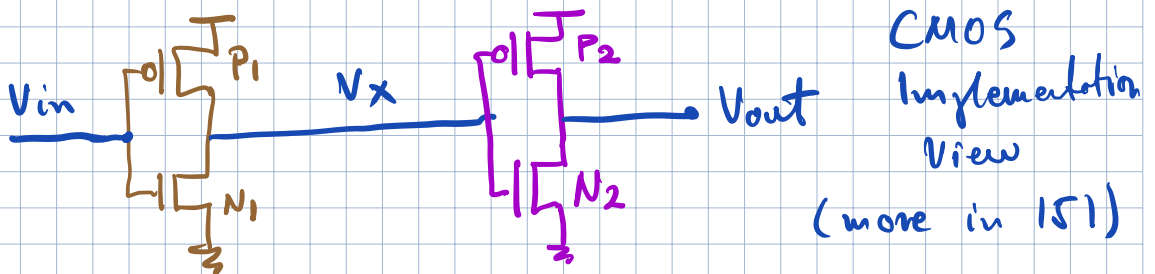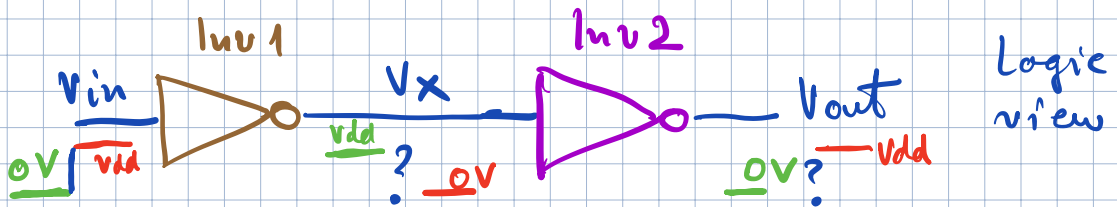Now we can use this to solve transistor circuits with RC model.



RC model view

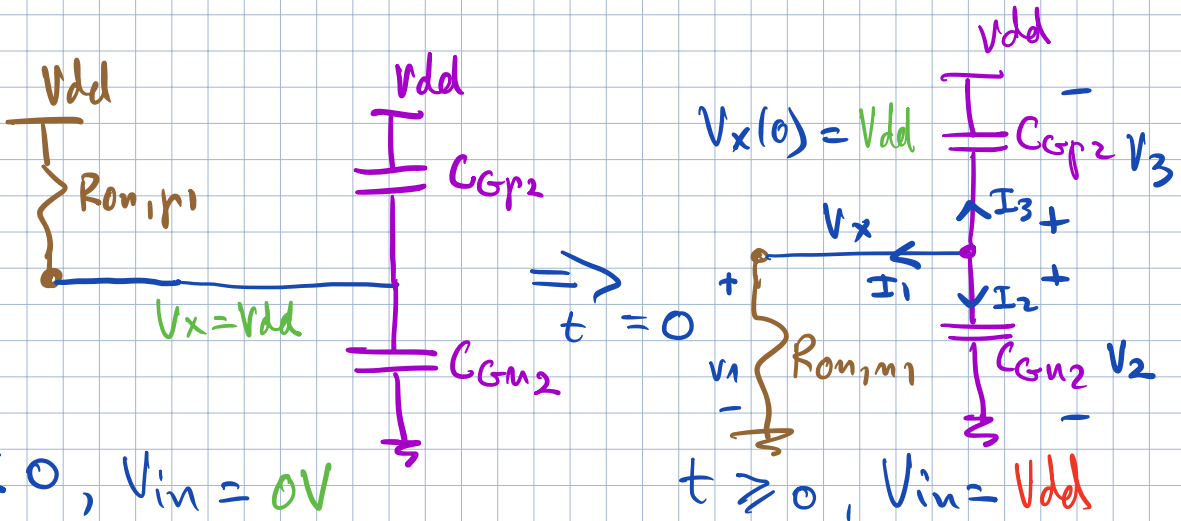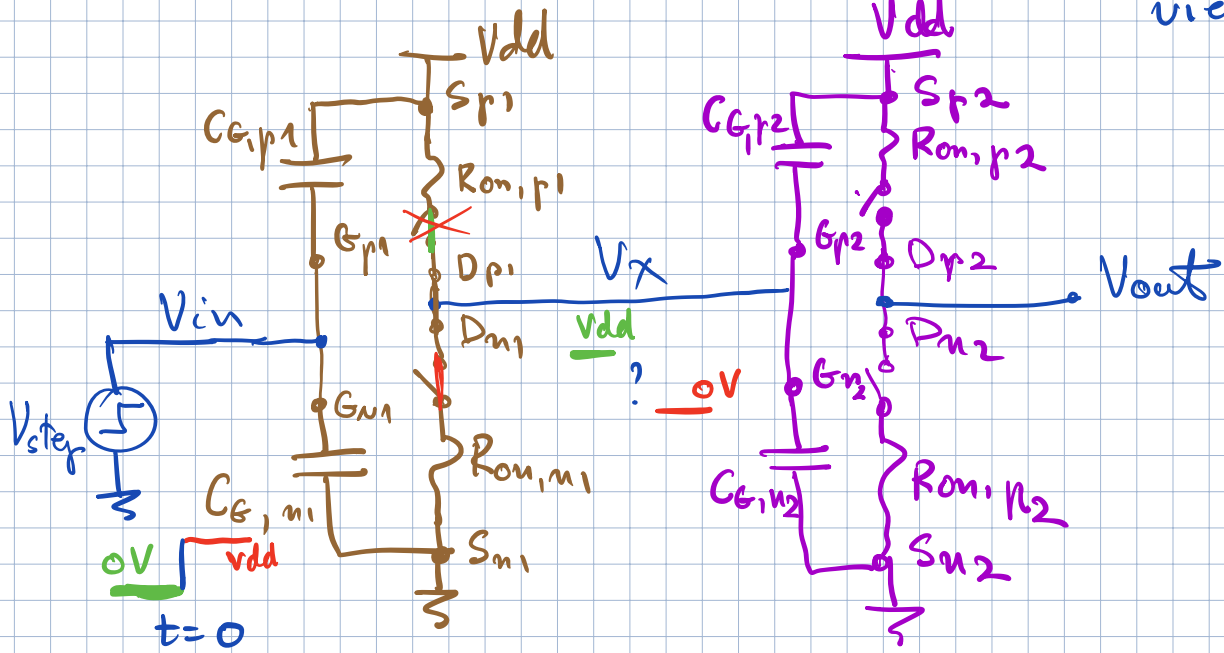

KCL: $I_1 + I_2 + I_3 = 0$

Elements: $V_1 = I_1 \cdot R_{on,m1}$

$$I_2 = C_{Gn2} \frac{dV_2}{dt}$$

$$I_3 = C_{Gp2} \frac{dV_3}{dt}$$

voltages:

$$V_1 = V_x$$

$$V_2 = V_x$$

$$V_3 = V_x - V_{dd}$$

Sub. into KCL:

$$\frac{V_1}{R_{on,n1}} + C_{gn2} \frac{dV_2}{dt} + C_{gp2} \frac{dV_3}{dt} = 0$$

$$\frac{V_x}{R_{on,n1}} + C_{gn2} \frac{dV_x}{dt} + C_{gp2} \frac{d}{dt}(V_x - V_{dd}) = 0$$

$$\frac{V_x}{R_{on,n1}} + C_{gn2} \frac{dV_x}{dt} + C_{gp2} \frac{d}{dt} V_x = 0$$

$$\frac{V_x}{R_{on,n1}} + (C_{gn2} + C_{gp2}) \frac{d}{dt} V_x = 0$$

$$\frac{d}{dt} V_x(t) = - \frac{V_x}{R_{on,n1} \cdot (C_{gn2} + C_{gp2})}$$

$$\tau = R_{on,n1} (C_{gn2} + C_{gp2})$$

determines
the speed
of transition.

Already have a solution for this:

$$t \geq 0: V_x(t) = V_x(0) e^{-\frac{t}{\tau}}$$

$$V_x(0) = V_{dd} \Rightarrow V_x(t) = V_{dd} \cdot e^{-\frac{t}{\tau}}$$