

Lecture 8

(1)

* Solving systems of diff. eqns. with Phasors
* i.e. transforming systems of diff. eqs.
into systems of linear eqns.

Refresher:

$$\frac{d}{dt} x(t) = \lambda x(t) + b u(t) \quad , \quad \text{when } u(t) = k \cdot e^{st}$$

$$t \geq 0: \quad x(t) = \underbrace{\left(x(0) - \frac{bk}{s-\lambda}\right) e^{\lambda t}}_{\text{annoying term}} + \underbrace{\frac{bk}{s-\lambda} e^{st}}_{\text{Nice term}}$$

annoying term
transient solution
b/c of initial conditions

Nice term, same form
as input (steady-state
solution)

Want the transient (first) part to disappear for $t \rightarrow \infty$

$$\text{If } \lambda < 0, \quad e^{\lambda t} \xrightarrow{t \rightarrow \infty} 0 \quad \text{and} \quad x(t) \xrightarrow{t \rightarrow \infty} \underbrace{\frac{bk}{s-\lambda} e^{st}}_{\text{steady-state solution}}$$

What about complex λ ?

$$e^{\lambda t} = e^{(\lambda_r + j\lambda_i)t} = e^{\lambda_r t} \cdot e^{j\lambda_i t} = e^{\lambda_r t} (\cos(\lambda_i t) + j \sin(\lambda_i t))$$

$$\text{so if } \lambda_r < 0 \quad e^{\lambda_r t} \xrightarrow{t \rightarrow \infty} 0 \quad \& \quad x(t) \xrightarrow{t \rightarrow \infty} \frac{bk}{s-\lambda} e^{st}$$

(steady-state solution)

(1) $\frac{d}{dt} \vec{x}(t) = A \vec{x}(t) + \vec{u}(t)$ system of diff. eqns. (2)

Let's consider inputs of the form $\sim e^{st}$ and assert that the solutions are $\sim e^{st}$, valid $s \neq \lambda$ and $\text{Re}(\lambda) < 0$, in steady-state.

$\vec{u}(t) = \vec{u} e^{st}$, \vec{u} vector of constants

Assert: $\vec{x}(t) = \vec{x} e^{st}$, \vec{x} vector of constants
 steady-state soln.

$\frac{d}{dt} \vec{x}(t) = \vec{x} \frac{d}{dt} e^{st} = s \vec{x} e^{st}$

$s \vec{x} e^{st} = A \vec{x} e^{st} + \vec{u} e^{st}$

$s \vec{x} = A \vec{x} + \vec{u}$

(2)

$$(sI - A) \vec{x} = \vec{u}$$

$$\vec{x} = (sI - A)^{-1} \vec{u}$$

system of lin. equations

Remember: $s \neq \lambda$


so $sI - A$ has no nullspace & is therefore invertible

$\vec{x}(t) = (sI - A)^{-1} \vec{u} e^{st}$

solution to (1) for $\vec{u}(t) = \vec{u} e^{st}$, under $s \neq \lambda$ & $\text{Re}(\lambda) < 0$

Can we use this for det directly?

(3)

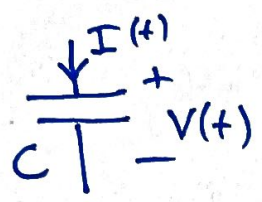

$$I(t) = C \frac{d}{dt} V(t)$$


$$\left. \begin{array}{l} \text{Assent: } I(t) = \hat{I} e^{st} \\ V(t) = \hat{V} e^{st} \end{array} \right\} \frac{V(t)}{I(t)} = \frac{\hat{V}}{\hat{I}}$$

$$I(t) = \hat{I} e^{st} = C \frac{d}{dt} (\hat{V} e^{st}) = C \hat{V} \frac{d}{dt} (e^{st}) = s C \hat{V} e^{st}$$

$$\hat{I} e^{st} = s C \hat{V} e^{st}$$

$$\boxed{\frac{\hat{V}}{\hat{I}} = \frac{1}{sC}}$$

(capacitor s-impedance)

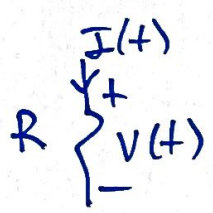


$$\begin{array}{l} v(t) = \hat{V} e^{st} \\ I(t) = \hat{I} e^{st} \end{array}$$

$$\begin{array}{l} v(t) = R I(t) \\ \hat{V} e^{st} = R \hat{I} e^{st} \end{array}$$

$$\boxed{\frac{\hat{V}}{\hat{I}} = R}$$

(resistor s-impedance)

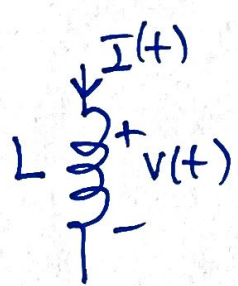


$$\begin{array}{l} v(t) = \hat{V} e^{st} \\ I(t) = \hat{I} e^{st} \end{array}$$


$$\begin{aligned} v(t) &= L \frac{d}{dt} I(t) \\ \hat{V} e^{st} &= L \frac{d}{dt} (\hat{I} e^{st}) \\ &= L \hat{I} \frac{d}{dt} (e^{st}) \\ \hat{V} e^{st} &= s L \hat{I} e^{st} \end{aligned}$$

$$\boxed{\frac{\hat{V}}{\hat{I}} = sL}$$

(inductor s-impedance)

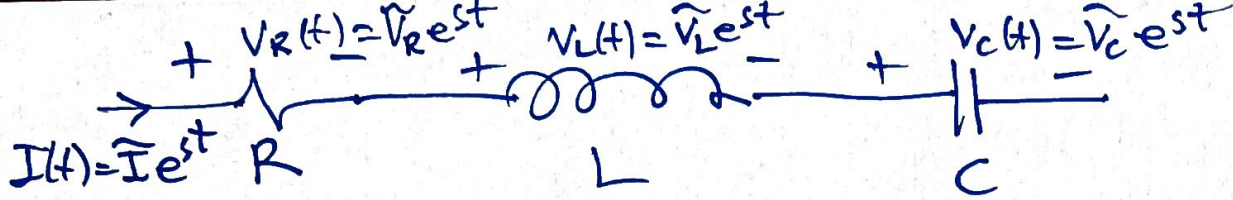

(24)

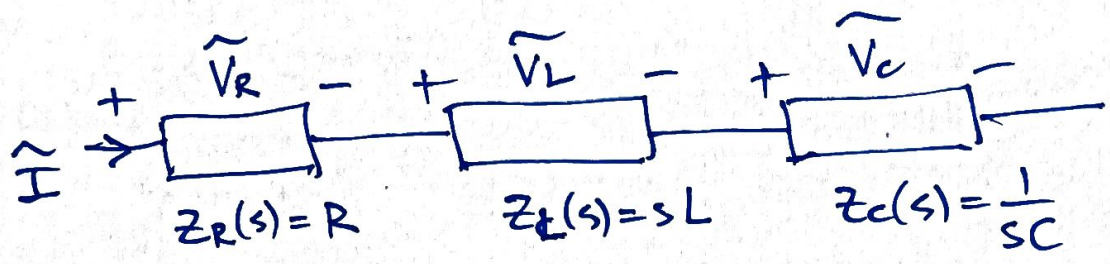

$$\widehat{V}_R = \widehat{I} Z_R \quad \widehat{V}_L = \widehat{I} Z_L \quad \widehat{V}_C = \widehat{I} Z_C \quad \left(\begin{array}{l} \text{Ohm's} \\ \text{law} \\ \text{for with} \\ s\text{-impedances} \end{array} \right)$$

For sinusoidal :

$$u(t) = U \cos(\omega t + \phi) = U \frac{e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)}}{2}$$

$$u(t) = \frac{U e^{j\phi}}{2} \cdot e^{j\omega t} + \frac{U e^{-j\phi}}{2} e^{-j\omega t} \quad (\text{real})$$

$\underbrace{\quad}_{\widehat{u}_1 = \widetilde{u}} \quad \underbrace{\quad}_{e^{s_1 t}} \quad \underbrace{\quad}_{\widehat{u}_2 = \overline{\widetilde{u}}} \quad \underbrace{\quad}_{e^{s_2 t}}$
 $\underbrace{\quad}_{s_1 = j\omega} \quad \underbrace{\quad}_{s_2 = -j\omega}$

always complex-conjugates

b/c $u(t)$ is real!

$$u(t) = \widehat{u} e^{s_1 t} + \overline{\widehat{u}} e^{s_2 t}$$

Use superposition to solve for the first & second component.

$$\vec{x}(t) = \vec{\widehat{x}}_1 e^{s_1 t} + \vec{\widehat{x}}_2 e^{s_2 t} \quad (\text{solution form})$$

For $s_1 = j\omega$: $M_1 = s_1 I - A(s_1) = j\omega I - A(j\omega)$

From (2)

$$M_1 \vec{x}_1 = \vec{u}$$

$$\vec{x}_1 = M_1^{-1} \vec{u}$$

independent sources

circuit topology

element currents & voltages $\begin{bmatrix} \vec{I} \\ \vec{V} \end{bmatrix}$

For $s_2 = -j\omega$: $M_2 = s_2 I - A(s_2) = -j\omega I - A(-j\omega) = -j\omega I - \bar{A}(j\omega) = \bar{M}_1$

$$M_2 \vec{x}_2 = \vec{u}$$

$$\vec{x}_2 = M_2^{-1} \vec{u}$$

$$\vec{x}_2 = \bar{M}_1^{-1} \vec{u} = \overline{M_1^{-1} \vec{u}} = \overline{\vec{x}_1}$$

so $\vec{x}(t) = \vec{x}_1 e^{s_1 t} + \vec{x}_2 e^{s_2 t}$ (superposition)

$$\vec{x}(t) = \vec{x}_1 e^{j\omega t} + \overline{\vec{x}_1} e^{-j\omega t}$$
 (real)

complex conjugates so

always so only need to solve for \vec{x}_1 .

so, all solutions :

$$\vec{V}(t) = \vec{V} e^{j\omega t} + \vec{V} e^{-j\omega t}$$

$$\vec{I}(t) = \vec{I} e^{j\omega t} + \vec{I} e^{-j\omega t}$$

so we only need to find (\vec{V}, \vec{I}) .

For sinusoidal inputs : \vec{V}, \vec{I} are phasors
(functions of $s = j\omega$)

s -impedances are called impedances.

Phasors turn IBB problems into IBA problems!

$$C \frac{+}{-} \frac{I(t)}{V(t)}$$

$$V(t) = V_0 \cos(\omega t + \phi)$$

$$V(t) = \underbrace{\frac{V_0}{2} e^{j\phi}}_{\vec{V}} e^{j\omega t} + \underbrace{\frac{V_0}{2} e^{-j\phi}}_{\vec{V}} e^{-j\omega t}$$


$$I(t) = C \frac{d}{dt} V(t) = C \frac{d}{dt} (\vec{V} e^{j\omega t} + \vec{V} e^{-j\omega t})$$

$$= \underbrace{j\omega C \vec{V} e^{j\omega t}}_{\vec{I}} + \underbrace{(-j\omega) C \vec{V} e^{-j\omega t}}_{\vec{I}}$$

$$= \hat{I} e^{j\omega t} + \hat{I} e^{-j\omega t}, \quad \hat{I} = j\omega C \vec{V}$$

$$\frac{\vec{V}}{\vec{I}} = z_C(s = j\omega) = \frac{1}{j\omega C}$$

Example 1: RC circuit

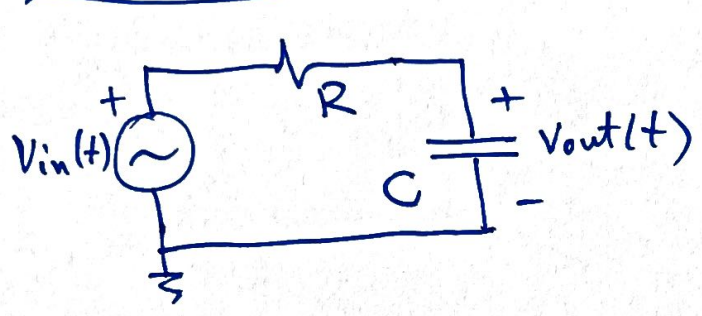


$$V_{in}(t) = V_{in} \cdot \cos(\omega t + \phi)$$

$$V_{out}(t) = ?$$

step 1: Write the independent sources as exponentials to determine the source phasors.

$$V_{in}(t) = \underbrace{\frac{V_{in}}{2} e^{j\phi} e^{+j\omega t}}_{\hat{V}_{in} \text{ phasor}} + \underbrace{\frac{V_{in}}{2} e^{j\phi} e^{-j\omega t}}_{\hat{V}_{in}}$$

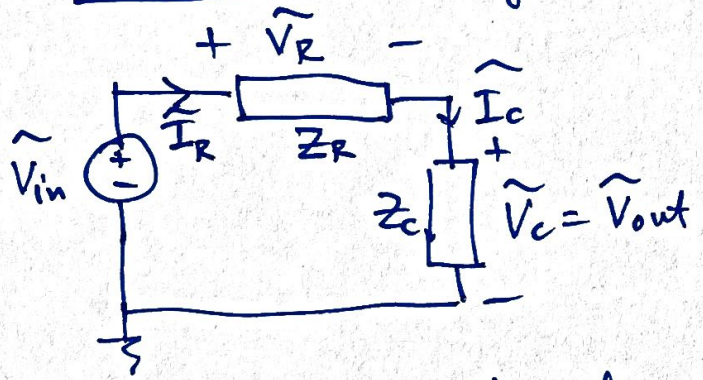step 2: Transform the circuit to phasor domain



$$Z_R = R \quad Z_C = \frac{1}{j\omega C}$$

step 3: Write down the circuit equations

Elements: $\hat{V}_R = Z_R \hat{I}_R \quad \hat{V}_C = Z_C \hat{I}_C$


KCL: $\hat{I}_R = \hat{I}_C$

Voltages: $\hat{V}_R = \hat{V}_{in} - \hat{V}_C \quad , \quad \hat{V}_C = \hat{V}_{out}$

step 4: Solve the circuit

$$\hat{V}_{out} = \hat{V}_C = \frac{Z_C}{Z_C + Z_R} \hat{V}_{in} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \hat{V}_{in} = \frac{1}{1 + j\omega RC} \hat{V}_{in}$$
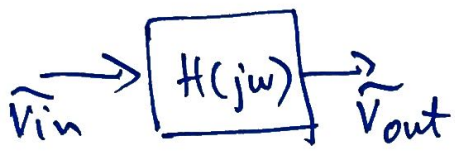
$$\tilde{V}_{out}(j\omega) = \frac{1}{1+j\omega RC} \cdot \tilde{V}_{in}(j\omega)$$



$$H(j\omega) = \frac{\tilde{V}_{out}(j\omega)}{\tilde{V}_{in}(j\omega)}$$

transfer function

For our Low-pass RC example:

$$H_{LP}(j\omega) = \frac{1}{1+j\omega RC} = \frac{1-j\omega RC}{1+(\omega RC)^2}$$


$$|H_{LP}(j\omega)| = \frac{1}{|1+j\omega RC|} = \frac{1}{\sqrt{1+(\omega RC)^2}}$$

$$\angle H_{LP}(j\omega) = -\arctan(\omega RC)$$

$$\tilde{V}_{out} = |\tilde{V}_{out}| e^{j\angle \tilde{V}_{out}}$$

$$\tilde{V}_{in} = |\tilde{V}_{in}| e^{j\angle \tilde{V}_{in}}$$

$$H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$$

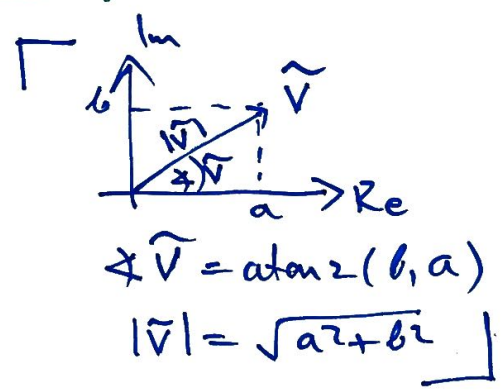

$$\tilde{V}_{out} = |\tilde{V}_{out}| e^{j\angle \tilde{V}_{out}} = \tilde{V}_{in} \cdot H(j\omega) =$$

$$= |\tilde{V}_{in}| e^{j\angle \tilde{V}_{in}} \cdot |H(j\omega)| e^{j\angle H(j\omega)}$$

$$= |H(j\omega)| |\tilde{V}_{in}| \cdot e^{j(\angle H(j\omega) + \angle \tilde{V}_{in})}$$

$$|\tilde{V}_{out}| = |H(j\omega)| \cdot |\tilde{V}_{in}|$$

$$\angle \tilde{V}_{out} = \angle H(j\omega) + \angle \tilde{V}_{in}$$

sty 5: Convert to time domain

(69)

$$\begin{aligned}V_{out}(t) &= \widehat{V}_{out} e^{j\omega t} + \overline{\widehat{V}_{out}} e^{-j\omega t} \\&= |\widehat{V}_{out}| e^{j\angle \widehat{V}_{out}} \cdot e^{j\omega t} + |\widehat{V}_{out}| e^{-j\angle \widehat{V}_{out}} \cdot e^{-j\omega t} \\&= |\widehat{V}_{out}| e^{j(\omega t + \angle \widehat{V}_{out})} + |\widehat{V}_{out}| e^{-j(\omega t + \angle \widehat{V}_{out})} \\&= 2 |\widehat{V}_{out}| \cos(\omega t + \angle \widehat{V}_{out})\end{aligned}$$

Similarly: $V_{in}(t) = \underbrace{2 |\widehat{V}_{in}|}_{V_{in}} \cos(\omega t + \underbrace{\angle \widehat{V}_{in}}_{\phi})$

$$V_{out}(t) = 2 |H_{LP}(j\omega)| \underbrace{|\widehat{V}_{in}|}_{\frac{V_{in}}{2}} \cos(\omega t + \underbrace{\angle \widehat{V}_{in}}_{\phi} + \angle H_{LP}(j\omega))$$

$$= 2 \frac{1}{\sqrt{1+(\omega RC)^2}} \cdot \frac{V_{in}}{2} \cos(\quad)$$

$$= \frac{V_{in}}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + \phi + \angle H_{LP}(j\omega))$$

\downarrow
 $-\arctan(\omega RC, 1)$