

Lecture 10

(21)

* Design example - bandpass filter



V_{in} components :

| | freq | amplitude | |
|------------------------|--------|-----------|------------------|
| signal | 600 Hz | 1 mV | } interference X |
| (alternate current) AC | 60 Hz | 10 mV | |
| fluorescent light | 60 kHz | 20 mV | |

Design goal: Want to attenuate the interference

(AC and fluorescent) components by $100\times$, but keep the signal.


$$V_{in}(t) = V_{AC} \cos(\omega_{AC}t + \phi_{AC}) + V_S \cos(\omega_S t + \phi_S) + V_F \cos(\omega_F t + \phi_F)$$

$$\omega_{AC} = 2\pi \cdot 60 \text{ Hz} = 377 \frac{\text{rad}}{\text{s}}$$

$$\omega_S = 2\pi \cdot 600 \text{ Hz}$$

$$\omega_F = 2\pi \cdot 60 \text{ kHz}$$

strategy:

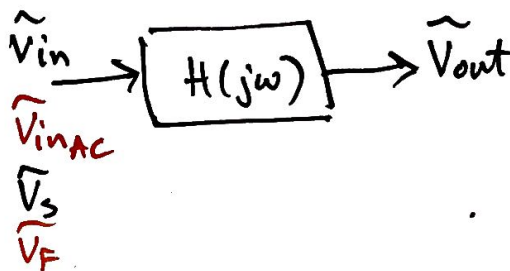



$$V_{out}(t) = |H(j\omega_{AC})| \cdot V_{AC} \cdot \cos(\omega_{AC}t + \phi_{AC} + \angle H(j\omega_{AC}))$$

$$+ |H(j\omega_S)| \cdot V_S \cdot \cos(\omega_S t + \phi_S + \angle H(j\omega_S))$$


$$+ |H(j\omega_F)| \cdot V_F \cdot \cos(\omega_F t + \phi_F + \angle H(j\omega_F))$$

Design goal:

$$|H(j\omega_c)| = \frac{1}{100} \quad |H(j\omega_p)| = \frac{1}{100}$$

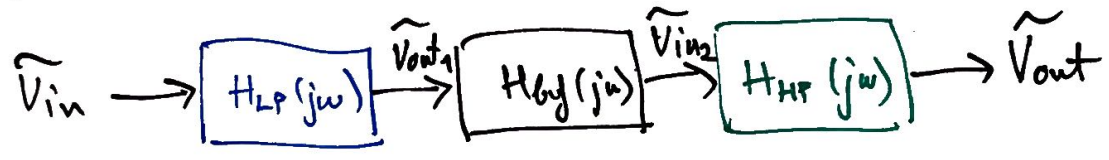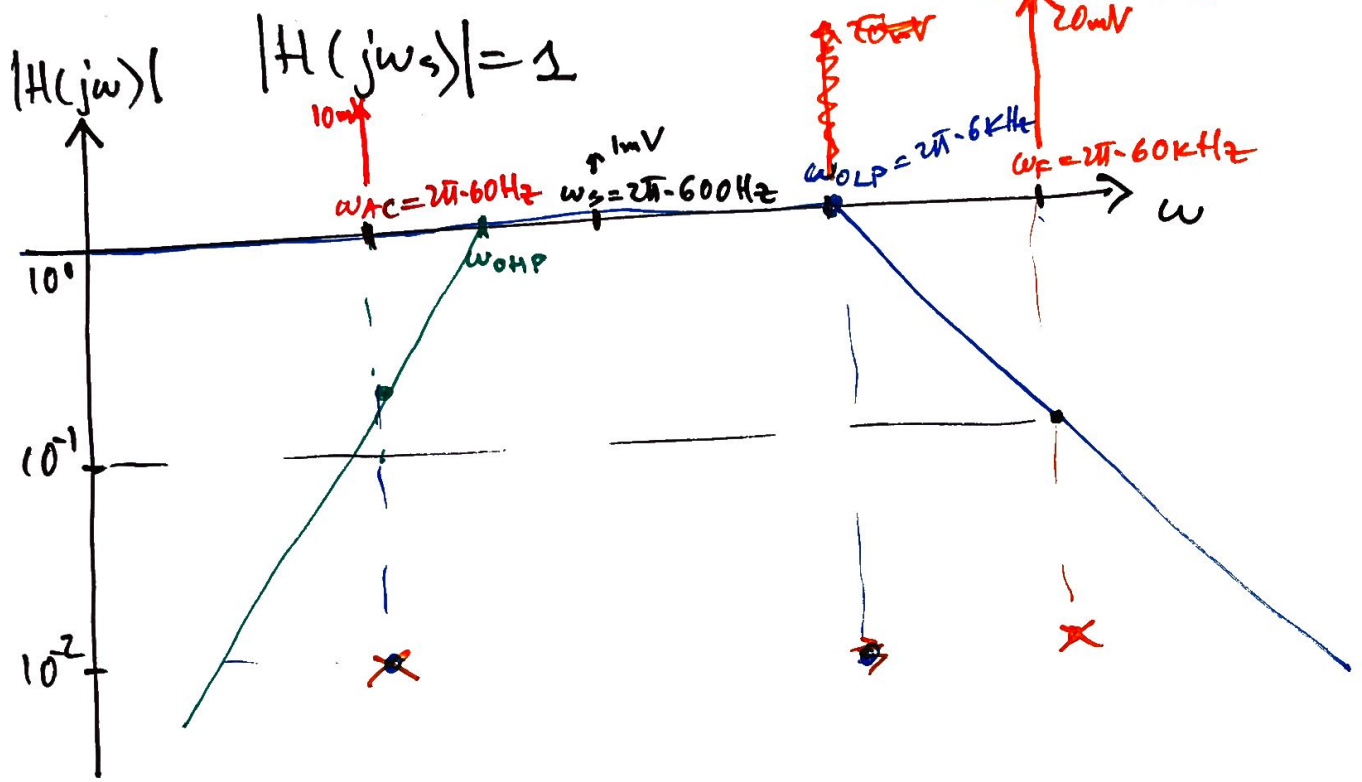


$H_{LP}(j\omega)$ - a "low-pass" filter

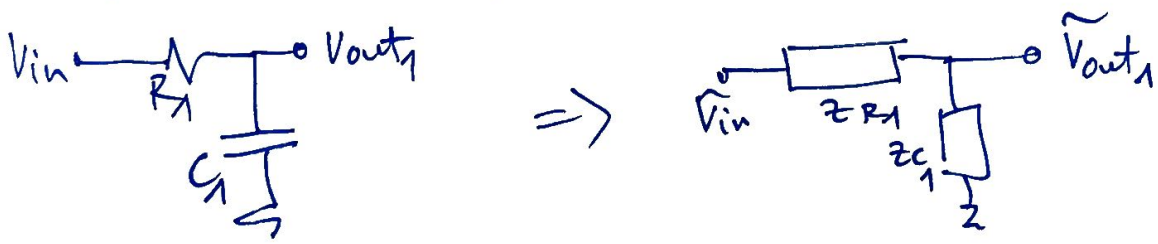


$$H_{LP}(j\omega) = \frac{\widehat{V}_{out1}}{\widehat{V}_{in}} = \frac{1}{1 + j \frac{\omega}{\omega_{OLP}}} \quad , \quad \omega_{OLP} = \frac{1}{R_1 C_1}$$

$H_{HP}(j\omega)$ - a "high-pass" filter

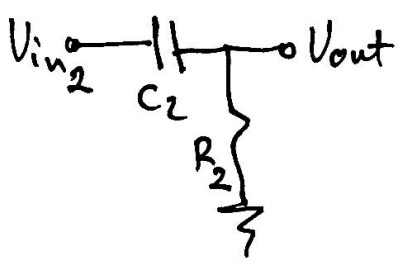

=>

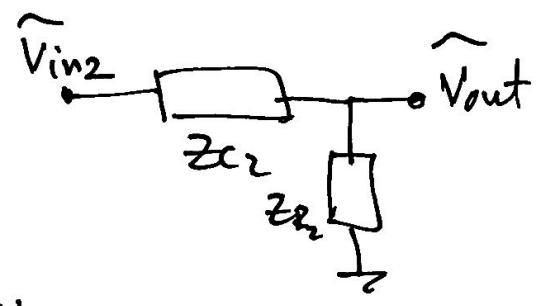

$$H_{HP}(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in2}} = \frac{j \frac{\omega}{\omega_{OHP}}}{1 + j \frac{\omega}{\omega_{OHP}}} = \frac{1}{1 - j \frac{\omega_{OHP}}{\omega}}, \quad \omega_{OHP} = \frac{1}{R_2 C_2}$$

$$H(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}} = \frac{\widehat{V}_{out}}{\widehat{V}_{in2}} \cdot \underbrace{\frac{\widehat{V}_{in2}}{\widehat{V}_{out1}}}_{H_{HP}(j\omega)} \cdot \underbrace{\frac{\widehat{V}_{out1}}{\widehat{V}_{in}}}_{H_{LP}(j\omega)} =$$

$$= \frac{1}{1 + j \frac{\omega}{\omega_{OLP}}} \cdot \frac{1}{1 - j \frac{\omega_{OHP}}{\omega}}$$

Need to choose ω_{OLP} & ω_{OHP} .

Compromise - want to attenuate the interference w/o attenuating the signal.

$$\omega_{OHP} = \sqrt{\omega_{AC} \cdot \omega_s}$$

$$\log \omega_{OHP} = \frac{1}{2} \log \omega_{AC} + \frac{1}{2} \log \omega_s$$

$$\omega_{OLP} = \sqrt{\omega_s \cdot \omega_F}$$

$$\omega_{OHP} = \frac{1}{R_2 C_2}, \quad \omega_{OLP} = \frac{1}{R_1 C_1}$$


$$\omega_{OHP} = \sqrt{2\pi \cdot 60\text{Hz} \cdot 2\pi \cdot 600\text{Hz}} = 2\pi \cdot 190\text{Hz}$$

$$\omega_{OLP} = \sqrt{2\pi \cdot 600\text{Hz} \cdot 2\pi \cdot 60\text{kHz}} = 2\pi \cdot 6\text{kHz}$$

Pick a reasonable C:

$$C_1 = 1\text{ nF} \Rightarrow R_1 = \frac{1}{\omega_{\text{OLP}} \cdot C_1} = 26\text{ k}\Omega$$
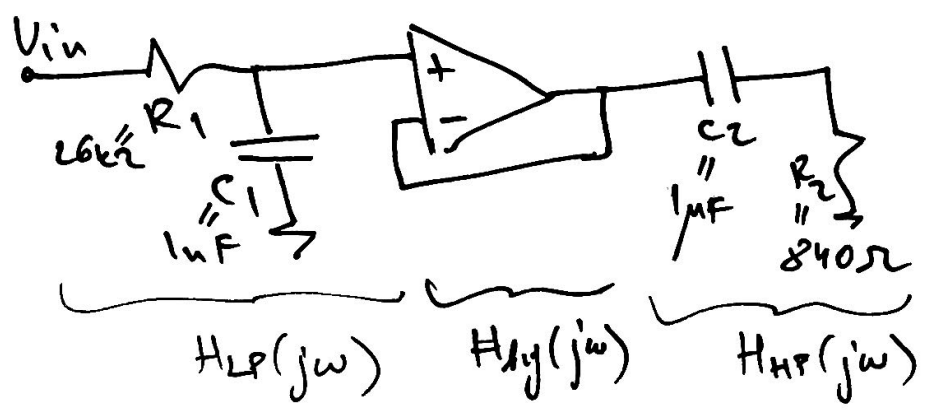
$$C_2 = 1\text{ }\mu\text{F} \Rightarrow R_2 = \frac{1}{\omega_{\text{OHP}} \cdot C_2} = 840\Omega$$




Check: Evaluate the TF $H(j\omega)$ @ $\omega_{AC}, \omega_s, \omega_F$

| ω | $ H_{LP}(j\omega) $ | $ H_{HP}(j\omega) $ | $ H(j\omega) $ | $V_{in} \cdot H(j\omega) = V_{out}$ |
|----------------------------|---|--|-----------------------------|---|
| $2\pi \cdot 60\text{ Hz}$ | $\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 60\text{ Hz}}{6\text{ kHz}}\right)^2}} \approx 1$ | $\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 190\text{ Hz}}{2\pi \cdot 60\text{ Hz}}\right)^2}} \approx 0.3$ | $1 \cdot 0.3 \approx 0.3$ | $10\text{ mV} \cdot 0.3 = 3\text{ mV}$ |
| $2\pi \cdot 600\text{ Hz}$ | $\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 600\text{ Hz}}{6\text{ kHz}}\right)^2}} \approx 1$ | ≈ 0.95 | $1 \cdot 0.95 \approx 0.95$ | $1\text{ mV} \cdot 0.95 = 0.95\text{ mV}$ |
| $2\pi \cdot 60\text{ kHz}$ | $\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 60\text{ kHz}}{6\text{ kHz}}\right)^2}} = 0.1$ | ≈ 1 | $1 \cdot 0.1 = 0.1$ | $20\text{ mV} \cdot 0.1 = 2\text{ mV}$ |

Wanted $\frac{1}{100}$ for $|H_{HP}(j\omega_{AC})|$ & $|H(j\omega_F)|$
 but only got $0.3 \leftarrow 0.1$ - not quite enough. 😞


Can keep going ...

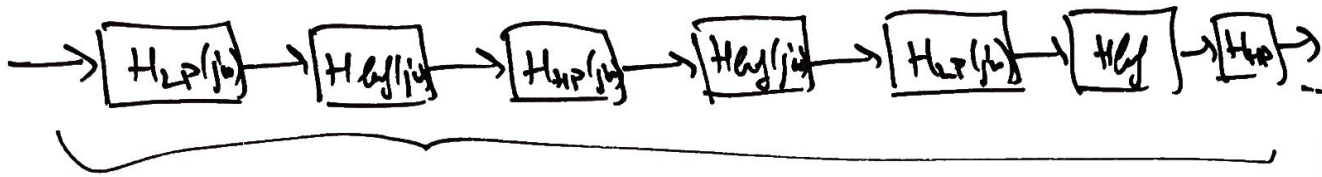

$$H_{tot}(j\omega) = H_{LP}(j\omega) H_{HP}^m(j\omega)$$

$$|H_{tot}(j\omega_{AC})| = \frac{1}{100} = 1^m \cdot 0.3^m \Rightarrow m=4$$

$$|H_{tot}(j\omega_F)| = \frac{1}{100} = 0.1^m \cdot 1^m \Rightarrow \cancel{m=2} \\ m=2$$

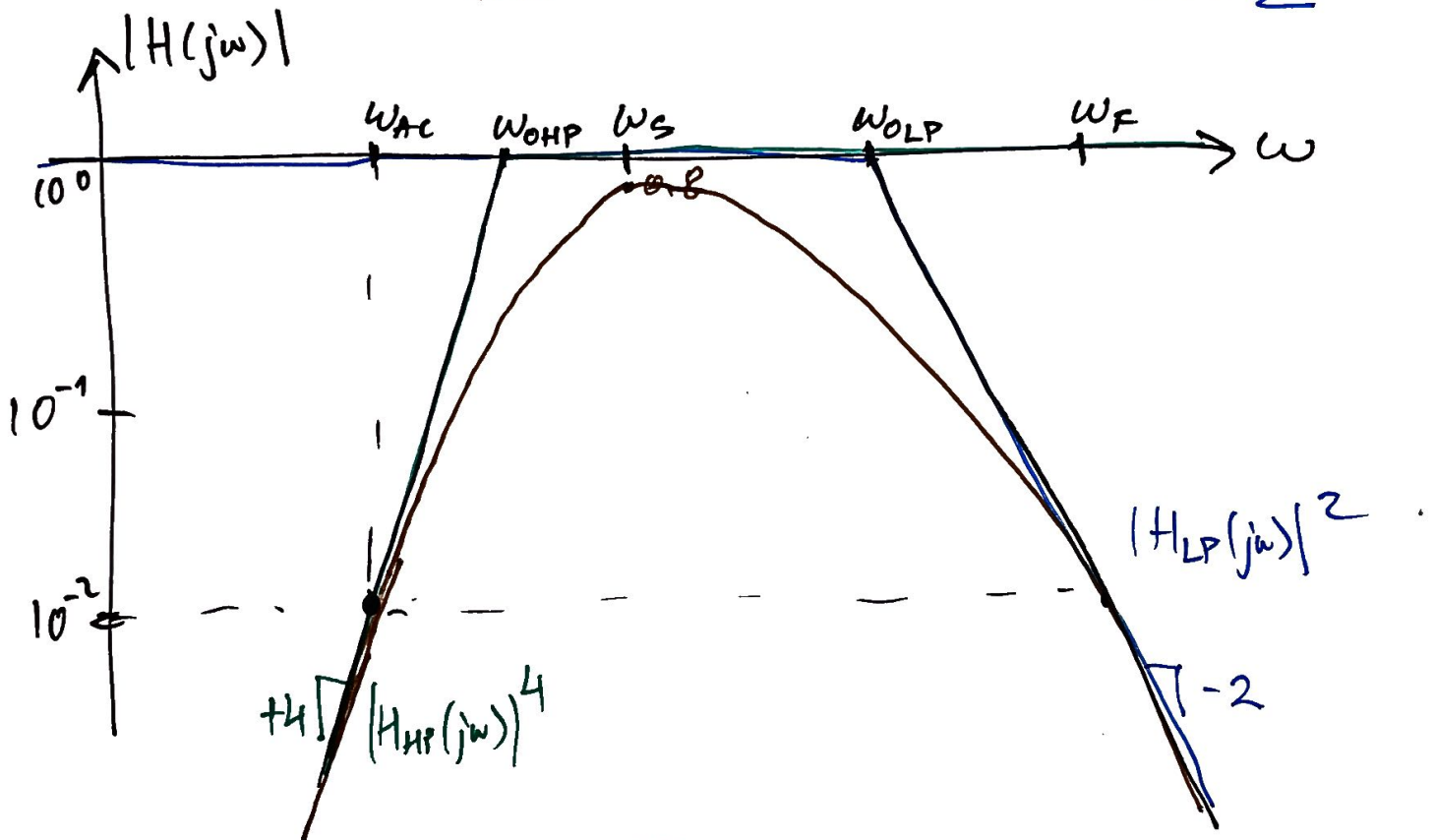

$$|H_{tot}(j\omega_S)| = 1^m \cdot 0.95^m = 0.8 \text{ (o.k. but not great)}$$

$$H_{tot}(j\omega) = \frac{\left(j \frac{\omega}{\omega_{HP}}\right)^4}{\left(1 + j \frac{\omega}{\omega_{HP}}\right)^4 \cdot \left(1 + j \frac{\omega}{\omega_{LP}}\right)^2}$$

In general:

$$H(j\omega) = K \frac{(j\omega)^{N_{z0}} \cdot (1 + j\frac{\omega}{\omega_{z1}}) \dots (1 + j\frac{\omega}{\omega_{zn}})}{(j\omega)^{N_{p0}} (1 + j\frac{\omega}{\omega_{p1}}) \dots (1 + j\frac{\omega}{\omega_{pm}})}$$

← origin zeros
↑ origin poles

ω_{zn} - zeroes
 ω_{pm} - poles


} control systems terminology
(105, 120, ...)

What if our desired signal is at 100 Hz?

- Our previous design won't work 😞

Need a different filter!

Inductor to the rescue!

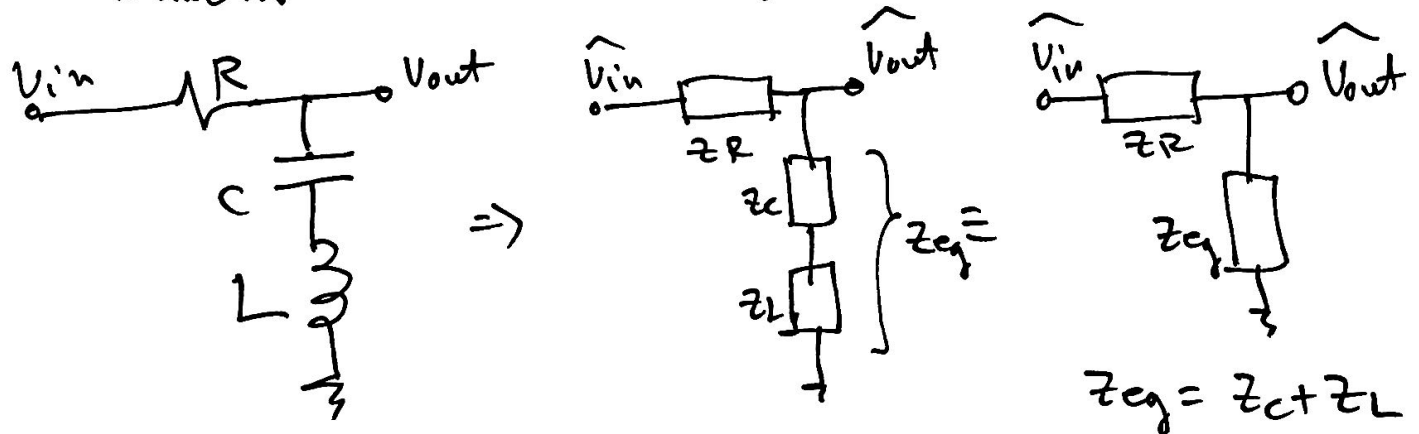

$$z_{eq} = z_C + z_L = \frac{1}{j\omega C} + j\omega L = j\left(\omega L - \frac{1}{\omega C}\right) \text{ Fantastic!}$$


$$H(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}} = \frac{z_{eq}}{z_{eq} + z_R}$$

say $z_{eq}(j\omega_0) = 0 = j\left(\underbrace{\omega_0 L - \frac{1}{\omega_0 C}}_0\right)$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$|H(j\omega_0)| = \left| \frac{\cancel{z_{eq}(j\omega_0)}^0}{z_{eq}(j\omega_0) + z_R} \right| = \left| \frac{0}{z_R} \right| = 0$$
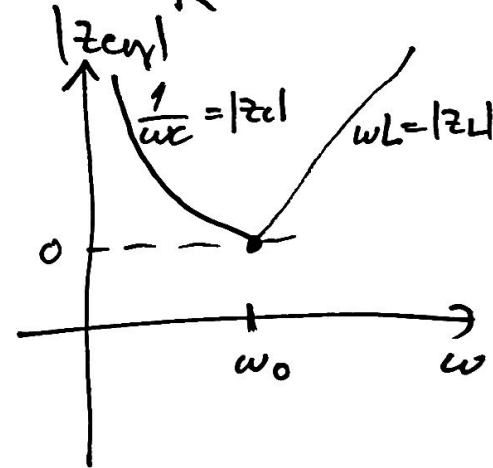
$$H(j\omega) = \frac{j(\omega L - \frac{1}{\omega C})}{R + j(\omega L - \frac{1}{\omega C})}$$



$$\omega_0 = \omega_{AC} = 2\pi \cdot 60 \text{ Hz}$$


$$C = 100 \mu\text{F} \Rightarrow L = 70 \text{ mH}$$



$$H(j\omega_0) = 0$$

"2\pi \cdot 60 \text{ Hz}"

$$H(j2\pi \cdot 55 \text{ Hz}) = \frac{j \cdot 3.5 \Omega}{R + j3.5 \Omega} \quad \text{for } R = 3 \Omega$$

$$H(j2\pi \cdot 65 \text{ Hz}) = \frac{j4.7 \Omega}{R + j4.7 \Omega} \quad \text{for } |H(j2\pi \cdot 55, 65)| \approx 0.5$$

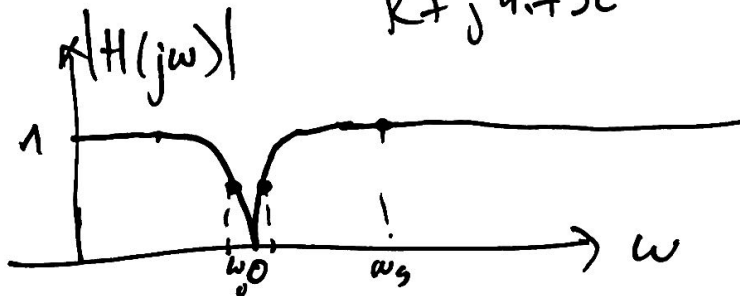

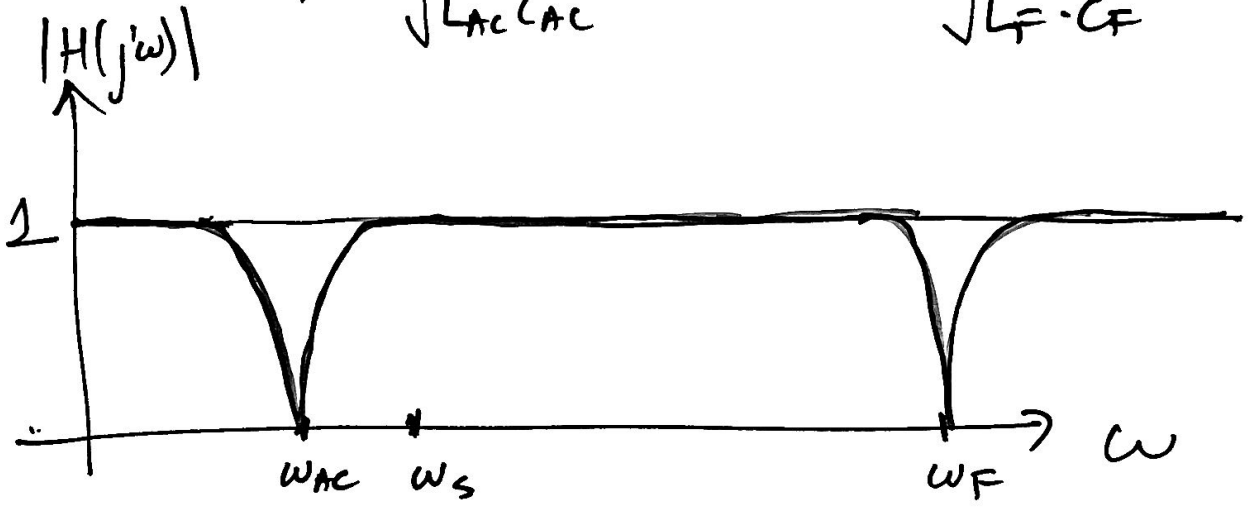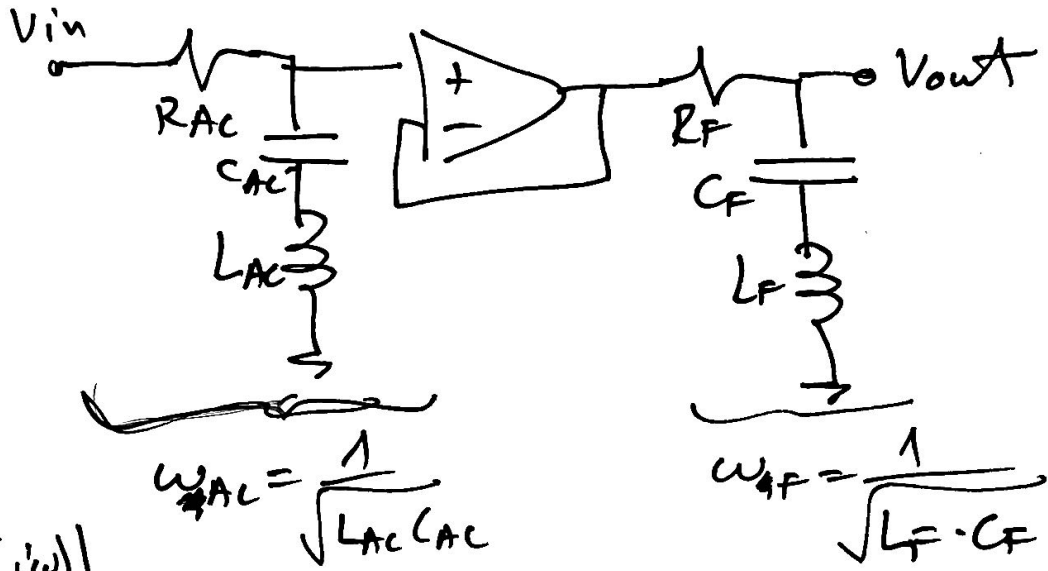

Band-pass:

