

1. NMOS Logic Inverter

(a) We have an NMOS logic implementation of an inverter shown below. The circuit has a voltage input $V_{in}(t) = t, t \geq 0, (V_{in}(t) = 0\text{ V for } t \leq 0)$ seen below.



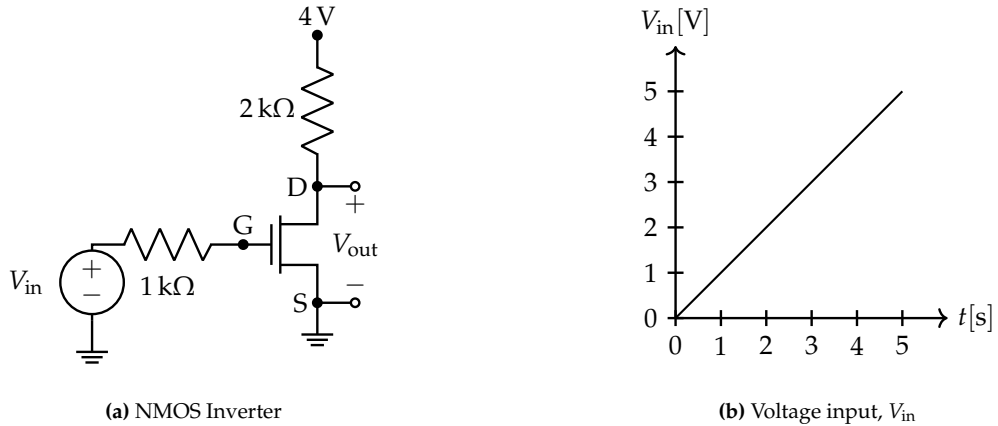


Figure 1: Circuit figure and input signal.

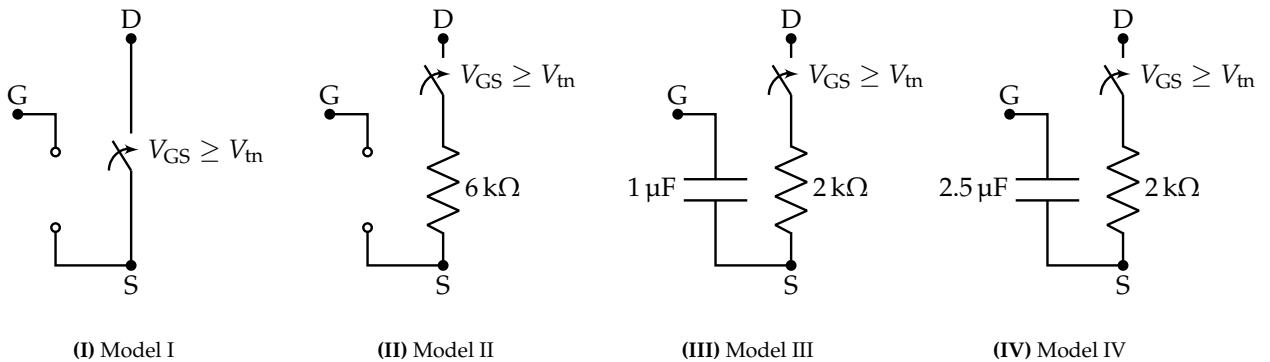
For the transistor models below, define the threshold voltage as $V_{tn} = 2\text{ V}$. **Match each NMOS transistor model, plugged into the NMOS inverter circuit, with its corresponding V_{out} plot on the next page.** (Note: All capacitors are fully discharged at $t = 0$.)



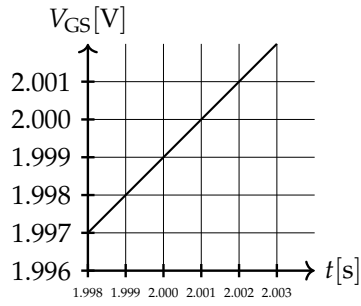
(HINT: You can use the below graphs to evaluate V_{GS} for Models III and IV. We recommend using a scratch page to draw out the NMOS Inverter circuit with the various transistor models plugged in.)




(a) V_{GS} for Model III

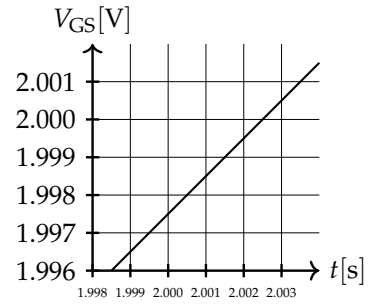


(b) V_{GS} for Model IV

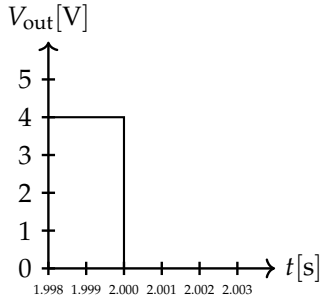


(A) Plot A

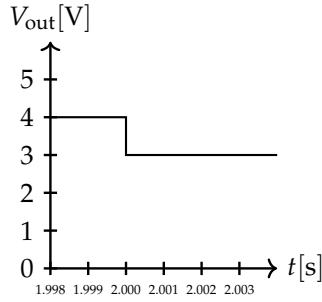


(B) Plot B

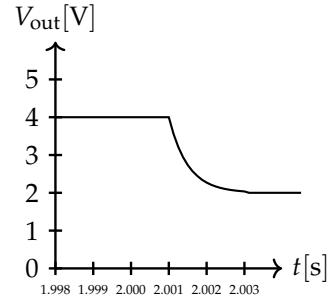


(C) Plot C

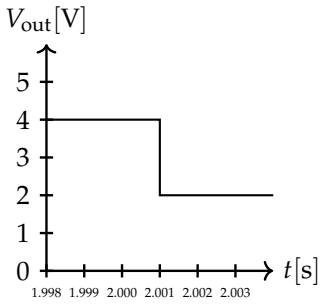

(D) Plot D

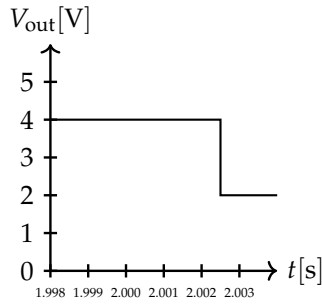

(E) Plot E

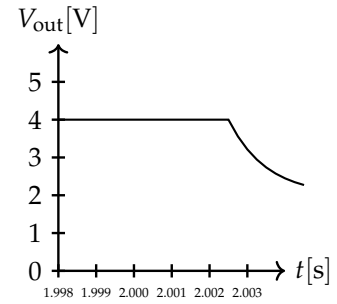

(F) Plot F

Model #	Plot A	Plot B	Plot C	Plot D	Plot E	Plot F
I	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
II	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
III	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>
IV	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>	<input type="radio"/>

2. An RC Circuit with a Dependent Source

Consider the following circuit ($V_{out}(0) = 0$):

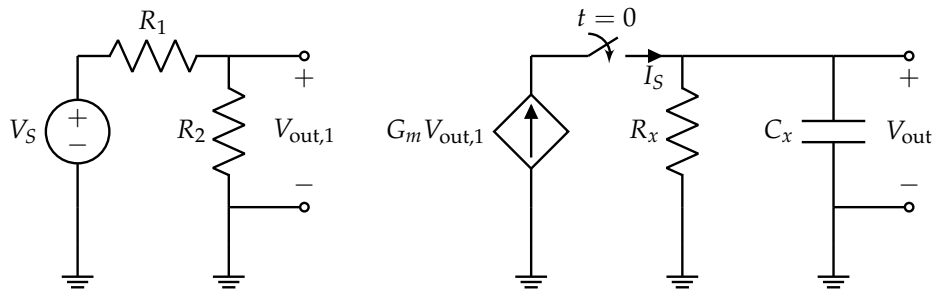


Figure 5

(a) Find the differential equation for V_{out} .

(b) Find the time constant τ of the circuit.

- (c) **Draw a sketch of $V_{out}(t)$ for $t > 0$.** Make sure to include the initial value, asymptotic value, and the approximate value at the time constant (all in terms of the given variables). (*HINT: You can do this without solving the differential equation.*)

Contributors:

- Nikhil Jain.
- Chancharik Mitra.