

### 1. Introduction to Inductors

An inductor is a circuit element analogous to a capacitor; its voltage is proportional to the derivative of the current across it. That is:

$$V_L(t) = L \frac{dI_L(t)}{dt} \quad (1)$$

When first studying capacitors, we analyzed a circuit where a current source was directly attached to a capacitor. In Figure 1, we form the counterpart circuit for an inductor:

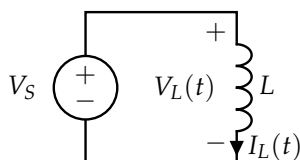
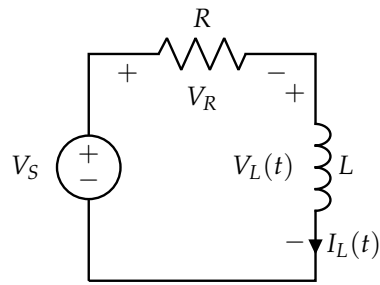


Figure 1: Inductor in series with a voltage source.

- (a) **What is the current through an inductor as a function of time? If the inductance is  $L = 3 \text{ H}$ , what is the current at  $t = 6 \text{ s}$ ?** Assume that the voltage source turns from  $0 \text{ V}$  to  $5 \text{ V}$  at time  $t = 0 \text{ s}$ , and there's no current flowing in the circuit before the voltage source turns on, i.e.  $I_L(0) = 0 \text{ A}$ .

- (b) Now, we add some resistance in series with the inductor, as in Figure 2.


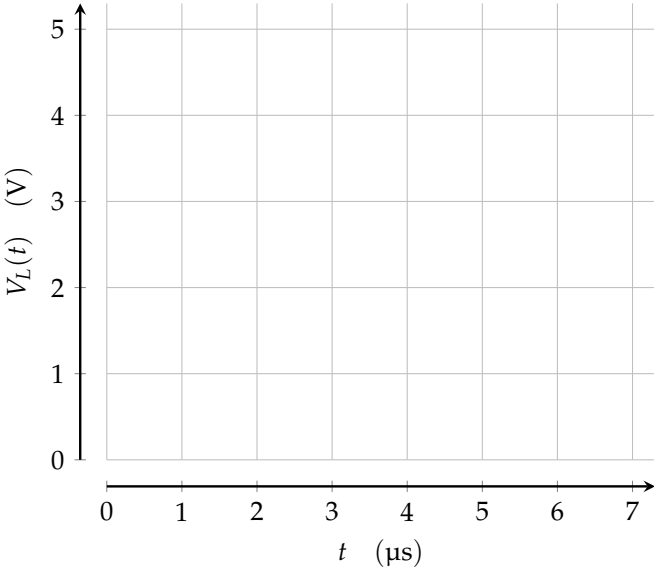


**Figure 2:** Inductor in series with a voltage source.

**Solve for the current  $I_L(t)$  and voltage  $V_L(t)$  in the circuit over time, in terms of  $R, L, V_S, t$ . Note that  $I_L(0) = 0$  A. Try to solve this equation by inspection. Otherwise, you can use the following integral for the particular solution (with the proper values and functions):**

$$e^{-st} \int e^{st} b(t) dt$$

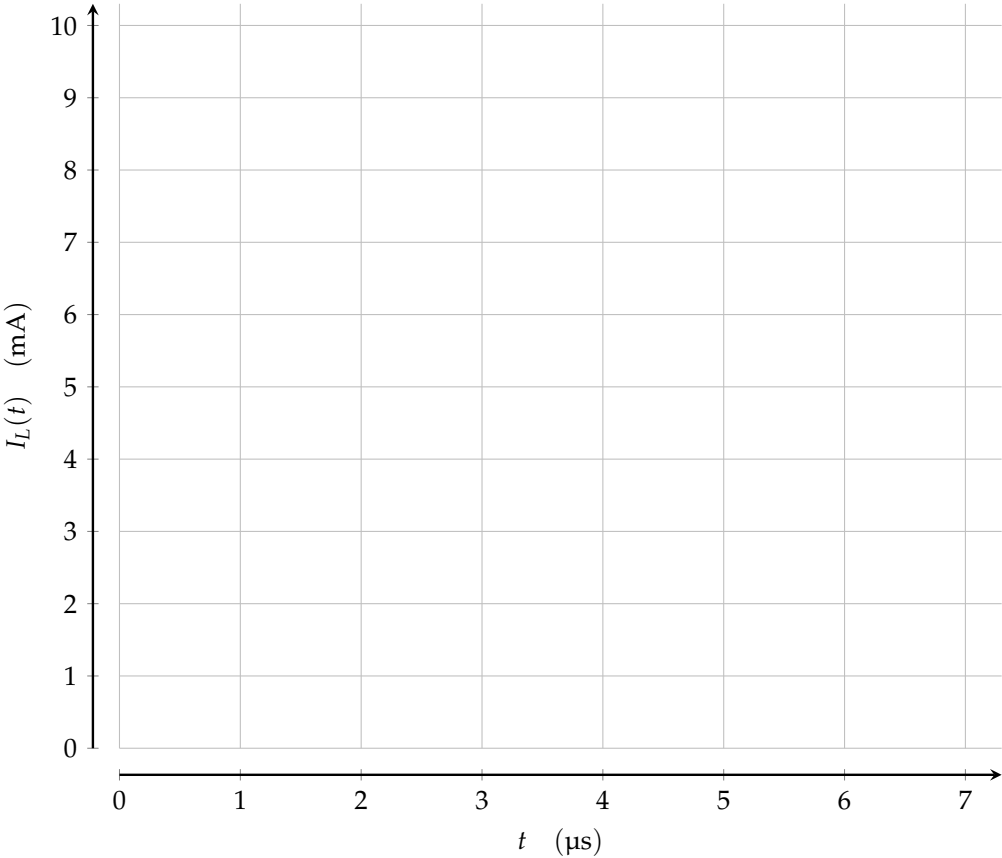- (c) **Suppose  $R = 500 \Omega, L = 1 \text{ mH}, V_S = 5 \text{ V}$ . Plot the current through and voltage across the inductor ( $I_L(t), V_L(t)$ ), as these quantities evolve over time.**



## 2. RL Circuit Solution Methods

Consider the following circuit:

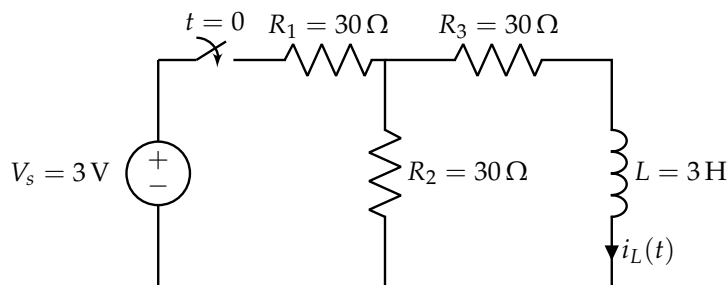


Figure 3

Before time  $t = 0$ , the circuit reaches a steady state. At time  $t = 0$ , the switch is closed. Our goal is to find the differential equation for the current through the inductor ( $i_L(t)$ ). One method to approach this problem is to simply use Node Voltage Analysis (NVA). To start, we would define the node voltages in our circuit (including a ground node).

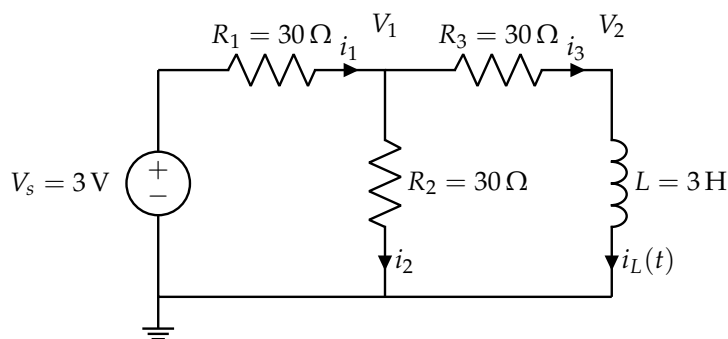


Figure 4

Then, we can set up a system of equations using KCL/KVL to find our desired differential equation.

First, let's perform KCL on the node with defined voltage  $V_1$ .

$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 \frac{V_s - V_1}{R_1} &= \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_3} \\
 \frac{3 - V_1}{30} &= \frac{V_1 - 0}{30} + \frac{V_1 - V_2}{30} \\
 V_1 &= 1 + \frac{V_2}{3}
 \end{aligned}$$

Now, let's perform KCL on the node with the defined voltage  $V_2$ .

Note that  $V_2 - 0 = V_2$  is the voltage across the inductor so by the inductor I-V relationship,  $V_2 = L \frac{di_L}{dt} = 3 \frac{di_L}{dt}$ .

$$i_3 = i_L$$

$$\begin{aligned} \frac{V_1 - V_2}{R_3} &= i_L \\ \frac{V_1 - V_2}{30} &= i_L \\ \frac{V_1}{30} &= \frac{V_2}{30} + i_L \\ \frac{1}{30} \left( 1 + \frac{V_2}{3} \right) &= \frac{V_2}{30} + i_L \\ \frac{1}{45} V_2 + i_L &= \frac{1}{30} \\ \frac{1}{45} \left( 3 \frac{di_L}{dt} \right) + i_L &= \frac{1}{30} \\ \frac{di_L}{dt} + 15i_L &= \frac{1}{2} \end{aligned}$$

Thus, we have found the differential equation! However, this method required solving a system of equations; is there another way?

- (a) Another way to approach the problem is to use equivalence. Simplify the voltage source and resistor network into a voltage source and resistor using Thevenin equivalence. Then, reconnect the inductor and **find the differential equation for  $i_L(t)$** .

For reference, here is the circuit that we want to simplify using Thevenin equivalence:

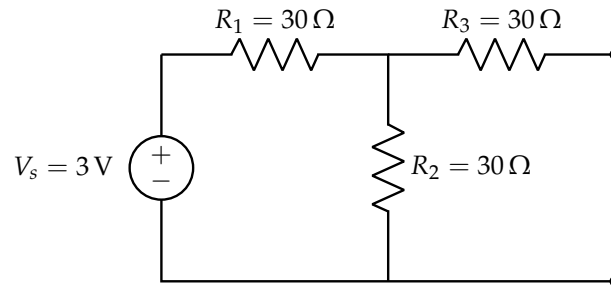


Figure 5

(HINT: Your final differential equation should be the same as the one from the problem introduction.)

- (b) Now, let's start solving the differential equation. First, **find the initial condition  $i_L(0)$  for our system**. Remember that the current through the inductor cannot change instantaneously (since this would correspond to infinite voltage through the inductor I-V relationship) so  $i_L(0)$  will be the same as the steady state value from  $t < 0$ .

*(HINT: If there is no voltage/current sources connected to this system, can there be any nonzero currents / voltage differences in the system during steady-state?)*

- (c) **(OPTIONAL)** Now that we have our differential equation and initial condition, we can now solve for the current  $i_L(t)$  as a function of time. **Solve the system for  $i_L(t)$** . If you can, try to solve this by inspection. Otherwise, you can use the following integral to find the particular solution (remember to use the values/functions that correspond to this specific differential equation):

$$e^{-st} \int e^{st} b(t) dt$$

**Contributors:**

- Anish Muthali.
- Neelesh Ramachandran.
- Kumar Krishna Agrawal.
- Nikhil Jain.