

Note 3 along with corresponding lectures are most relevant to this discussion worksheet.

**1. Analyzing a Second-Order Circuit (Adapted from Hambley Example 4.5)**

A DC source is connected to a series RLC circuit by a switch that closes at  $t = 0$  as shown in Figure 3. The initial conditions are  $i(0) = 0$  and  $v_C(0) = 0$ .

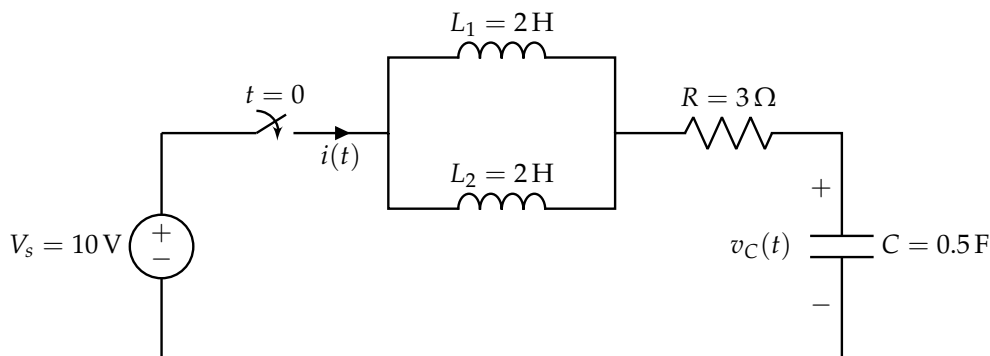


Figure 1: RLC Circuit

(a) Find the equivalent inductance and redraw the circuit as a standard series RLC.

**Solution:** Recall that the equivalent inductance of two inductors in parallel is given by  $L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2}\right)^{-1}$ .  
 Therefore,

$$L = \left(\frac{1}{2} + \frac{1}{2}\right)^{-1} = 1\text{ H} \tag{1}$$

The resulting circuit is as follows:

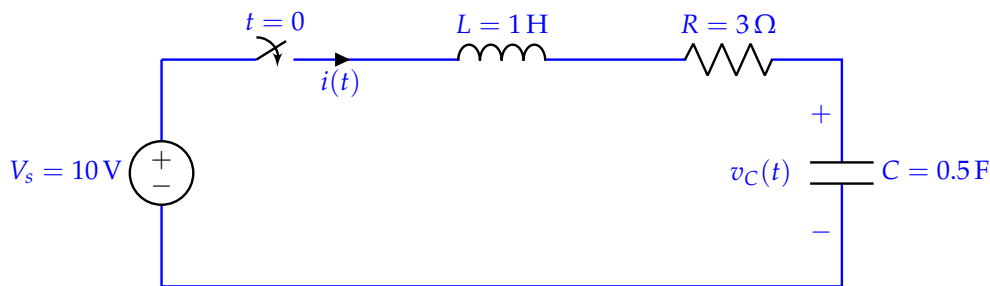


Figure 2: RLC Circuit

(b) Write the differential equation for  $v_C(t)$

**Solution:** First, we can write an express for the current in terms of the voltage across the capacitance:

$$i(t) = C \frac{dv_C(t)}{dt} \tag{2}$$

Then, writing a KVL equation for the circuit, we have:

$$v_L(t) + v_R(t) + v_C(t) = V_s \quad (3)$$

$$L \frac{di(t)}{dt} + Ri(t) + v_C(t) = V_s \quad (4)$$

$$(5)$$

Substituting in the expression for current  $i(t)$ , we get:

$$LC \frac{d^2v_C(t)}{dt^2} + RC \frac{dv_C(t)}{dt} + v_C(t) = V_s \quad (6)$$

$$\frac{d^2v_C(t)}{dt^2} + \frac{R}{L} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = \frac{V_s}{LC} \quad (7)$$

(c) **Solve for  $v_C(t)$  if  $R = 3\Omega$ .**

**Solution:**

**Step 1: Solve for the homogeneous solution:**

Our equation is in the form:

$$\frac{d^2x(t)}{dt^2} + 2\frac{\zeta}{\tau} \frac{dx(t)}{dt} + \frac{1}{\tau^2} x(t) = f(t) \quad (8)$$

where  $f(t) = \frac{V_s}{LC}$  which is a constant. Thus, we know that our solution for  $v_C(t)$  will be a combination of the particular solution  $v_{Cp}(t)$  and the complementary solution  $v_{Cc}(t)$ .

Since we have a DC source, we know that the transient or complementary solution will go to 0 over time. Thus, our current and voltage are steady/constant and we can replace inductors with short circuits and capacitors with open circuits. This leads us to determine that  $v_{Cp}(t) = V_s = 10\text{ V}$ .

Next, we will find the complementary solution  $v_{Cc}(t)$  or the homogeneous solution of our differential equation. When finding the complementary solution, we will follow the following 3 steps:

- i. Determine the damping ratio and roots of the characteristic equation
- ii. Select the appropriate form for the homogeneous solution, depending on the value of the damping ratio
- iii. Add the homogeneous solution to the particular solution and determine the values of the coefficients ( $K_1$  and  $K_2$ ) based on initial conditions.

Here, we have  $R = 3\Omega$ , so

$$\tau = \sqrt{LC} = \frac{1}{\sqrt{2}} \quad (9)$$

and the damping ratio  $\zeta = \frac{R\tau}{2L} = \frac{3\sqrt{2}}{4}$ . Since  $\zeta > 1$ , we have an overdamped case. **Important:** We consider the exponential candidate solution for our homogeneous solution (i.e.  $v_h = e^{st}$ ). Using this, our differential equation decomposes into:

$$s^2 e^{st} + 3s e^{st} + 2e^{st} = 0 \quad (10)$$

We can view this equation as being in quadratic form (i.e. use the quadratic formula!)

Solving for the roots of our characteristic equation we have:

$$s_1 = -\frac{\zeta}{\tau} + \frac{1}{\tau}\sqrt{\zeta^2 - 1} \quad (11)$$

$$= -1.5 + \sqrt{2}\sqrt{\frac{18}{16}} - 1 \quad (12)$$

$$= -1 \quad (13)$$

and

$$s_2 = -\frac{\zeta}{\tau} - \frac{1}{\tau}\sqrt{\zeta^2 - 1} \quad (14)$$

$$= -1.5 - \sqrt{2}\sqrt{\frac{18}{16}} - 1 \quad (15)$$

$$= -2 \quad (16)$$

**Step 2: Solve for the particular solution using steady-state analysis (note: refer to part d for more details on this):**

We know that the homogeneous solution has the form  $K_1e^{s_1t} + K_2e^{s_2t}$  leading us to have the general solution:

$$v_C(t) = v_{Cp}(t) + v_{Cc}(t) = 10 + K_1e^{s_1t} + K_2e^{s_2t} \quad (17)$$

**Step 3: Utilize the initial conditions to solve for solution coefficients:**

Now, we will find the values of  $K_1$  and  $K_2$  using the given initial conditions. It is given  $v_C(0) = 0$  V. This gives us that:

$$10 + K_1 + K_2 = 0 \quad (18)$$

Furthermore, since  $i(0) = 0$  A we also know that  $i(0) = C\frac{dv_C(0)}{dt}$  and thus  $\frac{dv_C(0)}{dt} = 0$ . Taking the derivative of Equation 17 and plugging in  $t = 0$ , we get

$$s_1K_1e^{s_1(0)} + s_2K_2e^{s_2(0)} = 0 \quad (19)$$

$$s_1K_1 + s_2K_2 = 0 \quad (20)$$

Now, solving the systems of equations, we get that  $K_1 = -20$  and  $K_2 = 10$ . Substituting these values into Equation 17, we get our final solution:

$$v_C(t) = 10 - 20e^{-t} + 10e^{-2t} \quad (21)$$

(d) **Redraw the circuit in steady state and find the steady state value for  $v_C(t)$ .**

**Solution:** Recall that at steady state, inductors act as shorts and capacitors act as open circuits. Using this knowledge, our redrawn circuit is as follows:


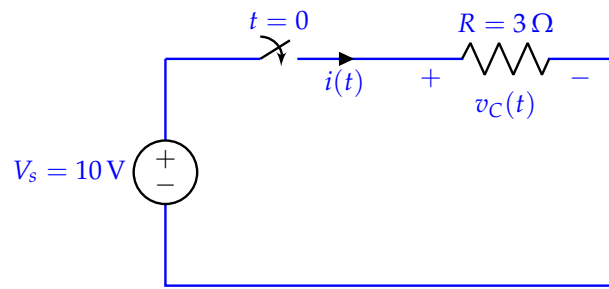



Figure 3: RLC Circuit

Because no current flows into the node with an open circuit,  $v_C(t) = V_S = 10\text{ V}$ .

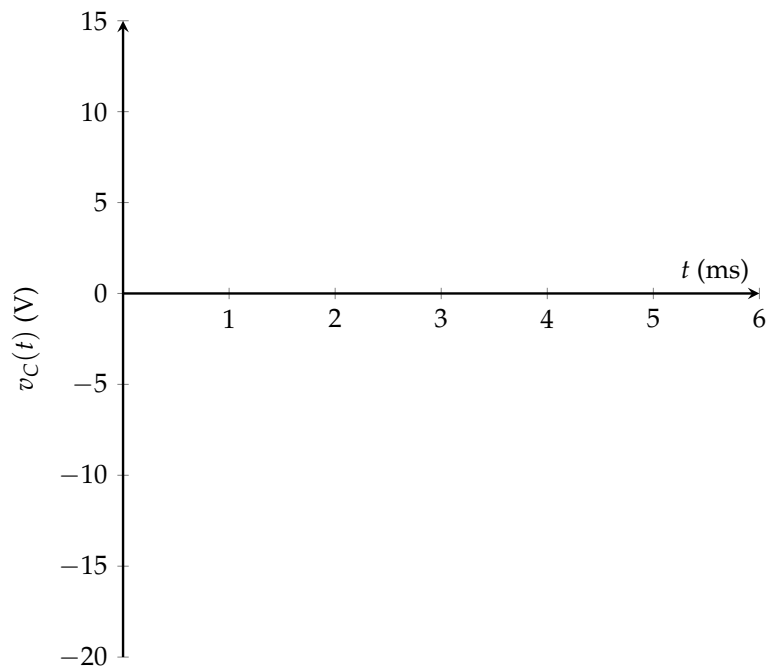- (e) Plot the equation you calculated for  $v_C(t)$ . It may be helpful to draw out each term in your general solution and then add them together.



**Solution:**

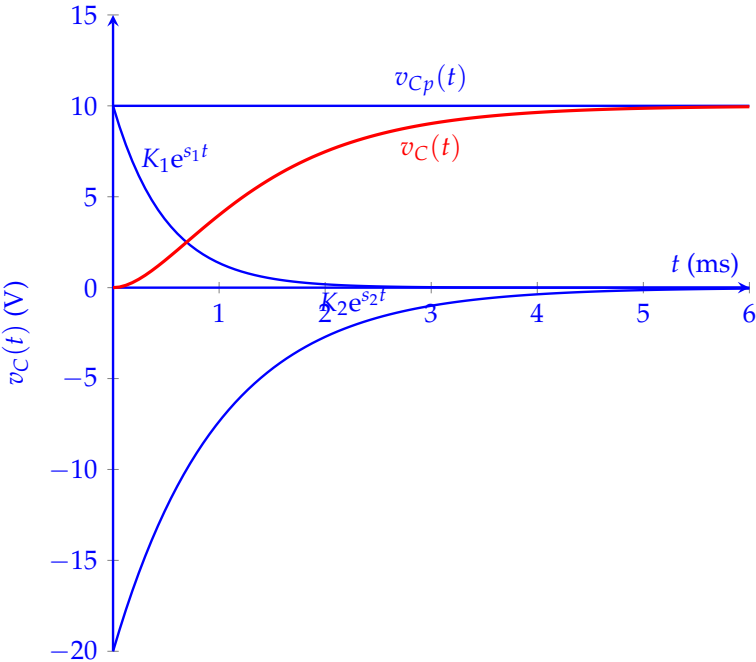

**Contributors:**

- Chancharik Mitra.
- Nikhil Jain.