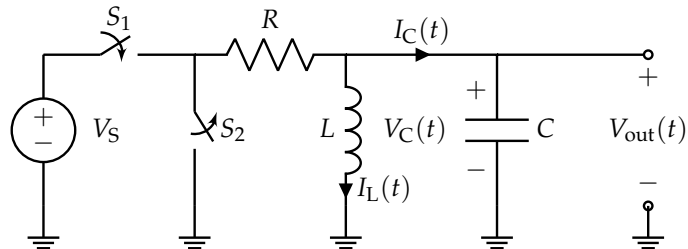


## Discussion 4A

### 1. RLC Circuit from Time to Frequency

Consider the following circuit fed by a constant voltage source  $V_S$ .



The switch  $S_1$ , open for  $t < 0$ , closes at  $t = 0$ , and the switch  $S_2$ , closed for  $t < 0$ , opens at  $t = 0$ . Assume  $V_C(0) = 0$  and  $I_L(0) = 0$ .

- (a) **Derive a set of two differential equations, one for  $I_L(t)$ , the current through the inductor, and one for  $V_C(t)$ , the voltage across the capacitor.** Write your answer in terms of  $R$ ,  $L$ ,  $C$ ,  $V_S$ , and constants.

- (b) **Using your answers from the previous part, create a vector differential equation with the state vector being  $\vec{x}(t) = \begin{bmatrix} V_C(t) \\ I_L(t) \end{bmatrix}$ .** Write your answers in terms of  $R$ ,  $L$ ,  $C$ ,  $V_S$ , and constants.

- (c) Regardless of your answer to the previous part, suppose the vector differential equation is given by

$$\frac{d}{dt} \vec{x}(t) = \underbrace{\begin{bmatrix} -4 & -6 \\ \frac{1}{2} & 0 \end{bmatrix}}_A \vec{x}(t) + \underbrace{\begin{bmatrix} 4 \\ 0 \end{bmatrix}}_{\vec{b}} V_S \quad (1)$$

**First, find the eigenvalues of the matrix  $A$ .**

- (d) **Next, find the eigenvectors that will form your  $V$  basis.**

(e) **Now, in order to diagonalize the system, write  $A$  in terms of  $V$ ,  $V^{-1}$ , and  $\Lambda$ .**

(f) **With  $\vec{x}(0) = \vec{0}$ , solve for  $\vec{x}(t)$  and find the asymptotic/steady-state behavior as  $t \rightarrow \infty$ .**