

1. AC Power Calculations (Hambley Example 5.7)

Suppose you are given the circuit in Figure 1, where the phasor for current $i(t)$ is calculated to be $\frac{\sqrt{2}}{10}e^{-\frac{3\pi}{4}j}$.

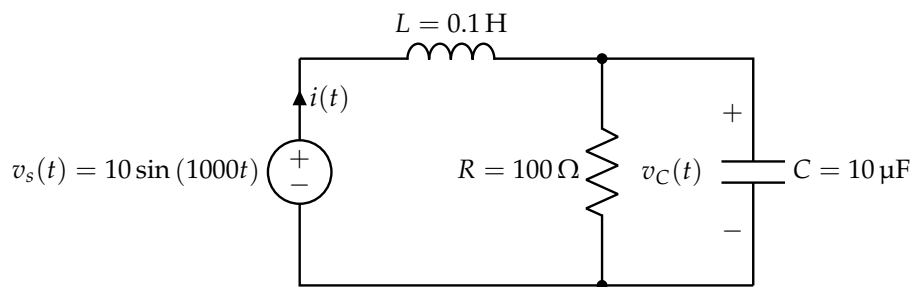
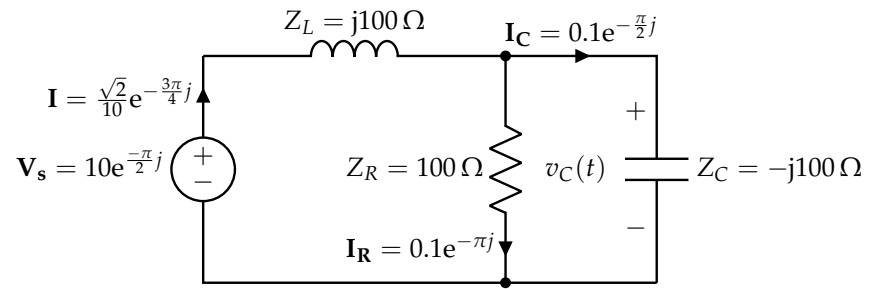


Figure 1: RLC Circuit

(a) Compute the power and reactive power taken from the source in the circuit provided in Figure 1.

(b) Compute the power and reactive power delivered to each element in the circuit. Assume you are given the computed currents in Figure 2.

**Figure 2:** RLC Circuit

2. Hambley P5.83

(a) Find the Thevenin and Norton equivalent circuits for the circuit shown in Figure 3.

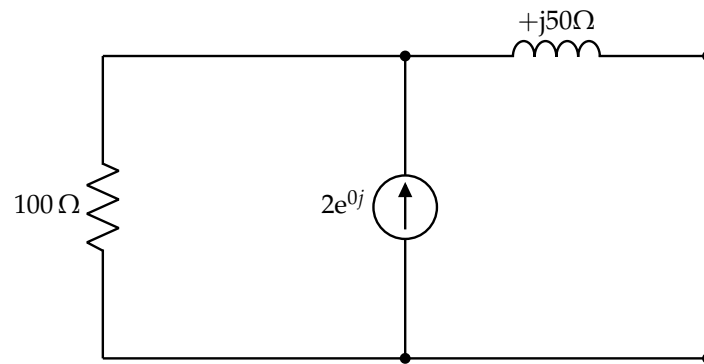


Figure 3: P5.83

(b) Find the maximum power that this circuit can deliver to a load if the load can have any complex impedance. *Hint: Think about which impedance value for the load would optimize the power expression.*

(c) Repeat the previous part, but this time the load is purely resistive.

Contributors:

- Chancharik Mitra.
- Nikhil Jain.