



The background image shows a detailed microchip layout with various functional blocks highlighted by dashed yellow boxes. The labels include 'RX' (Receiver), 'LO Buffer' (Local Oscillator Buffer), 'Hybrid', 'Wilkinson' (referring to a Wilkinson power divider), 'LO Buffer' (another instance), and 'TX' (Transmitter). The layout features a dense grid of circuit traces and components.

# EECS 16B

## Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran  
Department of Electrical Engineering and Computer Sciences, UC Berkeley,  
[niknejad@berkeley.edu](mailto:niknejad@berkeley.edu)

# **Module 2: RC Circuits, Digital Logic Gates, and Transfer Functions**


EECS 16B

# RC Circuits

---

- Solve RC with and without inputs
  - “Natural” response and “forced” response
  - “Moving Average” (Convolution Integral)
- Step Response
- Pulse Response
- Preview: Sinusoidal Steady-State Response
- Low Pass vs High Pass
- Introduction to Transistors

# Capacitor Discharge: Linear

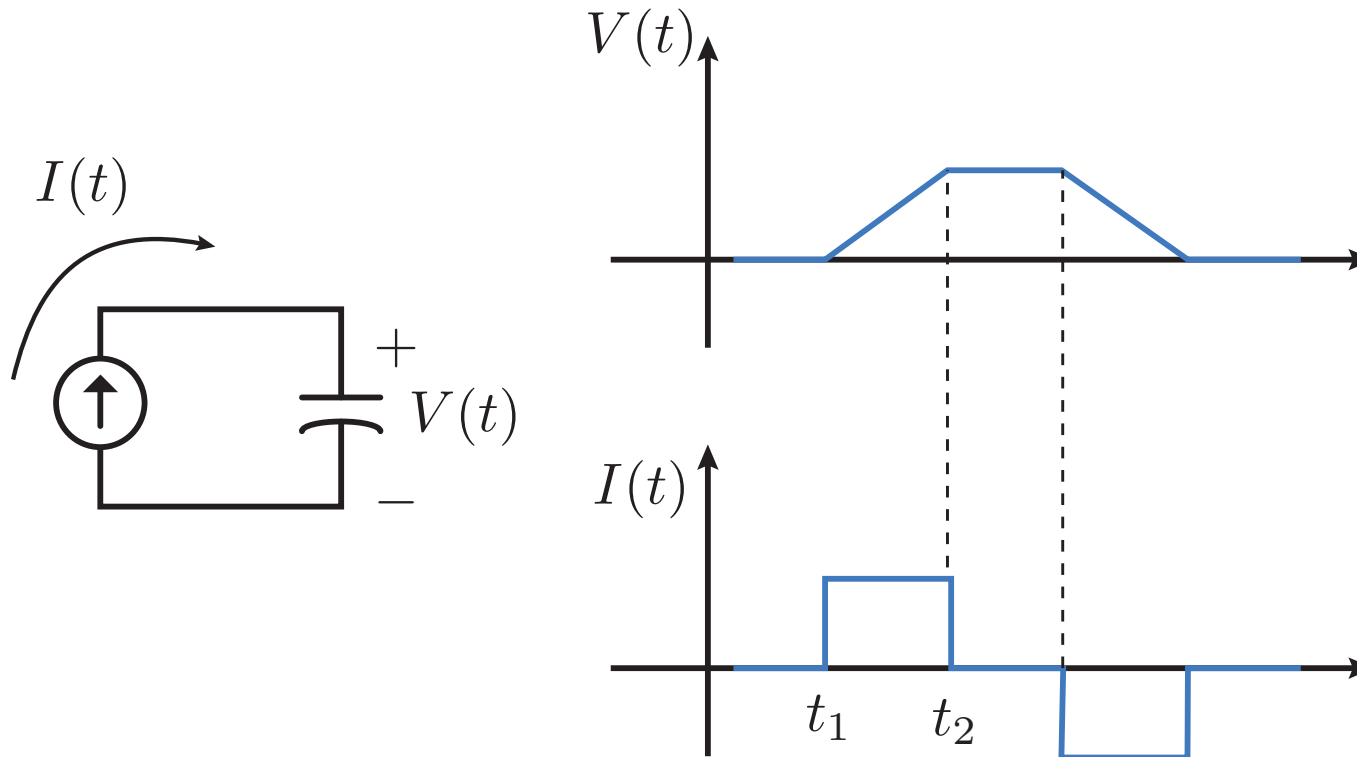

# Capacitor Discharge

---

- Water analogy: Rate of outflow is not constant but depends on the height of the water in the tank (the pressure)

# RC Circuit

---

- Can't solve by “inspection”, need to solve differential equation

# RC Solution

---

- Easy to guess for first-order equation

# Capacitor Has “Memory”

---

- A resistive circuit without capacitors has no memory, the transfer function is instantaneous and if the input goes to zero, the output immediately goes to zero.



# Circuit as a System

---

- Consider inputs (independent voltage/current sources) and outputs (voltages or currents at any node or in any branch of the circuit). Dependent sources are not inputs.

# Linear Constant Coefficient Differential Eq.

---

- Homogenous solution: No inputs. Sometimes called the “natural” solution
- Forced response or a *particular* solution

# Superposition

---

- Equation is linear, so a superposition of solutions is also a solution.

# Uniqueness

---

- Note that for a first-order differential equation, there can be at most one unique solution for the homogenous case

# RC Circuit with Inputs

---

- Now consider an arbitrary source connected to an RC circuit.

# Solution with Inputs (Integrating Factor)

---

# Complete Solution

---

# RC Circuits with DC Inputs

---



# Switching Circuits

---

# Step Response

---

# Source Superposition

---

# Pulse Response

---

# Smearing Out Pulses

---

# Reformulation of General Solution

---

# “Moving Average” Interpretation

---

# “Slow Pass” Circuit (Low Pass Filter)

---

- Suppose a function does not change much on the RC time constant scale



# “Fast Pass” Circuit (High Pass)

---

- Now take the output across the resistor. The transfer function can be written as:

# Preview: Sinusoidal Steady State

---

- Suppose we inject a sinusoidal tone. It's much easier to work with complex exponentials and take the real / imag. part later.

# Complex Exponential Solution

---

# Final “Transfer” Function

---

# Why It Worked: Going Around a Circle

---

- Summing many delayed copies of a complex exponential function still results in a complex exponential. Only magnitude and phase changes.

# “Natural” Eigenfunction Solution

---

# Low Pass for Sinusoidal Inputs

---


# Application: Filtering out Noise

---


- Listen to an audio signal and note that while speech and music has a lot of distinct tones, noise is random, with many high pitched and low-pitched parts.
- What if we use a “low pass” filter to get rid of high-pitched parts?




# MOS Capacitor

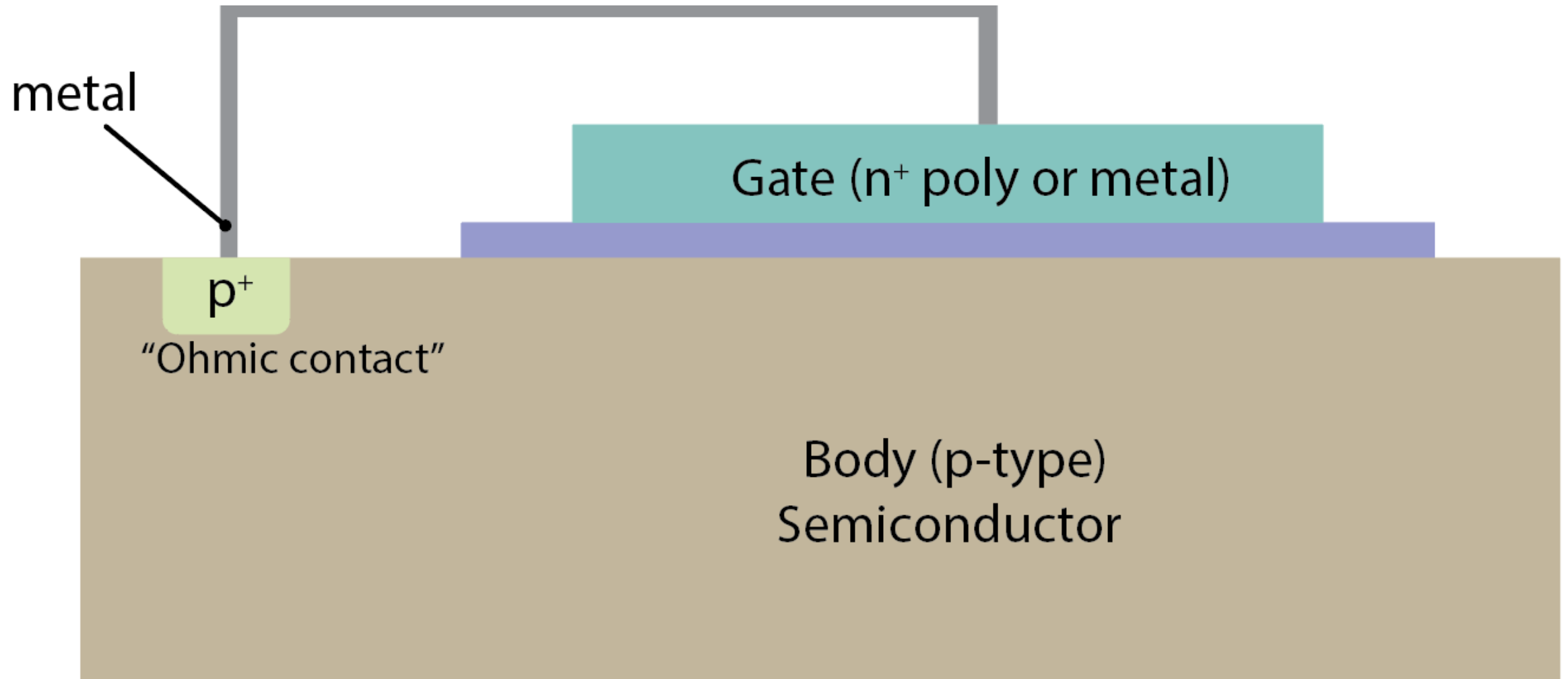

# Preview: Transistor

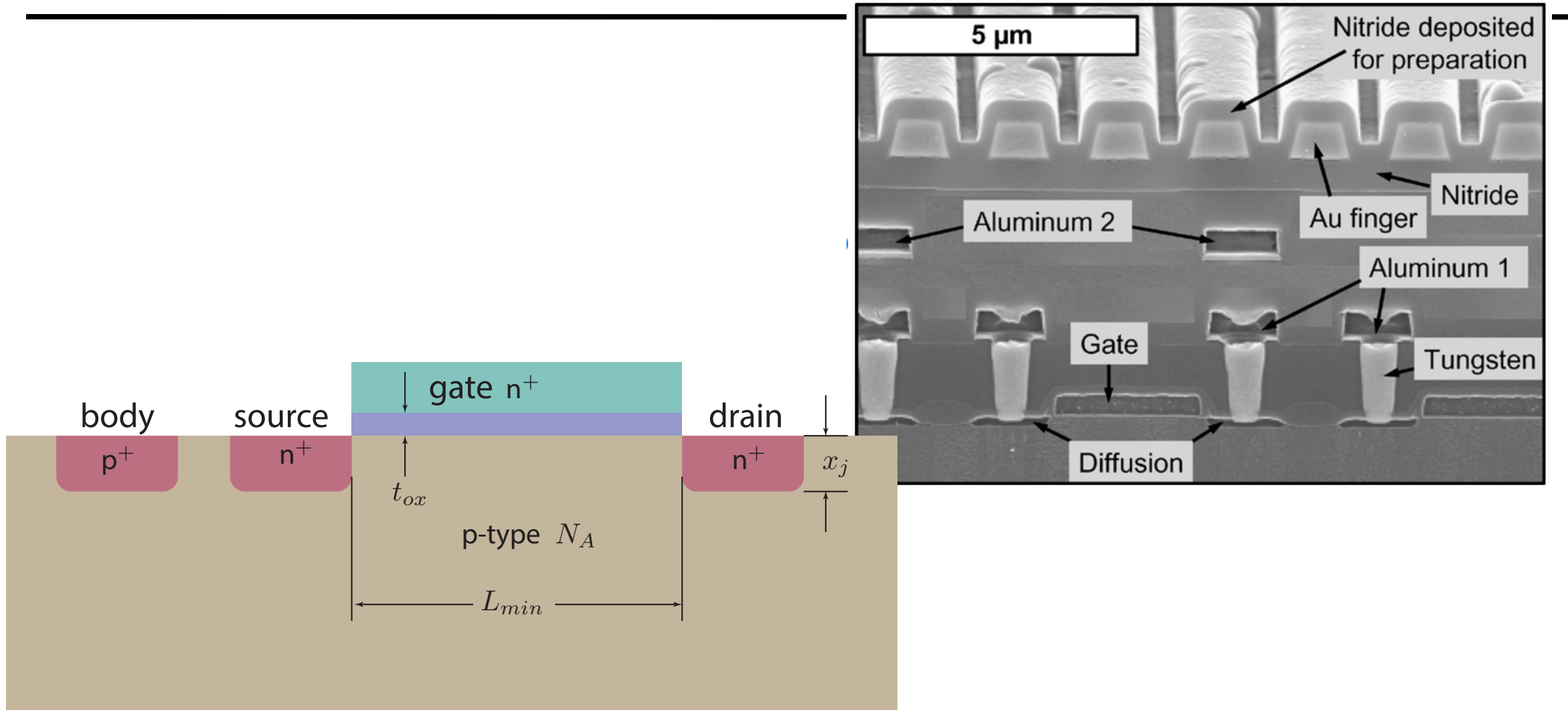


# DRAM

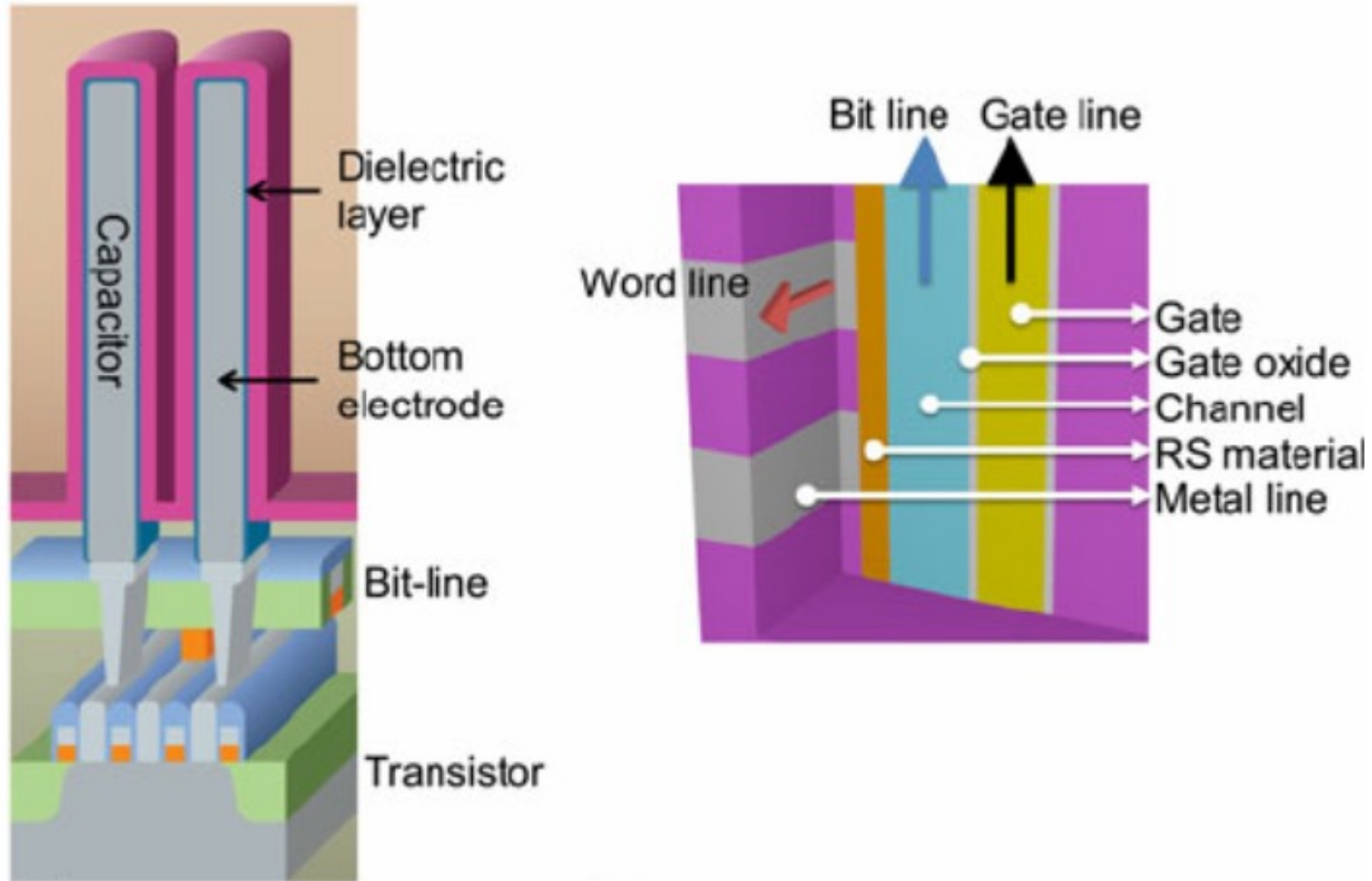

[https://www.researchgate.net/figure/Schematic-diagrams-of-a-DRAM-cells-which-consist-of-a-cell-transistor-and-capacitor\\_fig1\\_258797946](https://www.researchgate.net/figure/Schematic-diagrams-of-a-DRAM-cells-which-consist-of-a-cell-transistor-and-capacitor_fig1_258797946)

# MOS Transistor Schematic

---

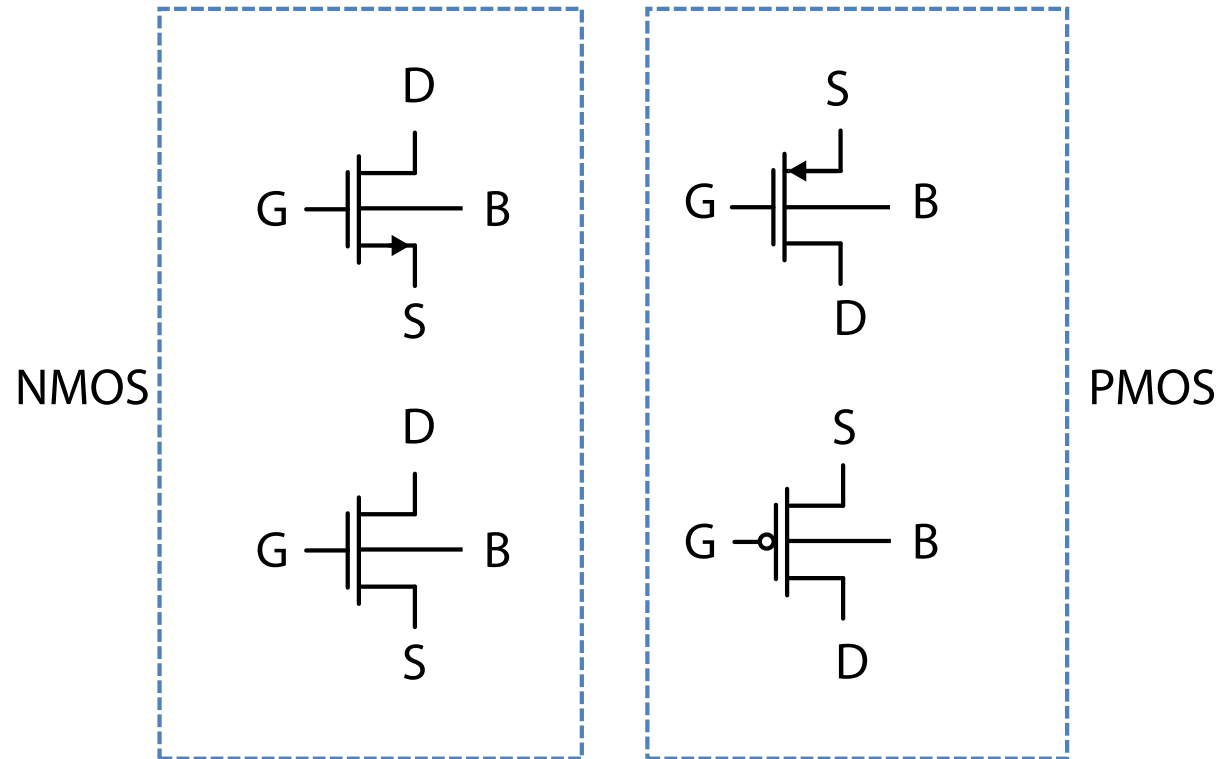

# Toy Physical Model of Transistor

---

- If we charge up the MOS capacitor, we create a channel that allows current to flow from the source to drain (electron flow)
- If the voltage at the gate is not sufficient to pass a threshold, the path is too resistive and we model it as an open circuit.

# Transistors Have Polarity

---

- You can build two kinds of transistors, ones that use electron flow to establish current and another that uses “holes” (positive charges with about twice the mass of electrons).
- Holes are legitimate quasi-particles that represent electrons moving among the various bonding states (valence band) in a crystal

# Transistor As Switch

---

# Transistor as a Transconductor

---

- The channel conductivity is modulated by the gate voltage.
- What's a circuit element that has this property?



# Op-Amp Model with RC

---