



The background image shows a detailed microchip layout with various functional blocks highlighted by dashed yellow boxes. The labels include 'RX' (Receiver), 'LO Buffer' (Local Oscillator Buffer), 'Hybrid', 'Wilkinson' (referring to a Wilkinson power divider), 'LO Buffer' (another instance), and 'TX' (Transmitter). The layout features a dense grid of circuit traces and components.

EECS 16B

Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran
Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu


Module 3: CMOS Models and Digital Logic Gates and Applications

EECS 16B


Outline

- Introduction to Transistors
- Simple Transistor Models
- Logic Gates
- Maximum Clock Rates : RC Circuit
- Op-amp settling behavior
- Applications:
 - Analog-to-Digital Conversion (ADC)
 - Digital-to-Analogaog Conversion (DAC)
 - Maximum conversion times : RC Circuits !


MOS Capacitor

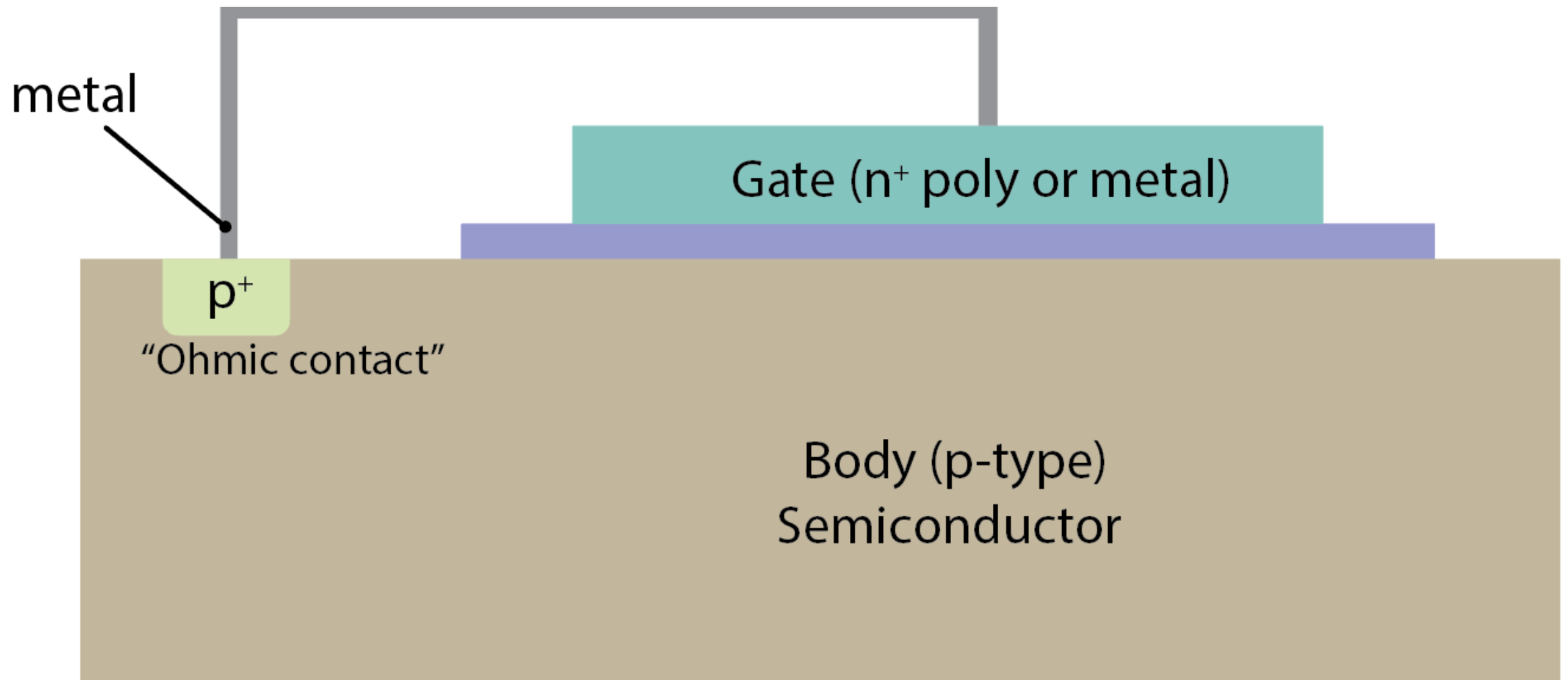

Preview: Transistor

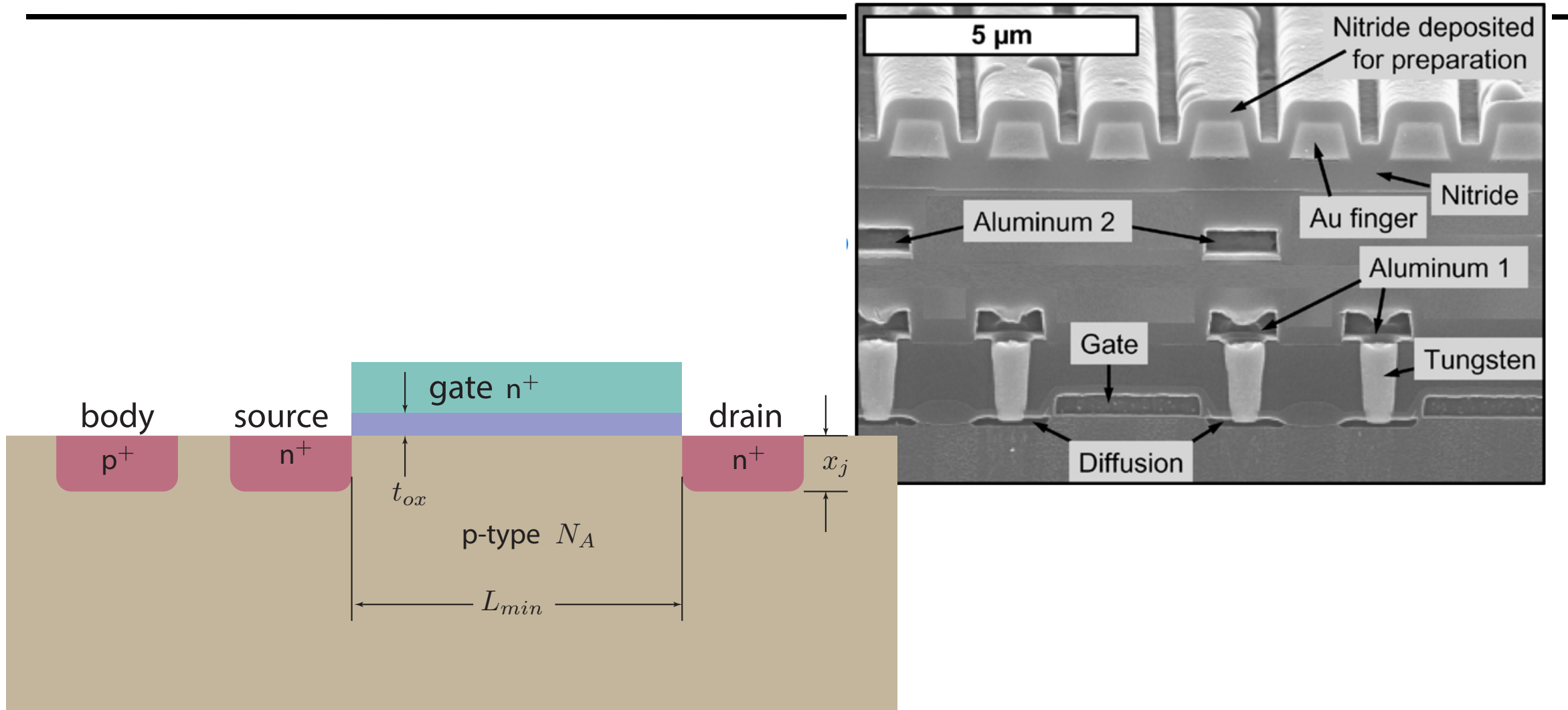

MOS Transistor Schematic

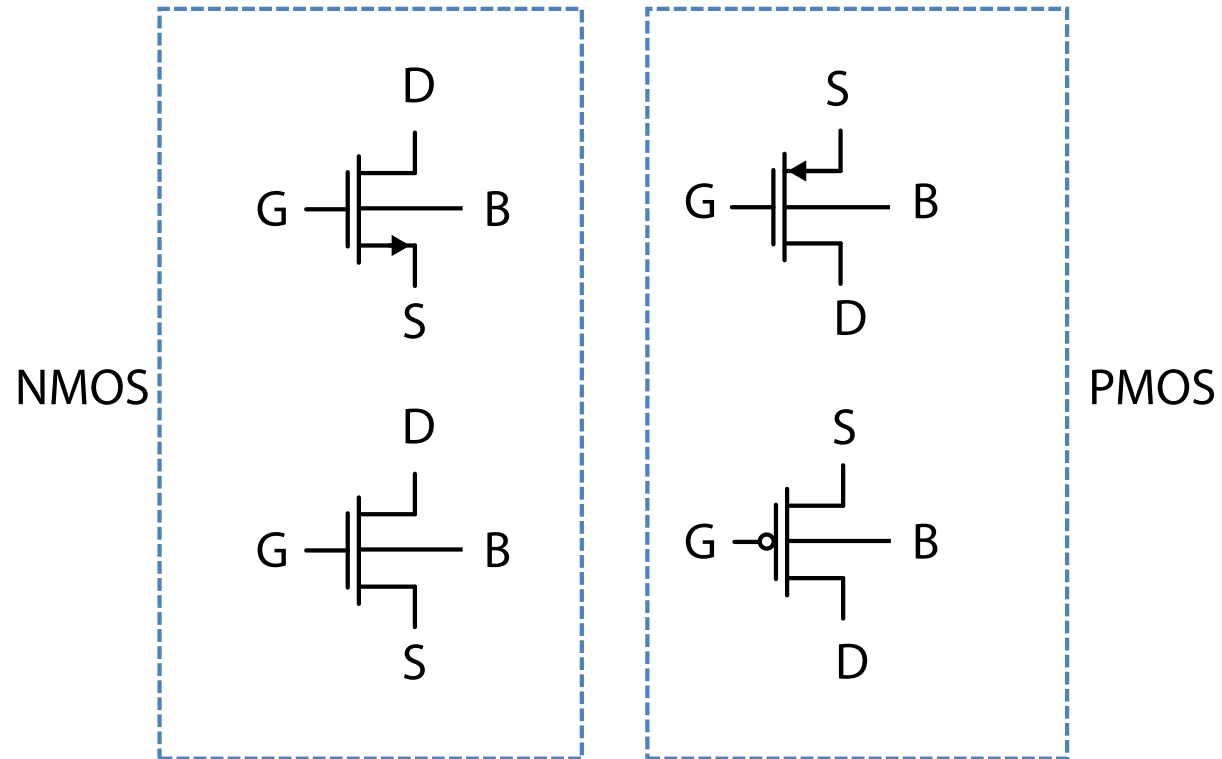

Toy Physical Model of Transistor

- If we charge up the MOS capacitor, we create a channel that allows current to flow from the source to drain (electron flow)
- If the voltage at the gate is not sufficient to pass a threshold, the path is too resistive and we model it as an open circuit.

Transistors Have Polarity

- You can build two kinds of transistors, ones that use electron flow to establish current and another that uses “holes” (positive charges with about twice the mass of electrons).
- Holes are legitimate quasi-particles that represent electrons moving among the various bonding states (valence band) in a crystal

Transistor As Switch

Transistor I-V Curve

- Constant current and “switch” region

Switch On-Resistance

Switch Gate Capacitance

Switch Off Capacitance

Transistor as a Transconductor

- The channel conductivity is modulated by the gate voltage.
- What's a circuit element that has this property?

CMOS Inverter

Logic Gates

Differential Equations for Inverter


I-V Curve Again

Op-Amp Model with RC

Amplifier Settling Time


Applications

R-2R Ladder Digital-to-Analog Converter

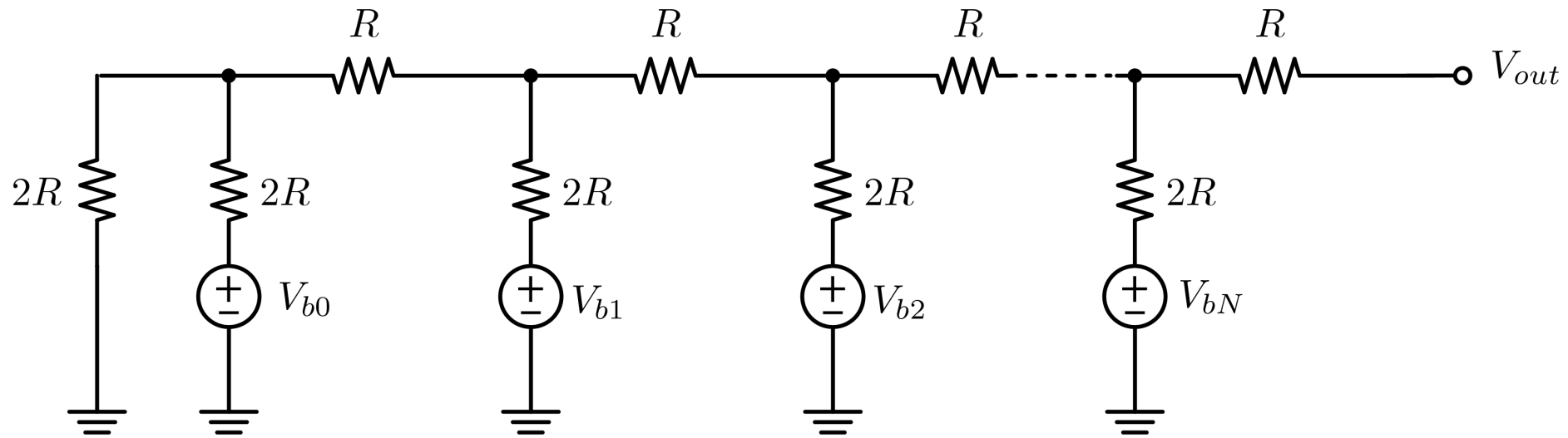

How to set all these “digital” voltages?

Switches

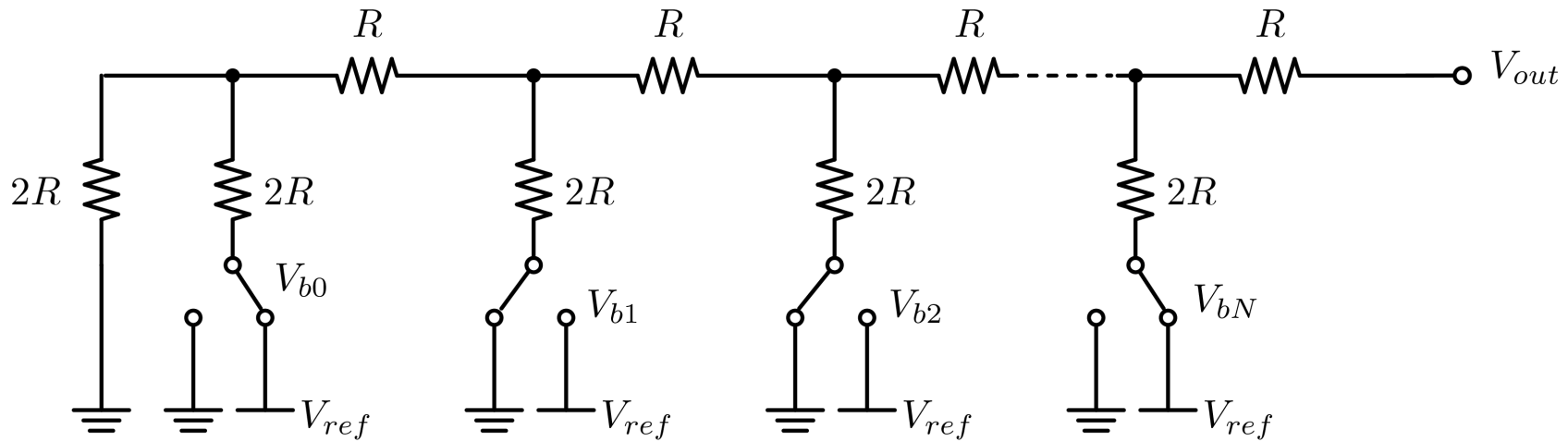


CMOS Gates

Remember Superposition and Equivalence?


R-2R Ladder Digital-to-Analog Converter

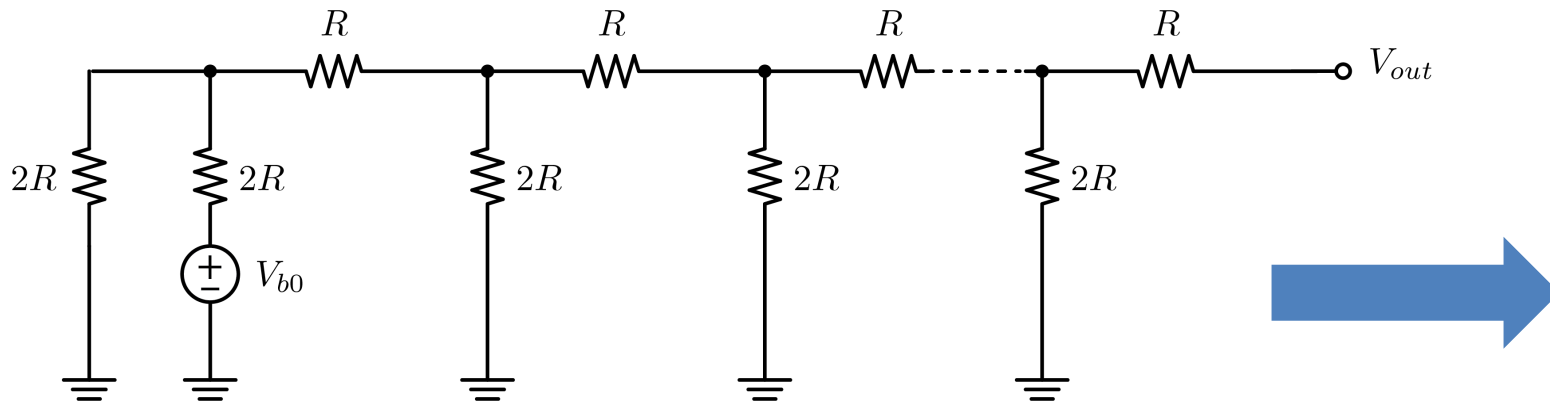Use superposition: Start with first voltage source:



R-2R Ladder Digital-to-Analog Converter

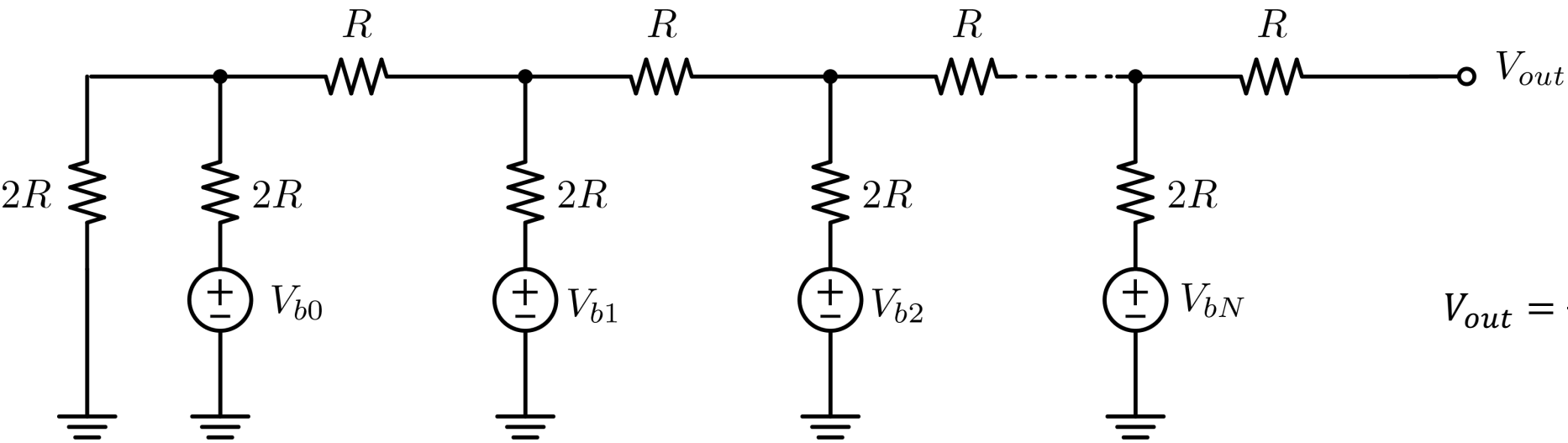Adding all contributions from the sources




$$V_{out} = \frac{V_{b0}}{2^N} + \frac{V_{b1}}{2^{N-1}} + \dots + \frac{V_{bN}}{2}$$

How fast can we “convert”?

Analog to Digital Conversion

Say we want to convert an analog signal to a 2 bit digital signal \rightarrow 4 levels

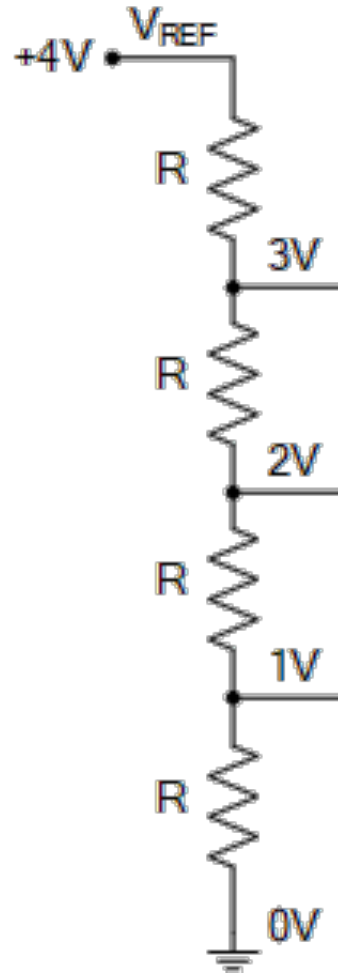

Lab 2: SAR (Successive Approximation Resistor) ADC

