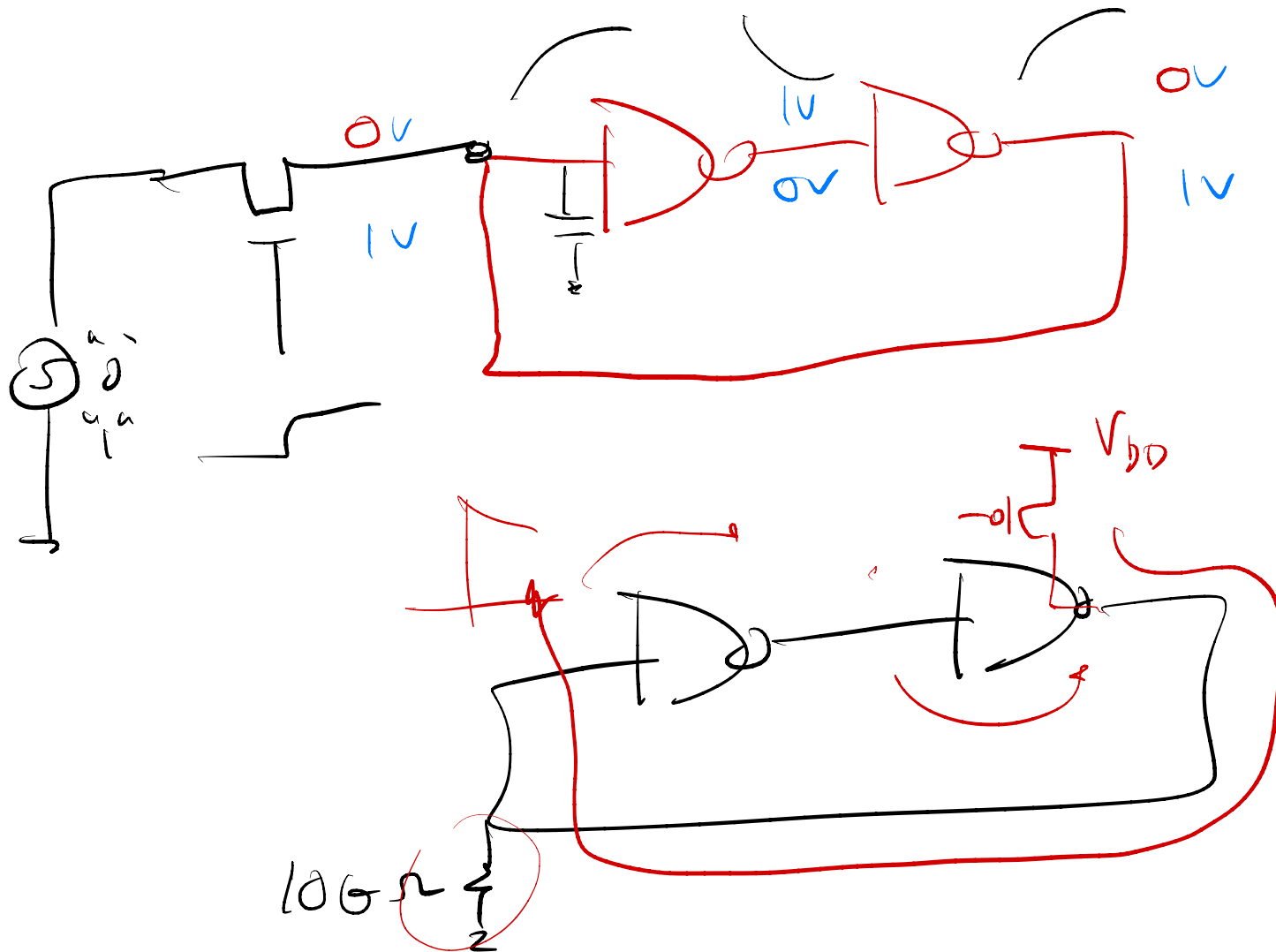


Module 3: CMOS Models and Digital Logic Gates and Applications


EECS 16B

Static RAM (SRAM)



BISTABLE

DRAM

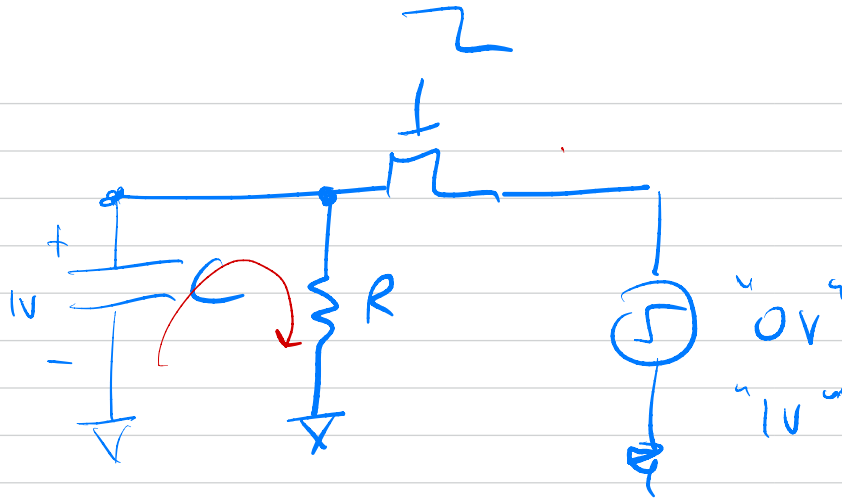


$$\tau = RC$$

$$= R \cdot 10 \text{ fF}$$


$$= R \cdot 10 \times 10^{-15}$$

$$R = 100 \text{ G}\Omega = 10^2 \times 10^9 = 10^{11}$$

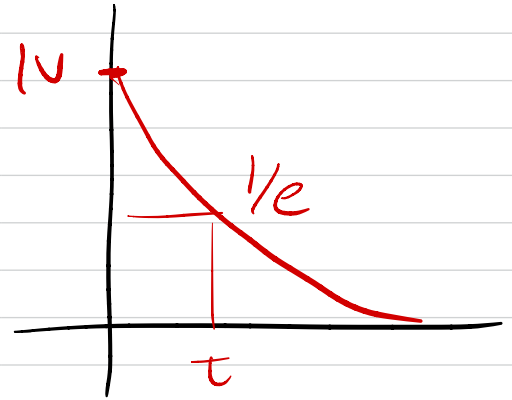
$$\tau = 10^{11} \times 10 \times 10^{-15} = 10^{-3}$$



Ring Oscillator

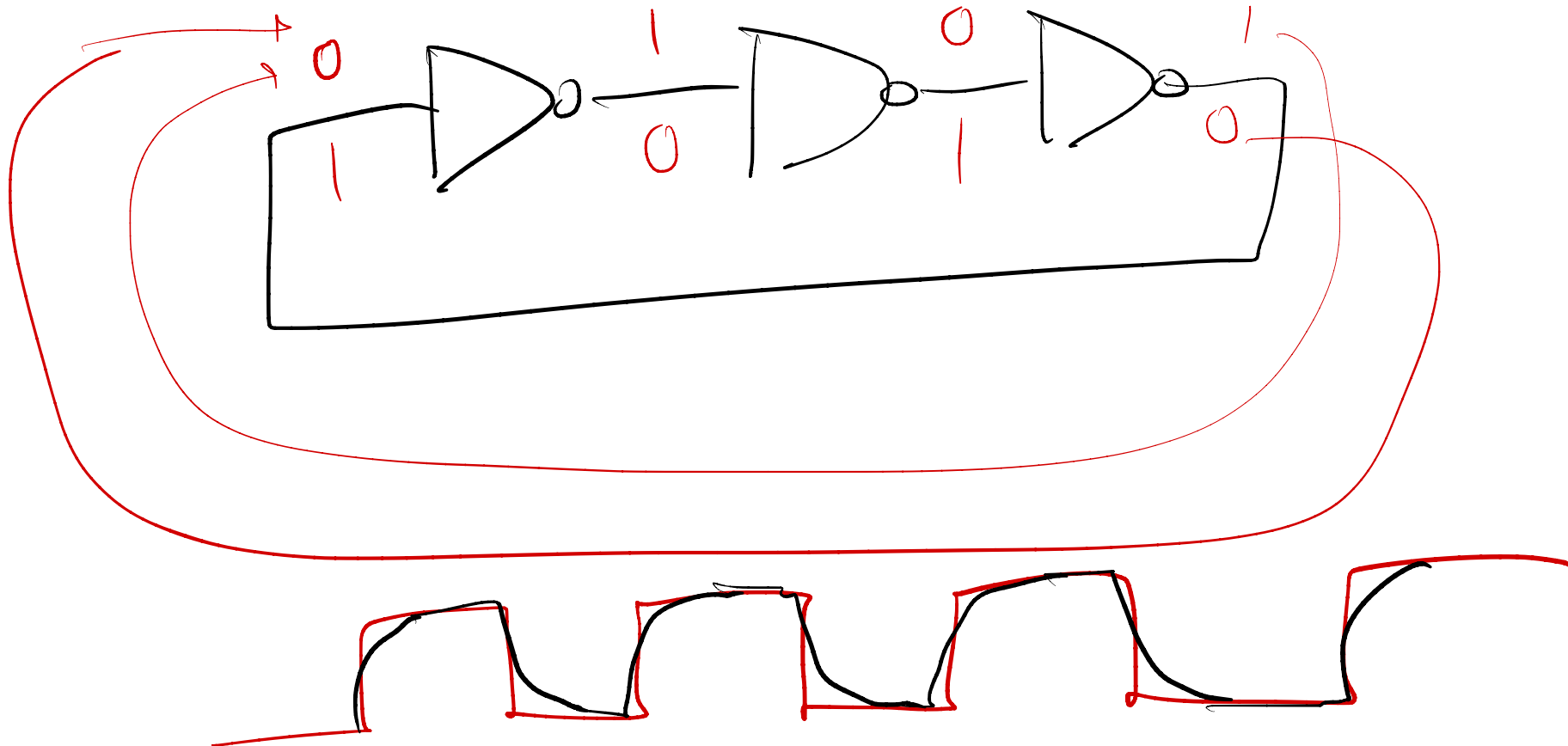


V_{DD}

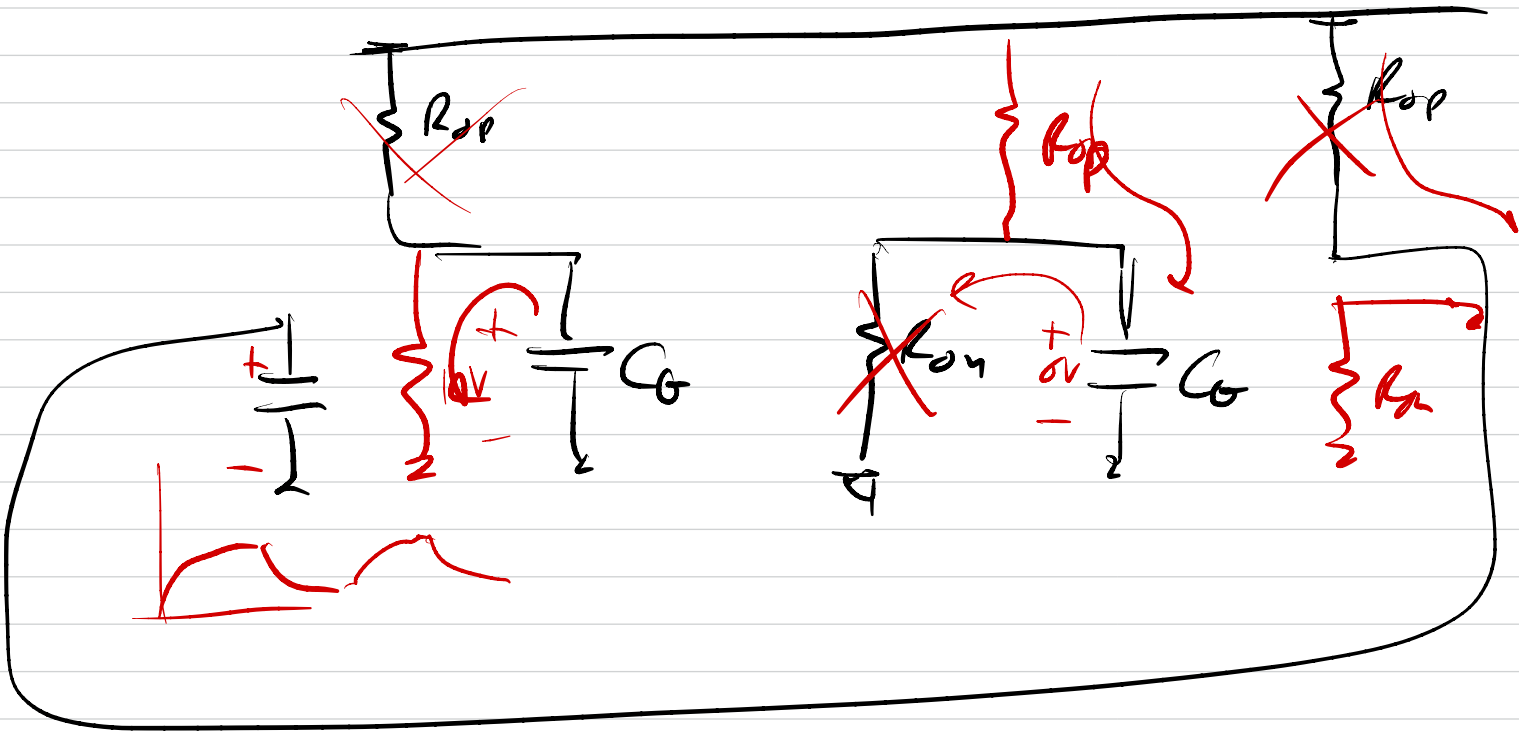


Differential Equations for Inverter

HW & DISC

I-V Curve Again

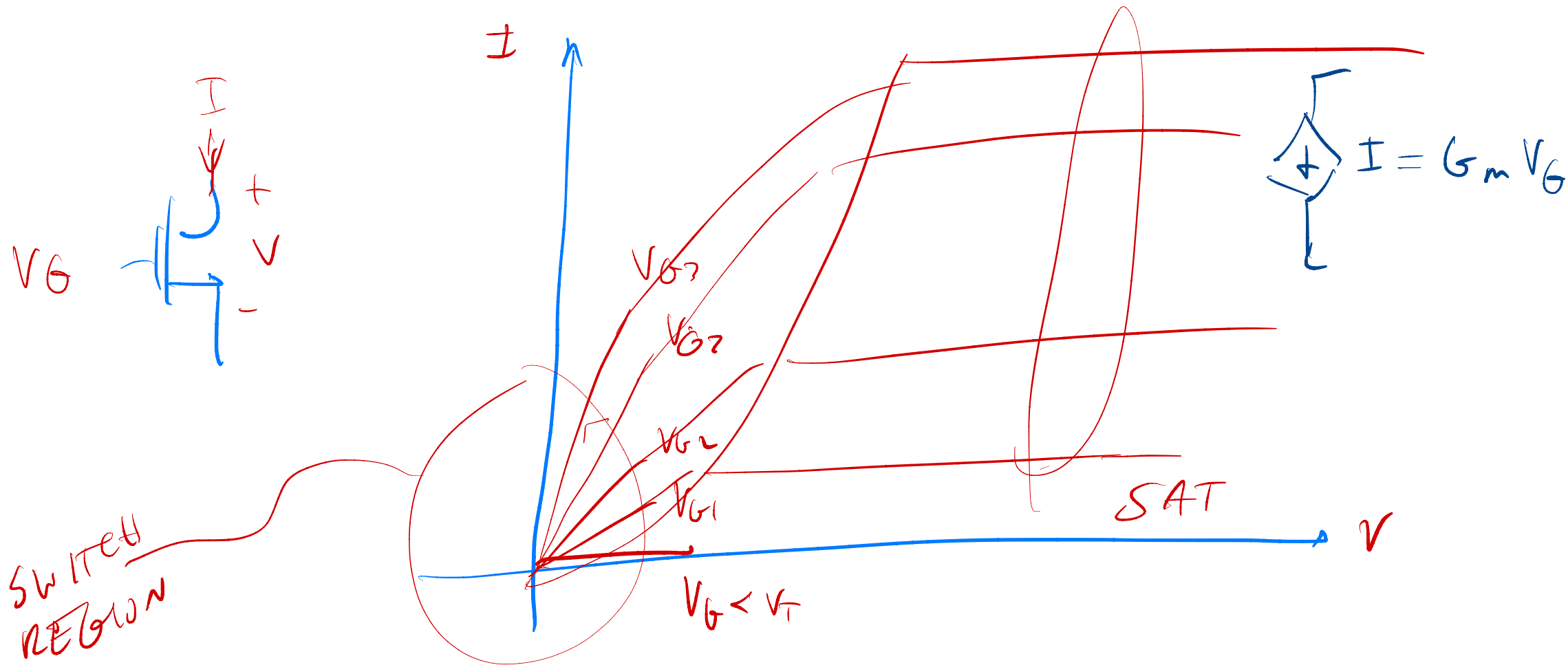



~~Op~~-Amp Model with RC

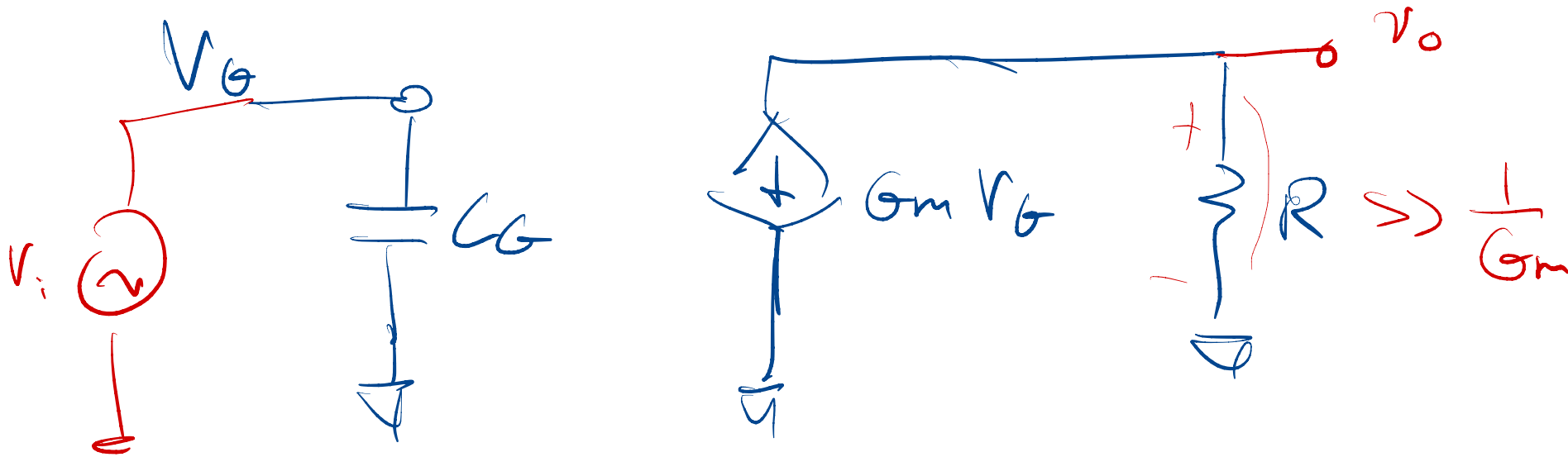

$$v_o = (-G_m V_G) \cdot R = -G_m R V_i$$

$$A_v = -G_m R \gg 1$$

16A / 16B

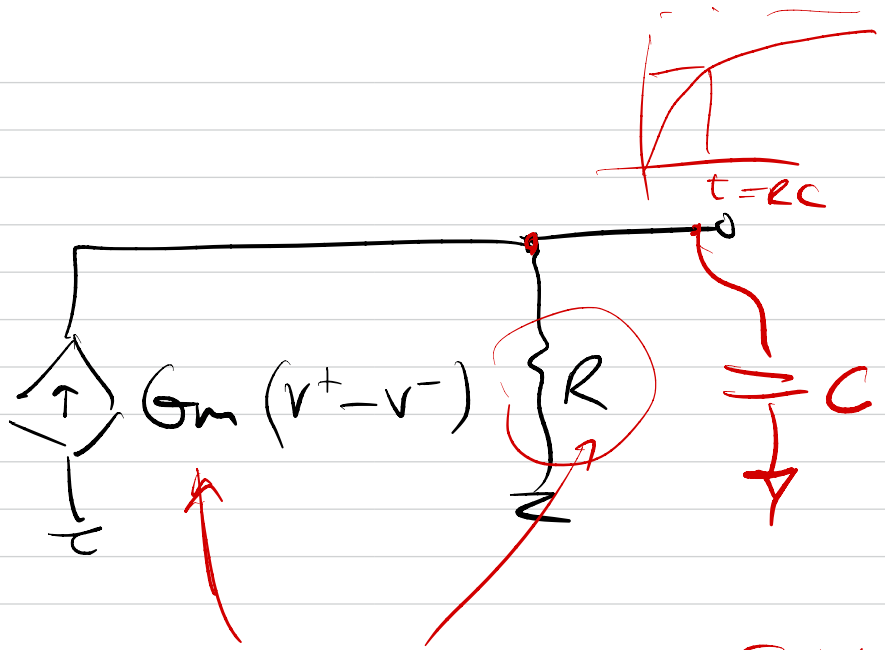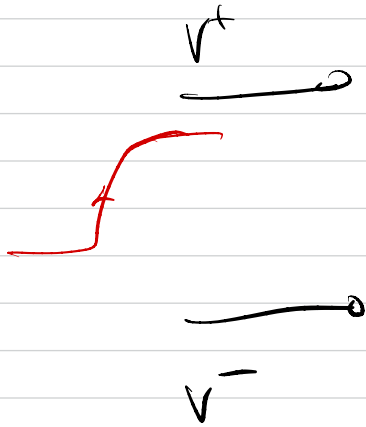


$$R C \frac{dv}{dt} + \frac{v}{R} = R G_m (v^+ - v^-) = \begin{cases} LV \ t_{90} \\ \text{or } t_{c0} \end{cases}$$

$$\tau \frac{dv}{dt} + v = u(t)$$

Input (constant)

Solution By Inspection

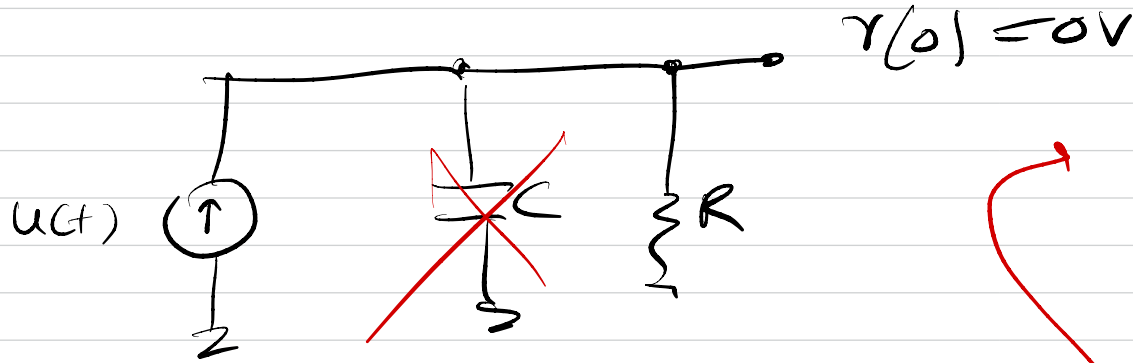


Capacitors
are
open
circuit


Predict Steady-state Solution

$$\tau \frac{dv}{dt} + v = u(t)$$

$v \sim \text{constant}$


$$\frac{dv}{dt} = 0$$

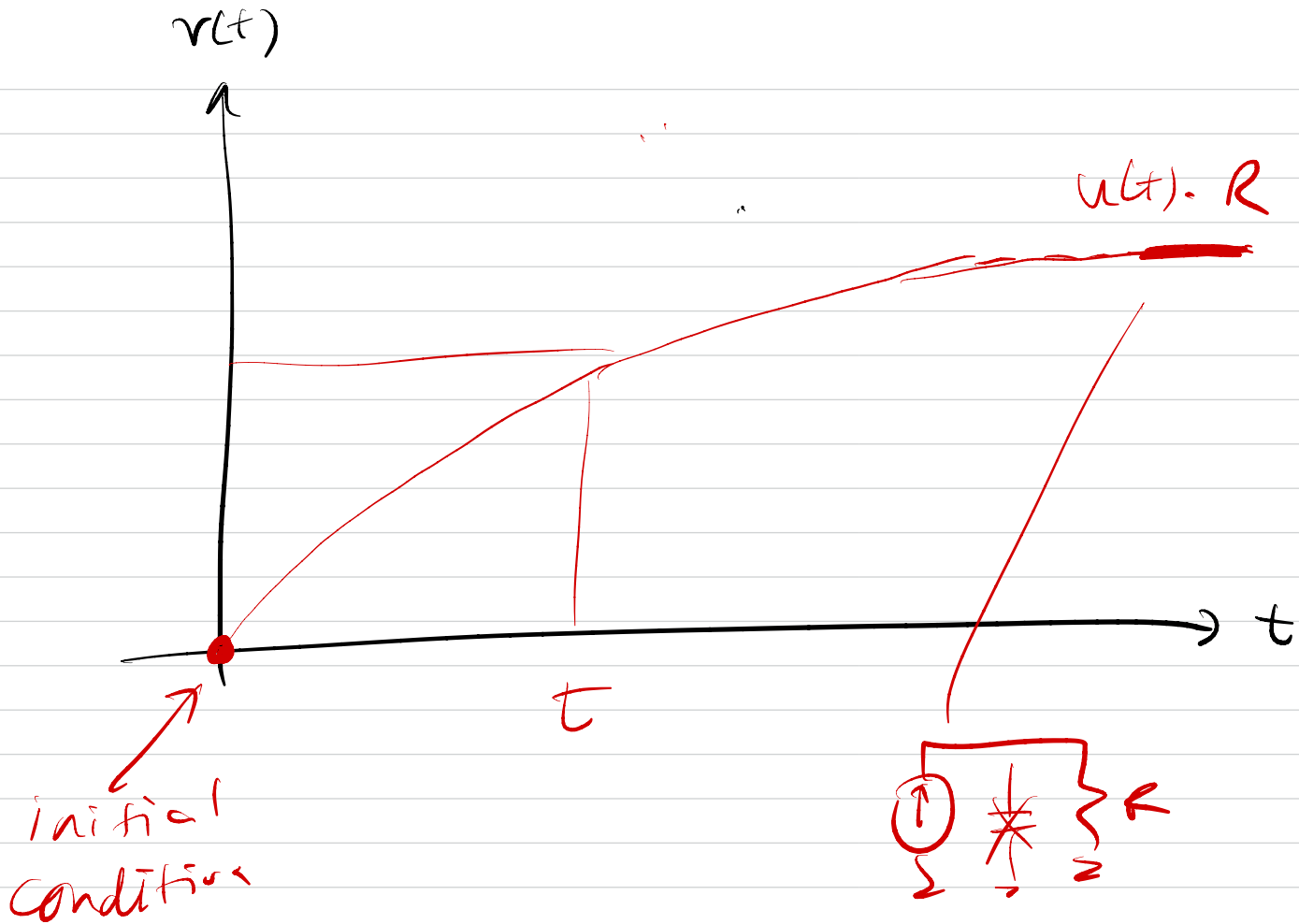

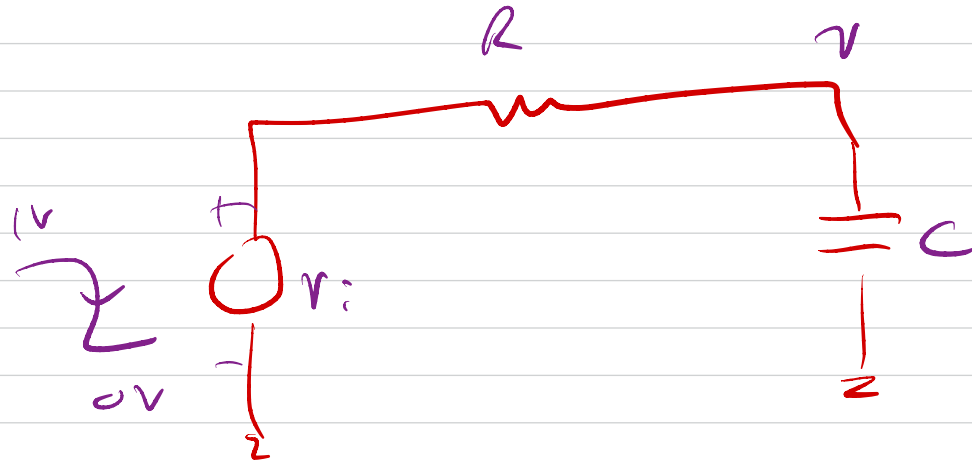

$$V(0) = 1V$$

$$V(\infty) = ?$$

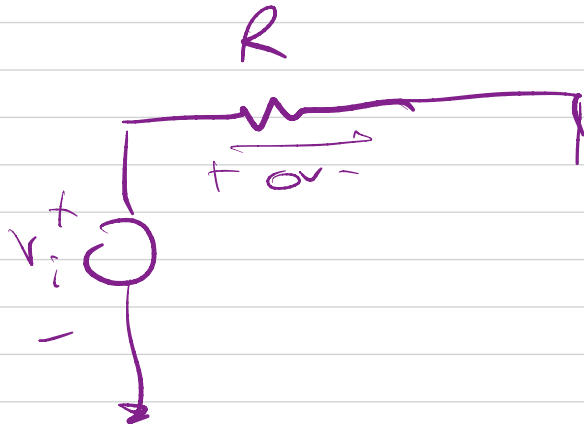


$$V(\infty) = v_i = 0V$$




Amplifier Settling Time

Applications

ADCs and DACs

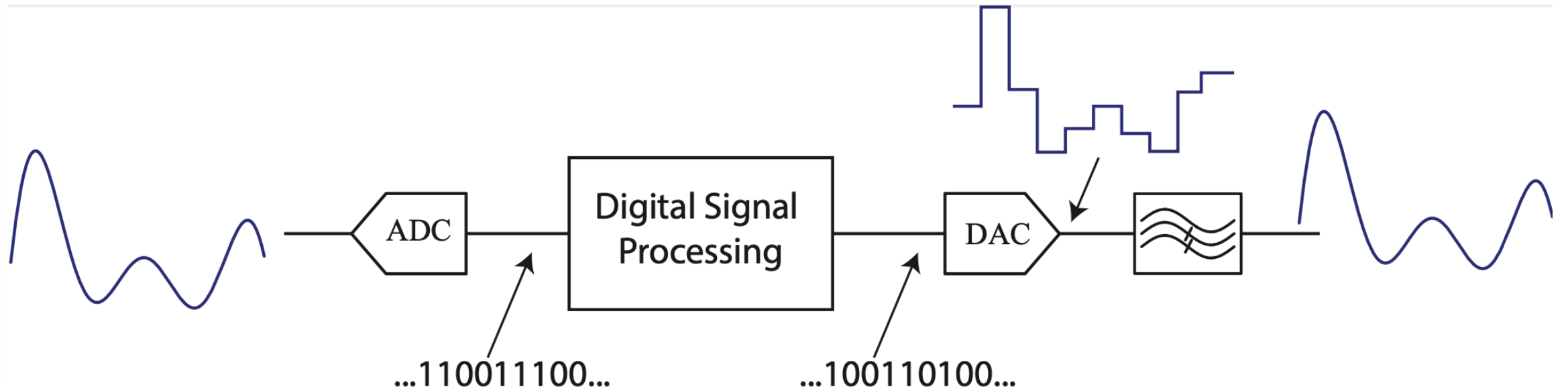

R-2R Ladder Digital-to-Analog Converter

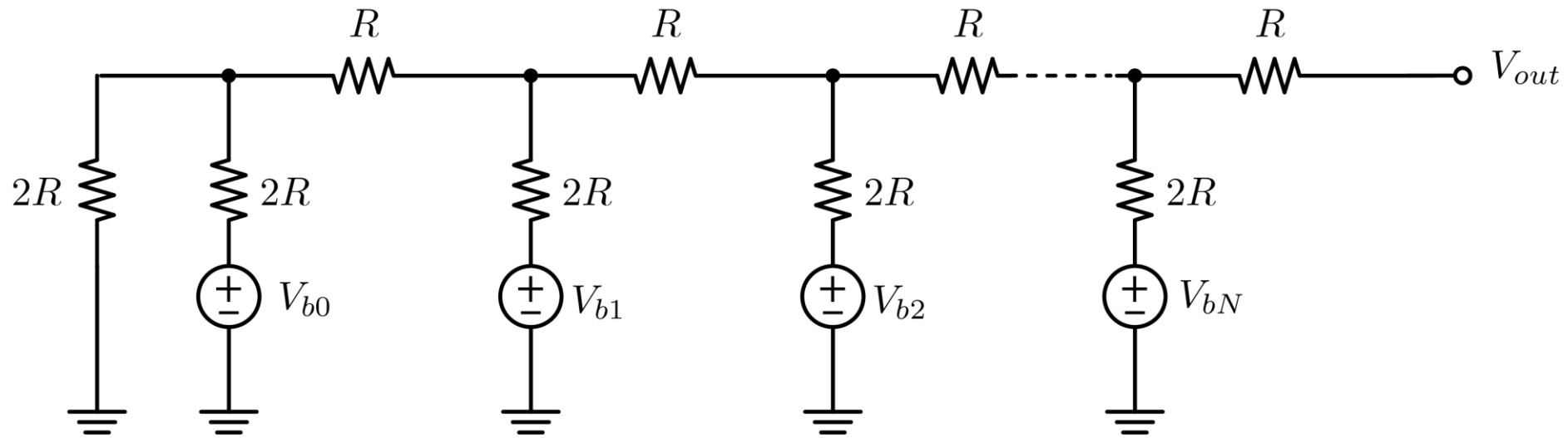


How to set all these “digital” voltages?

Remember Superposition and Equivalence?


R-2R Ladder Digital-to-Analog Converter

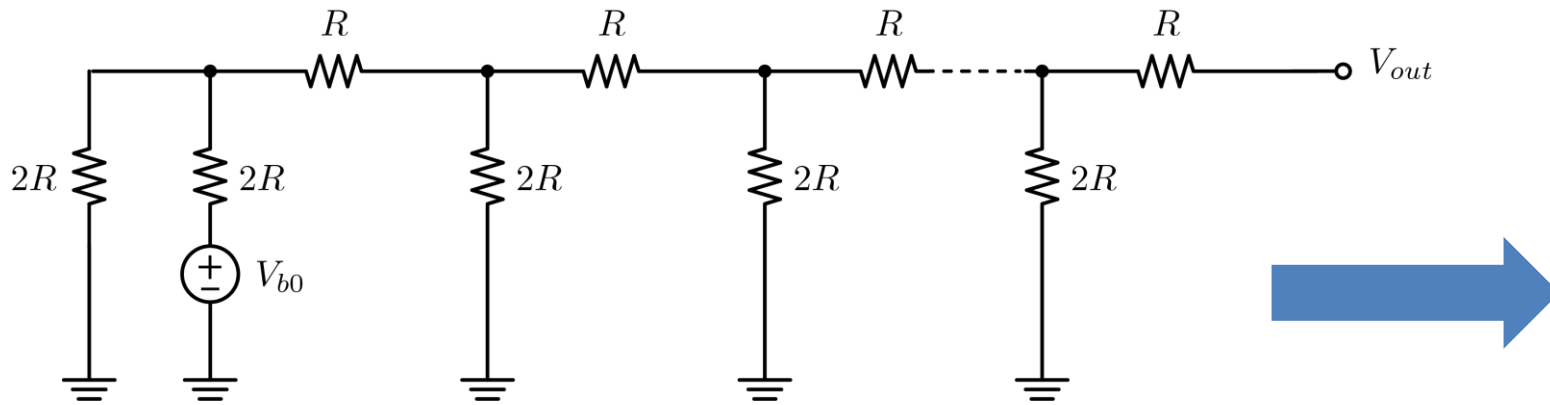Use superposition: Start with first voltage source:





R-2R Ladder Digital-to-Analog Converter

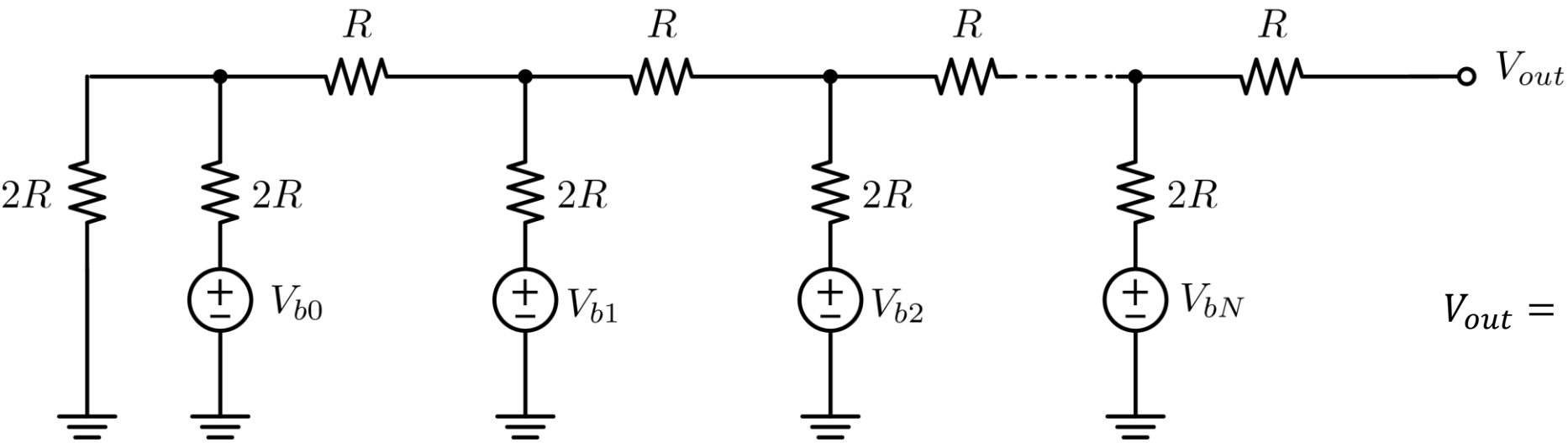Adding all contributions from the sources



$$V_{out} = \frac{V_{b0}}{2^N} + \frac{V_{b1}}{2^{N-1}} + \dots + \frac{V_{bN}}{2}$$

Switches

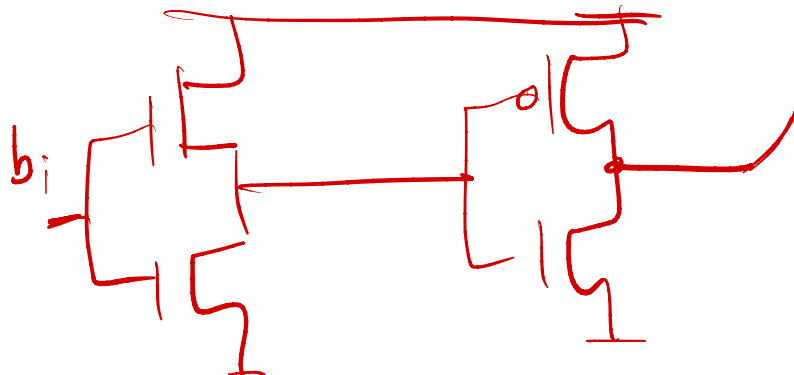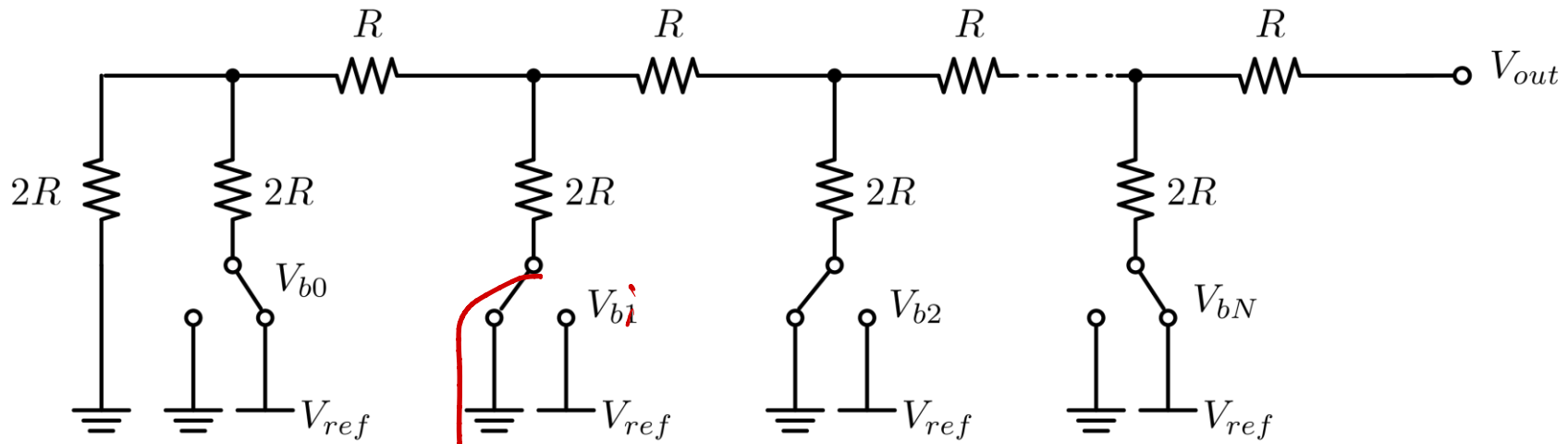


CMOS Gates

How fast can we “convert”?

- If there were no capacitors, we could do it instantly !


Analog to Digital Conversion

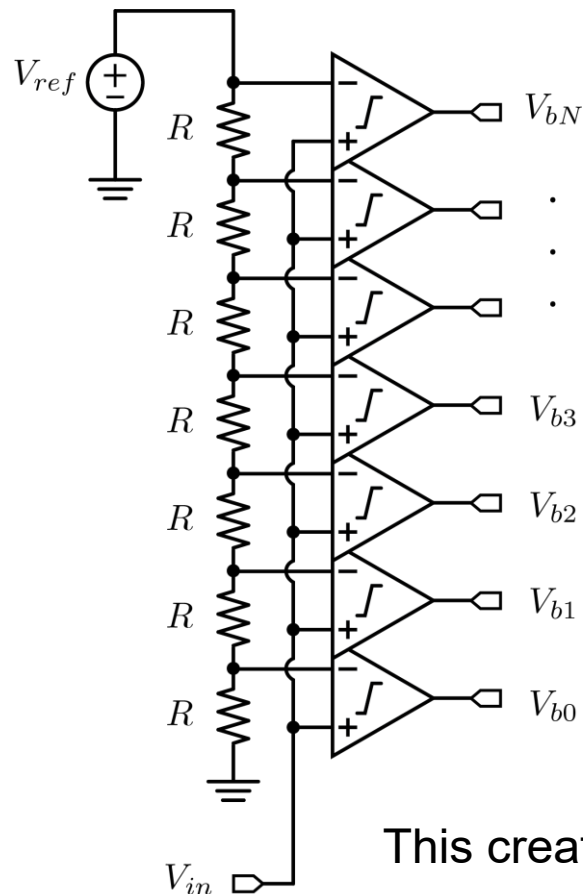

- Very fast massively parallel architecture
- Requires 2^N comparators (specialized op-amps)
- Op-amps have input capacitance
- Power consumption is high for fast operation


This creates a “Thermometer” digital code. Need to convert to binary for most applications:

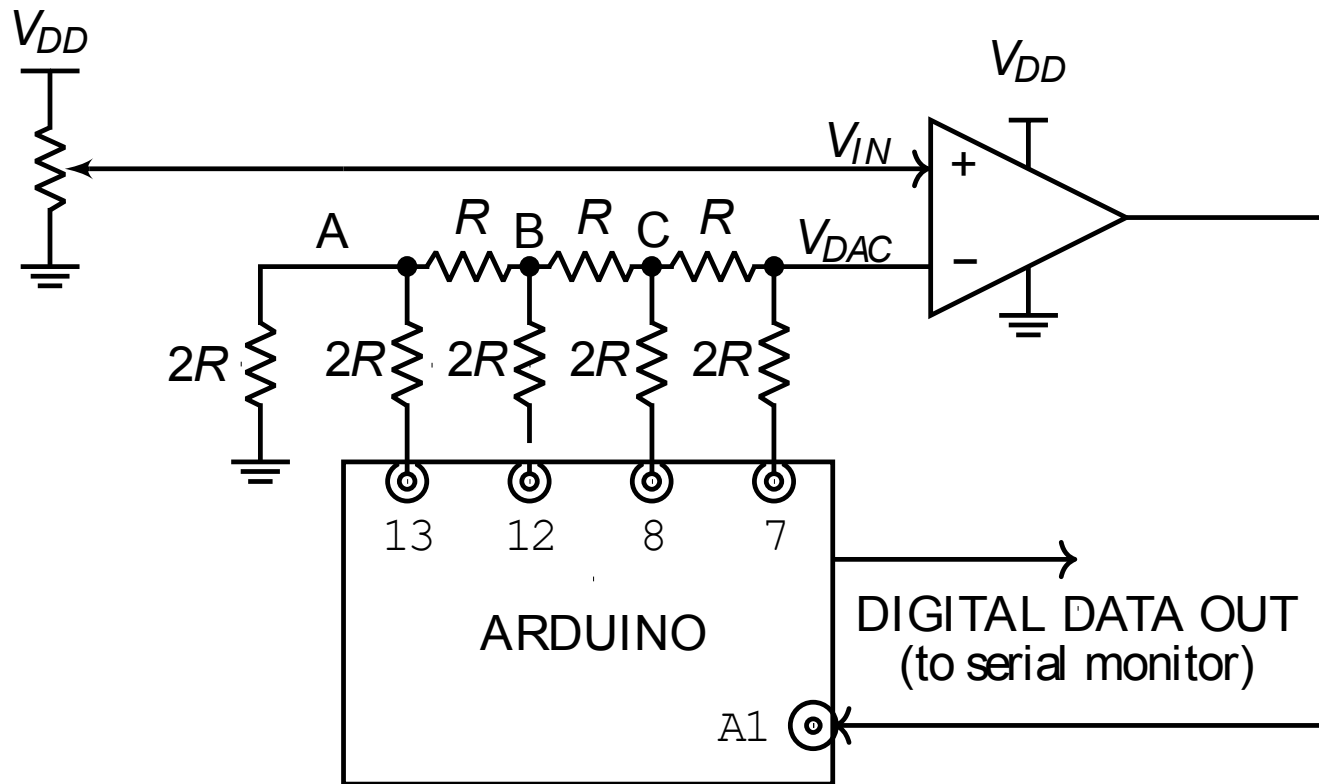Lab 2: SAR (Successive Approximation Resistor) ADC



- Use a DAC to guess signal and find best digital representation
- Can do this in $\log(N)$ steps (“guessing game”)

RC Integrator Idea

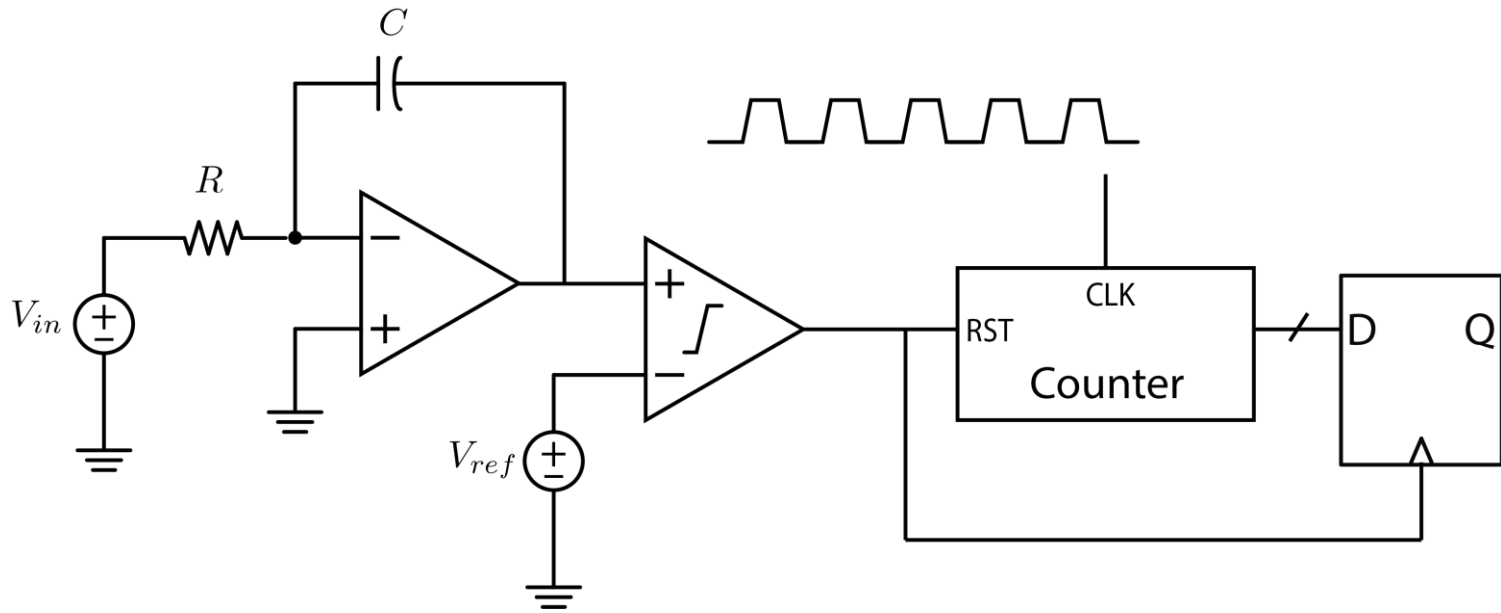

- RC + op-amp creates a ramp with slope proportional to input
- Count how long it takes to reach a reference value
- Counter is digital representation