



The background image shows a detailed microchip layout with various functional blocks highlighted by dashed yellow boxes. Labels in yellow text identify these blocks: 'RX' (Receiver), 'LO Buffer' (Local Oscillator Buffer), 'Hybrid', 'Wilkinson' (referring to a Wilkinson power divider), 'LO Buffer' (another instance), and 'TX' (Transmitter). The layout features a dense grid of circuit traces and components.

EECS 16B

Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran
Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu

Module 6: Vector Differential Equations and State-Space Representation

EECS 16B

Summary

- Systematic method to setup VDE
- How to solve vector differential equation (VDE)
- Solution of VDE in eigenspace with sources
- Steady-state solution of VDE
- Example

Example

- Suppose we have the following circuit.

-
- We can by “inspection” (KCL/KVL) setup a VDE. The key point is to write all voltages and currents only in terms of the “state” variables
 - The state variables are the voltages of the capacitors and the currents of the inductors.

Systematic Way of Setting Up VDE

- There are efficient systematic ways of setting up the VDE but that's beyond what we've learned in 16AB (see **Basic Circuit Theory by** Desoer and Kuh)
- We'll use repeated application of Thevenin's theorem

Replace State Variables

- For each capacitor C or inductor L ,
 - Replace it with a source that has the same voltage / current as the state variable
 - Inductors become independent current sources
 - Capacitors become independent voltage sources
- Note that everything about the circuit is known for time t
- How does the system evolve?

Evolution of a Particular State

- For each state variable L/C
 - Look into the circuit from the terminals of the L/C using the modified schematic
 - Find the Thevenin equivalent voltage and Thevenin equivalent resistance seen by this terminal (or Norton)
 - Note these sources are going to be a function of only the actual sources and the state variables
 - Write a simple first-order differential equation for the state transition
- You now have the VDE

Example Circuit

Complete VDE

- Key points: For the matrix A , each row is a linear combination of the sources ... the sources are the true external stimuli and the other state variables

Solve VDE Using Diagonalization

VDE Solution (cont)

Eigenvalues of A

- Recall how we find the eigenvalues. Essentially, we solve an algebraic equation and find n roots for a system with n state variables
- Each root is a possible “mode” of the overall system
- These eigenvalues only depend on the values of LCR in the circuit and not on the sources. They are a “natural” part of the circuit

Solution for Eigenvalue k

- Consider the homogeneous solution. Each equation is simply a first-order system that we've met before (RC circuit)
- The time constant is NOT related to "RC"

Stable Solution

- The only difference is that the eigenvalue is actually in general a complex quantity since it's the eigenvalues of the matrix A
- For the system to be stable, we need to ensure that all the eigenvalues have a negative real part !

What are the Initial Conditions?

- Note that the initial conditions are a linear combination of the circuit initial conditions (state variables)

Forced Response

- Since we've reduced the system to simple constant coefficient linear differential equations, we know the forced response !
- Note that the sources are also transformed into the eigenspace through the matrix Q^{-1}

Steady-State DC Response

Forced Response in Steady-State

- What happens to all the natural modes of the circuit?

Detailed Example

Steady-State Sinusoidal Response

AC Analysis

- Can we get here directly without setting up all the VDE and solving it ?