



The background image shows a detailed microchip layout with various functional blocks highlighted by dashed yellow boxes. The labels include 'RX' (Receiver), 'LO Buffer' (Local Oscillator Buffer), 'Hybrid', 'Wilkinson' (referring to a Wilkinson power divider), 'LO Buffer' (another instance), and 'TX' (Transmitter). The layout features a dense grid of circuit traces and components.

EECS 16B

Designing Information Devices and Systems II


Prof. Ali Niknejad and Prof. Kannan Ramchandran
Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu

Module 6: Vector Differential Equations and State-Space Representation

EECS 16B


Summary

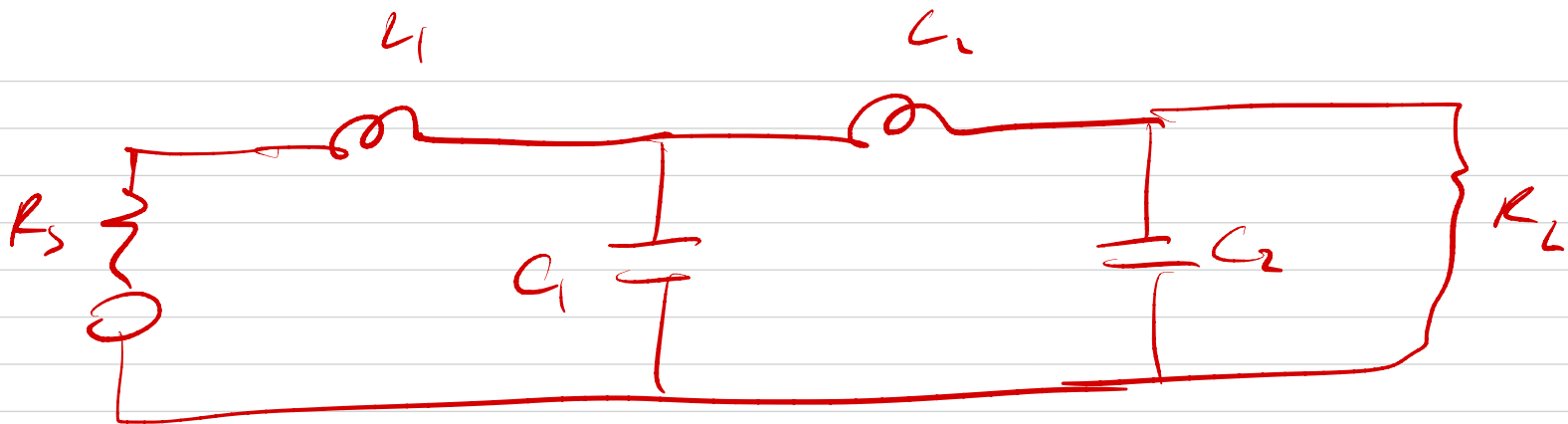- Systematic method to setup VDE
- How to solve vector differential equation (VDE)
- Solution of VDE in eigenspace with sources
- Steady-state solution of VDE
- Example



$$\vec{x} = \begin{pmatrix} v_{C1} \\ v_{C2} \\ i_{L1} \\ i_{L2} \end{pmatrix}$$


\vec{x} is the state of the system

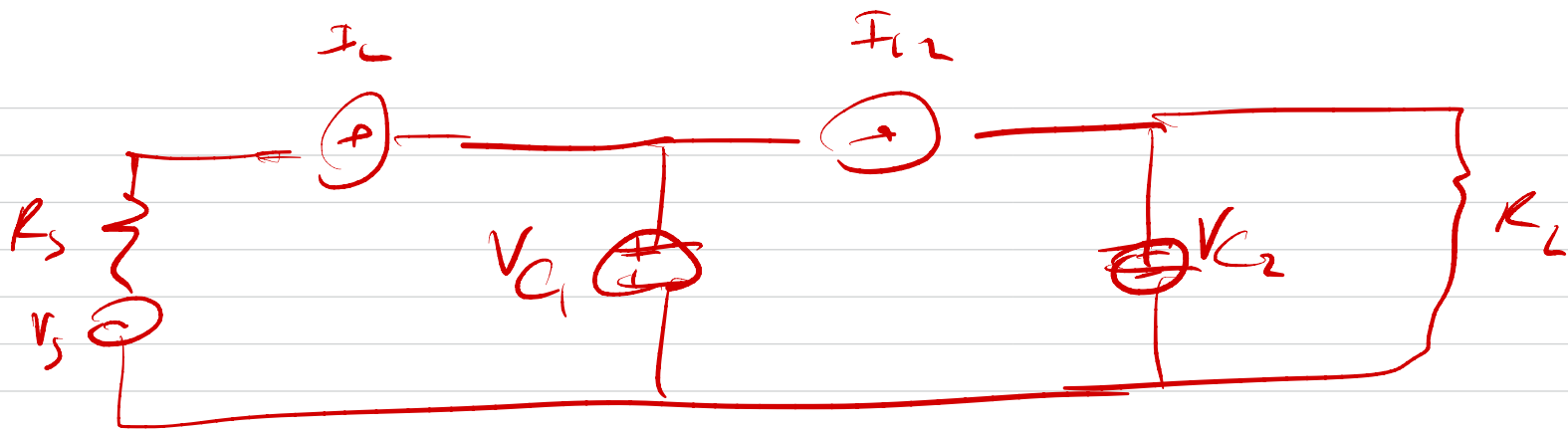

$$\vec{x}^o = A \vec{x} + \vec{b}_s$$

Example

- Suppose we have the following circuit.

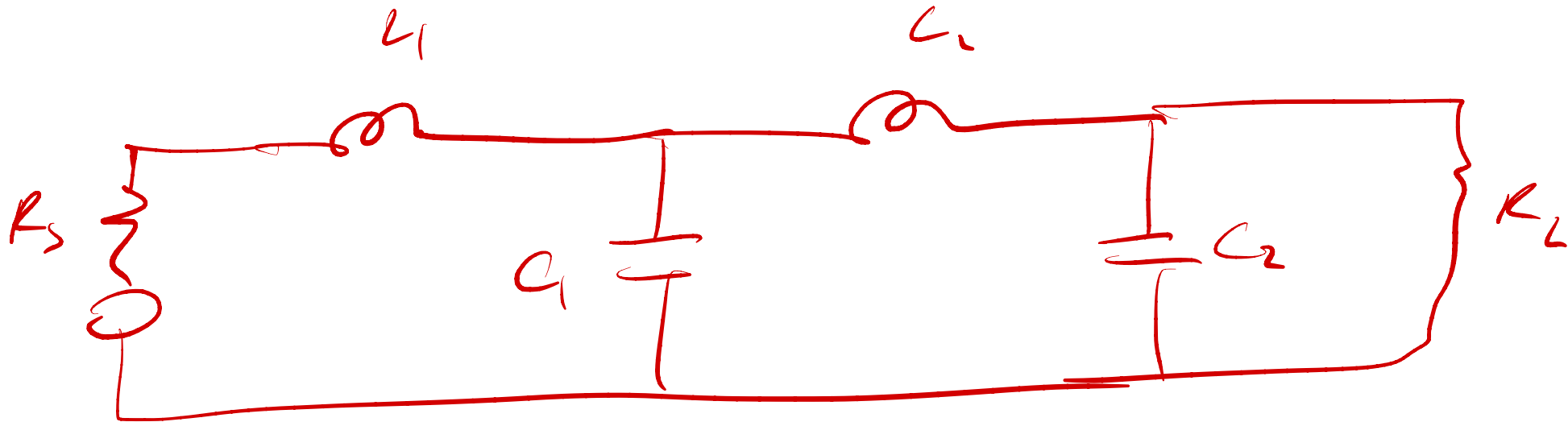

-
- We can by “inspection” (KCL/KVL) setup a VDE. The key point is to write all voltages and currents only in terms of the “state” variables
 - The state variables are the voltages of the capacitors and the currents of the inductors.

Systematic Way of Setting Up VDE

- There are efficient systematic ways of setting up the VDE but that's beyond what we've learned in 16AB (see **Basic Circuit Theory** by Desoer and Kuh) *+ Chua*
- We'll use repeated application of Thevenin's theorem
OR Norton


Replace State Variables

- For each capacitor C or inductor L ,
 - Replace it with a source that has the same voltage / current as the state variable
 - Inductors become independent current sources
 - Capacitors become independent voltage sources
- Note that everything about the circuit is known for time t
- How does the system evolve?



Evolution of a Particular State

- For each state variable L/C
 - Look into the circuit from the terminals of the L/C using the modified schematic
 - Find the Thevenin equivalent voltage and Thevenin equivalent resistance seen by this terminal (or Norton)
 - Note these sources are going to be a function of only the actual sources and the state variables
 - Write a simple first-order differential equation for the state transition
- You now have the VDE

Example Circuit

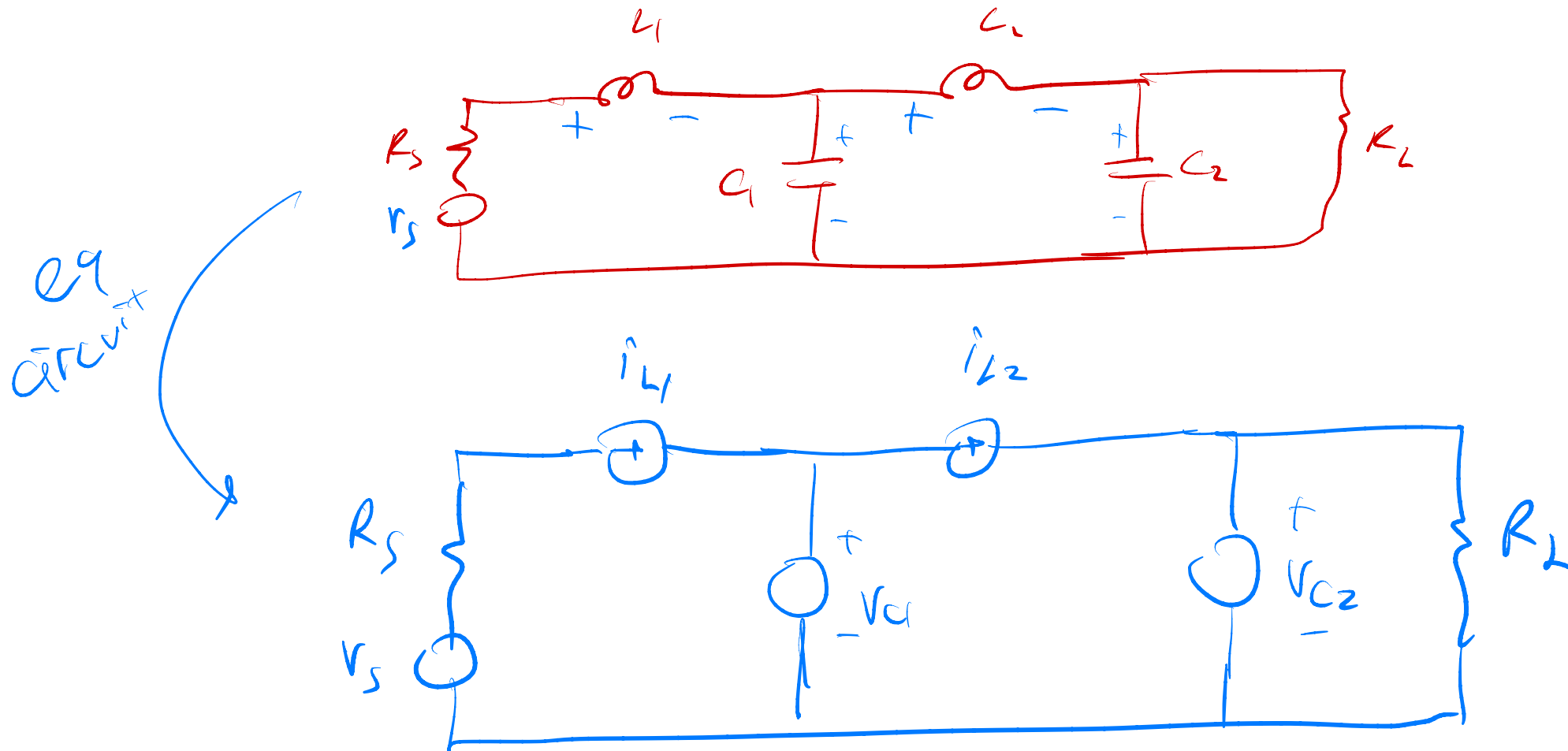


C1

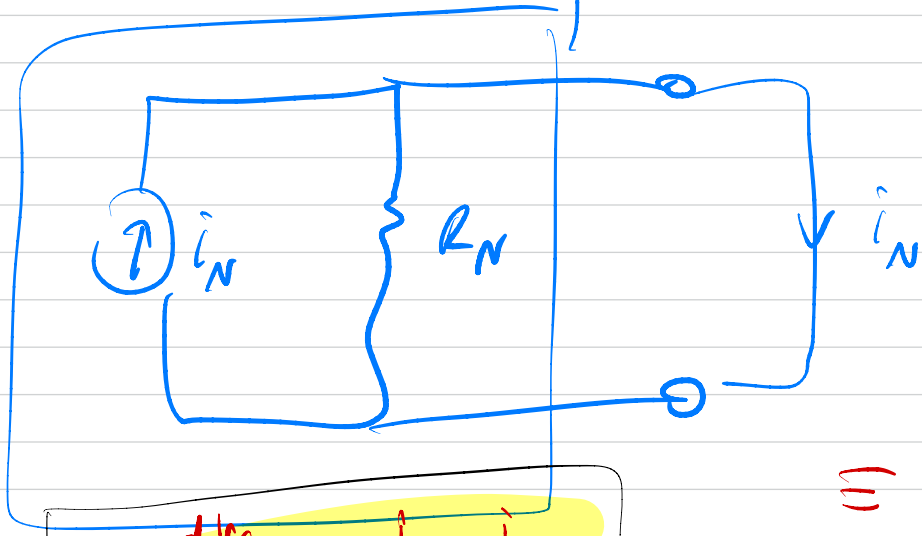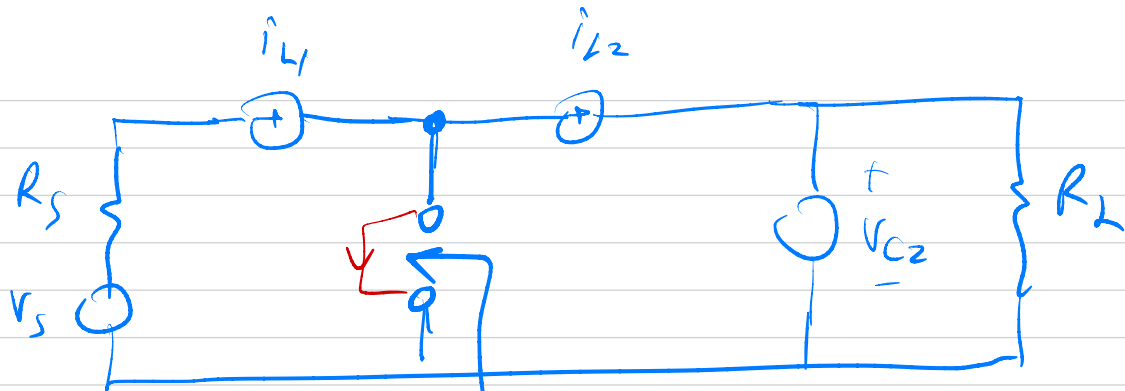


$$C_1 \frac{dv_C}{dt} = i_{L1} - i_{L2}$$

$$i_N = i_{L1} - i_{L2}$$

$$R_N = \infty \Omega$$

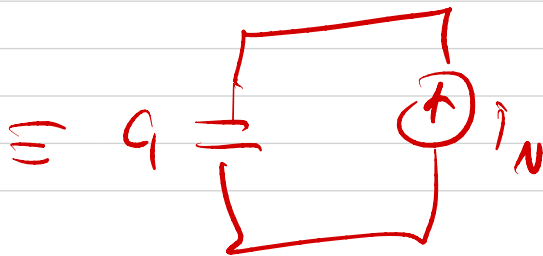


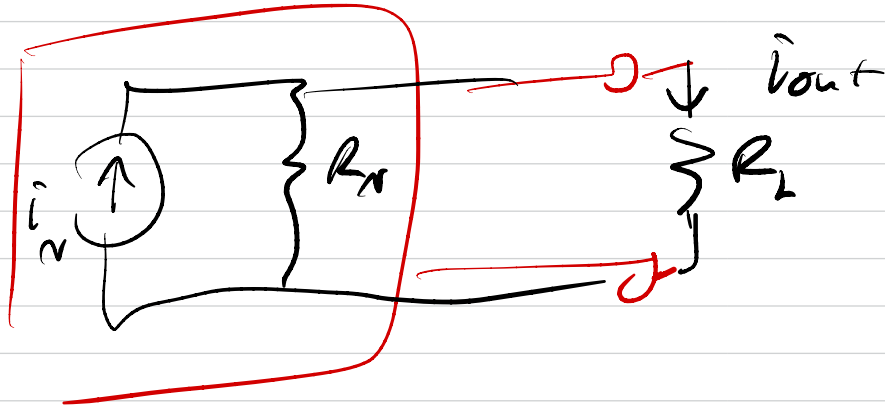

$$i_{out} = \frac{R_N}{R_N + R_L} \cdot i_N \quad \left. \vphantom{\frac{R_N}{R_N + R_L}} \right\} \text{current divider}$$


$$\underline{\approx} i_N \quad \text{As } R_N \rightarrow \infty \Omega$$

C₂

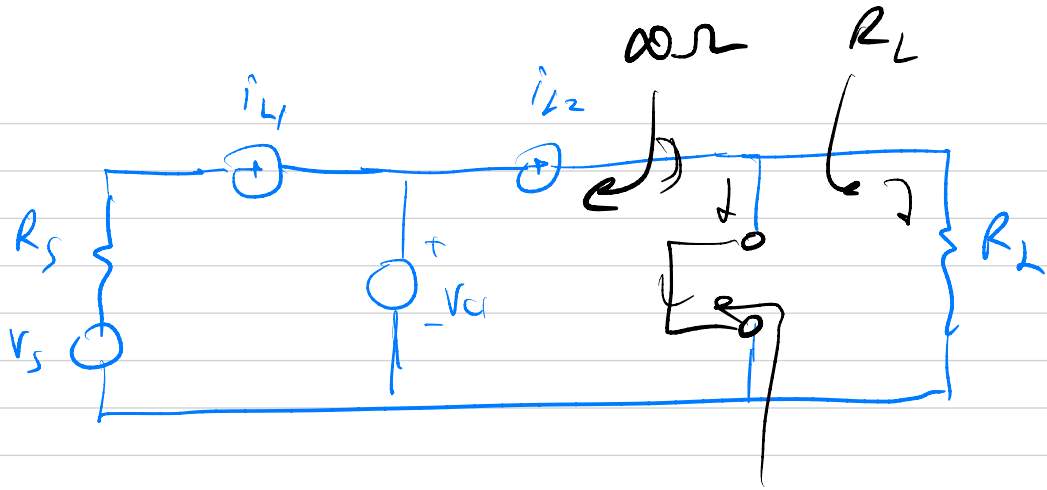

$$\hat{i}_N = \hat{i}_{L2}$$



$$R_N = R_L$$

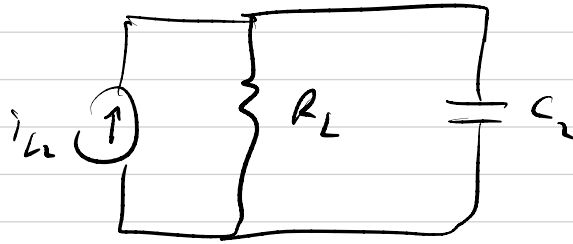

$$C_2 \frac{dv_{C2}}{dt} = i_{L2} - \frac{v_{C2}}{R_L}$$

state variables


L_1

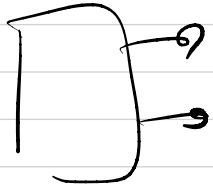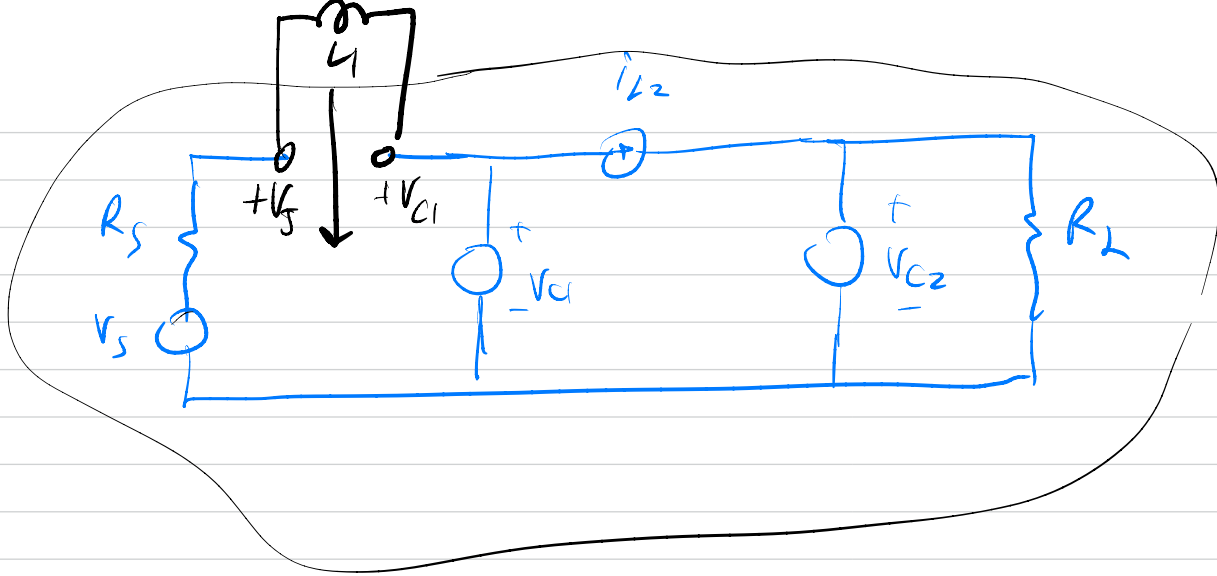


$$V_{oc} = V_{TH} = v_s - v_{c1}$$

$$R_{TH} = R_s$$
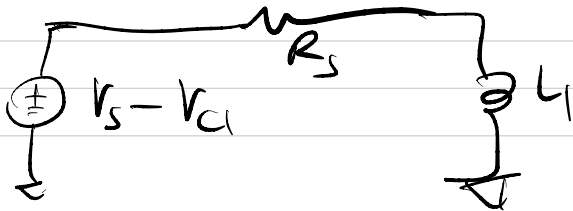
$$L_1 \frac{di_{L_1}}{dt} = v_s - v_{c1} - i_{L_1} \cdot R_s$$



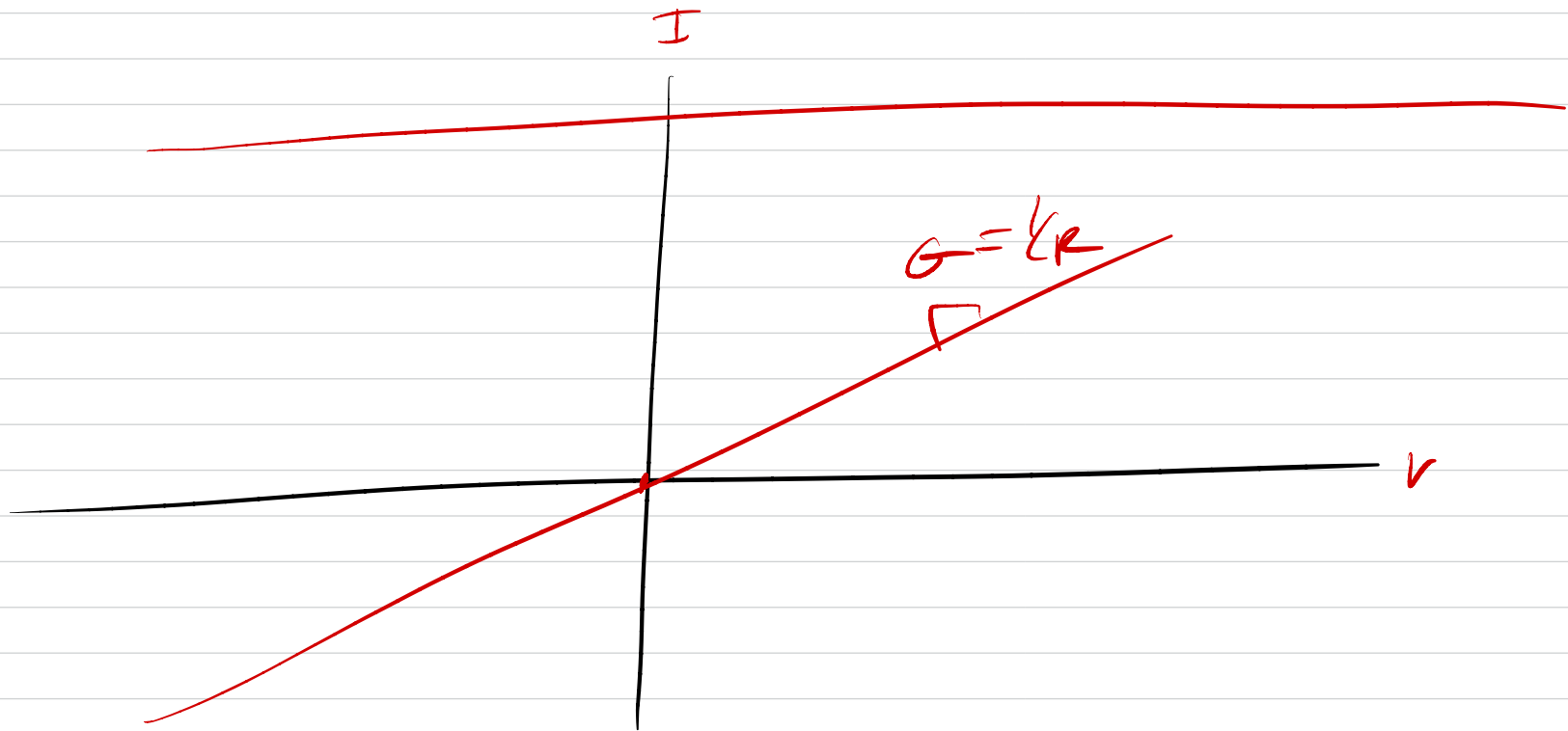

L_2

$$L_2 \frac{di_2}{dt} = v_{c1} - v_{c2}$$

do at home

$$\frac{dx}{dt} =$$

$$\frac{d}{dt}$$

$$\begin{pmatrix} v_{c1} \\ v_{c2} \\ i_{L1} \\ i_{L2} \end{pmatrix}$$

$$\underbrace{\hspace{10em}}_x$$

$$= \begin{pmatrix} 0 & 0 & 1 & -\frac{1}{C_1} \\ 0 & -\frac{1}{R_1 C_2} & 0 & \frac{1}{C_2} \\ -1 & 0 & \frac{R_1}{L_1} & 0 \\ \frac{1}{L_2} & -\frac{1}{L_2} & 0 & 0 \end{pmatrix} x +$$

$$\begin{pmatrix} 0 \\ 0 \\ \frac{1}{L_1} \\ 0 \end{pmatrix} v_s$$

A

Complete VDE

- Key points: For the matrix A , each row is a linear combination of the sources ... the sources are the true external stimuli and the other state variables

$$\frac{d\vec{x}}{dt} = A\vec{x} + \vec{b}_s$$

$$\frac{d\vec{x}}{dt} = Q\Lambda\left[Q^{-1}\vec{x}\right] + \vec{b}_s$$

$$\left(\frac{d}{dt}Q^{-1}\vec{x}\right) = Q^{-1}Q\Lambda\vec{u} + Q^{-1}\vec{b}_s = \Lambda\vec{u} + \vec{b}_s$$

Solve VDE Using Diagonalization

$$Q^{-1} \dot{\vec{x}} = \Lambda \vec{u} + \vec{b}_s$$

$$Q^{-1} \dot{\vec{x}} = Q^{-1} \frac{d}{dt} \vec{x} = \frac{d}{dt} (Q^{-1} \vec{x}) = \frac{d}{dt} \vec{u} = \dot{\vec{u}}$$

$$\dot{\vec{u}} = \Lambda \vec{u} + \vec{b}_s$$

$$\boxed{\frac{d}{dt} \vec{u} = \Lambda \vec{u} + \vec{b}_c}$$

VDE Solution (cont)

$$\frac{d}{dt} u_1 = \lambda_1 u_1 + \tilde{b}_{s1}$$

1st order
constant coefficient
diff eq.

$$\frac{du_1}{dt} = \lambda_1 u_1$$

$$u_1 = A e^{\lambda_1 t}$$

$$\cancel{A} \lambda_1 e^{\lambda_1 t} = \cancel{\lambda_1} \cancel{A} e^{\lambda_1 t}$$

$$1 = 1 \quad \checkmark$$