



The background image shows a detailed microchip layout with various functional blocks highlighted by dashed yellow boxes. The labels include 'RX' (Receiver), 'LO Buffer' (Local Oscillator Buffer), 'Hybrid', 'Wilkinson' (referring to a Wilkinson power divider), 'LO Buffer' (Local Oscillator Buffer), and 'TX' (Transmitter). The layout features a dense grid of circuit traces and components.

EECS 16B

Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran
Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu

Module 9: AC Analysis

EECS 16B


Summary

- Steady-state solution of VDE
- Concept of Impedance
- AC Circuits
- Examples

Review: Forced Solution

Forced Sinusoidal Solution

Example Circuit

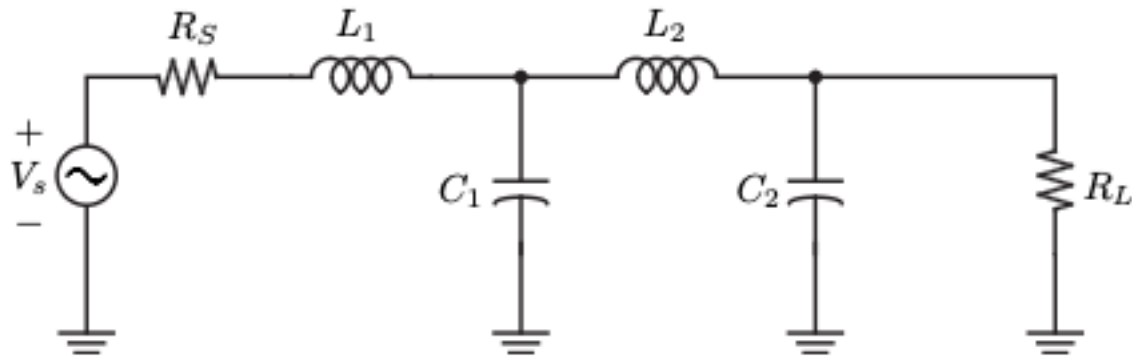


$$\vec{x} = (V_{C_1} \ V_{C_2} \ I_{L_1} \ I_{L_2})^T$$

$$\frac{d}{dt}\vec{x} = A\vec{x} + B\vec{b}_s$$

$$A = \begin{pmatrix} 0 & 0 & 1/C_1 & -1/C_1 \\ 0 & -1/R_L C_2 & 0 & 1/C_2 \\ -1/L_1 & 0 & -R_S/L_1 & 0 \\ 1/L_2 & -1/L_2 & 0 & 0 \end{pmatrix}$$
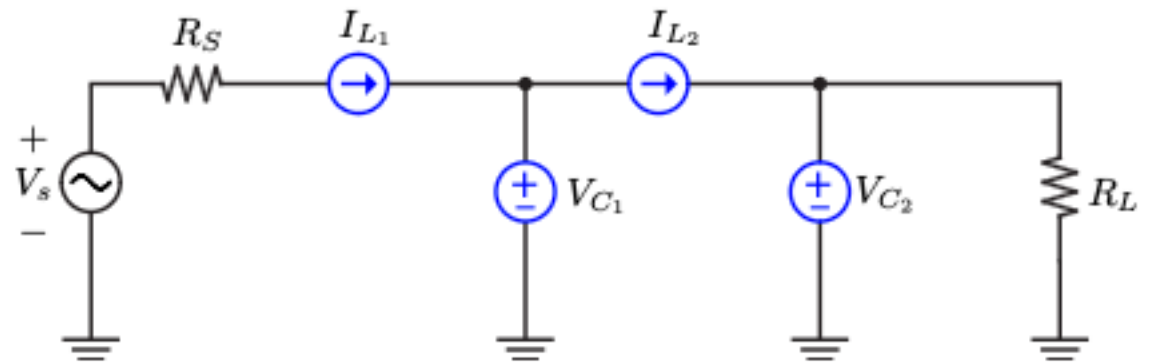
$$\kappa B = (0 \ 0 \ 1/L_1 \ 0)^T V_s.$$



Numerical Example

```
In[120]:= EV = Eigenvalues[A] ; EV // MatrixForm
```

```
Out[120]//MatrixForm=
```

$$\begin{pmatrix} -1.9034 \times 10^8 + 7.2085 \times 10^8 i \\ -1.9034 \times 10^8 - 7.2085 \times 10^8 i \\ -4.8545 \times 10^8 + 2.82637 \times 10^8 i \\ -4.8545 \times 10^8 - 2.82637 \times 10^8 i \end{pmatrix}$$


Note that the eigenvalues have an imaginary part close to the cut-off frequency of the filter (100 MHz):

```
In[121]:= Im[EV] / (2 Pi 100 × 10 ^ 6) // N
```

```
Out[121]= {1.14727, -1.14727, 0.449831, -0.449831}
```

$$\mathbf{bs} = \{\{0\}, \{0\}, \{1/L1\}, \{0\}\};$$
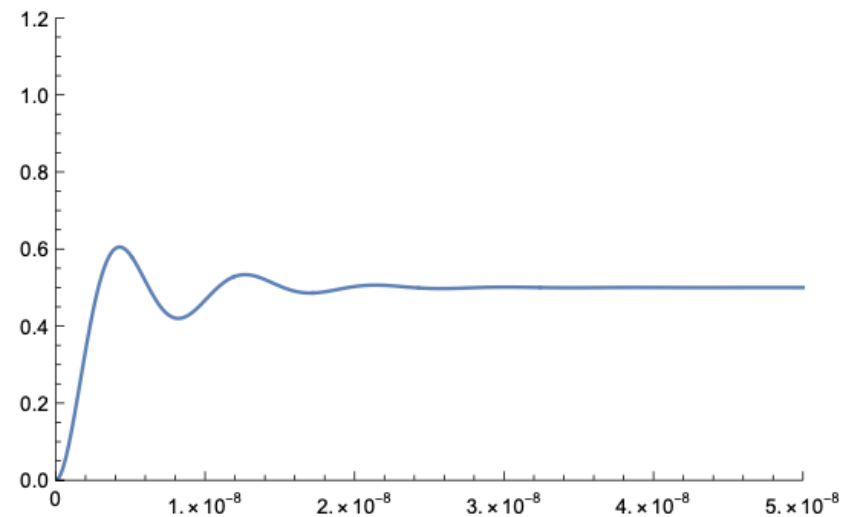
```
Plot[Re[xforce[t][[2]]], {t, 0, 5010^-9}, PlotRange->{{0, 5010^-9}, {0, 1.2}}
```



Forced Response

- Since we've reduced the system to simple constant coefficient linear differential equations, we know the forced response !
- Note that the sources are also transformed into the eigenspace through the matrix Q^{-1}

```
xforce[t_] = Q.MatrixExp[Dlam t].Qi.xi + Q.MatrixExp[Dlam t].Qi .Integrate[Q.MatrixExp[-Dlam sigma].Qi .bs , {sigma, 0, t}];
```


Steady-State DC Response

```
In[140]:= Limit[Q.MatrixExp[Dlam t].Qi .Integrate[Q.MatrixExp[-Dlam sigma ].Qi .bs , {sigma, 0, t}], t -> Infinity]
```

```
Out[140]= {{0.5}, {0.5 + 0. i}, {0.01 + 0. i}, {0.01}}
```

The final values are also easily derived from the basic vector equation by setting all derivatives to zero:

```
In[141]:= -Inverse[A] . bs
```


```
Out[141]= {{0.5}, {0.5}, {0.01}, {0.01}}
```

Sinusoidal Steady-State

```
w1 = 2 Pi 100 × 10 ^ 6;
```

```
In[143]:= xac1[t_] = Q.MatrixExp[Dlam t].Qi.xi + Q.MatrixExp[Dlam t].Qi.Integrate[Q.MatrixExp[-Dlam sigma].Qi.bs Cos[w1 sigma], {sigma, 0, t}];
```

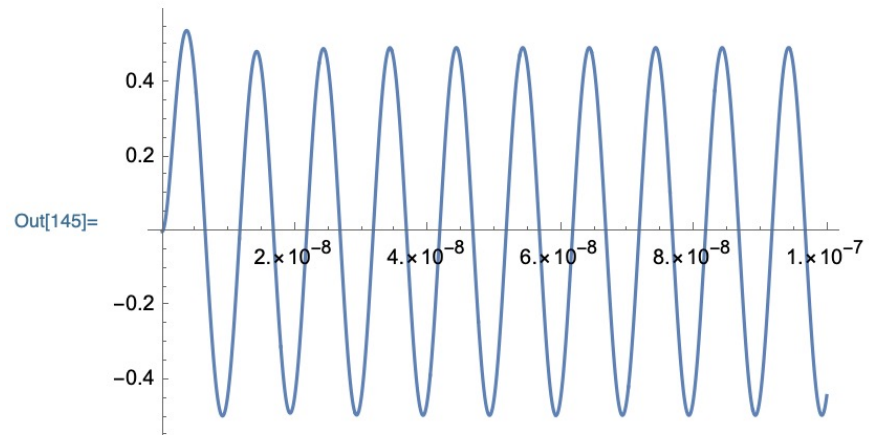
```
In[145]:= Plot[Re[xac1[t][[2]]], {t, 0, 100 × 10 ^ -9}]
```




Higher Frequency Response

```
xac2[t_] = Q.MatrixExp[Dlam t].Qi.xi + Q.MatrixExp[Dlam t].Qi.Integrate[Q.MatrixExp[-Dlam sigma].Qi.bs Cos[3 w1 sigma], {sigma, 0, t}];
```
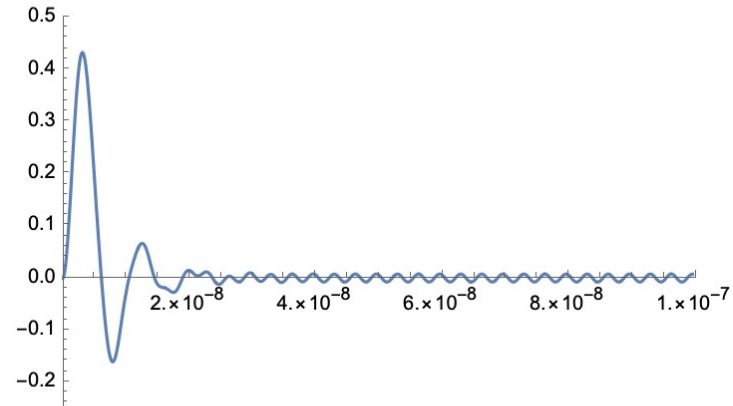
```
Plot[Re[xac2[t][[2]]], {t, 0, 100*10^-9}, PlotRange -> {{0, 100*10^-9}, {-0.25, 0.5}}]
```


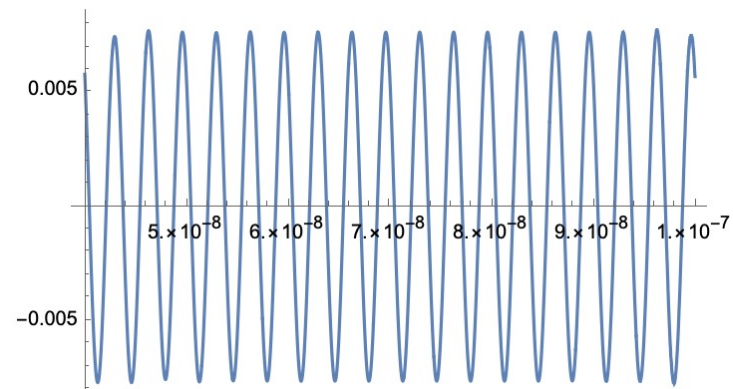
```
Plot[Re[xac2[t][[2]]], {t, 40*10^-9, 100*10^-9}]
```



Steady-State Sinusoidal Response

- Weighted integral perspective

Filter Design

Filter Properties

Response: Type:



Topology: Order:

Cutoff Frequency:

Passband Ripple (dB):

Input Impedance (Ω): Output Impedance (Ω):

Additional Settings
Component Values:

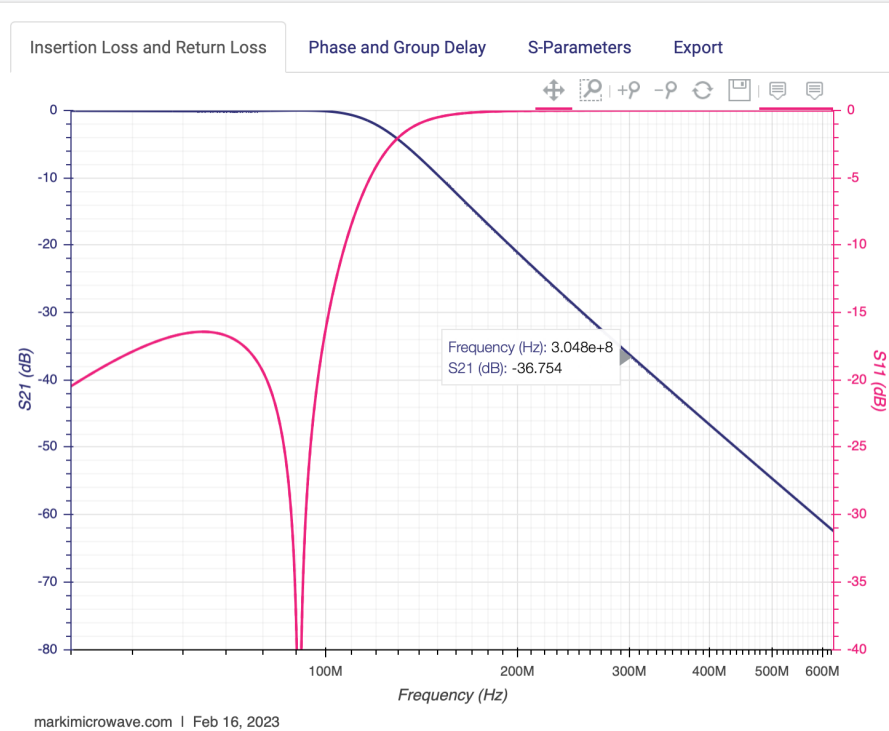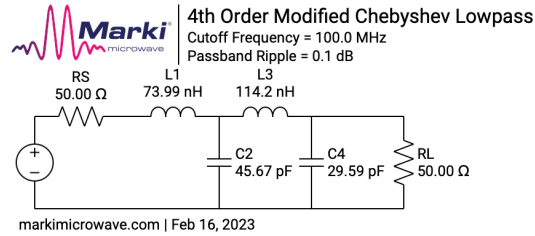

AC Analysis

- Can we get here directly without setting up all the VDE and solving it ?

“Phasors”

- A complex number by another name

Concept of Impedance

Reactance

Capacitors in AC Circuits

Inductors in AC Circuits

Direct Solution (no VDE required)

Phasor Algebra

- Same as any complex number

2nd Order AC Circuits
