



EECS 16B
Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran
Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu

Module 10: AC Networks and AC Power

EECS 16B

Summary

- AC Circuit Network Theorems
 - Voltage / current dividers
 - Source superposition
 - Thevenin/Norton
- AC Power
 - Average Power
 - Reactive Power
- Maximum power transfer theorem

Review AC Circuits

- Concept of Impedance
- AC equivalent circuit
- Concept of a “system” with AC circuits

AC Voltage Divider

AC Current Divider

AC Source Superposition

AC Thevenin/Norton

AC Power Flow

- Review passive sign convention

Instantaneous Power

Average Power

AC Power in Phasors

Alternate Forms

Inductors/Capacitors Store Energy

- Inductors and capacitors cannot dissipate energy.
- But charging a capacitor requires work, which is stored (not dissipated)
- It seems that we should account for this stored power in AC components

Reactive Power

Example: Real Inductor

- Concept of quality factor

Maximum Power Transfer Theorem

Applications: Solar Panel

Application: Power Matching

- Consider an inductive power link (RFID)