



EECS 16B

Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran

Department of Electrical Engineering and Computer Sciences, UC Berkeley,
niknejad@berkeley.edu

Module 10: AC Networks and AC Power


EECS 16B

Summary

- AC Circuit Network Theorems
 - Voltage / current dividers
 - Source superposition
 - Thevenin/Norton
- AC Power
 - Average Power
 - Reactive Power
- Maximum power transfer theorem


Review AC Circuits

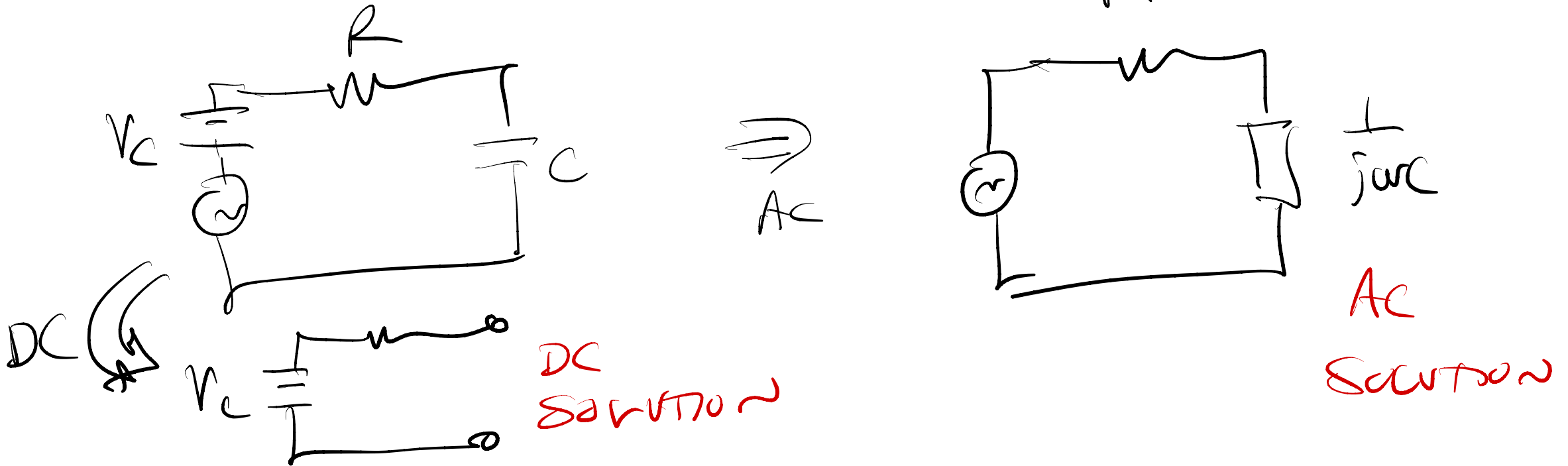- Concept of Impedance
- AC equivalent circuit
- Concept of a “system” with AC circuits



AC Voltage Divider

Current

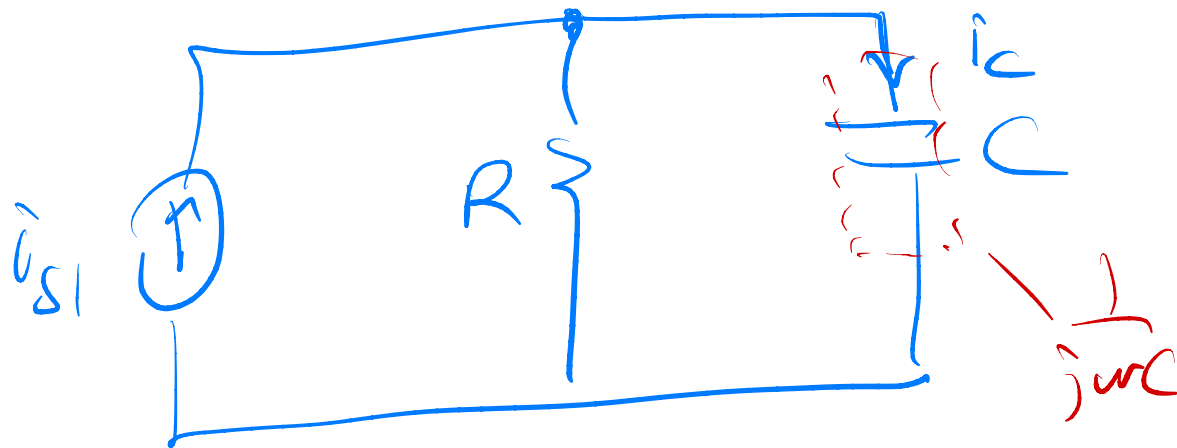

$$\hat{i}_c = \frac{Y_C}{Y_C + G} \hat{i}_{s1}$$

$$G = \frac{1}{R}$$

$$\hat{i}_c = \frac{j\omega C}{j\omega C + G} \hat{i}_{s1} = \frac{j\omega C}{G + j\omega C} \hat{i}_{s1}$$

$$H(j\omega) = \frac{\hat{i}_c}{\hat{i}_{s1}} = \frac{j\omega RC}{1 + j\omega RC} \hat{i}_{s1}$$

Reminder



$$\frac{i_2}{i_s} = \frac{G_2}{G_1 + G_2}$$

Serinity Check

o Check units


A/A



o DC solution

$\omega = 0$


$$H(j\omega) \Big|_{\omega=0} = \frac{j\omega RC}{1 + j\omega RC} \Big|_{\omega=0} = 0$$

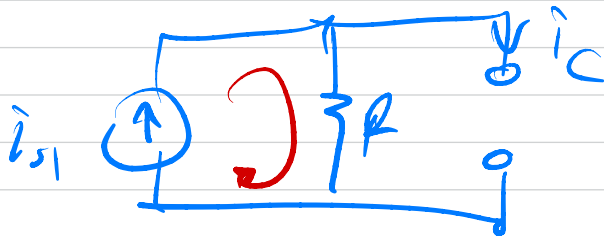

○ $\omega \rightarrow \infty$ VERY HIGH FREQ

$\frac{1}{\omega C} \rightarrow$ SHORTS

$\omega L \rightarrow$ OPENS

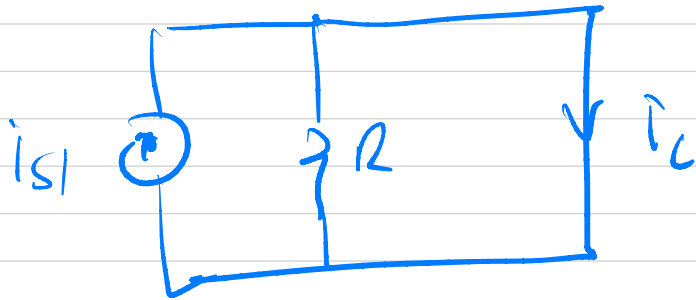

$$H(\omega) \Big|_{\omega \rightarrow \infty} = 1 \quad \checkmark$$

$$H(\omega) \Big|_{\omega=0} = \frac{j\omega RC}{1 + j\omega RC} \Big|_{\omega=0} = 1$$


AC Source Superposition



$$H_1 = \frac{j\omega RC}{1 + j\omega RC}$$

$$\frac{i_C}{i_{s2}} = 0$$

$$H_1 = 0$$

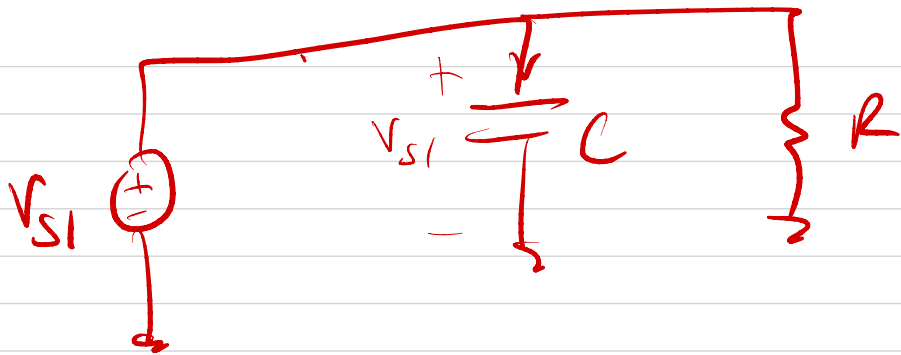


$$\hat{i}_C = \frac{V_{s1}}{1/j\omega C} = j\omega C V_{s1}$$

$$\frac{\hat{i}_C}{V_{s1}} = j\omega C$$



$\left\{ \begin{array}{l} \text{TURN OFF} \\ \text{OFF} \end{array} \right\} \left\{ \begin{array}{l} V_s \rightarrow \text{SHORT} \\ I_s \rightarrow \text{OPEN} \end{array} \right.$

AC Thevenin/Norton




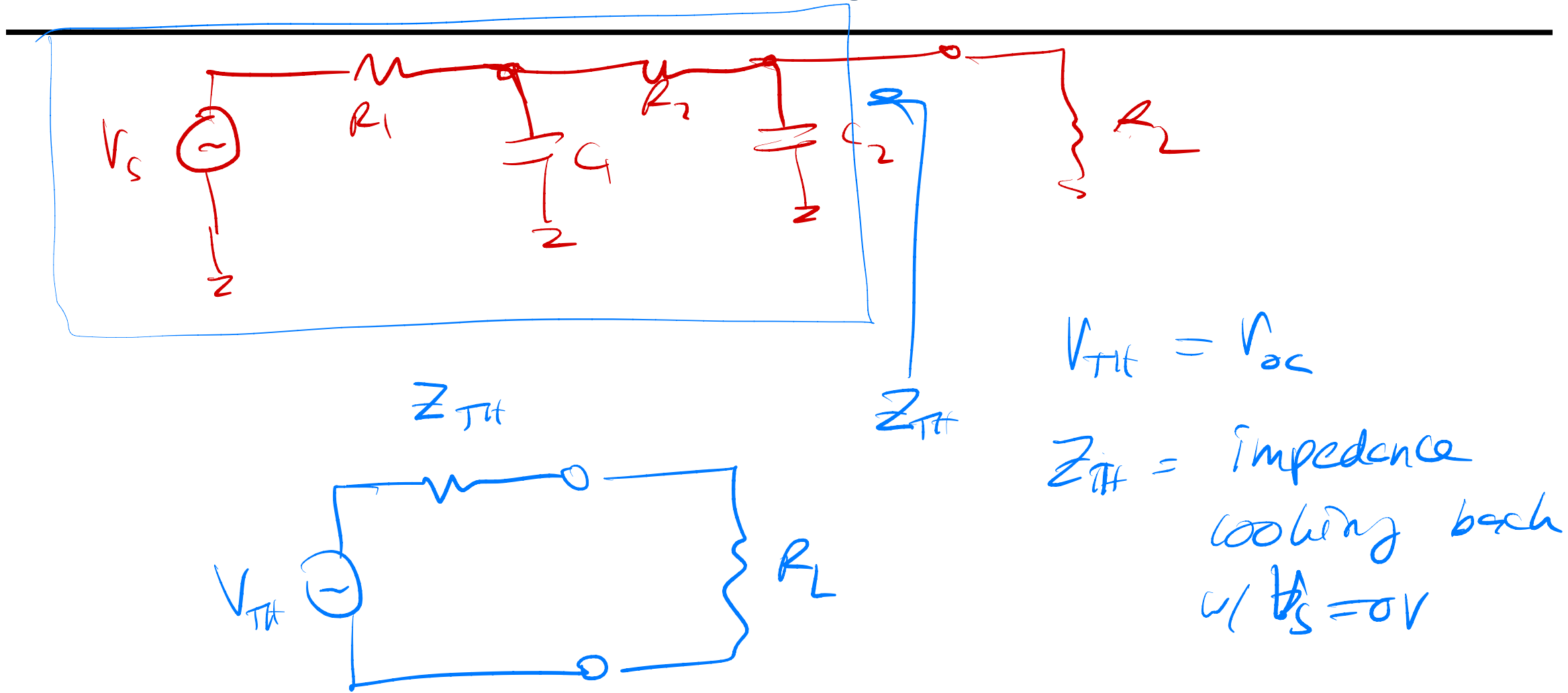


$$V_{TH} = V_{oc}$$

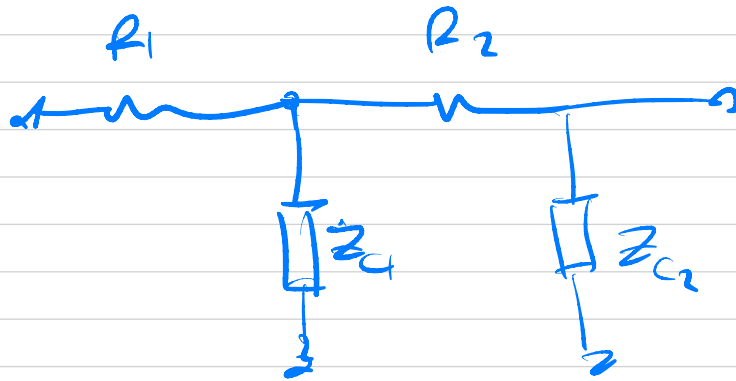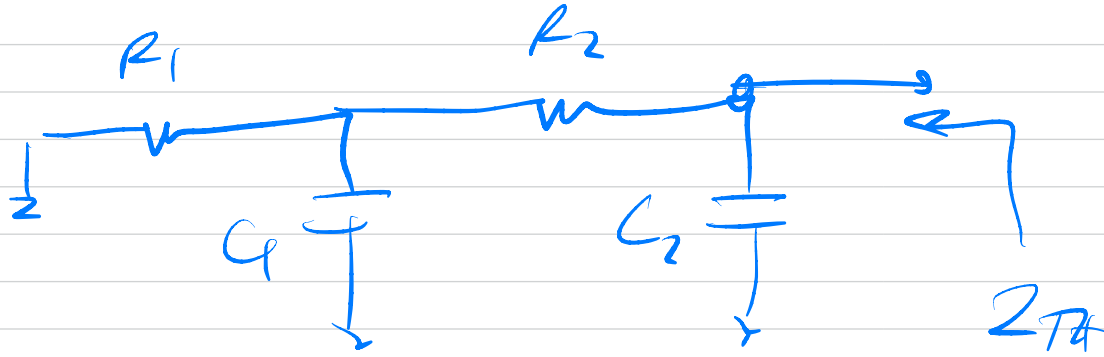Z_{TH} = Impedance
looking back
w/ $v_s = 0V$


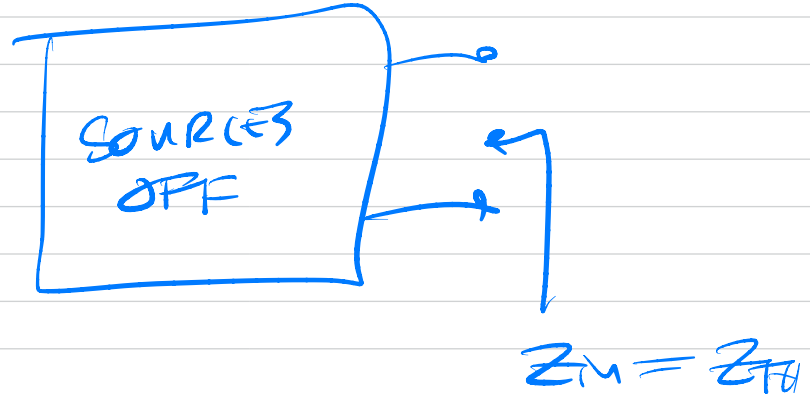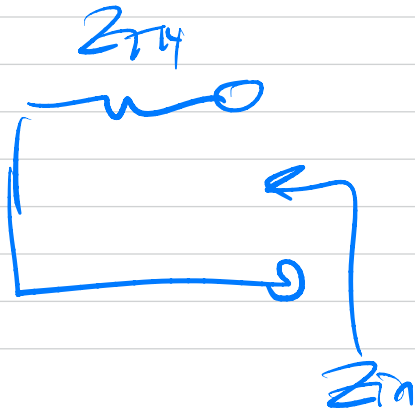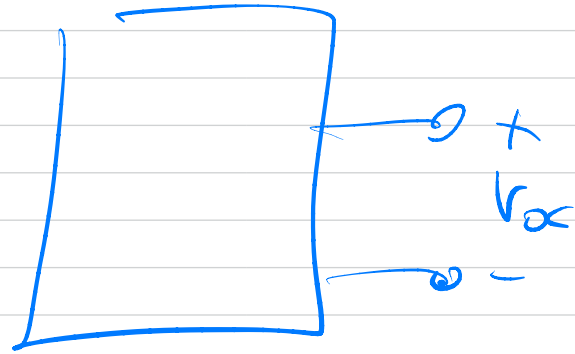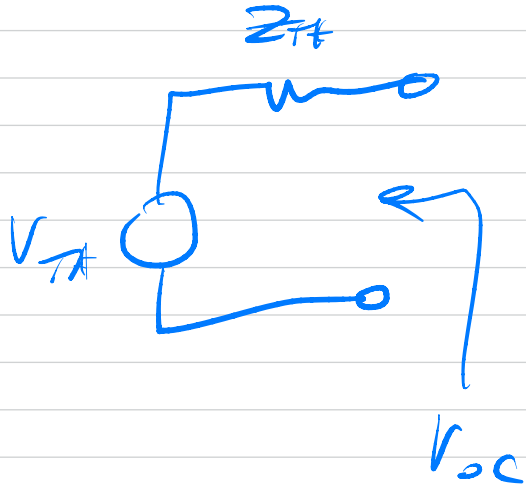
$$Z_{Td} = (R_1 \parallel Z_{c1} + R_2) \parallel Z_{c2}$$



$$Z_{in} = (R_1 \parallel Z_{C1} + R_2) \parallel Z_{C2}$$

$$(R_1 \parallel \frac{1}{j\omega C_1} + R_2) \parallel \frac{1}{j\omega C_2}$$

$$= \frac{R_1}{1 + j\omega R_1 C_1} + \frac{R_2 (1 + j\omega R_1 C_1)}{1 + j\omega R_1 C_1} \cdot \frac{1}{j\omega C_2}$$

$$\frac{R_1}{1 + j\omega R_1 C_1} + \frac{R_2 (1 + j\omega R_1 C_1)}{1 + j\omega R_1 C_1} + \frac{1}{j\omega C_2}$$

$$= \frac{R_1 + R_2 (1 + j\omega R_1 C_1)}{(R_1 + R_2 (1 + j\omega R_1 C_1)) j\omega C_2 + 1 + j\omega R_1 C_1}$$

$$Z_{TH}(j\omega) = \frac{N(j\omega)}{D(j\omega)}$$

$$N(j\omega) = R_1 + R_2 (1 + j\omega C_1 R_1) = b_1 + b_2 j\omega$$

$$D(j\omega) = \underbrace{(R_1 + R_2 (1 + j\omega R_1 C_1))}_{\text{linear}} j\omega C_2 + \underbrace{1 + j\omega R_1 C_1}_{\text{linear}}$$

quadratic


$$= a_1 + a_2 j\omega + a_3 (j\omega)^2$$

Roots of $N(j\omega) = 0$

zeros of Transfer func




Roots of $D(j\omega) = 0$

poles of transfer func

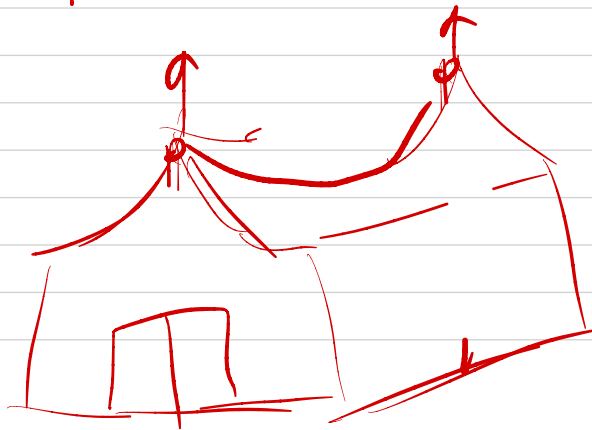

AC Power Flow

- Review passive sign convention

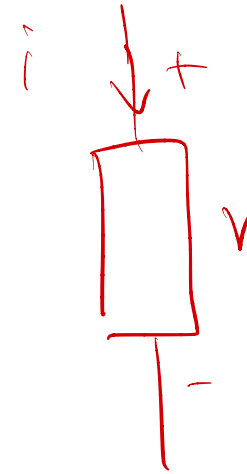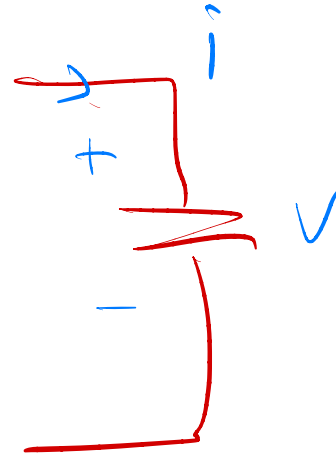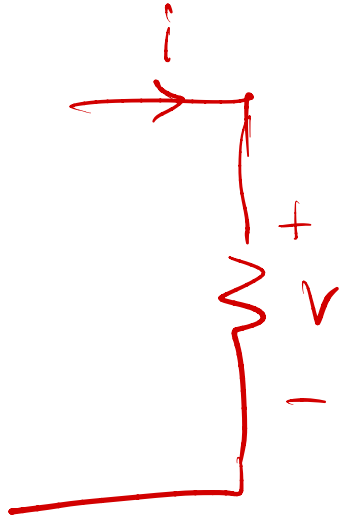

$$p(t) = i(t) \cdot v(t)$$

$$i = C \frac{dv}{dt} \geq 0$$
$$v > 0 \quad \frac{dv}{dt} > 0$$

$$\Rightarrow i(t) v(t) = p(t) \geq 0$$

$$\text{if } \frac{dV}{dt} < 0 \Rightarrow$$


$$P(t) = i(t) v(t) < 0$$

negative

positive

since $\frac{dV}{dt} < 0$

Supplying Energy

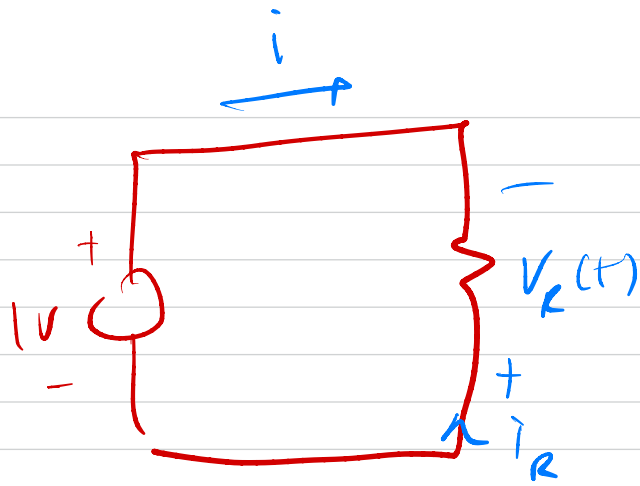


$$P_R(t) = V_R(t) \cdot i_R(t) \geq 0 \Rightarrow \text{dissipating power}$$

$$= (-1V) (-i)$$

$$= 1V \times i$$

Instantaneous Power

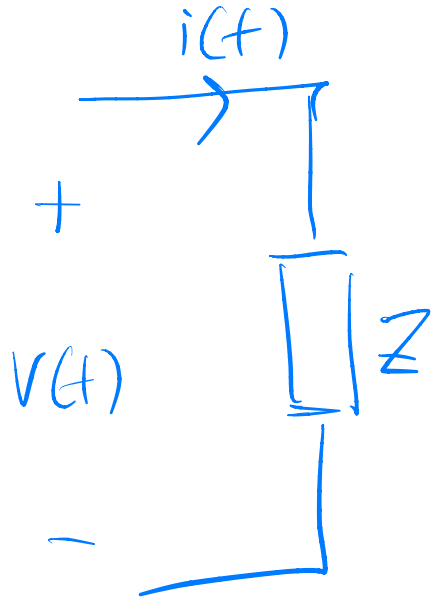

In sinusoidal steady state:

$$v(t) = V_0 \cos \omega t$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$I_0 = V_0 / |Z|$$

$$\phi = -\angle Z$$

$$v(t) = V_0 \cos \omega t$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$\cos(A+B) = \cos A \cos B - \sin A \sin B$$


$$p(t) = v(t) \cdot i(t)$$

$$= V_0 \cos \omega t \cdot I_0 (\cos \omega t \cos \phi - \sin \omega t \sin \phi)$$

$$= \underbrace{V_0 I_0 \cos \phi}_{\text{constant}} \cos^2 \omega t - \underbrace{V_0 I_0 \sin \phi}_{\text{constant}} \cos \omega t \sin \omega t$$

$$\frac{1 + \cos 2\omega t}{2}$$

$$\sin 2\omega t$$

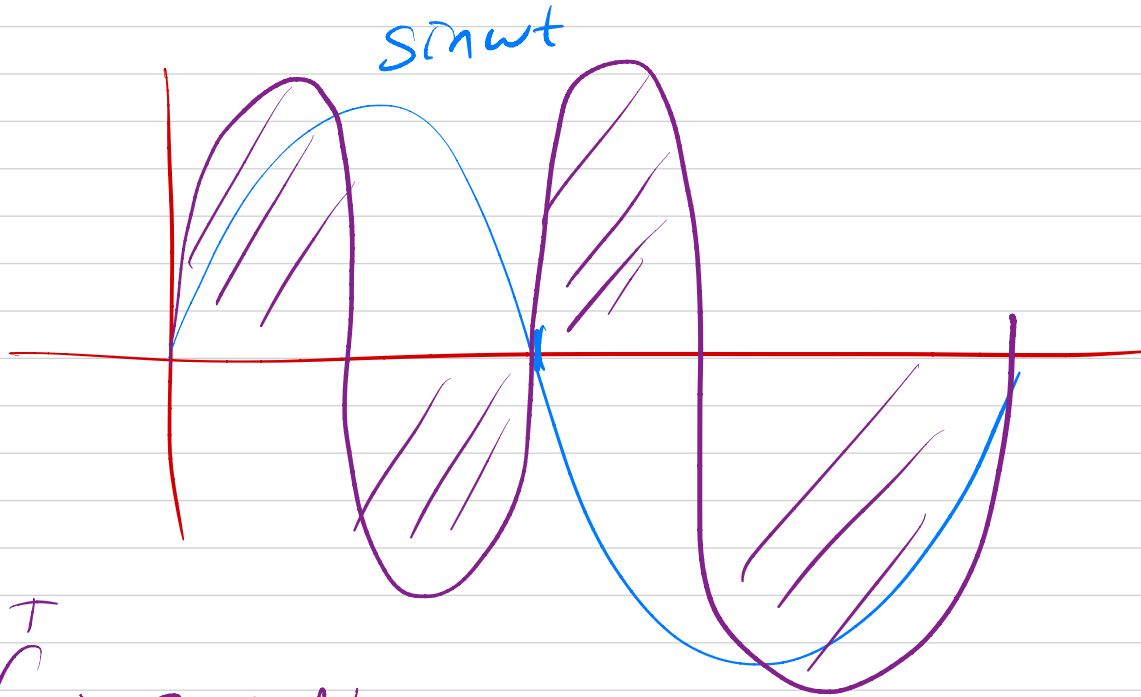

$$\int_0^T \sin 2\omega t \, dt = 0$$

Average Power

$$P_{av} = \frac{1}{T} \int_0^T P(t) dt$$

T : one cycle of $\cos \omega t$


$$\omega = \frac{2\pi}{T}$$

$$P_{av} = \frac{1}{T} \cos \phi \times V_o \times I_o \times \frac{1}{2} T$$

$$= \frac{1}{2} V_o \cdot I_o \cos \phi$$

— Average Power
Dissipated by
"Z"

Average Power Dissipated By R

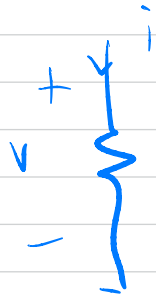

$$P_{av} = \frac{1}{2} V_0 I_0 \cos \phi$$

$\phi \equiv 0$ for resistor

$$P_{av} = \frac{1}{2} V_0 I_0 = \frac{1}{2} I_0 \cdot R \cdot I_0$$

$$= \frac{1}{2} I_0^2 R = I_{rms}^2 R$$

$$I_{rms} \triangleq \frac{I_0}{\sqrt{2}}$$

RMS : ROOT MEAN SQUARED

$$P_{av} = \frac{1}{2} V_0 I_0 \cos \phi$$

$$= V_{rms} \cdot I_{rms} \cdot \cos \phi$$

$$V_{rms} \triangleq \frac{V_0}{\sqrt{2}}$$

$$I_{rms} \triangleq \frac{I_0}{\sqrt{2}}$$

$$p(t) = v(t) i(t)$$

$$= i(t) \cdot R \times i(t) = i^2(t) \cdot R$$

$$P_{av} = \frac{1}{T} \int_T p(t) dt = R \int_T i^2(t) dt = I_{rms}^2 R$$

$$I_{rms} = \sqrt{\int_T i^2(t) dt}$$

(Note: The diagram shows a red arrow pointing from the square root symbol to the letter 'R' below it, and another red arrow pointing from the integral symbol to the letter 'M' below it. The letter 'S' is also present below the integral.)

AC Power in Phasors

$$P = \tilde{V} \cdot \tilde{I}$$

\tilde{V} is a phasor
 \tilde{I} is a phasor

$$\tilde{V} \cdot \tilde{I} \neq \frac{1}{2} V_0 I_0 \cos \phi$$

$$P_{av} = \frac{1}{2} V_0 I_0 \underbrace{\cos(\phi_v - \phi_i)}_{\phi}$$

$$\tilde{P}_{av} \triangleq \frac{1}{2} \tilde{V} \tilde{I}^*$$

$$\operatorname{Re}\{\tilde{P}_{av}\} = P_{av}$$

$$\tilde{P}_{av} = \frac{1}{2} \tilde{V} \tilde{I}^* \quad \tilde{I} = I_0 e^{j\phi_i}$$

$$= \frac{1}{2} \tilde{V} I_0 e^{-j\phi_i}$$

$$= \frac{1}{2} V_0 e^{j\phi_v} \cdot I_0 e^{-j\phi_i}$$

$$= \frac{1}{2} V_0 I_0 e^{j(\phi_v - \phi_i)}$$

$\underbrace{\hspace{10em}}_{\equiv \phi}$

$$\text{Re}\{\tilde{P}_{av}\} = \frac{1}{2} V_0 I_0 \cos \phi \quad \checkmark$$

$$\tilde{P}_{av} = \frac{\tilde{V}^* \tilde{I}}{2} = \frac{e^{-j\phi_v} V_0 I_0 e^{j\phi_i}}{2}$$


$$= \frac{1}{2} V_0 I_0 e^{j(\phi_i - \phi_v)}$$

$$\operatorname{Re}\{\tilde{P}_{av}\} = \frac{1}{2} V_0 I_0 \cos \phi_i - \phi_v$$

$$= \frac{1}{2} V_0 I_0 \cos \underbrace{\phi_v - \phi_i}_{\phi}$$



$$P_{av} = \operatorname{Re}\left\{ \frac{\tilde{V}_0 \tilde{I} + \tilde{I}^* \tilde{V}^*}{2} \right\}$$

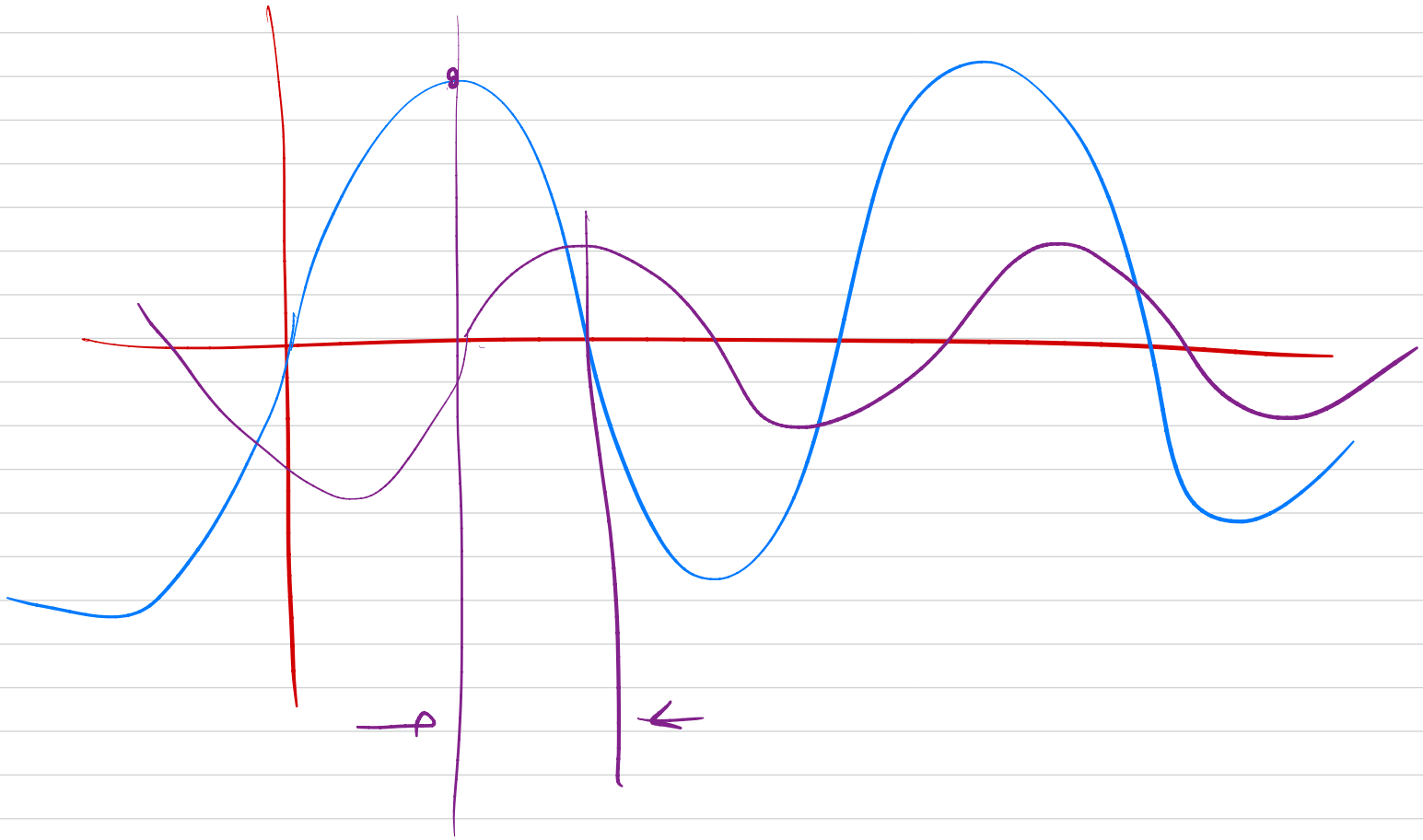


Ex 1

$$\frac{L^+}{L^-}$$


$$V = V_0 \cos \omega t$$

$$\tilde{I} = j\omega C \cdot V$$
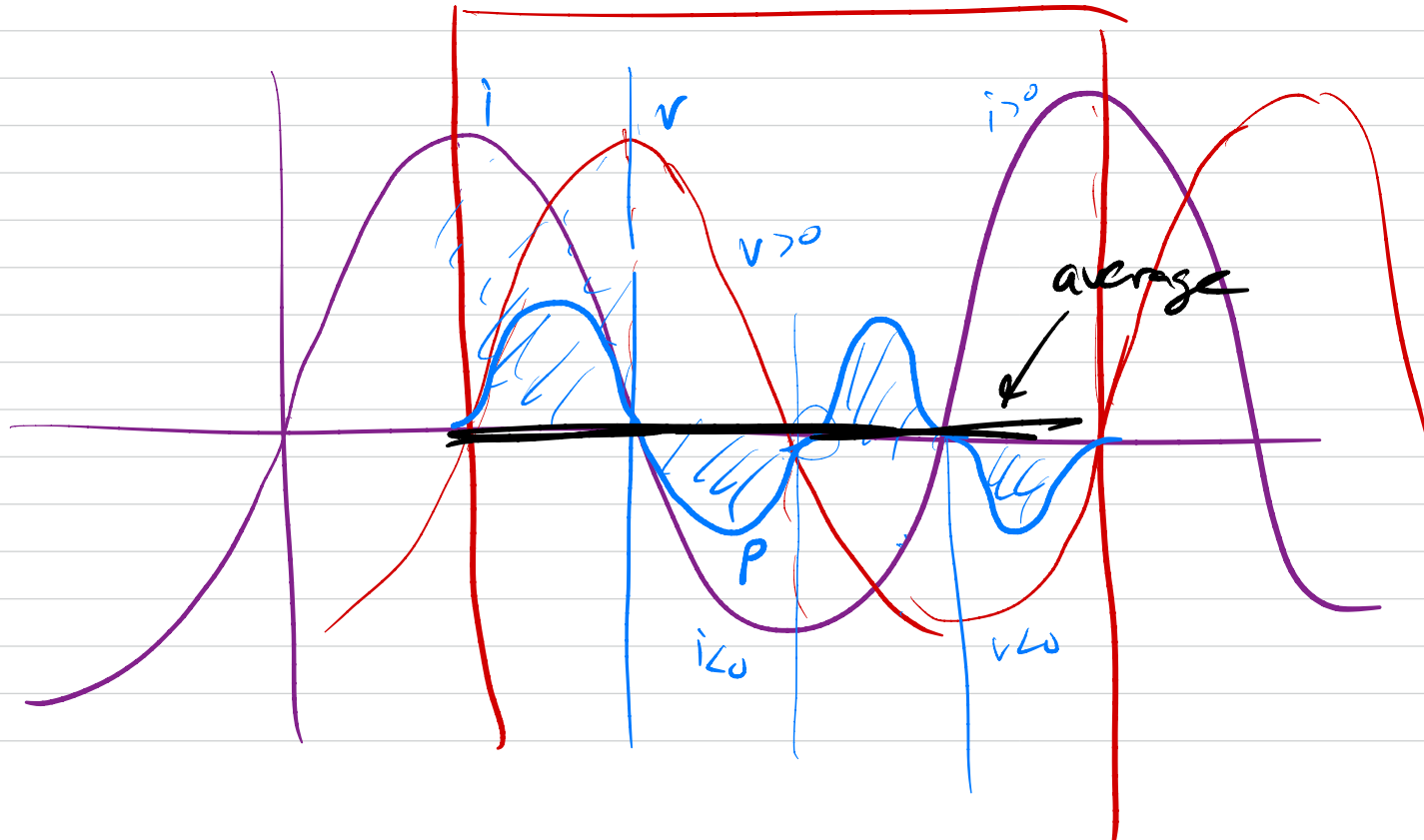
$$I = \omega C V_0 \cos(\omega t + 90^\circ)$$



Alternate Forms

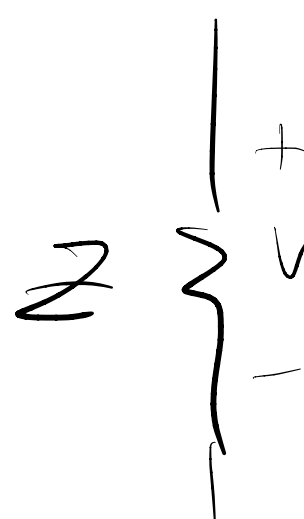

A circuit diagram showing an impedance Z connected to a voltage source V . The voltage source is represented by a vertical line with a '+' sign at the top and a '-' sign at the bottom. A wavy line representing the impedance Z is connected in parallel with the voltage source.

$$P_{av} = \frac{I \cdot V^{*}}{2}$$
$$= \frac{V}{Z} \cdot \frac{V^{*}}{2} = \frac{|V|^2}{2Z}$$
$$\operatorname{Re}(P_{av}) = \operatorname{Re} \left\{ \frac{|V|^2}{2Z} z^{*} \right\}$$
$$= \frac{|V|^2}{2|Z|^2} \operatorname{Re} \{ z \}$$

Inductors/Capacitors Store Energy

- Inductors and capacitors cannot dissipate energy.
- But charging a capacitor requires work, which is stored (not dissipated)
- It seems that we should account for this stored power in AC components

$$p(t) = \underbrace{\frac{1}{2} V_o I_o \cos \phi (1 + \cos 2\omega t)}_{P_{av}} + \underbrace{\left\{ \frac{1}{2} V_o I_o \sin \phi \sin 2\omega t \right\}}_{\text{reactive power}}$$

$\phi = \phi_v - \phi_i$

Reactive Power

$$P_{\text{react}}(t) = \frac{1}{2} V_0 I_0 \sin \phi \sin 2\omega t$$

$$\int_T P_{\text{react}}(t) dt = 0$$



$\pm 90^\circ$

maximize

reactive

power

$\mp 90^\circ$

stores power


when

-90° or

dissipates

power

Maximum Power Transfer Theorem

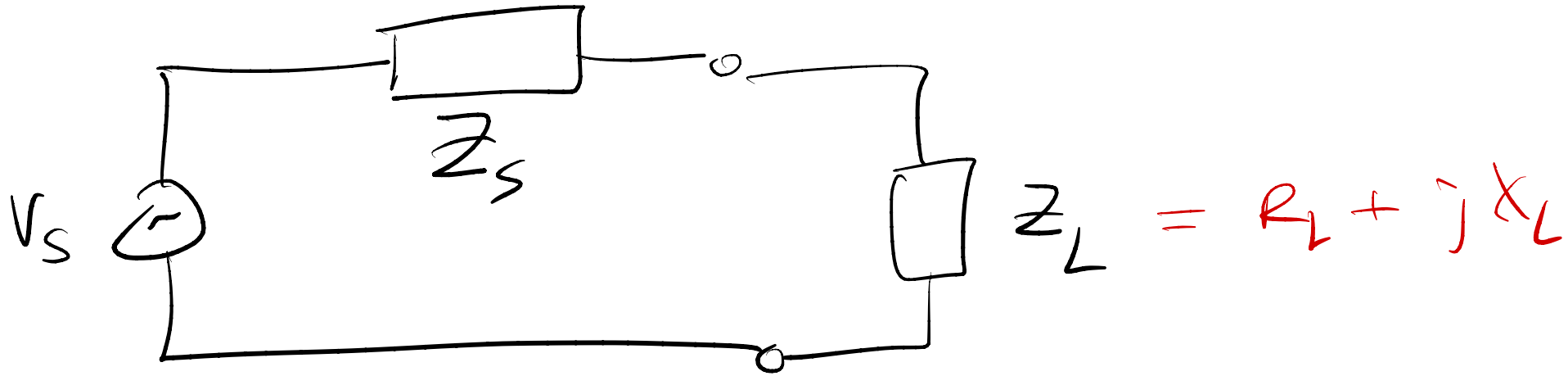

$$P_{av} = \frac{1}{2} \operatorname{Re} \{ V \cdot I^* \}$$



$$\frac{dP_{av}}{dX_L} = 0$$

$$\frac{dP_{av}}{dR_L} = 0$$


\Rightarrow solve

$$R_L = \operatorname{Re}(Z_s)$$
$$X_L = -\operatorname{Im}(Z_s)$$

Applications: Solar Panel

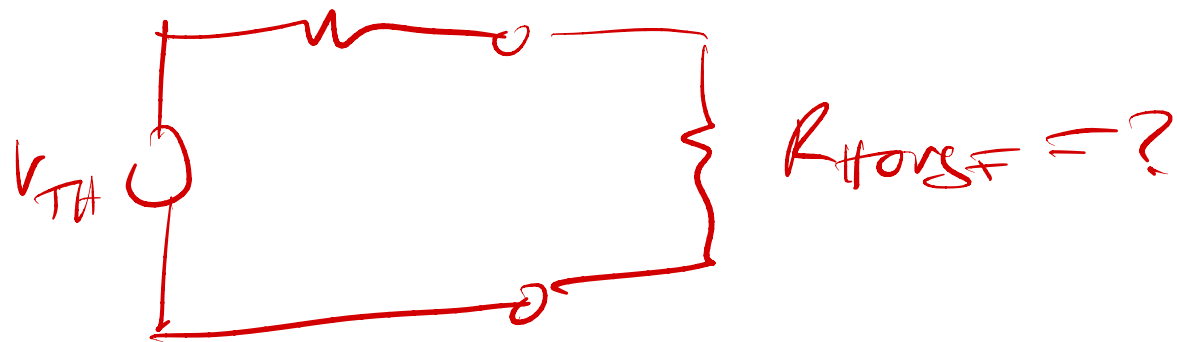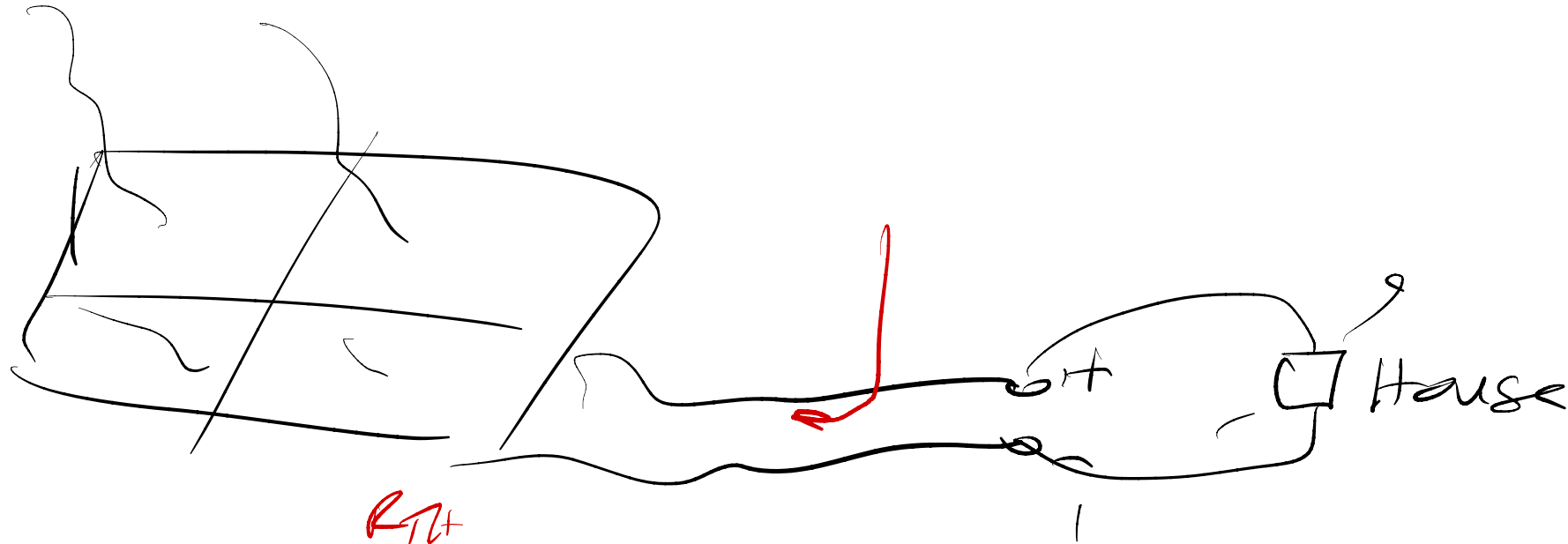
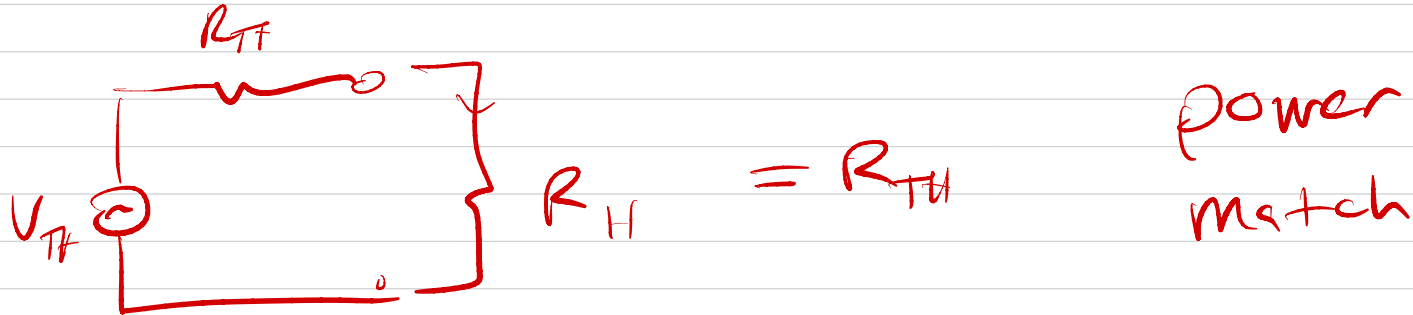
$$P_{\text{house}} = v \cdot i$$
$$= \frac{V \cdot V}{R_H} = i^2 R_H$$



$$\frac{dP_{\text{house}}}{dR} = 0 = \frac{d}{dR} \left(\frac{V_{TH}}{R_{TH} + R_H} \cdot R_H \right)$$

\Rightarrow SOLVE $R_H = R_{TH}$

