



# EECS 16B

## Designing Information Devices and Systems II

Prof. Ali Niknejad and Prof. Kannan Ramchandran

Department of Electrical Engineering and Computer Sciences, UC Berkeley,  
[niknejad@berkeley.edu](mailto:niknejad@berkeley.edu)

# **Module 10: AC Networks and AC Power**

EECS 16B


# Summary

---

- AC Circuit Network Theorems
  - Voltage / current dividers
  - Source superposition
  - Thevenin/Norton
- AC Power
  - Average Power
  - Reactive Power
- Maximum power transfer theorem
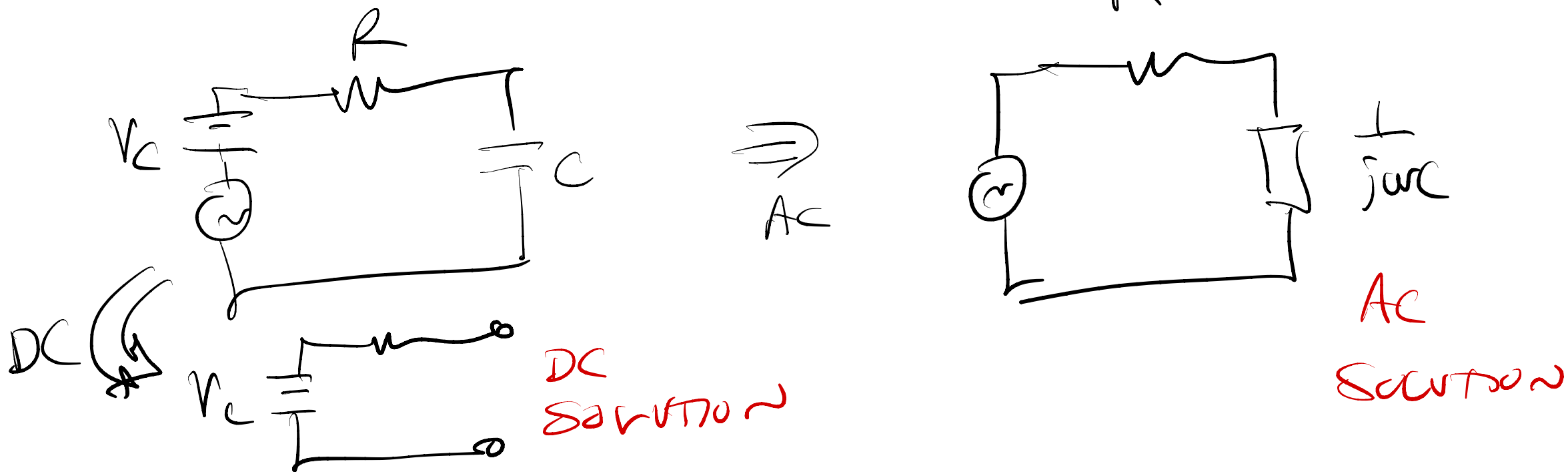
# Review AC Circuits


- Concept of Impedance
- AC equivalent circuit
- Concept of a “system” with AC circuits





# AC Voltage Divider

current

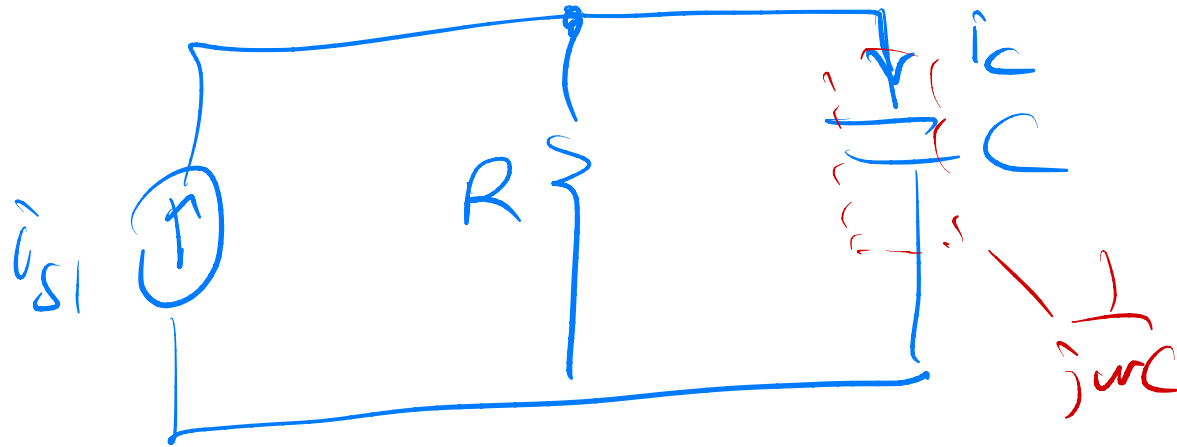

$$\hat{i}_C = \frac{Y_C}{Y_C + G} \hat{i}_{s1}$$

$$G = \frac{1}{R}$$

$$\hat{i}_C = \frac{j\omega C}{j\omega C + G} \hat{i}_{s1} = \frac{j\omega C}{G + j\omega C} \hat{i}_{s1}$$

$$H(j\omega) = \frac{\hat{i}_C}{\hat{i}_{s1}} = \frac{j\omega RC}{1 + j\omega RC} \hat{i}_{s1}$$

Reminder




$$\frac{i_2}{i_s} = \frac{G_2}{G_1 + G_2}$$

# Serinity Check

o Check units


A/A

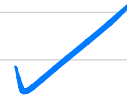

o DC solution

$\omega = 0$


$$H(j\omega) \Big|_{\omega=0} = \frac{j\omega RC}{1 + j\omega RC} \Big|_{\omega=0} = 0$$

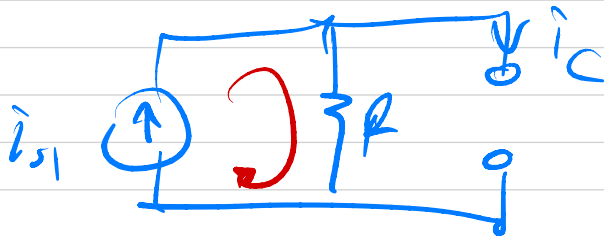

○  $\omega \rightarrow \infty$  VERY HIGH FREQ

$\frac{1}{\omega C} \rightarrow$  SHORTS

$\omega L \rightarrow$  OPENS

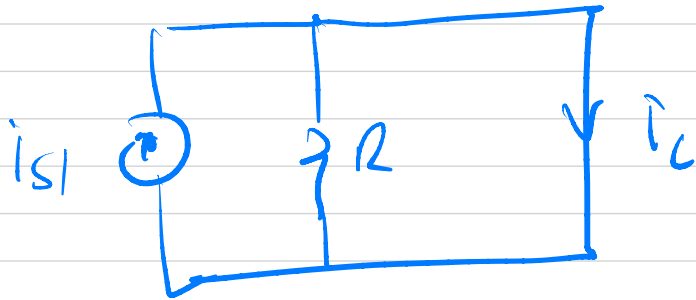

$$H(\omega) \Big|_{\omega \rightarrow \infty} = 1 \quad \checkmark$$

$$H(\omega) \Big|_{\omega=0} = \frac{j\omega RC}{1 + j\omega RC} \Big|_{\omega=0} = 1$$

# AC Current Divider

---

# AC Source Superposition




$$H_1 = \frac{j\omega RC}{1 + j\omega RC}$$

$$\frac{i_c}{i_{s2}} = 0$$

$$H_1 = 0$$



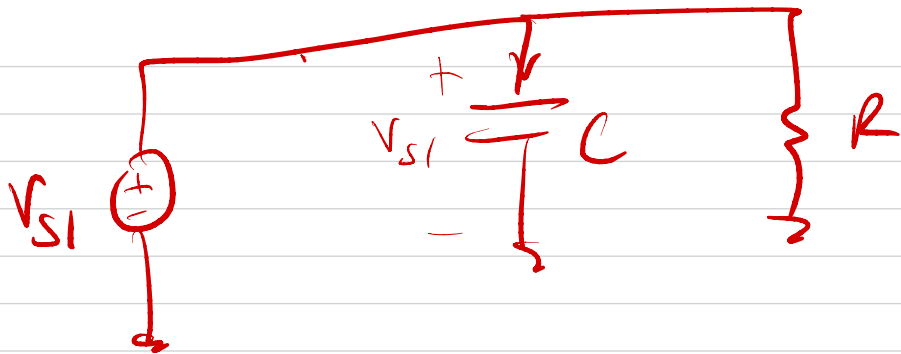




$$\hat{i}_C = \frac{V_{s1}}{1/j\omega C} = j\omega C V_{s1}$$

$$\frac{\hat{i}_C}{V_{s1}} = j\omega C$$





$\left\{ \begin{array}{l} \text{TURN OFF} \\ \text{OFF} \end{array} \right\} \left\{ \begin{array}{l} V_s \rightarrow \text{SHORT} \\ I_s \rightarrow \text{OPEN} \end{array} \right.$

# AC Thevenin/Norton

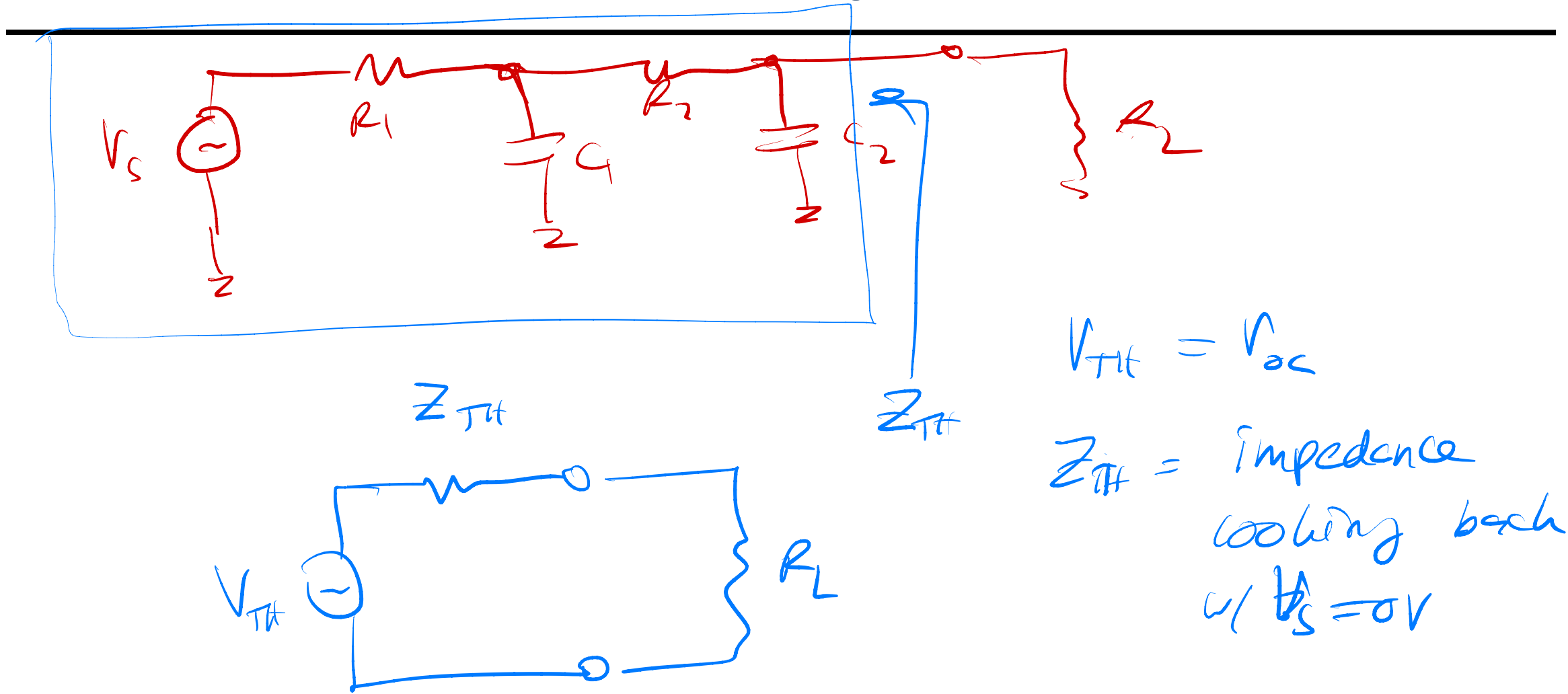

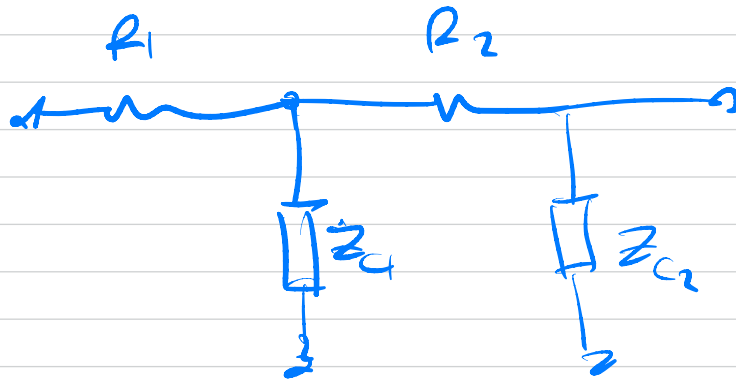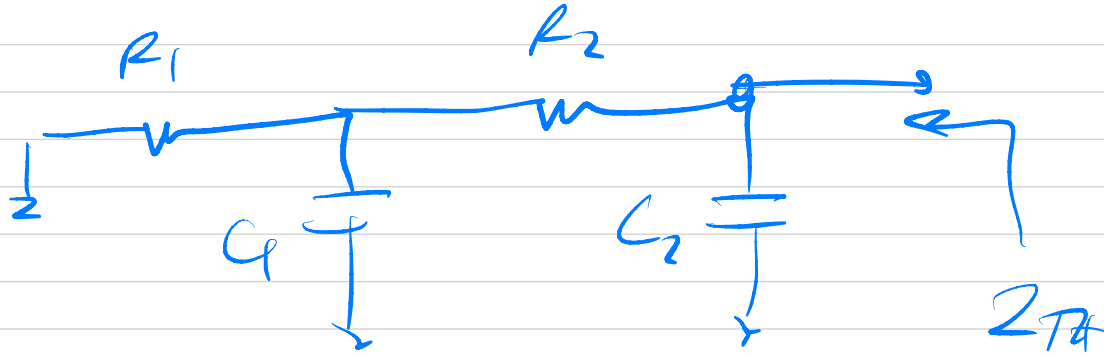
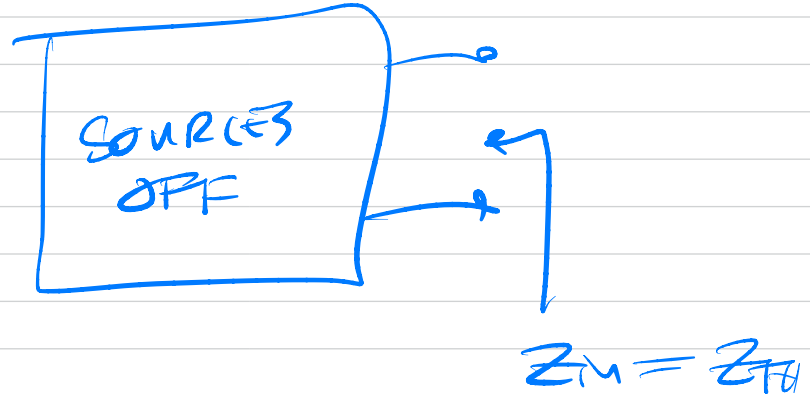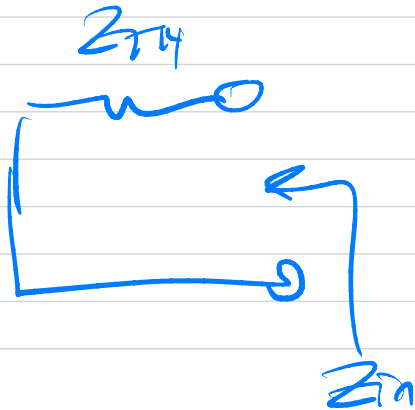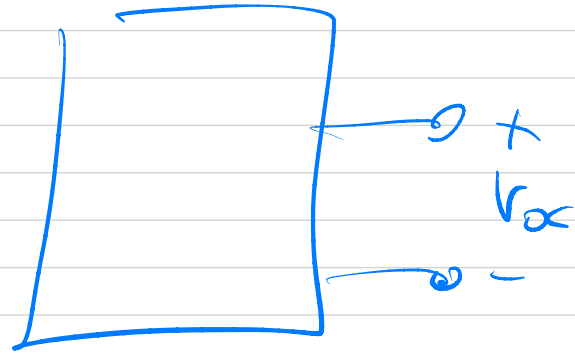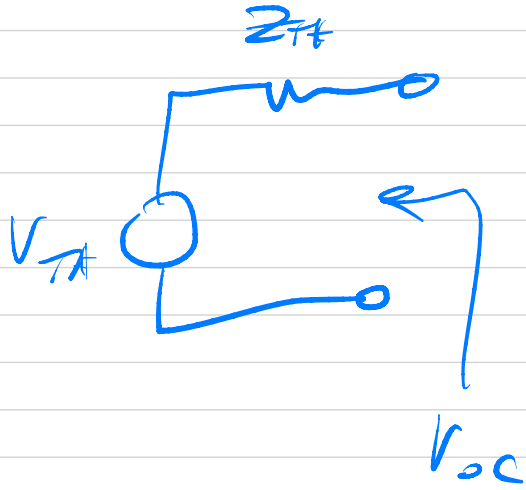
$$Z_{Td} = (R_1 \parallel Z_{c1} + R_2) \parallel Z_{c2}$$



$$Z_{in} = (R_1 \parallel Z_{C1} + R_2) \parallel Z_{C2}$$

$$(R_1 \parallel \frac{1}{j\omega C_1} + R_2) \parallel \frac{1}{j\omega C_2}$$

$$= \frac{R_1}{1 + j\omega R_1 C_1} + \frac{R_2 (1 + j\omega R_1 C_1)}{1 + j\omega R_1 C_1} \cdot \frac{1}{j\omega C_2}$$

$$\frac{R_1}{1 + j\omega R_1 C_1} + \frac{R_2 (1 + j\omega R_1 C_1)}{1 + j\omega R_1 C_1} + \frac{1}{j\omega C_2}$$

$$= \frac{R_1 + R_2 (1 + j\omega R_1 C_1)}{(R_1 + R_2 (1 + j\omega R_1 C_1)) j\omega C_2 + 1 + j\omega R_1 C_1}$$

$$Z_{TH}(j\omega) = \frac{N(j\omega)}{D(j\omega)}$$

$$N(j\omega) = R_1 + R_2 (1 + j\omega C_1 R_1) = b_1 + b_2 j\omega$$

$$D(j\omega) = \underbrace{(R_1 + R_2 (1 + j\omega R_1 C_1))}_{\text{quadratic}} j\omega C_2 + \underbrace{1 + j\omega R_1 C_1}_{\text{linear}}$$

↑  
linear

$$= a_1 + a_2 j\omega + a_3 (j\omega)^2$$




Roots of  $N(j\omega) = 0$

zeros of Transfer func




Roots of  $D(j\omega) = 0$

poles of transfer func

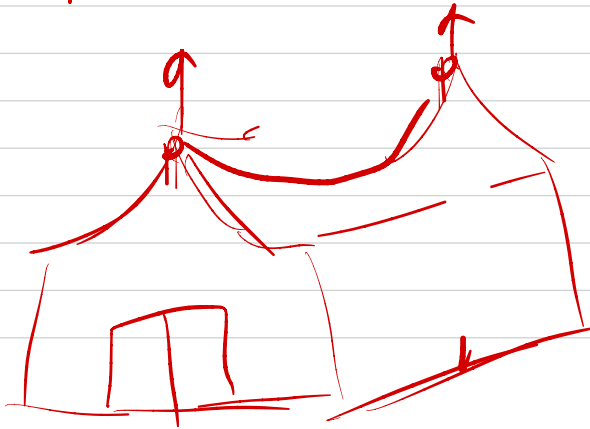

# AC Power Flow

- Review passive sign convention

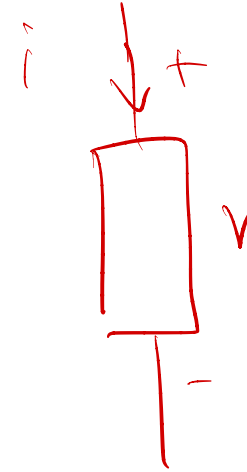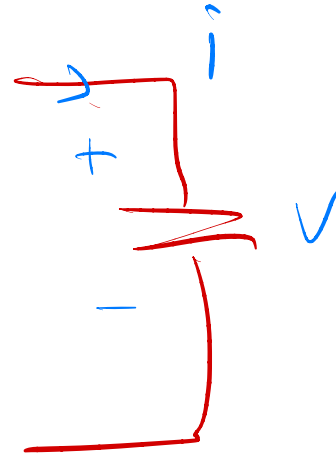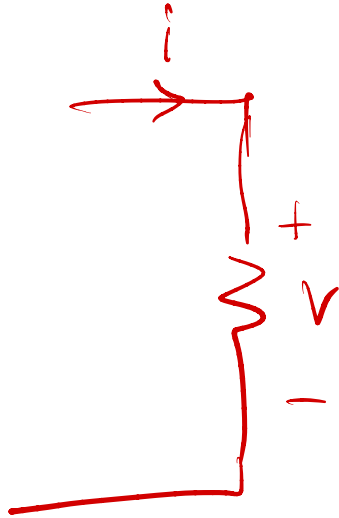

$$p(t) = i(t) \cdot v(t)$$

$$i = C \frac{dv}{dt} \geq 0$$
$$v > 0 \quad \frac{dv}{dt} > 0$$

$$\Rightarrow i(t) v(t) = p(t) \geq 0$$

$$\text{if } \frac{dU}{dt} < 0 \Rightarrow$$


$$P(t) = i(t) v(t) < 0$$

negative

positive

since  $\frac{dU}{dt} < 0$

Supplying Energy

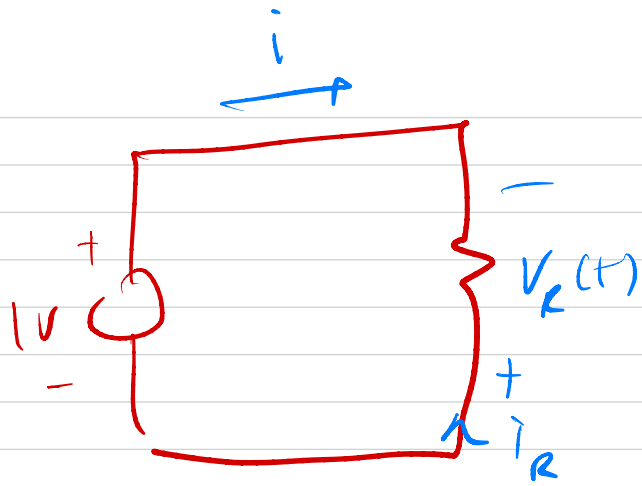


$$P_R(t) = V_R(t) \cdot i_R(t) \geq 0 \Rightarrow \text{dissipating power}$$

$$= (-1V) (-i)$$

$$= 1V \times i$$

# Instantaneous Power

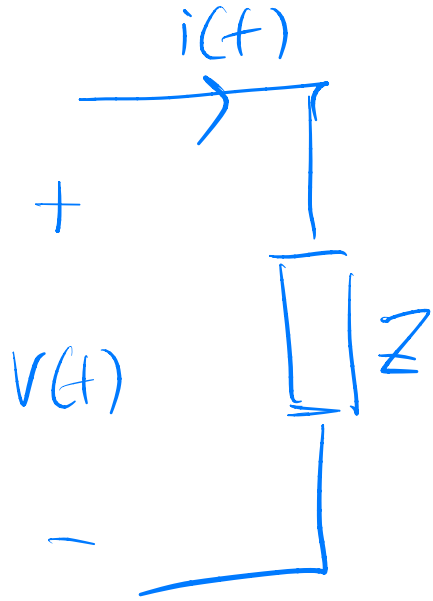

In sinusoidal steady state:

$$v(t) = V_0 \cos \omega t$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$I_0 = V_0 / |Z|$$

$$\phi = -\angle Z$$

$$v(t) = V_0 \cos \omega t$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$\cos(A+B) = \cos A \cos B - \sin A \sin B$$

$$p(t) = v(t) \cdot i(t)$$


$$= V_0 \cos \omega t \cdot I_0 (\cos \omega t \cos \phi - \sin \omega t \sin \phi)$$

$$= \underbrace{V_0 I_0 \cos \phi}_{\text{constant}} \cos^2 \omega t - \underbrace{V_0 I_0 \sin \phi}_{\text{constant}} \cos \omega t \sin \omega t$$

$$\frac{1 + \cos 2\omega t}{2}$$

$$\sin 2\omega t$$



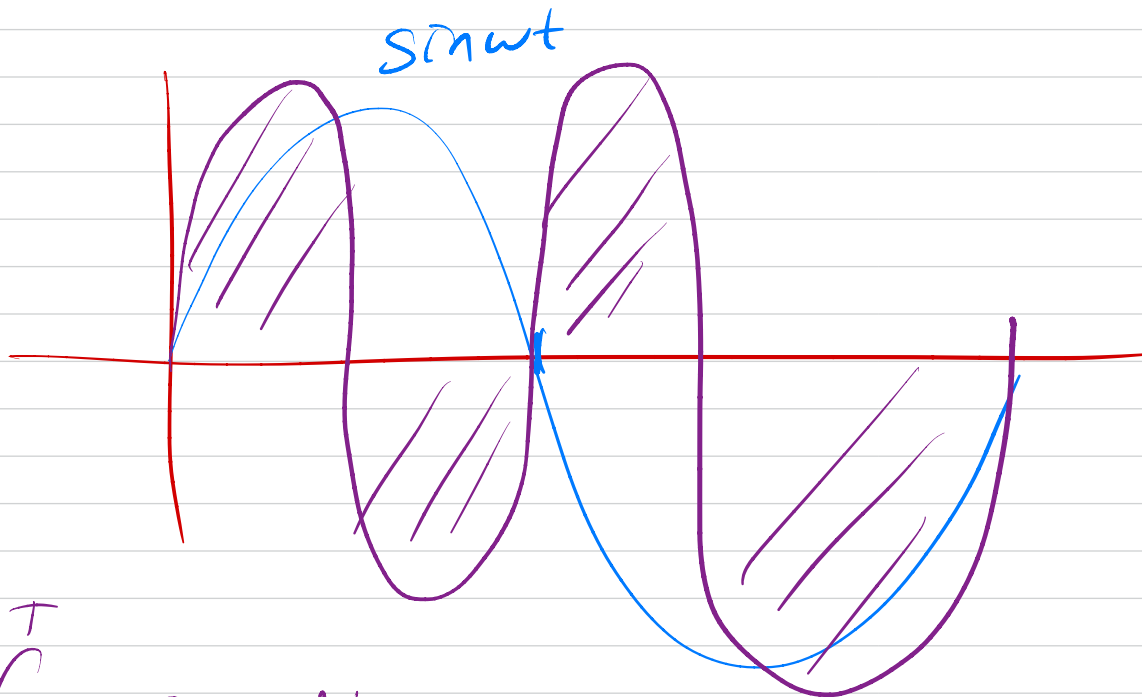

$$\int_0^T \sin 2\omega t \, dt = 0$$

# Average Power

$$P_{av} = \frac{1}{T} \int_0^T P(t) dt$$

$T$ : one cycle of  $\cos \omega t$


$$\omega = \frac{2\pi}{T}$$

$$P_{av} = \frac{1}{T} \cos \phi \times V_o \times I_o \times \frac{1}{2} T$$

$$= \frac{1}{2} V_o \cdot I_o \cos \phi$$

— Average Power  
Dissipated by  
"Z"

# Average Power Dissipated By R

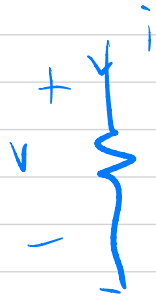

$$P_{av} = \frac{1}{2} V_0 I_0 \cos \phi$$

$$\phi \equiv 0 \text{ for resistor}$$

$$P_{av} = \frac{1}{2} V_0 I_0 = \frac{1}{2} I_0 \cdot R \cdot I_0$$

$$= \frac{1}{2} I_0^2 R = I_{rms}^2 R$$

$$I_{rms} \triangleq \frac{I_0}{\sqrt{2}}$$

RMS : ROOT MEAN SQUARED

$$P_{av} = \frac{1}{2} V_0 I_0 \cos \phi$$

$$= V_{rms} \cdot I_{rms} \cdot \cos \phi$$

$$V_{rms} \triangleq \frac{V_0}{\sqrt{2}}$$

$$I_{rms} \triangleq \frac{I_0}{\sqrt{2}}$$

$$p(t) = v(t) i(t)$$

$$= i(t) \cdot R \times i(t) = i^2(t) \cdot R$$

$$P_{av} = \frac{1}{T} \int_T p(t) dt = R \int_T i^2(t) dt = I_{rms}^2 R$$

$$I_{rms} = \sqrt{\int_T i^2(t) dt}$$

*(Note: The diagram includes red arrows pointing from the labels R, M, and S to the corresponding parts of the equation: R to the square root symbol, M to the integral symbol, and S to the variable i.)*

# AC Power in Phasors

$$P = \tilde{V} \cdot \tilde{I}$$

$\tilde{V}$  is a phasor  
 $\tilde{I}$  is a phasor

$$\tilde{V} \cdot \tilde{I} \neq \frac{1}{2} V_0 I_0 \cos \phi$$

$$P_{av} = \frac{1}{2} V_0 I_0 \underbrace{\cos(\phi_v - \phi_i)}_{\phi}$$

$$\tilde{P}_{av} \triangleq \frac{1}{2} \tilde{V} \tilde{I}^*$$

$$\operatorname{Re}\{\tilde{P}_{av}\} = P_{av}$$



$$\tilde{p}_{av} = \frac{1}{2} \tilde{v} \tilde{i}^* \quad \tilde{i} = I_0 e^{j\phi_i}$$

$$= \frac{1}{2} \tilde{v} I_0 e^{-j\phi_i}$$

$$= \frac{1}{2} V_0 e^{j\phi_v} \cdot I_0 e^{-j\phi_i}$$

$$= \frac{1}{2} V_0 I_0 e^{j(\phi_v - \phi_i)}$$

$\underbrace{\hspace{10em}}_{=\phi}$

$$\text{Re}\{\tilde{p}_{av}\} = \frac{1}{2} V_0 I_0 \cos\phi \quad \checkmark$$

$$\tilde{P}_{av} = \frac{\tilde{V}^* \tilde{I}}{2} = \frac{e^{-j\phi_v} V_0 I_0 e^{j\phi_i}}{2}$$


$$= \frac{1}{2} V_0 I_0 e^{j(\phi_i - \phi_v)}$$

$$\operatorname{Re}\{\tilde{P}_{av}\} = \frac{1}{2} V_0 I_0 \cos \phi_i - \phi_v$$

$$= \frac{1}{2} V_0 I_0 \cos \underbrace{\phi_v - \phi_i}_{\phi}$$



$$P_{av} = \operatorname{Re}\left\{ \frac{\tilde{V}_0 \tilde{I} + \tilde{I}^* \tilde{V}^*}{2} \right\}$$

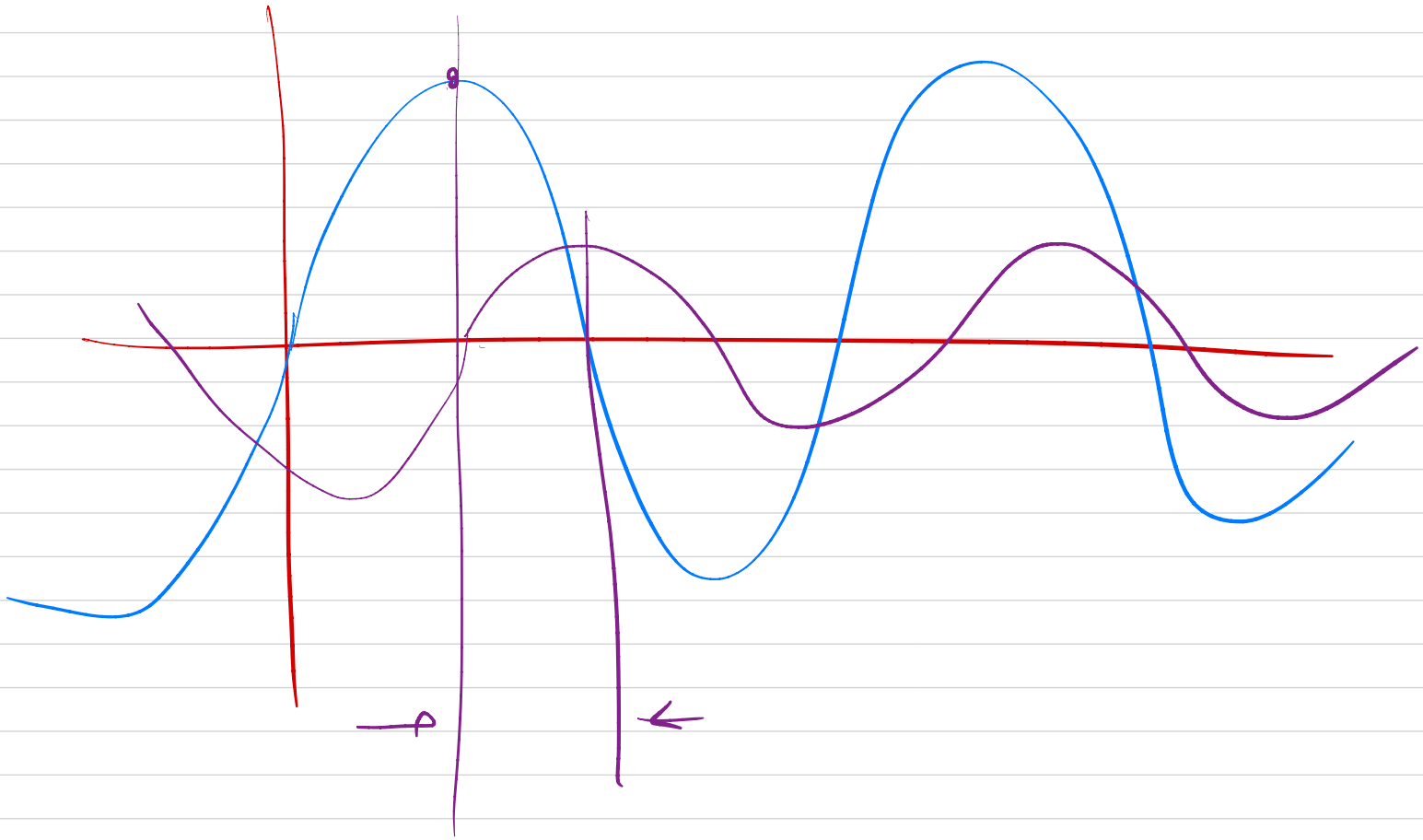


Ex 1

$$\frac{L^+}{L^-}$$


$$V = V_0 \cos \omega t$$

$$\tilde{I} = j\omega C \cdot V$$
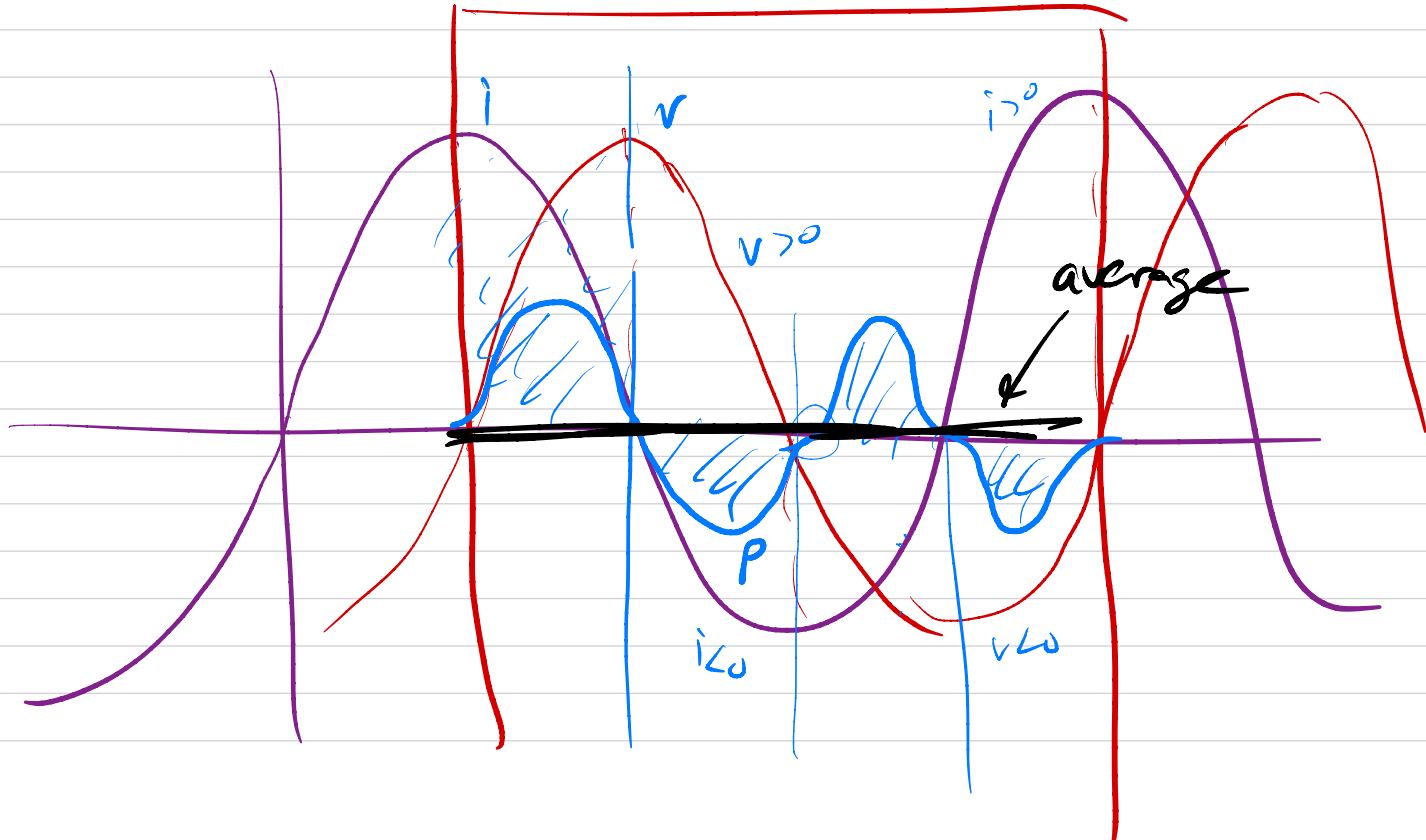
$$I = \omega C V_0 \cos(\omega t + 90^\circ)$$



# Alternate Forms

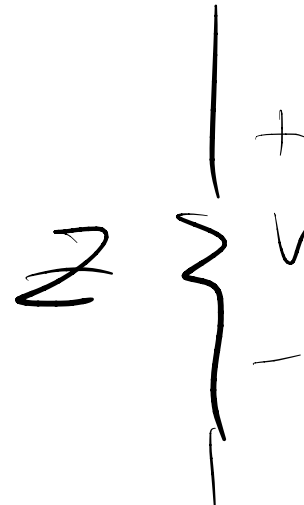

A circuit diagram showing an impedance  $Z$  connected to a voltage source  $V$ . The voltage source is represented by a vertical line with a '+' sign at the top and a '-' sign at the bottom. A wavy line representing the impedance  $Z$  is connected in parallel with the voltage source.

$$P_{av} = \frac{I \cdot V^{*}}{2}$$
$$= \frac{V}{Z} \cdot \frac{V^{*}}{2} = \frac{|V|^2}{2Z}$$
$$\operatorname{Re}(P_{av}) = \operatorname{Re} \left\{ \frac{|V|^2}{2Z} z^{*} \right\}$$
$$= \frac{|V|^2}{2|Z|^2} \operatorname{Re} \{ z \}$$

# Inductors/Capacitors Store Energy

- Inductors and capacitors cannot dissipate energy.
- But charging a capacitor requires work, which is stored (not dissipated)
- It seems that we should account for this stored power in AC components

$$p(t) = \underbrace{\frac{1}{2} V_o I_o \cos \phi (1 + \cos 2\omega t)}_{P_{av}} + \underbrace{\left\{ \frac{1}{2} V_o I_o \sin \phi \sin 2\omega t \right\}}_{\text{reactive power}}$$

$\phi = \phi_v - \phi_i$

# Reactive Power

---

$$P_{\text{react}}(t) = \frac{1}{2} V_0 I_0 \sin \phi \sin 2\omega t$$

$$\int_T P_{\text{react}}(t) dt = 0$$



$\pm 90^\circ$

maximize

reactive

power

$\mp 90^\circ$

stores power

when

$-90^\circ$  or

dissipates

power


# Example: Real Inductor

---

- Concept of quality factor



# Maximum Power Transfer Theorem

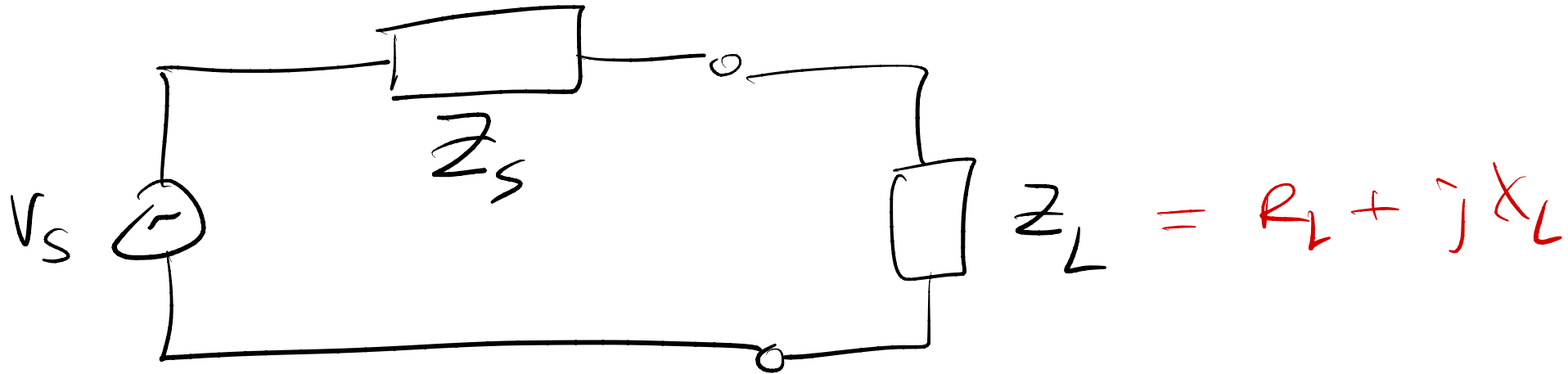

$$P_{av} = \frac{1}{2} \operatorname{Re} \{ V \cdot I^* \}$$



$$\frac{dP_{av}}{dX_L} = 0$$

$$\frac{dP_{av}}{dR_L} = 0$$


$\Rightarrow$  solve

$$R_L = \operatorname{Re}(Z_s)$$
$$X_L = -\operatorname{Im}(Z_s)$$

# Applications: Solar Panel

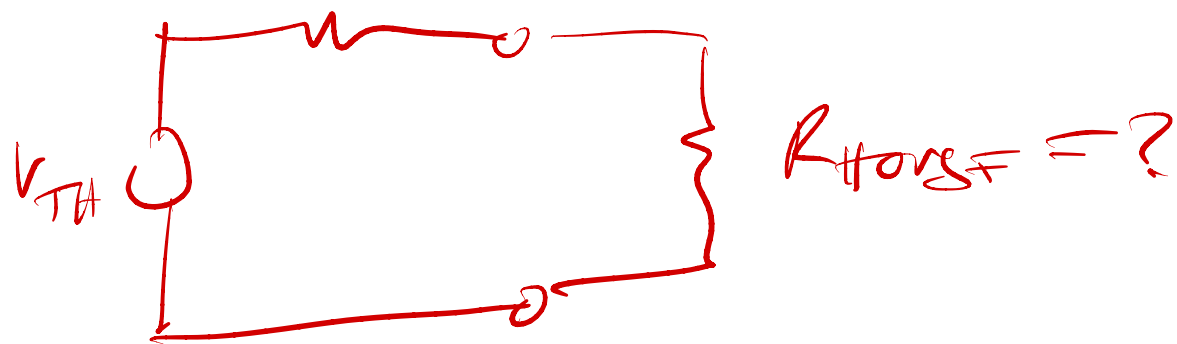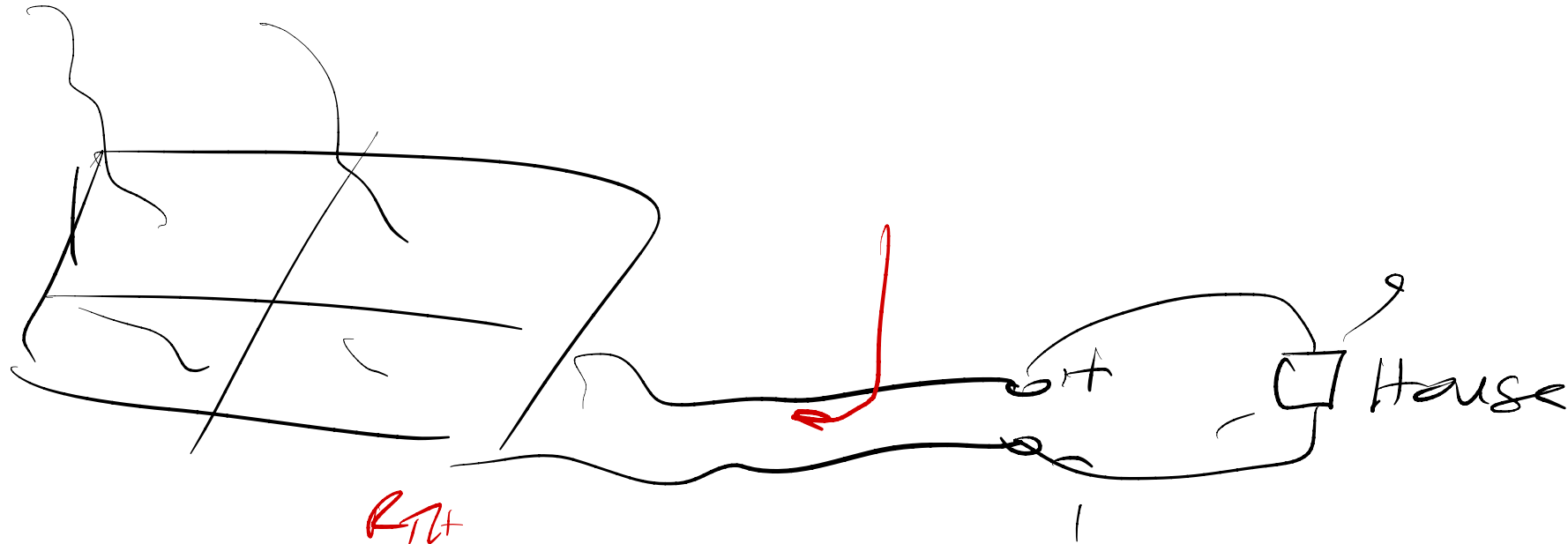

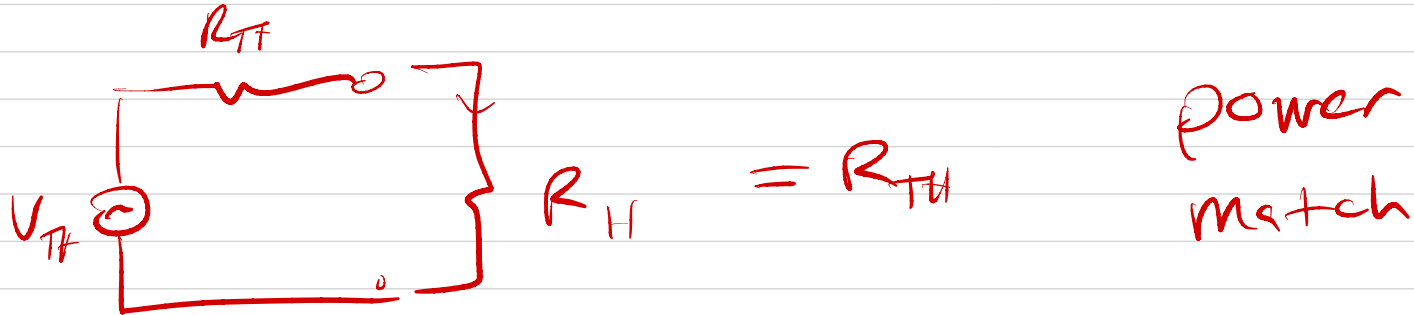
$$P_{\text{house}} = v \cdot i$$
$$= \frac{V \cdot V}{R_H} = i^2 R_H$$



$$\frac{dP_{\text{house}}}{dR} = 0 = \frac{d}{dR} \left( \frac{V_{TH}}{R_{TH} + R_H} \cdot R_H \right)$$

$\Rightarrow$  SOLVE  $R_H = R_{TH}$

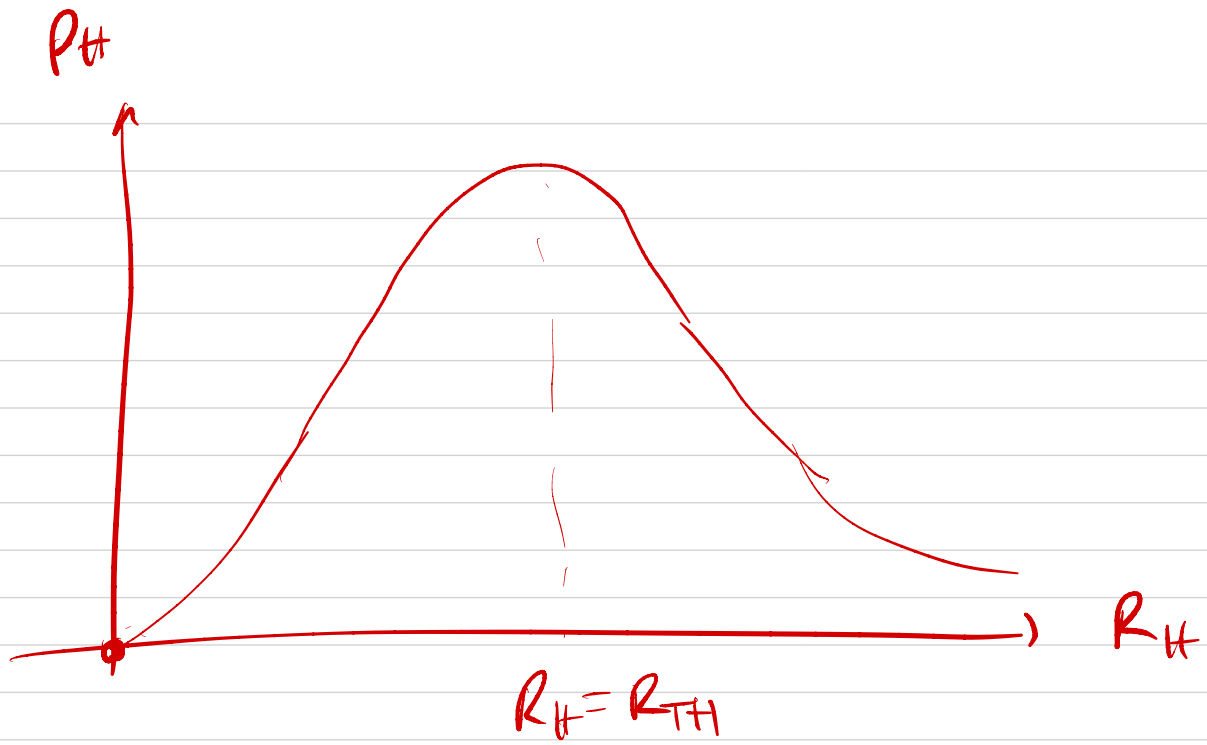


Power Flowing into load

$$P_L = \frac{1}{2} I^2 R_L$$

$$= \frac{1}{2} \left( \frac{V_S}{R_S + R_L} \right)^2 R_L$$

$$= \underbrace{\frac{1}{2} V_S^2}_K \frac{R_L}{(R_S + R_L)^2}$$
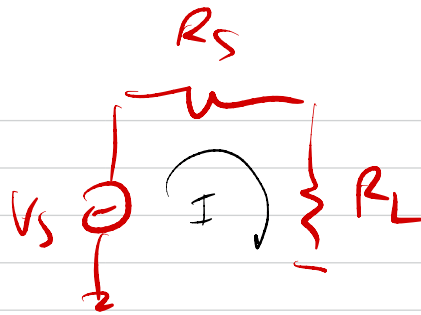
$$\frac{dP_L}{dR_L} = 0 = \frac{\cancel{K}}{(R_S + R_L)^2} + R_L \frac{-2}{(R_S + R_L)^3} \cancel{K}$$




$$\frac{dP_L}{dR_L} = 0 = \frac{k}{(R_S + R_L)^2} + R_L \frac{-2}{(R_S + R_L)^3} k$$

$$1 = \frac{2 R_L}{R_S + R_L}$$


$$R_S + R_L = 2 R_L$$

$$R_S = R_L$$

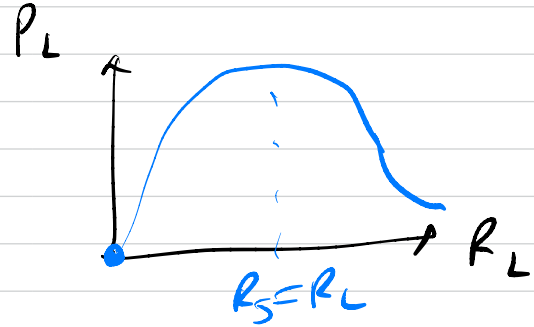

Matched Load  
Resistance!

# AC Impedance

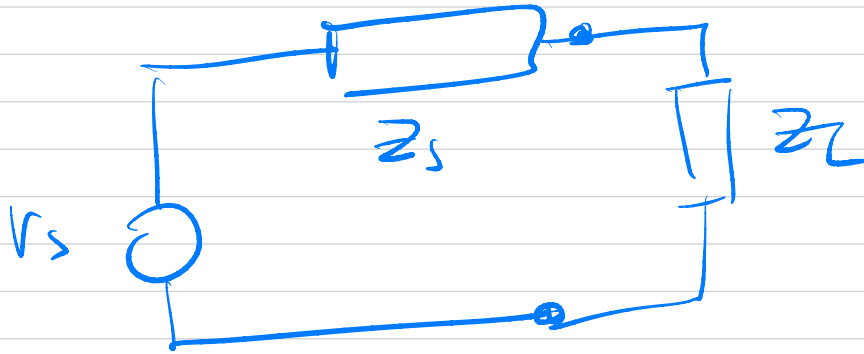


$$Z_s = R_s + jX_s$$

$$Z_L = R_L + jX_L$$

$Z_{Lopt}$  to max power transfer

$$\boxed{R_{Lopt} = R_s}$$

# AC Power

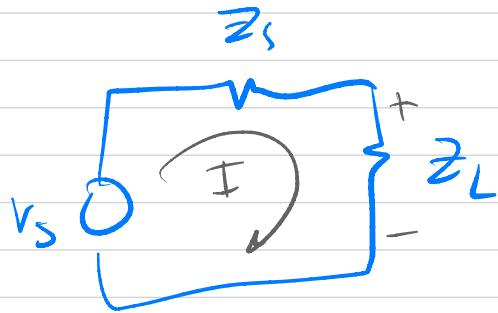

$$I = \frac{v_s}{z_s + z_L}$$

$$V_L = z_L I$$

$$I_L = I$$

$$P_L = \frac{1}{2} \operatorname{Re} \{ V_L I^* \} = \frac{1}{2} \operatorname{Re} \{ I V_L^* \}$$

$$= \frac{1}{2} \operatorname{Re} \left\{ \frac{v_s}{z_s + z_L} \cdot \left( \frac{v_s}{z_s + z_L} \right)^* z_L^* \right\}$$

$$= \frac{1}{2} \frac{|v_s|^2}{|z_s + z_L|^2} \operatorname{Re}(z_L)$$



$$P_L = \frac{1}{2} \frac{|V_s|^2}{|z_s + z_L|^2} \operatorname{Re}(z_L)$$

$\uparrow$   
 $R_L = R_s$

$$\frac{dP_L}{dX_L} = 0$$

$$P_L = \frac{1}{2} \frac{|V_s|^2}{(R_s + R_L)^2 + \underbrace{(X_s + X_L)^2}_{R_L}}$$

$$X_L = -X_s$$

# Conjugate Matched Load

$$Z_L = Z_S^*$$



$$R_L = R_S$$

$$X_L = -X_S$$



Max power  
transfer  
from the  
source to the  
load
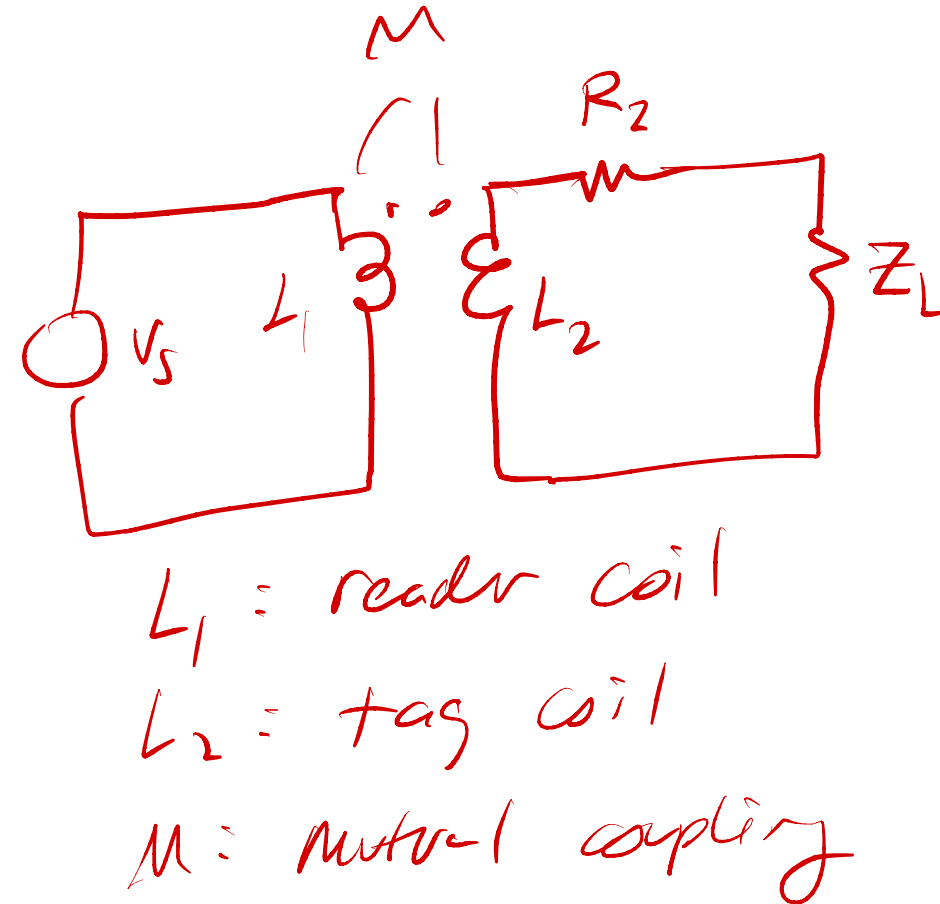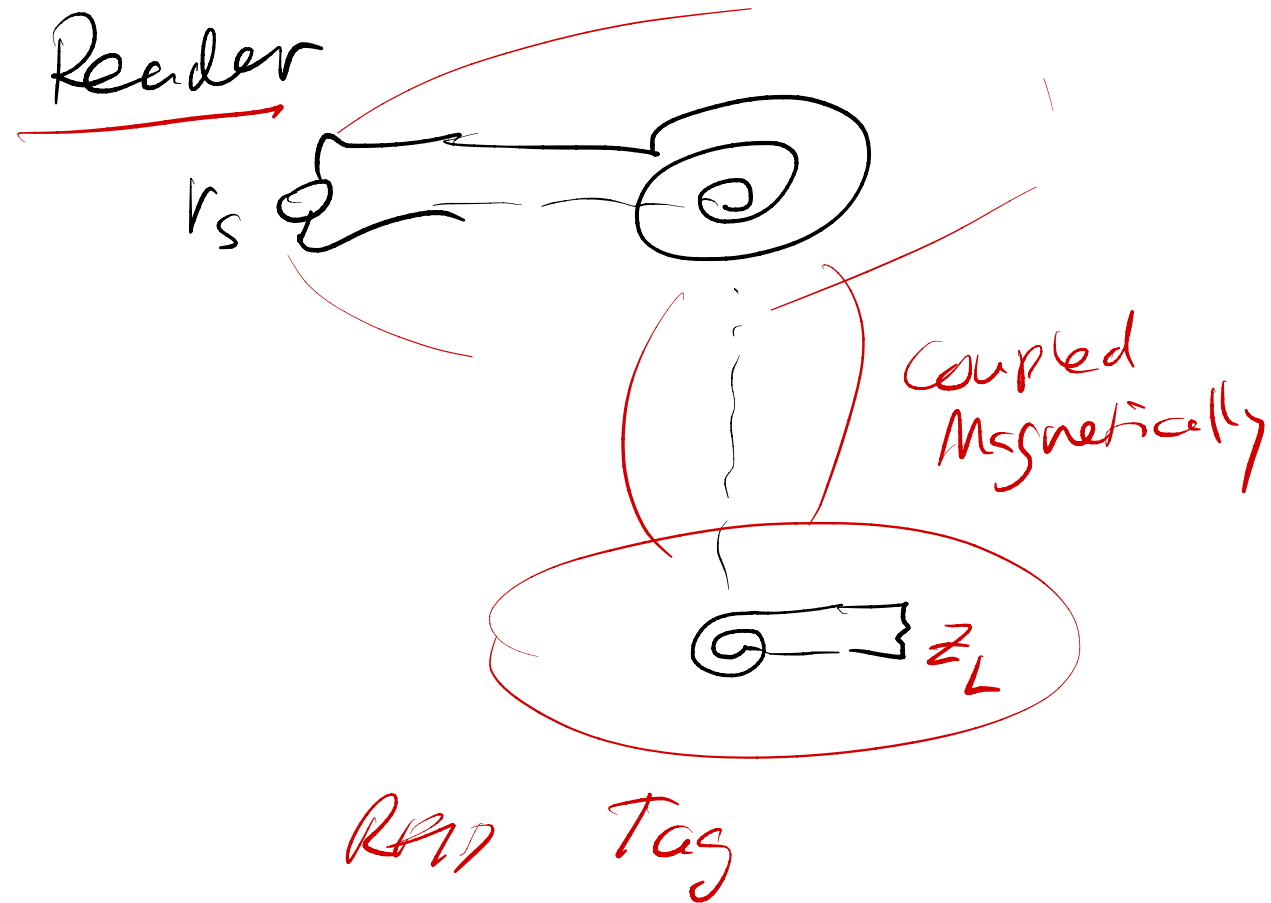
# Application: Power Matching

- Consider an inductive power link (RFID)



# Thvenin Eq

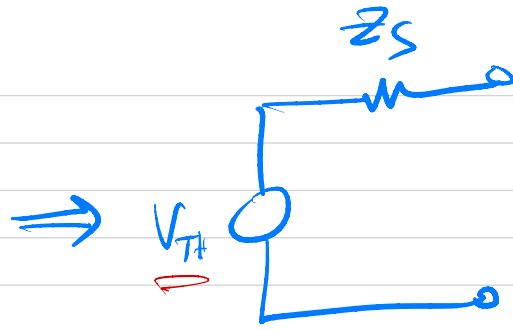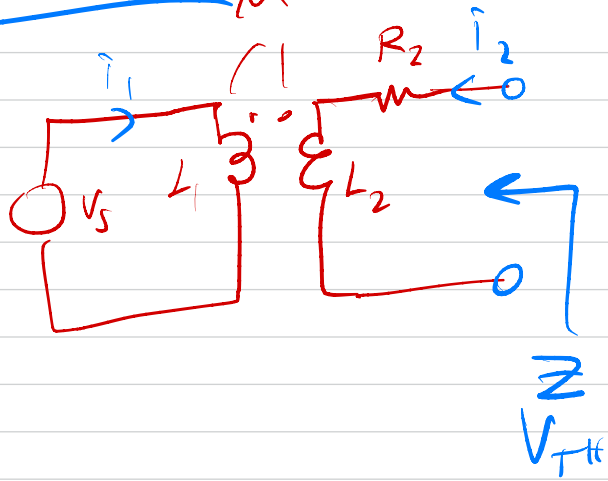

$$V_s = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = j\omega L_1 i_1 + j\omega M i_2$$

$$V_2 = j\omega M i_1 + j\omega L_2 i_2 \quad \left| \quad V_s = j\omega L_1 i_1 \right|_{i_2=0}$$

$$V_{oc} = V_2 \Big|_{i_2=0} = j\omega M i_1 \quad \left| \quad i_1 = \frac{V_s}{j\omega L_1} \right.$$

$$\frac{V_{TH}}$$

$$V_{oc} = j\omega M i_1 = j\omega M \frac{V_s}{j\omega L_1}$$


$$V_{oc} = \frac{M}{L_1} V_s$$

$$M = k \sqrt{L_1 L_2}$$


$$V_{oc} = k \cdot \sqrt{\frac{L_2}{L_1}} V_s$$

$$k \ll 1$$


$$k = 10^{-3}$$

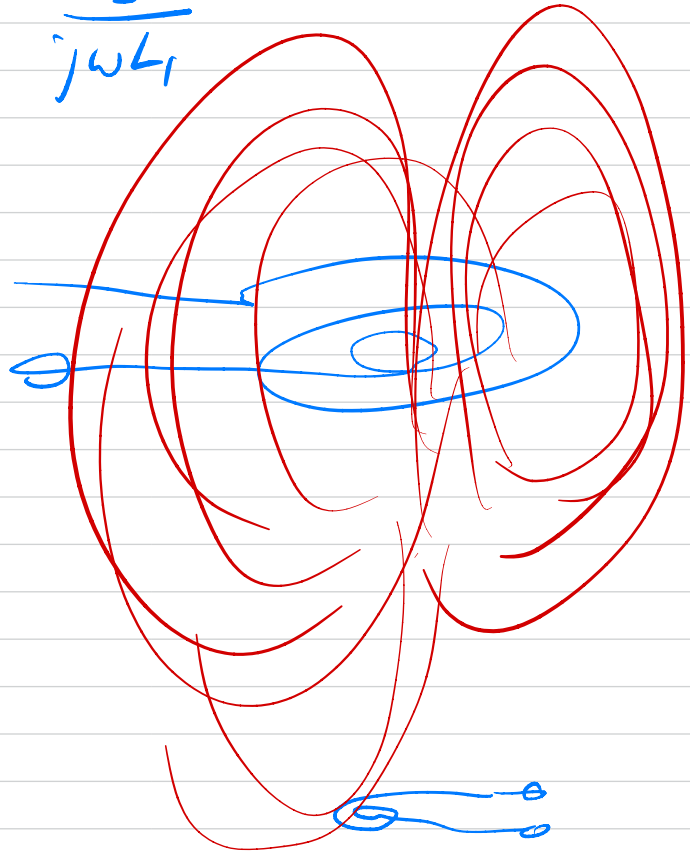

$Z_{TH}$

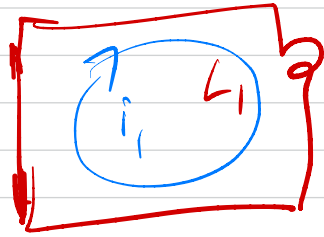



M

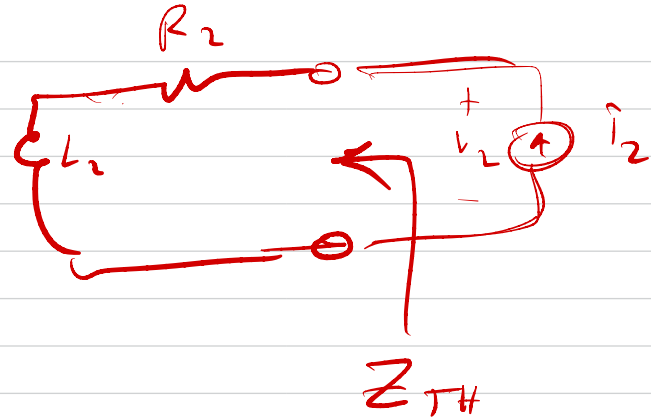

$$Z_{TH} \approx R_2 + j\omega L_2$$

---

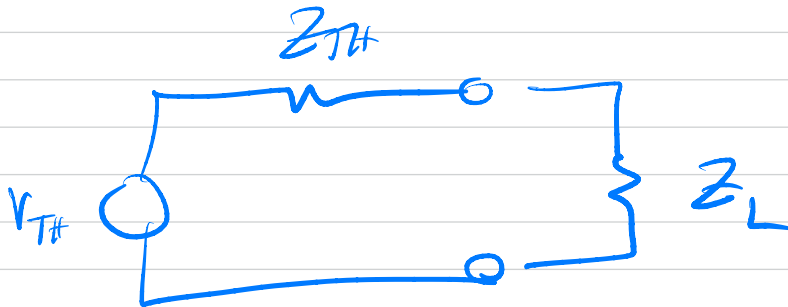

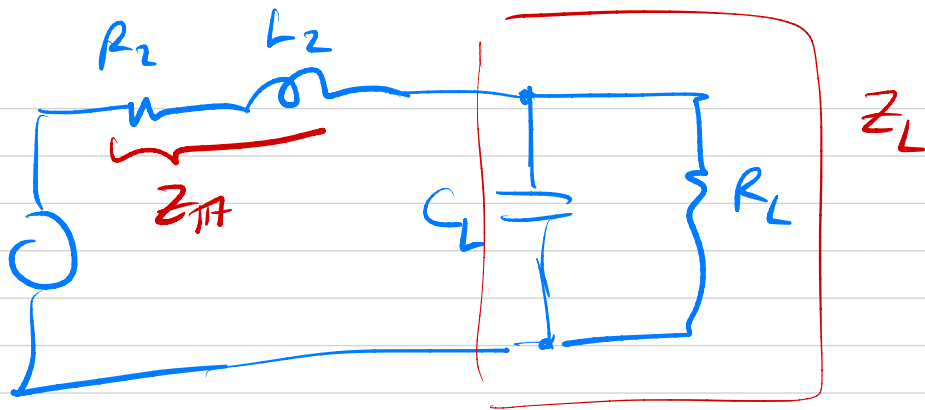


$$Z_L = Z_{TH}^* = \frac{R_L}{1 + j\omega R_L C_L} = \frac{R_L (1 - j\omega R_L C_L)}{1 + \omega^2 R_L^2 C_L^2}$$

$$\frac{R_L}{1 + \omega^2 R_L^2 C_L^2} = R_2 \quad \left| \quad \frac{+\omega R_L^2 C_L}{1 + \omega^2 R_L^2 C_L^2} = +\omega L_2$$


Real Part

Im Part

Why not series?

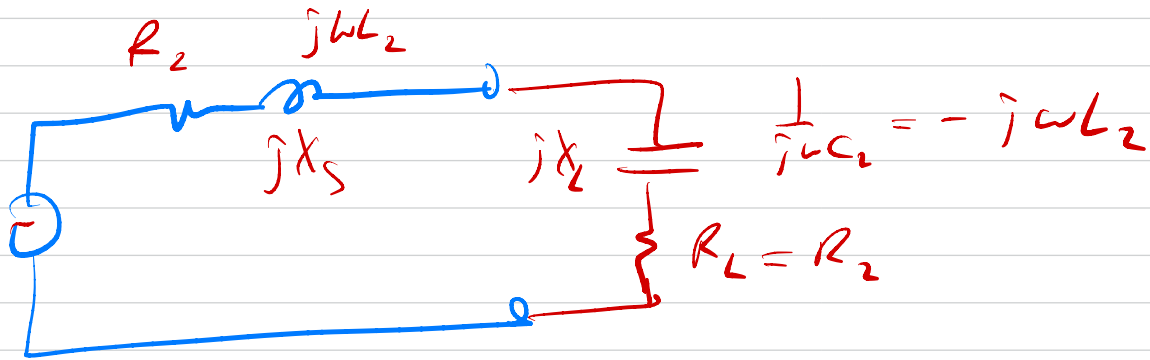

$\Downarrow$

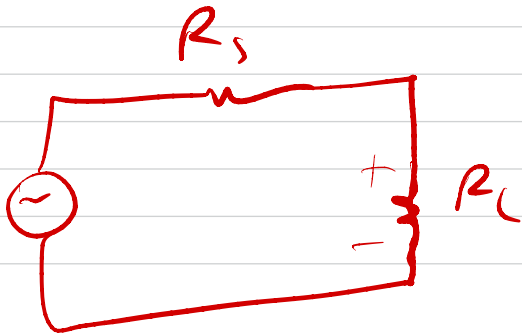

Valid under conjugate  
match at some  
 $\omega$



$$\frac{R_L}{1 + \omega^2 R_L^2 C_L^2} = R_2$$

$$\frac{+ \omega R_L^2 C_L}{1 + \omega^2 R_L^2 C_L^2} = + \omega L_2$$


$$Q \triangleq \frac{\omega L_2}{R_2} = \frac{\omega R_L^2 C_L}{R_L} = \omega C_L R_L$$

$$\frac{R_L}{1 + Q^2} = R_2$$

$$\frac{\omega^2 C_L^2 R_L^2 \frac{1}{\omega C_L}}{1 + Q^2} = \omega L_2$$



$$R_L = R_2 (1 + Q^2)$$
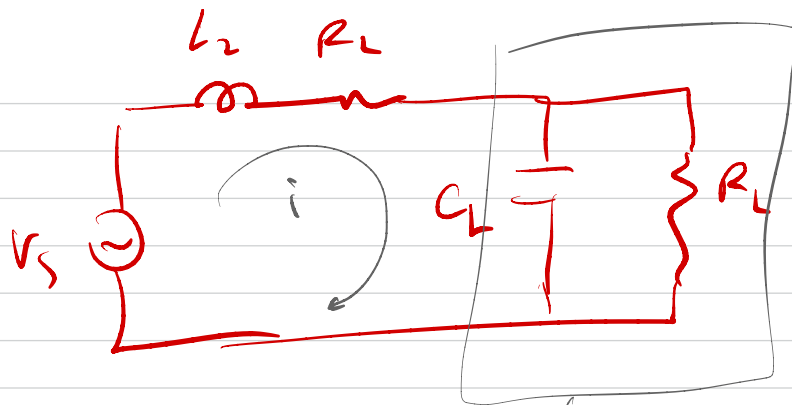
$$\frac{1}{\omega C_L} = \omega L_2 \frac{(1 + Q^2)}{Q^2}$$




$$i = \frac{V_s}{2R_2}$$

$$X_L = -X_S$$

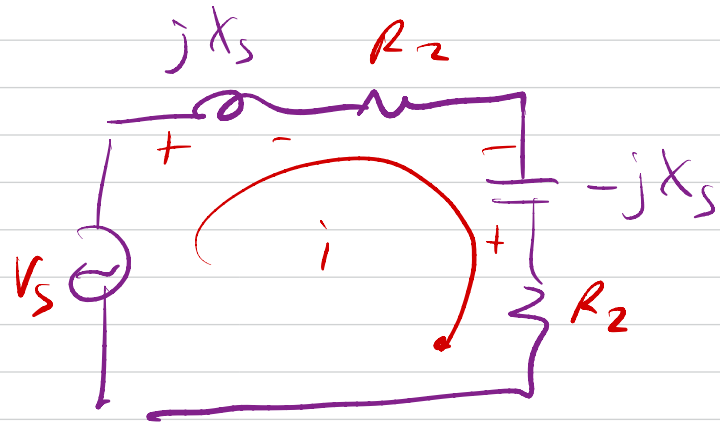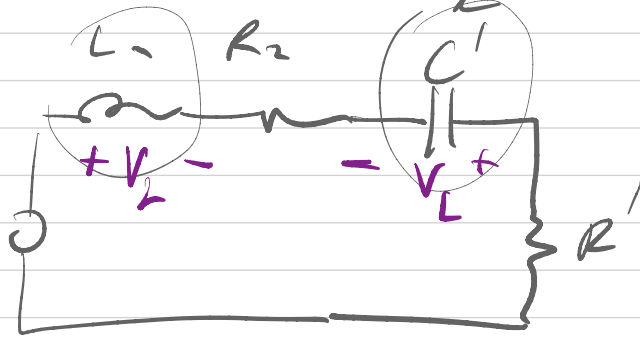
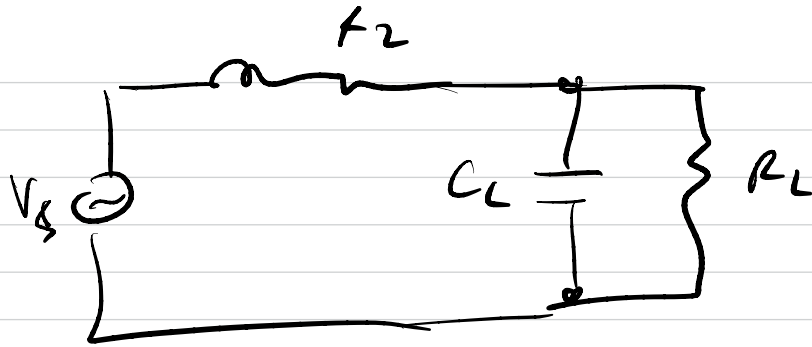
$$i = \frac{V_s}{2R_2} \quad \text{At } \omega$$




$$V_L = i \cdot Z_L = \frac{V_s}{2R_2} \cdot \frac{R_L}{1 + j\omega C_L R_L}$$

$$\left| \frac{V_L}{V_s} \right| = \frac{R_L}{2R_2} \sqrt{\frac{1}{1 + \omega^2 C_L^2 R_L^2}}$$

$$= \frac{R_2(1 + Q^2)}{2R_2} \cdot \frac{1}{\sqrt{1 + Q^2}}$$

$$\left| \frac{V_L}{V_S} \right| = \frac{1}{2} \frac{1+Q^2}{\sqrt{1+Q^2}} = \frac{1}{2} \sqrt{1+Q^2}$$


$$Q = \frac{\omega L_2}{R_2}$$

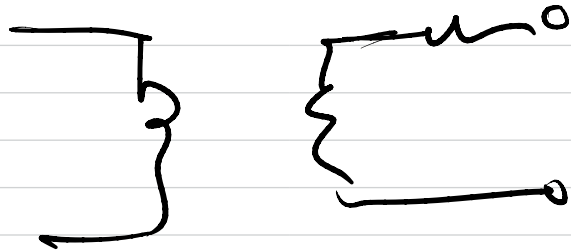

Say  $Q \sim 100$

$$\left| \frac{V_L}{V_S} \right| \approx \frac{1}{2} Q \sim 50mV$$

# Resonance

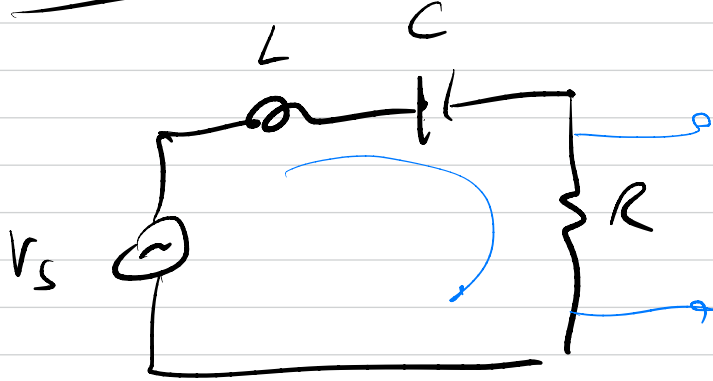

$$Z = j\omega L + \frac{1}{j\omega C} + R$$

$$V_R = \frac{V_s \cdot R}{Z} \Rightarrow H_R = \frac{V_R}{V_s} = \frac{R}{Z} = \frac{R}{R + \frac{1}{j\omega C} + j\omega L}$$

$$H_R(\omega) = \frac{j\omega CR}{1 + j\omega RC + (j\omega L)(j\omega C)}$$


$$H_R(\omega) = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

$$H_2(j\omega_0) = \frac{j\omega_0 RC}{\underbrace{(1 - \omega_0^2 LC)}_{=0} + j\omega_0 RC} = 1$$

$$\omega_0^2 LC = 1$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

[ Natural undamped resonant frequency ]

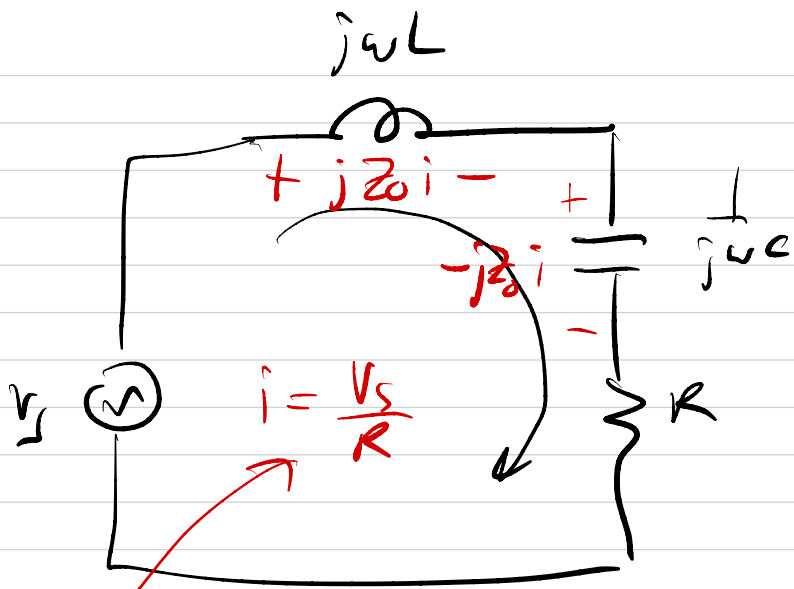

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\begin{aligned}
 Z_L &= j\omega_0 L = j \frac{L}{\sqrt{LC}} \\
 &= j \sqrt{\frac{L}{C}} = j Z_0
 \end{aligned}$$

$$\begin{aligned}
 Z_C &= \frac{1}{j\omega_0 C} = \frac{\sqrt{LC}}{jC} = \frac{1}{j} \sqrt{\frac{L}{C}} = -j \sqrt{\frac{L}{C}}
 \end{aligned}$$

at resonance

$$H_C(j\omega_0) = i \cdot \frac{1}{j\omega_0 C} = \frac{V_s}{R} \cdot \frac{1}{j\omega_0 C}$$

$$= V_s (-j) \frac{1}{\omega_0 RC}$$

$$= V_s (-j) \frac{\sqrt{LC}}{RC} \quad Z_0 = \sqrt{\frac{L}{C}}$$

$$= V_s (-j) \left( \frac{Z_0}{R} \right)$$

$$Z_0 = 1 \text{ k}\Omega$$

$$R = 1 \Omega$$



# Quality Factor

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Resonance


$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$H_R(j\omega) = \frac{j\omega CR}{1 + j\omega RC + (j\omega L)(j\omega C)}$$

$$H_R(j\omega) = \frac{j \frac{\omega}{\omega_0} (\omega_0 RC)}{1 + j \frac{\omega}{\omega_0} (\omega_0 RC) + \left(j \frac{\omega}{\omega_0}\right)^2}$$

$$H_R(j\omega) = \frac{j \frac{\omega}{Q\omega_0}}{1 + j \frac{\omega}{Q\omega_0} + \left(j \frac{\omega}{\omega_0}\right)^2}$$
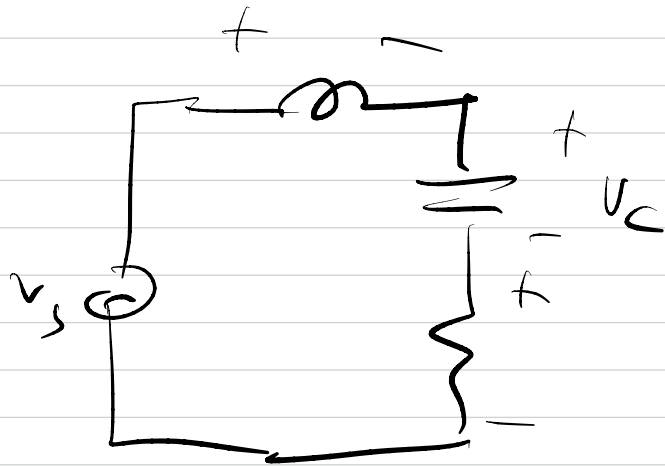
$$H_R(j\omega) = \frac{j \frac{\omega}{Q\omega_0}}{1 + j \frac{\omega}{Q\omega_0} + \left(\frac{\omega}{\omega_0}\right)^2} = \frac{N(j\omega)}{D(j\omega)}$$



$$D(j\omega) = (j\omega + p_1)(j\omega + p_2) \dots$$

Eigenvalues of the  
state-space rep. of  
the circuit

$$H_R(j\omega) = \frac{j \frac{\omega}{Q\omega_0}}{1 + \underbrace{j \frac{\omega}{Q\omega_0}}_{\text{real}} + \left(j \frac{\omega}{\omega_0}\right)^2}$$

$$1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2 = 0$$

$$\zeta = \frac{1}{2Q}$$

$$\omega_0^2 + \frac{s\omega_0}{Q} + s^2 = 0$$

$$s = -\frac{\omega_0}{2Q} \pm \frac{\sqrt{\left(\frac{\omega_0}{2}\right)^2 - 4\omega_0^2}}{2}$$

$$s^{\pm} = -\frac{\omega_0}{2Q} \pm \frac{\omega_0}{2} \sqrt{\left(\frac{1}{2}\right)^2 - 4}$$

$$s^{+/-} = -\frac{\omega_0}{2\alpha} \pm \frac{\omega_0}{2} \sqrt{\left(\frac{\gamma}{\alpha}\right)^2 - 4}$$

$< 0$


$$s^{+/-} = -\frac{\omega_0}{2\alpha} \pm \frac{\omega_0}{2} j \sqrt{4 - \frac{\gamma^2}{\alpha^2}}$$

$$= -\frac{\omega_0}{2\alpha} \pm \omega_0 j \sqrt{1 - \frac{\gamma^2}{(2\alpha)^2}}$$

$$= -\frac{\omega_0}{2\alpha} \pm \omega_0 j \sqrt{1 - \zeta^2}$$

# Bode Plots

$$10 \cdot \log \left\{ |H(j\omega)|^2 \right\} = 20 \log |H(j\omega)|$$

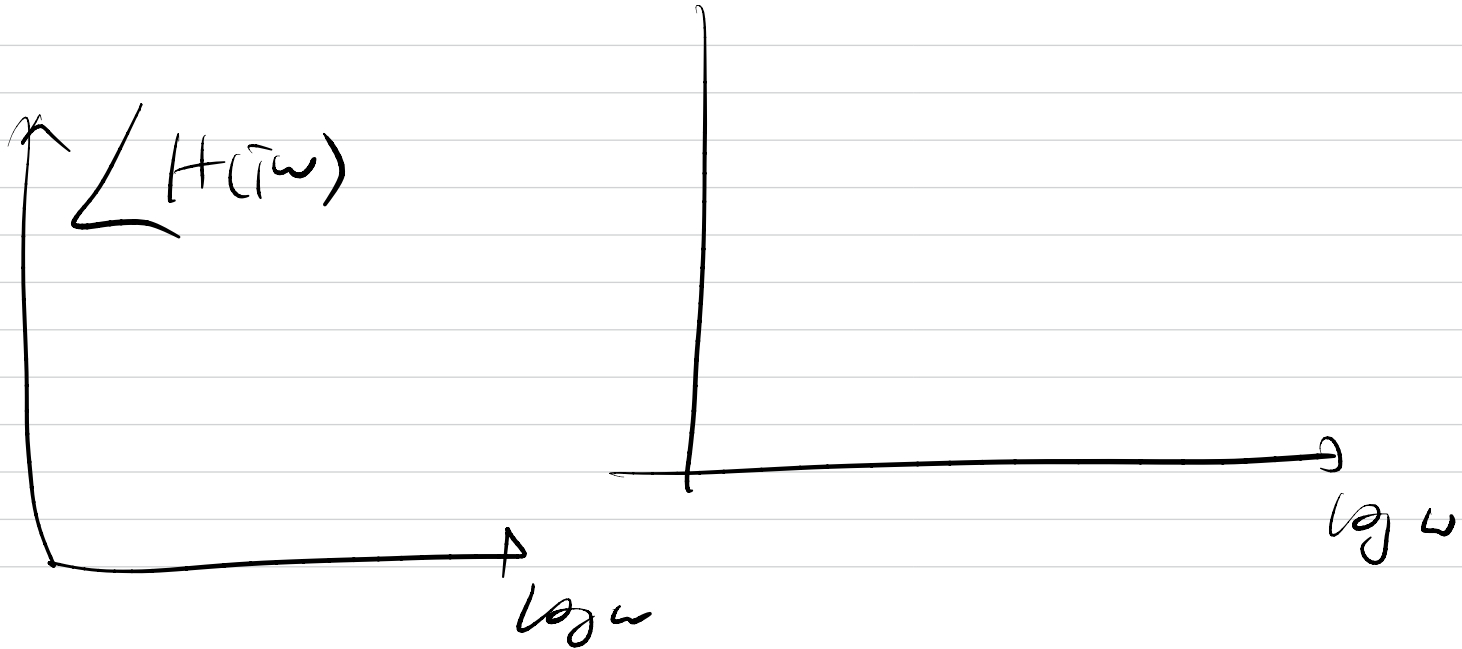

$$H(j\omega) = \frac{N(j\omega)}{D(j\omega)} = \frac{(j\omega + z_1)(j\omega + z_2) \dots}{(j\omega + p_1)(j\omega + p_2) \dots}$$

$$\log |H(j\omega)| = \log \frac{|j\omega + z_1| |j\omega + z_2| \dots}{|j\omega + p_1| |j\omega + p_2| \dots}$$

$$= \log |z_1 + j\omega| + \log |z_2 + j\omega| + \dots$$

$$- \log |j\omega + p_1| - \log |j\omega + p_2| + \dots$$

$$H(j\omega) = \frac{(1 + \frac{j\omega}{z_1}) (1 + \frac{j\omega}{z_2}) \dots}{(1 + \frac{j\omega}{p_1}) (1 + \frac{j\omega}{p_2}) \dots} K$$

$$20 \log \left| 1 + \frac{j\omega}{z_1} \right| = \begin{cases} 0 \text{ dB} & \frac{\omega}{z_1} \ll 1 \\ 20 \log \omega & \frac{\omega}{z_1} \gg 1 \end{cases}$$

$\hookrightarrow \frac{\omega}{z_1} \gg 1$

$$20 \log \left| \frac{\omega}{z_1} \right|$$

