

Discussion 1C

Su21 EECS16B



Notes made by

Rebecca Won





Q1

Transistor Review

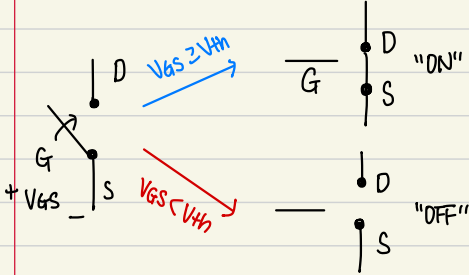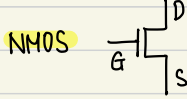


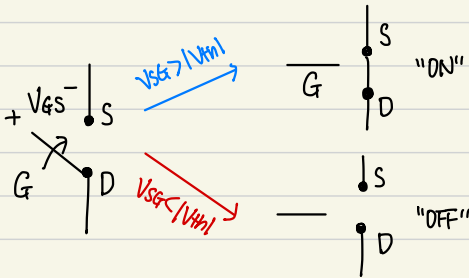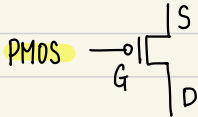Simple model
: think of transistor as a switch





Note : $0 < V_{th} < V_{DD}$


cheatsheet

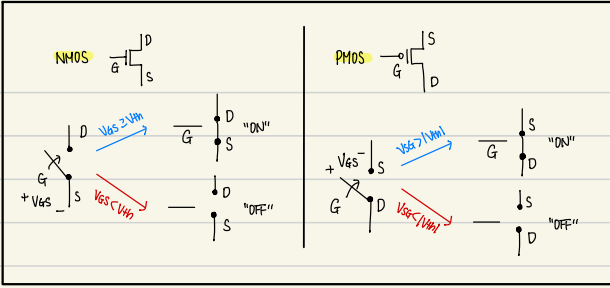

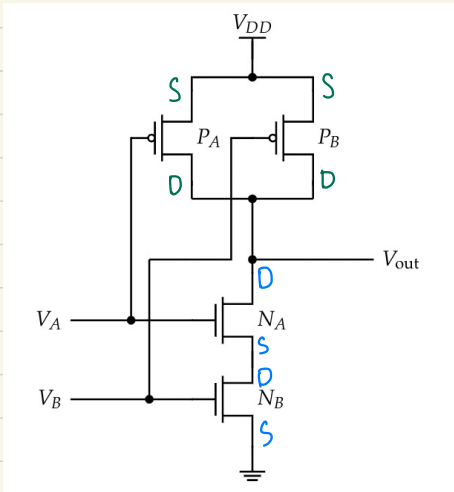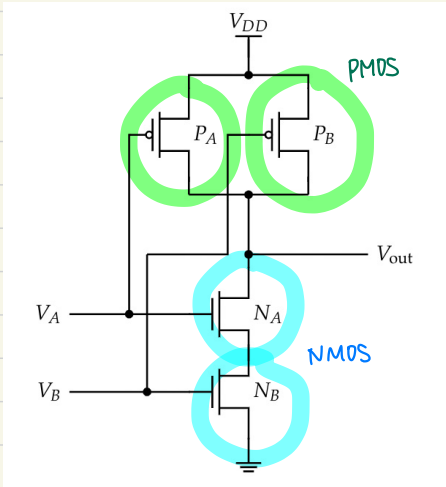a) (a) Label the gate, source, and drain nodes for the NMOS and PMOS transistors above.




cheatsheet

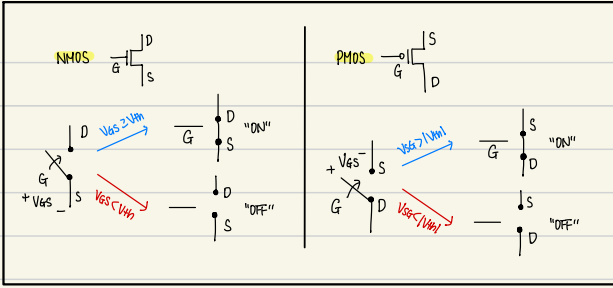


Note: $0 < V_{th} < V_{DD}$

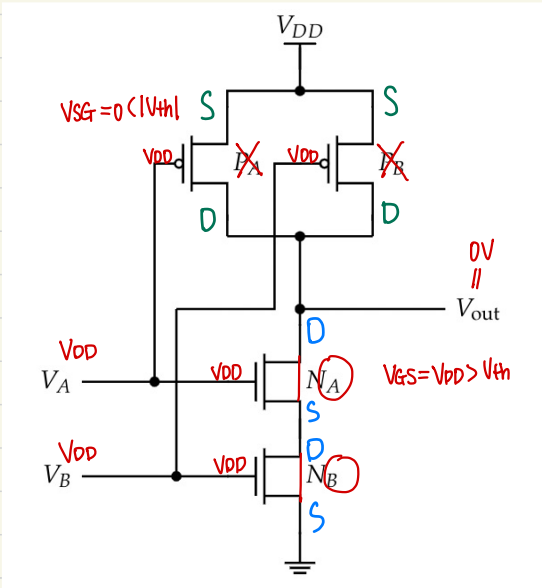b) $V_A = V_{DD}$, $V_B = V_{DD}$ $V_{out} = 0V$




→ Note: V_A is connected to P_A, N_A
 V_B " " P_B, N_B

cheatsheet

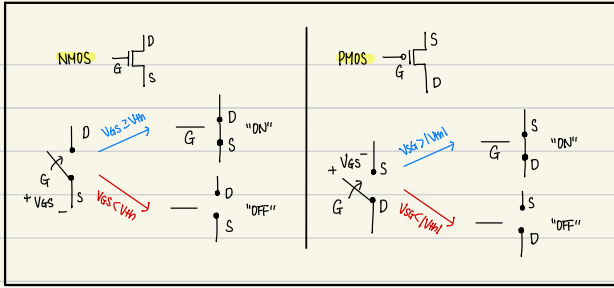

Note: $0 < V_{th} < V_{DD}$

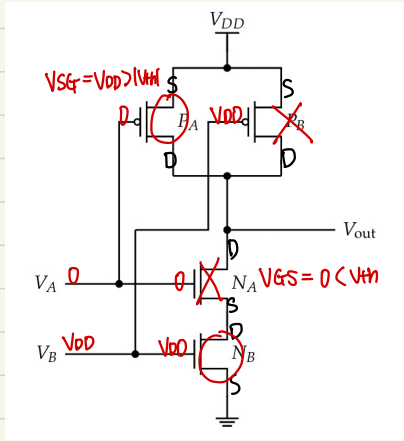
- c) $V_A = 0V, V_B = V_{DD}$ $V_{out} = V_{DD}$ (Since PA is closed connecting V_{out} to V_{DD} and PB is not connected to ground as NA is turned off)




So far we saw:

- | | | | |
|--------|-----|----------------|---|
| NA, NB | ON | $V_G = V_{DD}$ | } Knowing this, we can solve (d), (e) a lot faster! |
| | OFF | $V_G = 0$ | |
| PA, PB | ON | $V_G = 0$ | |
| | OFF | $V_G = V_{DD}$ | |

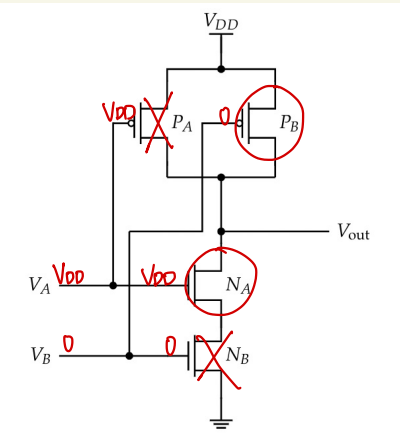- d) $V_A = V_{DD}, V_B = 0V$ $V_{out} = V_{DD}$



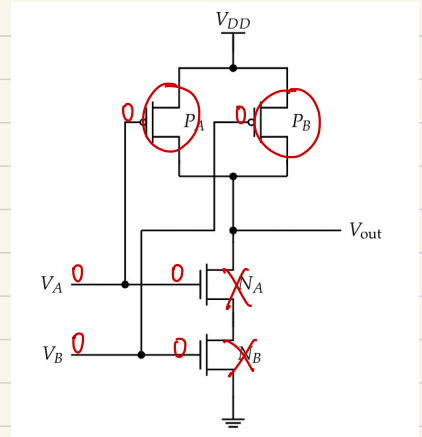- d) $V_A = 0V, V_B = 0V$ $V_{out} = V_{DD}$




f) Summarizing results from (b), (c), (d), (e) we get the truth table below:

V_A	V_B	V_{out}	
0	0	V_{DD}	-(d)
0	V_{DD}	V_{DD}	-(b)
V_{DD}	0	V_{DD}	-(c)
V_{DD}	V_{DD}	0	-(a)

Q2.

a)

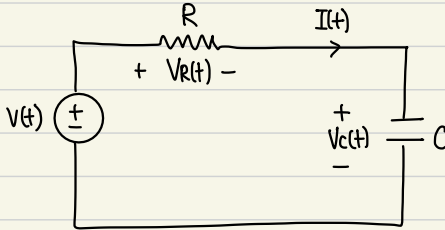(a) Starting from the given charge-voltage relation for a capacitor, find an equation that relates the current across the capacitor $I(t)$ with the voltage across the capacitor $V_C(t)$.




Start with capacitor equation: $Q(t) = CV_C(t)$

$$\frac{dQ(t)}{dt} = I(t) = C \frac{dV_C(t)}{dt}$$

$$\Rightarrow \frac{dV_C(t)}{dt} = \frac{I(t)}{C}$$

b)

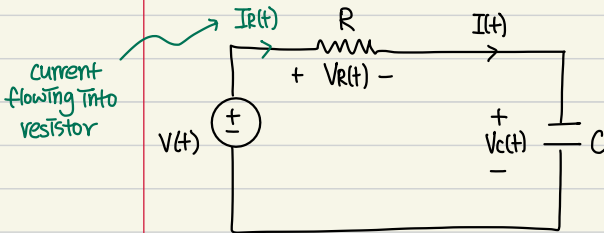(b) Analyzing the circuit, write an equation that relates the functions $I(t)$, $V_C(t)$, and $V(t)$.



① KCL $I_R(t) = I(t)$

② Convert KCL into V-R relationship

$$I_R(t) = \frac{V_R(t)}{R} = \frac{V(t) - V_C(t)}{R}$$

$$\frac{V(t) - V_C(t)}{R} - I(t) = 0 \Rightarrow V(t) = RI(t) + V_C(t)$$

c)

(c) So far, we have an equation that involves both $I(t)$ and $V_C(t)$. To solve this equation, we can remove $I(t)$ (one of the unknowns) using what we found in part 2.a. **Rewrite the previous equation in part 2.b in the form of a differential equation.** You will pick up with this in the next discussion.

$$\text{From a) } \frac{dV_C(t)}{dt} = I(t) \cdot \frac{1}{C} \rightarrow I(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$\text{From b) } RI(t) + V_C(t) = V(t)$$

← substitute

$$\Rightarrow RC \frac{dV_C(t)}{dt} + V_C(t) = V(t)$$

