

Discussion 3C

by Rebecca Worn


EECS16B Summer



Q1.

$$H(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} \quad \leftarrow \text{phasor domain}$$

a) RC circuit

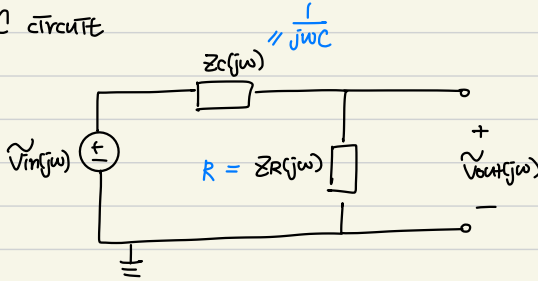

In phasor domain, we treat every element like a resistor
 \therefore can get \tilde{V}_{out} using voltage divider

$$\tilde{V}_{out} = \frac{Z_R}{Z_R + Z_c} \tilde{V}_{in}$$

||
 $H(j\omega)$

$$\therefore H(j\omega) = \frac{Z_R}{Z_c + Z_R} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$$


$$\omega \rightarrow 0, |H(j\omega)| = 0$$

$$\omega \rightarrow \infty, |H(j\omega)| \rightarrow 1$$

} High Pass Filter

(zero out the low frequency and maintains the high frequency)

b) LR circuit:

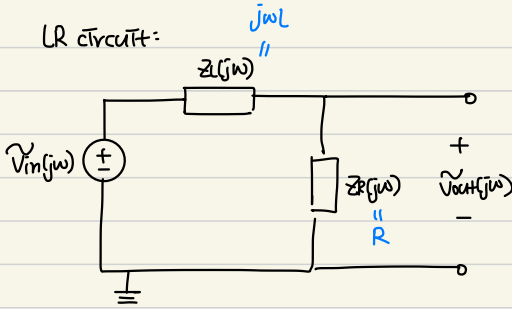


By voltage divider, $V_{out} = \frac{Z_R}{Z_L + Z_R} V_{in}$

$$H(j\omega) = \frac{R}{j\omega L + R}$$

$\omega \rightarrow 0, |H(j\omega)| = 1$
 $\omega \rightarrow \infty, |H(j\omega)| \rightarrow 0$


Low-pass Filter

c) RCR circuit:

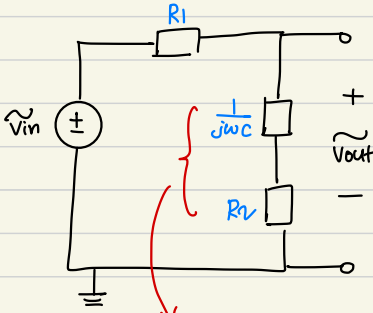

in series
 \oplus
 treat like
 resistors

\Leftrightarrow

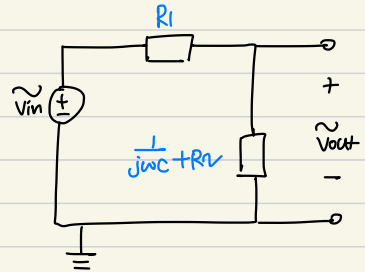

$$\therefore H(j\omega) = \frac{R_2 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{j\omega R_2 C + 1}{j\omega(R_1 + R_2)C + 1}$$

$\omega \rightarrow 0, |H(j\omega)| \rightarrow 1$
 $\omega \rightarrow \infty, |H(j\omega)| \rightarrow \frac{R_2}{R_1 + R_2}$

No name
 for this
 filter

d) $R = 1 \text{ k}\Omega$, $L = 25 \mu\text{H}$, $C = 10 \mu\text{F}$, $\omega = 100 \text{ rad/s}$

From part a) : $H(j\omega) = \frac{j\omega RC}{1+j\omega RC}$

$V_{in}(t) = 12 \sin(\omega t) = 12 \sin(100t)$

① Convert to phasor domain

$V_0 \cos(\omega t + \phi) \Leftrightarrow \frac{V_0}{\sqrt{2}} e^{j\phi}$

$V_{in}(t) = 12 \sin(100t) = 12 \cos(100t - \frac{\pi}{2})$ $\sin \theta = \cos(\theta - \frac{\pi}{2})$

$\therefore \tilde{V}_{in} = \frac{12}{\sqrt{2}} e^{j(-\frac{\pi}{2})} = 6 e^{-j\frac{\pi}{2}}$

② Calculate \tilde{V}_{out}

$\tilde{V}_{out} = H(j\omega) \tilde{V}_{in}$

$\tilde{V}_{out} = \left(\frac{j\omega RC}{1+j\omega RC} \right) \tilde{V}_{in} = \left(\frac{j 10^2 \cdot 10^{-3} \cdot 10^{-5}}{1 + j 10^2 \cdot 10^{-3} \cdot 10^{-5}} \right) \tilde{V}_{in} = \underbrace{\frac{j}{1+j}}_{\text{not in the polar form}} \tilde{V}_{in}$

③ Change $H(j\omega)$ into polar form


i.e. $H(j\omega) \rightarrow |H(j\omega)| e^{j\angle H(j\omega)}$

1) magnitude

$|H(j\omega)| = \left| \frac{j}{1+j} \right| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}}$

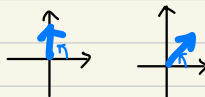2) phase

$\angle H(j\omega) = \angle(j) - \angle(1+j) = \frac{\pi}{2} - \frac{\pi}{4} = \frac{\pi}{4}$



$$\Rightarrow H(j\omega) = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}}$$

$$\tilde{V}_{out} = \left(\frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}} \right) (6e^{-j\frac{\pi}{4}})$$

$$= 3\sqrt{2} e^{j\frac{\pi}{4}}$$

④ Change back to time domain

$$V_0 \cos(\omega t + \phi) \Leftrightarrow \frac{V_0}{2} e^{j\phi} \quad \leftarrow \text{again use the formula from step 1}$$

$$\tilde{V}_{out} = \underbrace{3\sqrt{2}}_{\frac{V_0}{2}} e^{j\frac{\pi}{4}}$$


$$\Rightarrow V_{out}(t) = V_0 \cos(\omega t + \phi) = 6\sqrt{2} \cos(100t - \frac{\pi}{4})$$

In summary,

$$\begin{cases} V_{in}(t) = V_0 \cos(\omega t + \phi) = 12 \cos(100t - \frac{\pi}{2}) \\ V_{out}(t) = 6\sqrt{2} \cos(100t - \frac{\pi}{4}) = \underbrace{\frac{1}{\sqrt{2}}}_{|H(j\omega)|} \cdot 12 \cos(100t - \frac{\pi}{2} + \underbrace{\frac{\pi}{4}}_{\angle H(j\omega)}) \end{cases}$$

$$\Rightarrow V_{out}(t) = \underbrace{|H(j\omega)|}_{\text{scaled by } |H(j\omega)|} V_0 \cos(\omega t + \phi + \underbrace{\angle H(j\omega)}_{\text{shifted by } \angle H(j\omega)}) \quad \text{at a given } \omega$$

Q2.

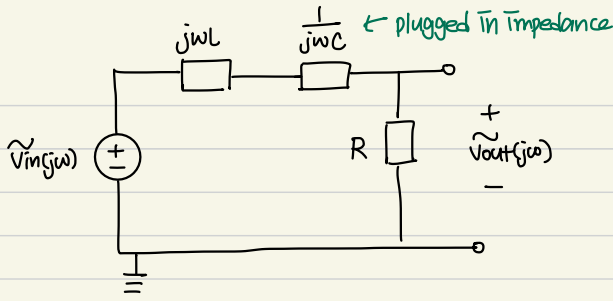

a) By voltage divider,

$$H(j\omega) = \frac{R}{j\omega L + \frac{1}{j\omega C} + R} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

b) $Z_{RLC} = Z_R + Z_L + Z_C = j\omega L + \frac{1}{j\omega C} + R = \underbrace{R}_{A(\omega)} + j \underbrace{(\omega L - \frac{1}{\omega C})}_{X(\omega)}$

Treat impedance as resistance

→ add them up if they're in series

$$X(\omega_n) = 0 \Rightarrow \omega L - \frac{1}{\omega C} = 0$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1$$

$$\omega^2 = \frac{1}{LC}$$

$$\therefore \omega = \sqrt{\frac{1}{LC}} \quad (\omega \geq 0)$$

$$\therefore \omega_n = \frac{1}{\sqrt{LC}}$$

$$c) \quad H(j\omega) = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$|H(j\omega)| = \left| \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \right| = \frac{|R|}{|R + j(\omega L - \frac{1}{\omega C})|}$$

$$= \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\textcircled{1} \quad \omega = \omega_n$$

$$|H(j\omega_n)| = \frac{R}{\sqrt{R^2 + (\omega_n L - \frac{1}{\omega_n C})^2}} = \frac{R}{\sqrt{R^2}} = \frac{R}{R} = 1$$

only term
that's dependent on ω_n

$$\omega_n L - \frac{1}{\omega_n C} = X(\omega_n) = 0 \quad \text{from part (b)}$$

$$\textcircled{2} \quad \omega = \frac{\omega_n}{10}$$

$$X\left(\frac{\omega_n}{10}\right) = X\left(\frac{1}{10\sqrt{LC}}\right)$$

$$= \frac{L}{10\sqrt{LC}} - \frac{10\sqrt{LC}}{C}$$

$$= \frac{\sqrt{L}}{10\sqrt{C}} - \frac{10\sqrt{L}}{\sqrt{C}} = \frac{\sqrt{L} - 100\sqrt{L}}{10\sqrt{C}} = -99 \cdot \frac{1}{10} \sqrt{\frac{L}{C}} = -9.9 \sqrt{\frac{L}{C}}$$

$$\textcircled{3} \quad \omega = 10\omega_n$$

$$X(10\omega_n) = X\left(\frac{10}{\sqrt{LC}}\right) = \frac{10L}{\sqrt{LC}} - \frac{\sqrt{LC}}{10C} = \frac{10\sqrt{L}}{\sqrt{C}} - \frac{\sqrt{L}}{10\sqrt{C}}$$

$$= \frac{100\sqrt{L} - \sqrt{L}}{10\sqrt{C}} = \frac{99\sqrt{L}}{10\sqrt{C}} = 9.9 \sqrt{\frac{L}{C}}$$

In summary,

$$\begin{cases} \omega = \omega_n & X(\omega) = 0 \\ \omega = \frac{\omega_n}{10} & X(\omega) = -q \cdot q \sqrt{\frac{L}{C}} \\ \omega = 10\omega_n & X(\omega) = q \cdot q \sqrt{\frac{L}{C}} \end{cases}$$

$$|H(j\omega)| = \frac{R}{\sqrt{R^2 + \underbrace{X(\omega)^2}_{>0}}}$$

$$X\left(\frac{\omega_n}{10}\right)^2 = X(10\omega_n)^2 = \left(q \cdot q \sqrt{\frac{L}{C}}\right)^2 = q \cdot q^2 \frac{L}{C}$$

$$\begin{aligned} \therefore |H(j\frac{\omega_n}{10})| &= |H(j10\omega_n)| \\ &= \frac{R}{\sqrt{R^2 + \underbrace{q \cdot q^2 \frac{L}{C}}_{>0}}} < 1 \end{aligned}$$

$$\Rightarrow |H(j\omega_n)| > |H(j\omega_n/10)| = |H(j10\omega_n)|$$

\Rightarrow "lets through" or maintains signal at $\omega = \omega_n$, and attenuates every other signal.