

# Discussion 3D

---


by Rebecca Won

EECS 16B Spring



# Q1.

a)

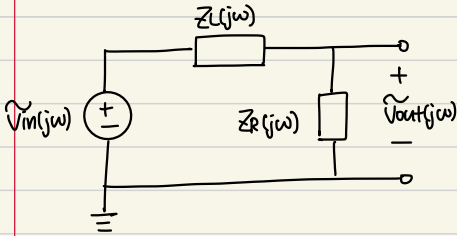

$$H(j\omega) = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L}$$

$$|H(j\omega)| = \left| \frac{R}{R + j\omega L} \right| = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$

$$\begin{aligned} \angle H(j\omega) &= \angle R - \angle (R + j\omega L) \\ &= 0 - \arctan\left(\frac{\omega L}{R}\right) \\ &= -\arctan\left(\frac{\omega L}{R}\right) \end{aligned}$$

$$\left\{ \begin{array}{l} \text{Magnitude: } \omega=0, |H(j\omega)| = \frac{R}{\sqrt{R^2}} = 1 \\ \omega \rightarrow \infty, |H(j\omega)| \rightarrow 0 \end{array} \right.$$

$$\begin{aligned} \text{Phase: } \omega=0, \angle H(j\omega) &= -\arctan\left(\frac{\omega L}{R}\right) = 0 \\ \omega \rightarrow \infty, \angle H(j\omega) &= -\arctan\left(\frac{\omega L}{R}\right) \\ &= -\arctan\left(\frac{\omega L}{R}\right) \xrightarrow{\omega \rightarrow \infty} -\frac{\pi}{2} \end{aligned}$$

b)  $H(j\omega) = \frac{R}{R + j\omega L}$

$|H(j\omega)| = \frac{R}{\sqrt{R^2 + (\omega L)^2}} = \frac{1}{\sqrt{2}}$  at cutoff frequency  $\omega = \omega_c$

$\Rightarrow (\omega_c L)^2 = R^2 \Rightarrow \omega_c L = R, \omega_c = \frac{R}{L}$

↓



$\frac{R}{\sqrt{R^2 + R^2}} = \frac{R}{\sqrt{2R^2}} = \frac{1}{\sqrt{2}}$

Plugging in given values,

$\omega_c = \frac{100}{100 \cdot 10^{-6}} = 10^6 \frac{\text{rad}}{\text{s}}$

c)

$\omega$	$10^4$	$10^5$	$10^6$	$10^7$	$10^8$
$ H(j\omega) $	1.00	0.995	0.707	0.100	0.01
$\angle H(j\omega)$	$-0.6^\circ$	$-6^\circ$	$-45^\circ$	$-84^\circ$	$-89^\circ$

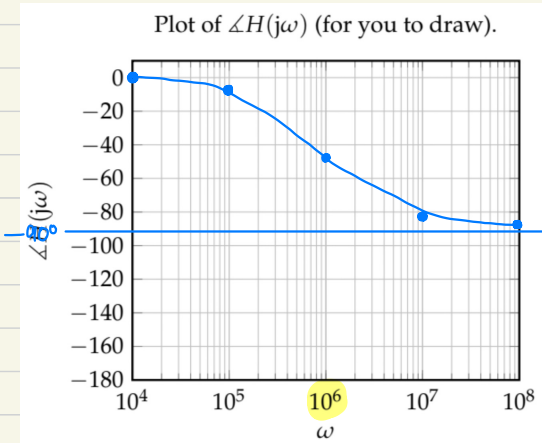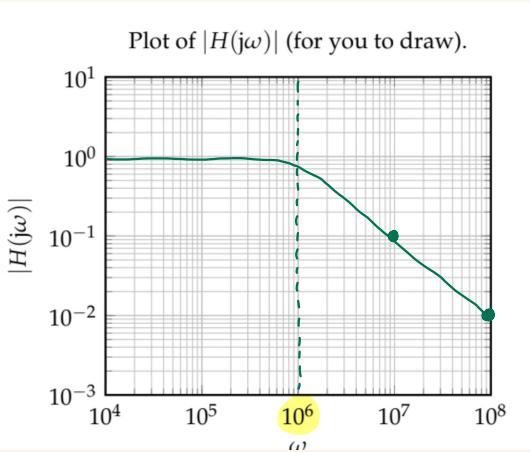

d)

fig 1a



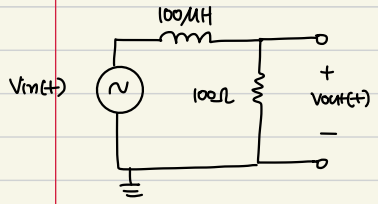


fig 3a

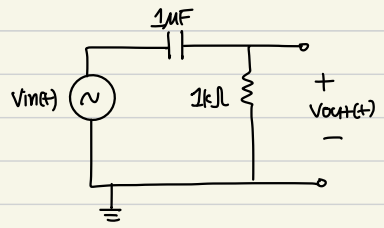

i) Connect w/ unity gain buffer

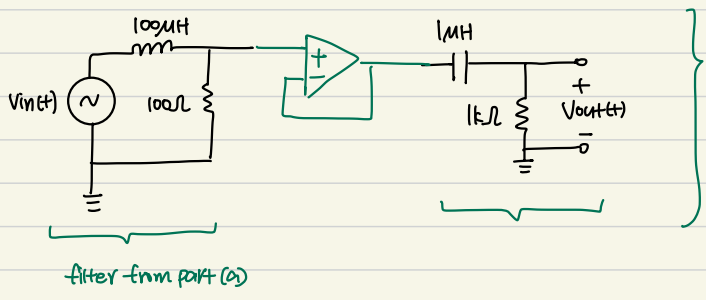

ii) magnitude plot

Recall:

$$\begin{cases} \text{1st filter} : \tilde{V}_{int} = H_1(j\omega) \tilde{V}_{in} \\ \text{2nd filter} : \tilde{V}_{out} = H_2(j\omega) \tilde{V}_{int} \end{cases} \Rightarrow \tilde{V}_{out} = \boxed{H_1(j\omega) \cdot H_2(j\omega)} \tilde{V}_{in}$$


↓  
transfer function of cascading filter

Convert transfer function into a polar form:

$$\begin{aligned} \tilde{V}_{out} &= |H_1(j\omega)| e^{j\phi_1} \cdot |H_2(j\omega)| e^{j\phi_2} \cdot \tilde{V}_{in} \\ &= \underbrace{|H_1(j\omega)| |H_2(j\omega)|}_{V_o \cos(\omega t + \phi)} e^{j(\phi_1 + \phi_2)} \cdot \tilde{V}_{in} \end{aligned}$$

$V_o \cos(\omega t + \phi) \Leftrightarrow \frac{V_o}{2} e^{j\phi}$

$$\rightarrow V_{out(t)} = \underbrace{|H_1(j\omega)| \cdot |H_2(j\omega)|}_{|H_{total}(j\omega)|} V_o \cos(\omega t + \phi + \underbrace{\phi_1 + \phi_2}_{\phi_{total}})$$

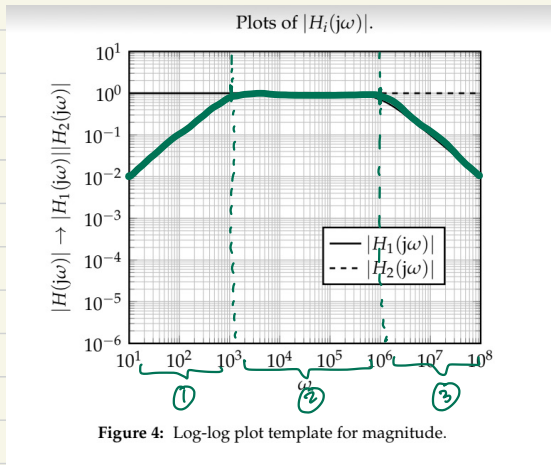

$$|H_{total}(j\omega)| = |H_1(j\omega)| \cdot |H_2(j\omega)|$$

①  $|H_1| = 1$

$$|H_{total}| = |H_2|$$

②  $|H_1| = |H_2| = 1$

$$|H_{total}| = 1 \cdot 1 = 1$$

③  $|H_2| = 1$

$$|H_{total}| = |H_1|$$

iii) phase plot

$$\angle H_{\text{total}}(j\omega) = \angle H_1(j\omega) + \angle H_2(j\omega)$$

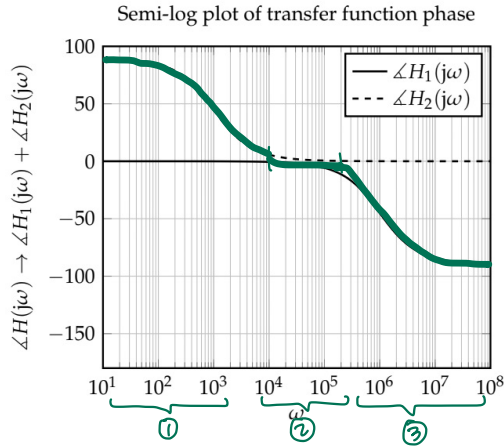


Figure 5: Plot template for phase.

①  $\angle H_1 = 0 \rightarrow \angle H_{\text{total}} = \angle H_2$

②  $\angle H_1 = 0$   
 $\angle H_2 = 0 \rightarrow \angle H_{\text{total}} = 0$


③  $\angle H_2 = 0 \rightarrow \angle H_{\text{total}} = \angle H_1$

Q2.


$L = 100\text{mH}$ ,  $C = 1\text{mF}$ ,  $R_1 = 100\Omega$ ,  $R_2 = 1\text{k}\Omega$

a) Bode Plot  $\Rightarrow$  straight line approximation

$\omega_c = 10^6 \text{ rad/s}$

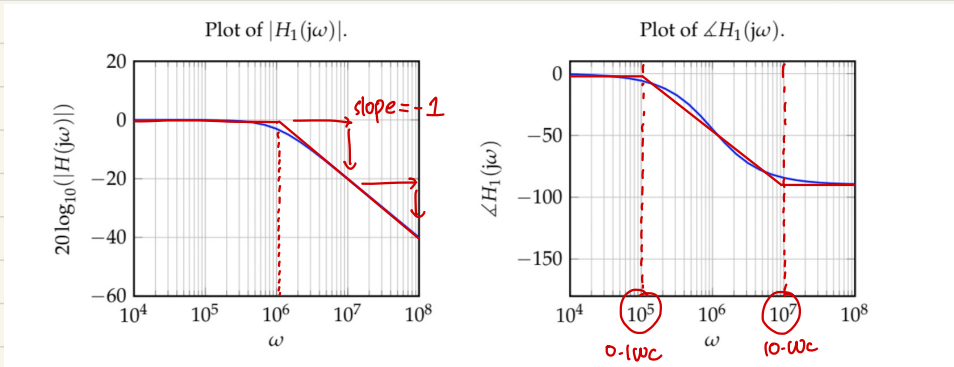

b)  $\omega_c = 10^3 \text{ rad/s}$

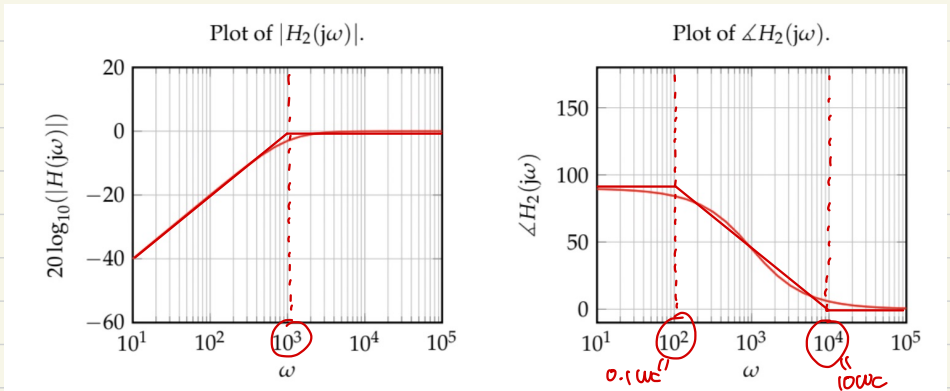



c)

