


# Lecture 4

\* Sensing


\* Non-homogeneous diff. eqns.  
with continuous inputs

Signal source  
(neural signal / electrode)  
voice / mic-board

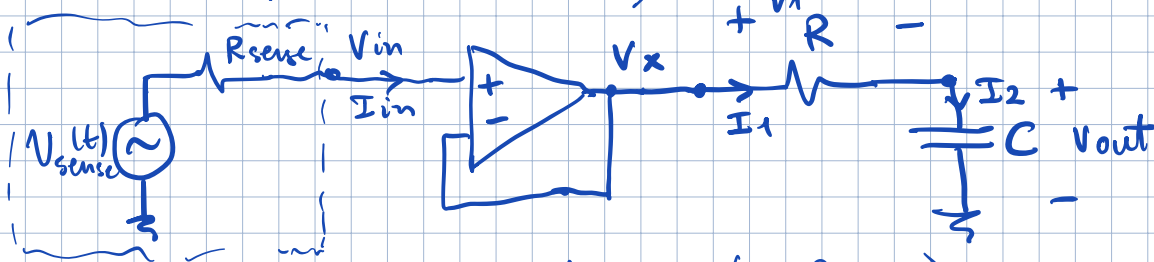Want this circuit to  
filter / separate low-frequency  
signal of interest from high-freq  
interference



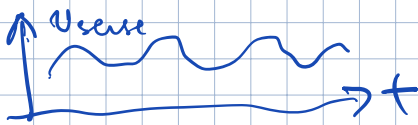Thevenin  
model of  
the sensor signal  
source



$$V_{in} = V_{sense} \quad (\text{b/c } I_{in} = 0)$$

$$V_x = V_{in} \quad (\text{buffer})$$

$$V_1 = V_x - V_{out}$$

$$\text{KCL: } I_1 = I_2$$

$$\text{Elements: } V_1 = I_1 \cdot R$$

$$I_2 = C \frac{dV_{out}}{dt}$$

From KCL & Elements:

$$\frac{V_1}{R} = C \frac{dV_{out}}{dt}$$

$$\frac{V_x - V_{out}}{R} = C \frac{dV_{out}}{dt}$$

(also directly  
from NVA  
nodal voltage  
analysis)

$$\frac{V_{sense} - V_{out}}{R} = C \frac{dV_{out}}{dt}$$

(b.c.  
 $V_x = V_{in} = V_{sense}$ )

$$\frac{dV_{out}(t)}{dt} = -\frac{V_{out}(t)}{RC} + \frac{V_{sense}(t)}{RC}$$

$V_{sense}(t)$   
is a  
continuous  
time  
signal

In disc. & hnw:

$$(1) \quad V_{out}(t) = \underbrace{V_{out}(0) \cdot e^{-\frac{t}{RC}}}_{\substack{\text{homogeneous} \\ \text{solution} \\ \text{"response to initial} \\ \text{condition"}}} + \underbrace{\frac{1}{RC} \int_0^t V_{sense}(\theta) e^{-\frac{1}{RC}(t-\theta)} d\theta}_{\substack{\text{non-homogeneous solu.} \\ \text{"response to continuous time} \\ \text{input"}}} , t \geq 0$$

The circuit "computes" this solution!

General form:  $\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$

Let's try to compute the response for  $u(t)$ 's of interest.

For our  
circuit  
 $\lambda = -\frac{1}{RC}$   
 $u(t) = V_{sense}$   
 $x(t) = V_{out}$

Example 1:  $u(t) = e^{st}$ ,  $s \neq 0$

$$(2) \quad \frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t), \quad t \geq 0$$

can solve:

$$\begin{aligned} x(t) &= x(0) e^{\lambda t} - \lambda \int_0^t u(\theta) e^{\lambda(t-\theta)} d\theta \\ &= x(0) e^{\lambda t} - \lambda e^{\lambda t} \int_0^t \underbrace{e^{s\theta} \cdot e^{-\lambda\theta}}_{e^{(s-\lambda)\theta}} d\theta \end{aligned}$$

or Guess & check:

$$x(t) = K e^{st}, \quad t \geq 0$$

From (2)  $K \cdot s \cdot \cancel{e^{st}} = \lambda \cdot K \cdot \cancel{e^{st}} - \lambda \cancel{e^{st}}$

$$Ks = \lambda K - \lambda$$

$$K(s - \lambda) = -\lambda$$

$$K = -\frac{\lambda}{s - \lambda} \Rightarrow x_1(t) = -\frac{\lambda}{s - \lambda} e^{st}$$

To complete, add a homogeneous soln.

$$x(t) = K_2 e^{\lambda t} + K \cdot e^{st}$$

$$x(0) = K_2 + K \Rightarrow K_2 = x(0) - K$$

$$= x(0) + \frac{\lambda}{s - \lambda}$$

$$x(t) = \left( x(0) + \frac{\lambda}{s - \lambda} \right) e^{\lambda t} - \frac{\lambda}{s - \lambda} e^{st}$$

Example 2:  $u(t) = \cos(\omega t)$

$$\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$$

$$x(t) = x(0) e^{\lambda t} - \lambda \int_0^t u(\theta) e^{\lambda(t-\theta)} d\theta, \quad t \geq 0$$

$$= x(0) e^{\lambda t} - \lambda \int_0^t \cos(\omega \theta) e^{\lambda(t-\theta)} d\theta$$

$$= x(0) e^{\lambda t} - \lambda e^{\lambda t} \int_0^t \cos(\omega \theta) e^{-\lambda \theta} d\theta$$

From calc:

$$\int \cos(bx) e^{ax} dx = \frac{e^{ax}}{a^2 + b^2} (b \sin(bx) + a \cos(bx))$$

$$x(t) = x(0) e^{\lambda t} - \lambda e^{\lambda t} \left( \frac{e^{-\lambda t}}{\lambda^2 + \omega^2} (\omega \sin(\omega t) - \lambda \cos(\omega t)) - \frac{1}{\lambda^2 + \omega^2} (0 - \lambda) \right)$$

$$x(t) = x(0) e^{\lambda t} - \frac{\lambda}{\lambda^2 + \omega^2} (\omega \sin(\omega t) - \lambda \cos(\omega t)) - \frac{\lambda^2}{\lambda^2 + \omega^2} e^{\lambda t}$$

$$x(t) = \underbrace{(x(0) - \frac{\lambda^2}{\lambda^2 + \omega^2}) e^{\lambda t}}_{(1)} - \frac{\lambda}{\lambda^2 + \omega^2} (\omega \sin(\omega t) - \lambda \cos(\omega t))_{(2)}$$

$t \rightarrow \infty$  (steady-state),  $\lambda < 0$

①  $\rightarrow 0$  b.c.  $\lambda < 0$  (in RC  $\lambda = -\frac{1}{RC}$ )


② for  $\lambda = -\frac{1}{RC}$

$$x(t) = \frac{\frac{1}{RC} \omega \sin(\omega t) + \left(\frac{1}{RC}\right)^2 \cos(\omega t)}{\left(\frac{1}{RC}\right)^2 + \omega^2}$$

②  $x(t) = \frac{\omega RC \sin(\omega t) + \cos(\omega t)}{1 + (\omega RC)^2}$

Remember the trig identity:
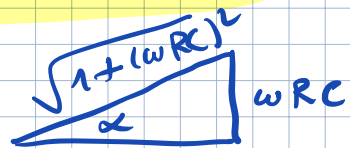
$$\cos(\alpha) \cos(\beta) + \sin(\alpha) \sin(\beta) = \cos(\alpha - \beta)$$



$$\alpha = \arctan(\omega RC, 1)$$

$$x(t) = \frac{1}{\sqrt{1+(\omega RC)^2}} \left( \frac{1}{\sqrt{1+(\omega RC)^2}} \cos(\omega t) + \frac{\omega RC}{\sqrt{1+(\omega RC)^2}} \sin(\omega t) \right)$$

$\cos(\alpha)$                        $\sin(\alpha)$

$$x(t) = \frac{1}{\sqrt{1+(\omega RC)^2}} \cos(\omega t - \alpha)$$

$$x(t) = \frac{1}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + \theta)$$

$\theta = -\alpha$   
 $\theta = -\arctan(\omega RC, 1)$

Remember:  $x(t) = \cos(\omega t)$ ,  $\omega$  - angular frequency  
 $\omega = 2\pi \cdot f = 2\pi \cdot \frac{1}{T}$ , where  $T$  is the period. [rad/s]

$$\text{Case 1: } \omega \gg \frac{1}{RC} \Rightarrow \omega RC \gg 1$$

$$x(t) \approx 0$$

$$\text{Case 2: } \omega \ll \frac{1}{RC} \Rightarrow \omega RC \ll 1$$

$$x(t) = \cos(\omega t + \theta)$$

Our system (circuit) is a "low-pass" filter with  $\frac{1}{RC}$  cut-off frequency.

Frequencies below  $\frac{1}{RC}$  pass

Frequencies above  $\frac{1}{RC}$  are attenuated

Can also arrive here with a guess:

$$\text{Guess: } x(t) = A \cos(\omega t + \theta)$$

do this for:

$$u(t) = V_{\text{sense}} \cos(\omega t)$$

$$\text{System: } \frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$$

$$-A \omega \sin(\omega t + \theta) = \lambda A \cos(\omega t + \theta) - \lambda V_{\text{sense}} \cos(\omega t)$$

$$V_{\text{sense}} \cos(\omega t) = A \cos(\omega t + \theta) + \frac{A \omega}{\lambda} \sin(\omega t + \theta)$$

$$= A \left( \cos(\omega t + \theta) + \frac{\omega}{\lambda} \sin(\omega t + \theta) \right)$$

$$\lambda = -\frac{1}{RC}$$

$$V_{\text{sense}} \cos(\omega t) = A (1 \cdot \cos(\omega t + \theta) - \omega RC \sin(\omega t + \theta))$$

$$V_{\text{sense}} \cdot \cos(\omega t) = A \sqrt{1 + (\omega RC)^2} \left( \frac{1}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t + \theta) - \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \sin(\omega t + \theta) \right)$$

$\frac{\sqrt{1 + (\omega RC)^2}}{\alpha} \quad \omega RC \quad \alpha = \arctan 2(\omega RC, 1)$

$$V_{\text{sense}} \cos(\omega t) = A \sqrt{1 + (\omega RC)^2} (\cos(\alpha) \cos(\omega t + \theta) - \sin(\alpha) \sin(\omega t + \theta))$$

$$V_{\text{sense}} \cos(\omega t) = A \sqrt{1 + (\omega RC)^2} \cos(\omega t + \theta + \alpha)$$

$$V_{\text{sense}} = A \cdot \sqrt{1 + (\omega RC)^2} \quad \& \quad \omega t = \omega t + \theta + \alpha$$

$$A = \frac{V_{\text{sense}}}{\sqrt{1 + (\omega RC)^2}}$$

$$\theta + \alpha = 0$$

$$\theta = -\alpha = -\arctan 2(\omega RC, 1)$$

Back to our guess:  $x(t) = A \cos(\omega t + \theta)$

solution:

$$x_d(t) = \frac{V_{\text{sense}}}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t + \theta)$$

$\theta = -\arctan 2(\omega RC, 1)$

more general:

$$x(t) = x(t_0) e^{\lambda(t-t_0)} - \lambda \int_{t_0}^t u(\theta) e^{\lambda(t-\theta)} d\theta \quad , t \geq t_0$$