

Lecture 5

* Systems of differential equations


* Higher-order diff. eqn. systems

* Circuits w. multiple C's

* Vector diff. eqns.

* Diagonalization

Circuits example - a more complex system:

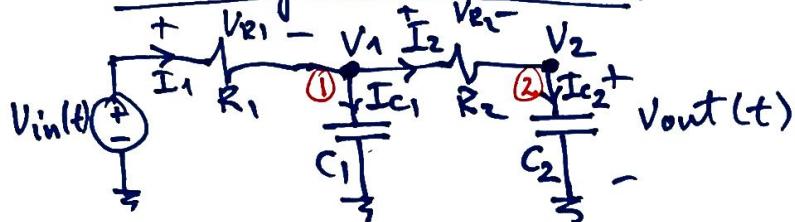Two-capacitor circuit:

KCL: $I_2 = I_{C_2}$

$I_1 = I_2 + I_{C_1}$

Elements: $I_{C_1} = C_1 \frac{dV_1}{dt}$
 $I_{C_2} = C_2 \frac{dV_2}{dt}$

$V_{R_1} = I_1 \cdot R_1$

$V_{R_2} = I_2 \cdot R_2$

From NVA directly:

(1) $\frac{V_{in} - V_1}{R_1} = C_1 \frac{dV_1}{dt} + \frac{V_1 - V_2}{R_2}$

(2) $\frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt} \Rightarrow V_1 = V_2 + R_2 C_2 \frac{dV_2}{dt}$

$$R_1 C_1 R_2 C_2 \frac{d^2 V_2}{dt^2} + (R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{dV_2}{dt} + V_2 - V_{in} = 0$$

(2nd order diff. eq) - not yet know how to solve it.

Back to our system:

$$① \frac{V_{in} - V_1}{R_1} = C_1 \frac{dV_1}{dt} + \frac{V_1 - V_2}{R_2}$$

$$② \frac{V_1 - V_2}{R_2} = C_2 \frac{dV_2}{dt}$$

$$① \frac{dV_1}{dt} = -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right)V_1 + \frac{V_2}{R_2 C_1} + \frac{V_{in}}{R_1 C_1}$$

$$② \frac{dV_2}{dt} = \frac{V_1}{R_2 C_2} - \frac{V_2}{R_2 C_2}$$

In matrix-vector form

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) & \frac{1}{R_2 C_1} \\ \frac{1}{R_2 C_2} & -\frac{1}{R_2 C_2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} \frac{1}{R_1 C_1} \\ 0 \end{bmatrix} V_{in}$$

only know how to solve:

$$\frac{d}{dt} x(t) = \lambda x(t) + b u(t)$$

Example: Assume: $R_1 = \frac{1}{3} M\Omega$, $R_2 = \frac{1}{2} M\Omega$ (l3)

$$C_1 = C_2 = 1 \mu F = 10^{-6}$$

$$(a) \frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} V_{in}$$

solutions for $t \geq 0$.

"Magic" change of variables:

$$(b) u_1 = V_2$$

$$(c) u_2 = V_1 + 2V_2$$

Assume:

$$V_{in} = 1V \quad t < 0$$

$$\downarrow \text{or} \quad t \geq 0$$

$$V_1(0) = 1V$$

$$V_2(0) = 1V$$

$$\begin{aligned} \frac{d}{dt} u_1 &\stackrel{(b)}{=} \frac{d}{dt} V_2 \stackrel{(a)}{=} 2V_1 - 2V_2 \stackrel{(c)}{=} 2(u_2 - 2V_2) - 2V_2 = \\ &= 2u_2 - 4V_2 - 2V_2 = 2u_2 - 6V_2 \stackrel{(b)}{=} 2u_2 - 6u_1 \end{aligned}$$

$$(d) \frac{d}{dt} u_1 = \cancel{2u_2 - 6u_1} \quad -6u_1 + 2u_2$$

$$\begin{aligned} \frac{d}{dt} u_2 &\stackrel{(c)}{=} \frac{d}{dt} (V_1 + 2V_2) = \frac{d}{dt} V_1 + 2 \frac{d}{dt} V_2 \stackrel{(a)}{=} -5V_1 + 2V_2 + \\ &\quad + 2(2V_1 - 2V_2) = \\ &= -5V_1 + 2V_2 + 4V_1 - 4V_2 = \\ &= -V_1 - 2V_2 \stackrel{(c)}{=} -u_2 \quad \text{Wahoo!} \end{aligned}$$

$$(e) \underbrace{\frac{d}{dt} u_2 = -u_2}_{\text{homogeneous scalar diff-eq}}$$

$$u_2(t) = u_2(0) e^{-t}, \quad t \geq 0 \Rightarrow \text{know how to solve for } u_2$$

$$u_2(0) \stackrel{(c)}{=} V_1(0) + 2V_2(0) = 1V + 2 \cdot 1V = 3V$$

$$(g) \boxed{u_2(t) = 3 \cdot e^{-t}, t \geq 0}$$

(84)

Now, go back to (d)

$$\frac{d}{dt} u_1 = -6u_1 + 2u_2$$

$$\boxed{\frac{d}{dt} u_1 = -6u_1 + 6e^{-t}, t \geq 0}$$

$$\begin{aligned} \lambda &= -6 \\ s &= -1 \end{aligned}$$

$$u_1(t) = k_2 e^{-6t} - \frac{-6 \cdot e^{-t}}{-1 - (-6)}$$

$$u_1(t) = k_2 e^{-6t} + \frac{6}{5} e^{-t}$$

$$u_1(0) = k_2 + \frac{6}{5}$$

$$u_1(0) \stackrel{(6)}{=} v_2(0) = 1V \Rightarrow k_2 = 1 - \frac{6}{5} = -\frac{1}{5}$$

$$(g) \boxed{u_1(t) = -\frac{1}{5} e^{-6t} + \frac{6}{5} e^{-t}}$$

so, we solved for $u_1(t)$ & $u_2(t) \Rightarrow$

\Rightarrow back-solve for $v_1(t)$ & $v_2(t)$

$$\begin{aligned} v_1(t) &\stackrel{(6)(8)}{=} u_2(t) - 2u_1(t) \stackrel{(1+g)}{=} 3e^{-t} - 2\left(-\frac{1}{5}e^{-6t} + \frac{6}{5}e^{-t}\right) \\ &= 3e^{-t} + \frac{2}{5}e^{-6t} - \frac{12}{5}e^{-t} \end{aligned}$$

$$(h) \boxed{v_1(t) = \frac{3}{5}e^{-t} + \frac{2}{5}e^{-6t}}$$

Remember (lecture 4)

$$\frac{d}{dt} x(t) = \lambda x(t) - \lambda u(t)$$

$$u(t) = e^{st}$$

$$x(t) = k_2 e^{\lambda t} - \frac{\lambda}{s-\lambda} e^{st}$$

$$x(0) = k_2 - \frac{\lambda}{s-\lambda}$$

$$(i) V_2(t) \stackrel{(b)}{\equiv} u_1(t) \stackrel{(g)}{=} -\frac{6}{5} e^{-t} + -\frac{1}{5} e^{-6t}$$

(5)

$$(a) \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{b'} v_{in}$$

$$(b) \& (c) \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \Leftrightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_W \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \quad (d)$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \frac{d}{dt} (W^{-1} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}) = W^{-1} \frac{d}{dt} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \stackrel{(a)}{=}$$

$$= \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \left(\underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{b'} v_{in} \right)$$

$$\stackrel{(j)}{=} \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \underbrace{\begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}}_A \underbrace{\begin{bmatrix} -2 & 1 \\ 1 & 0 \end{bmatrix}}_W \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 0 & 1 \\ 1 & 2 \end{bmatrix}}_{W^{-1}} \underbrace{\begin{bmatrix} 3 \\ 0 \end{bmatrix}}_{b'} v_{in}$$

$$\frac{d}{dt} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -6 & 2 \\ 0 & -1 \end{bmatrix}}_{W^{-1} A W} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} + \underbrace{\begin{bmatrix} 0 \\ 3 \end{bmatrix}}_{W^{-1} b'} v_{in}$$

upper-triangular, so we can
start at the bottom, solve & peel back.


Summary : Systems of diff. eqns.

(6)

$$(1) \quad \frac{d}{dt} \vec{x}(t) = A \vec{x}(t) + B \vec{u}(t), \quad \vec{x}(0), \quad \vec{x}(t) = ? \quad t \geq 0.$$

Native \vec{x} coordinates

"Nice" coordinates $\tilde{\vec{x}}$:

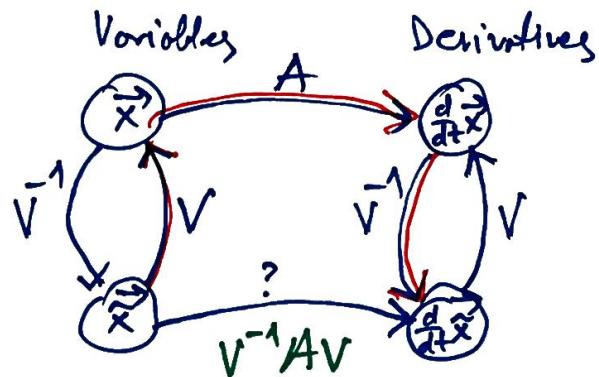

$$(2) \quad \vec{x}(t) = V \tilde{\vec{x}}(t)$$

$$(3) \quad \tilde{\vec{x}}(t) = V^{-1} \vec{x}(t)$$

$$\begin{aligned} \frac{d}{dt} \tilde{\vec{x}}(t) &\stackrel{(3)}{=} \frac{d}{dt} (V^{-1} \vec{x}(t)) = V^{-1} \frac{d}{dt} \vec{x}(t) = V^{-1} (A \vec{x}(t) + B \vec{u}(t)) \\ &= V^{-1} A \vec{x}(t) + V^{-1} B \vec{u}(t) \stackrel{(2)}{=} \\ &= V^{-1} A (V \tilde{\vec{x}}(t)) + V^{-1} B \vec{u}(t) \end{aligned}$$

$$(4) \quad \boxed{\frac{d}{dt} \tilde{\vec{x}}(t) = \underbrace{V^{-1} A V}_{\text{want this matrix to be "nice"}} \tilde{\vec{x}}(t) + V^{-1} B \vec{u}(t)}$$

want this matrix to be "nice"

e.g. $\begin{bmatrix} 1 & 0 & 0 \\ 0 & 2 & 0 \\ 0 & 0 & 3 \end{bmatrix}$

or even better

$$\begin{bmatrix} * & * & 0 \\ 0 & * & * \\ 0 & 0 & * \end{bmatrix}$$

(separable)
homogeneous
in $\tilde{x}_{i,j,k}$

(5) Don't forget :

$$\tilde{\vec{x}}(0) = V^{-1} \vec{x}(0)$$

(6) Go back to $\vec{x}(t)$: (2) $\vec{x}(t) = V \tilde{\vec{x}}(t)$