

# Lecture 9

(21)

## \* Filters

- \* Low-pass & high-pass examples
- \* Transfer functions
- \* Bode plot approximations
- \* Cascading filters

Objective: To find a steady state solution of the system in response to a sinusoidal inputs ( $\lambda_r < 0$ )

\* Sinusoidal inputs allow us to transform a system of diff. eqns. into a system of linear eqns. (Phasor domain)

## Phasor analysis:

Step 1: Write independent sources (inputs) as exponentials.

$$V_{si}(t) = \tilde{V}_{si} e^{j\omega t} + \bar{\tilde{V}}_{si} e^{-j\omega t}$$

$$I_{si}(t) = \tilde{I}_{si} e^{j\omega t} + \bar{\tilde{I}}_{si} e^{-j\omega t}$$

$\tilde{V}_{si}$  &  $\tilde{I}_{si}$  are phasors

Step 2: Transform the circuit into the phasor domain:

( $s$ -impedances where  $s = j\omega$ )  $\frac{\hat{V}_{el}}{\hat{I}_{el}} = Z_{el}(s = j\omega)$

$$\frac{\hat{V}_R}{\hat{I}_R} = Z_R(j\omega) = R, \quad \frac{\hat{V}_C}{\hat{I}_C} = Z_C(j\omega) = \frac{1}{j\omega C}, \quad \frac{\hat{V}_L}{\hat{I}_L} = Z_L(j\omega) = j\omega L$$

step 3 Cost branch & element equations in phasor domain (12)

$$\text{KCL: } \sum_{\substack{i \text{ into} \\ \text{the node}}} \hat{I}_i = 0$$

Ohm's law:

$$\widehat{V}_{el} = Z_{el} \cdot \hat{I}_{el}$$

$$\text{NVA: } \sum \frac{\widehat{V}_j - \widehat{V}_k}{Z_{jk}} = 0, \text{ KVL holds as well}$$

step 4: Solve for unknown variables:  $\widehat{V}_{el}$ ,  $\hat{I}_{el}$

step 5: Transform the phasor solutions ( $\widehat{V}_{el}$ ,  $\hat{I}_{el}$ ) into time-domain.

$$V_{el}(t) = \widehat{V}_{el} e^{j\omega t} + \overline{\widehat{V}_{el}} e^{-j\omega t}$$


$$I_{el}(t) = \hat{I}_{el} e^{j\omega t} + \overline{\hat{I}_{el}} e^{-j\omega t}$$

⇓


$$V_{el}(t) = 2 |\widehat{V}_{el}| \cos(\omega t + \angle \widehat{V}_{el})$$

$$I_{el}(t) = 2 |\hat{I}_{el}| \cos(\omega t + \angle \hat{I}_{el})$$

# Example 1 continued: Low-pass filter

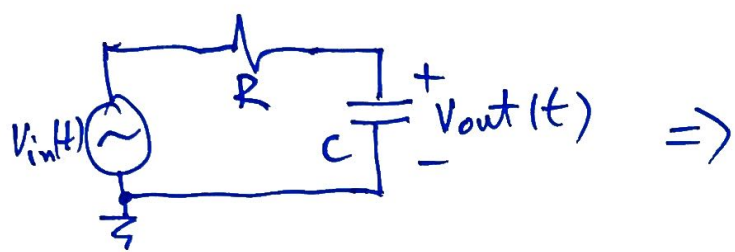

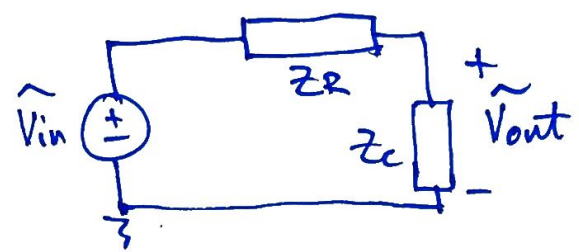$V_{in}(t) = V_{in} \cos(\omega_m t + \phi)$   
time-domain view



phasor-domain

$$\underline{\hat{V}_{out} = ?} \quad \Rightarrow \quad \underbrace{\frac{\hat{V}_{out}}{\hat{V}_{in}}}_{H_{LP}(j\omega)} = \frac{Z_C}{Z_C + Z_R}$$

$H_{LP}(j\omega)$  - transfer function

$$H_{LP}(j\omega) = \frac{Z_C}{Z_C + Z_R} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

$$H_{LP}(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$


$\omega_0 = \frac{1}{RC}$   
"cut-off" frequency

$$\hat{V}_{out} = H_{LP}(j\omega_{in}) \cdot \hat{V}_{in}$$


$$|H_{LP}(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \quad \begin{matrix} \omega \gg \omega_0 & \rightarrow & 0 \\ \omega \ll \omega_0 & \rightarrow & 1 \end{matrix}$$

$$\angle H_{LP}(j\omega) = -\text{atan2}\left(\frac{\omega}{\omega_0}, 1\right) \quad \begin{matrix} \omega \gg \omega_0 & \rightarrow & -\frac{\pi}{2} & (-90^\circ) \\ \omega \ll \omega_0 & \rightarrow & 0 & (0^\circ) \end{matrix}$$

$\omega$	$H_{LP}(j\omega)$	$ H_{LP}(j\omega) $	$\angle H_{LP}(j\omega)$
$\omega \ll \omega_0$	$\approx 1$	<u>1</u>	$\sim 0^\circ$
$0.1\omega_0$	$\frac{1}{1+j0.1}$	0.995	$-6^\circ$
$\omega_0$	$\frac{1}{1+j}$	$\frac{1}{\sqrt{2}} \approx 0.71$	$-45^\circ$
$10\omega_0$	$\frac{1}{1+j10}$	0.1	$-84^\circ$
$\omega \gg \omega_0$	$-\frac{j\omega_0}{\omega}$	$\frac{\omega_0}{\omega}$	$-90^\circ$

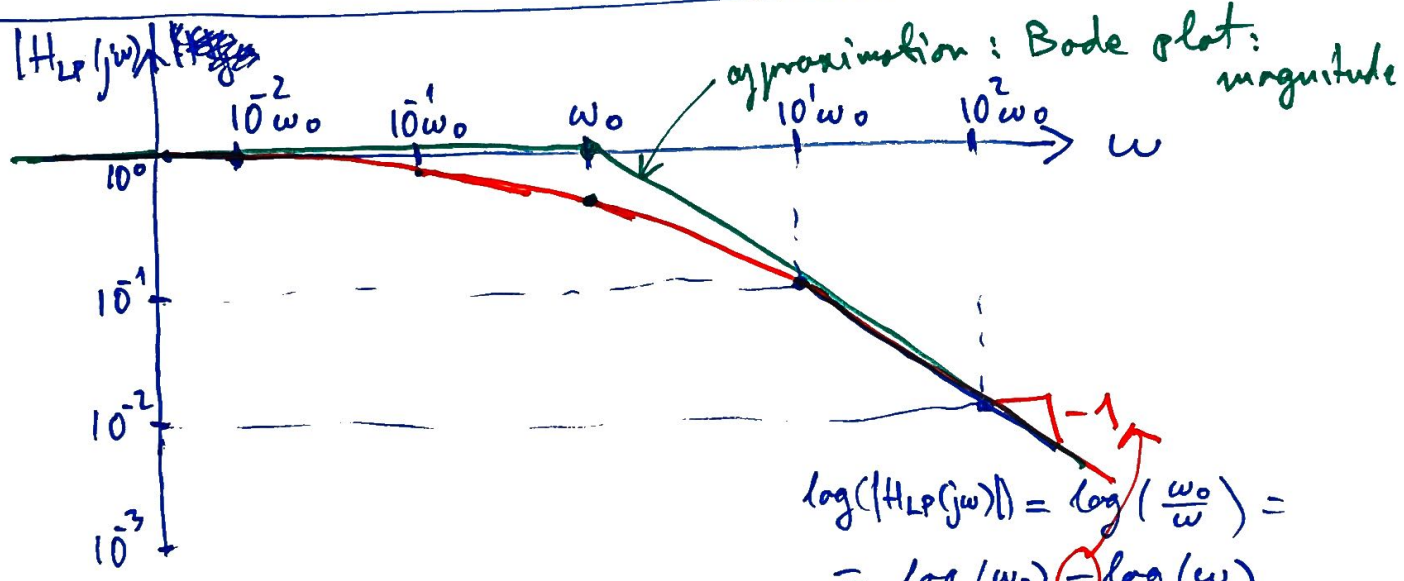

$$\log(|H_{LP}(j\omega)|) = \log\left(\frac{\omega_0}{\omega}\right) = \log(\omega_0) - \log(\omega)$$

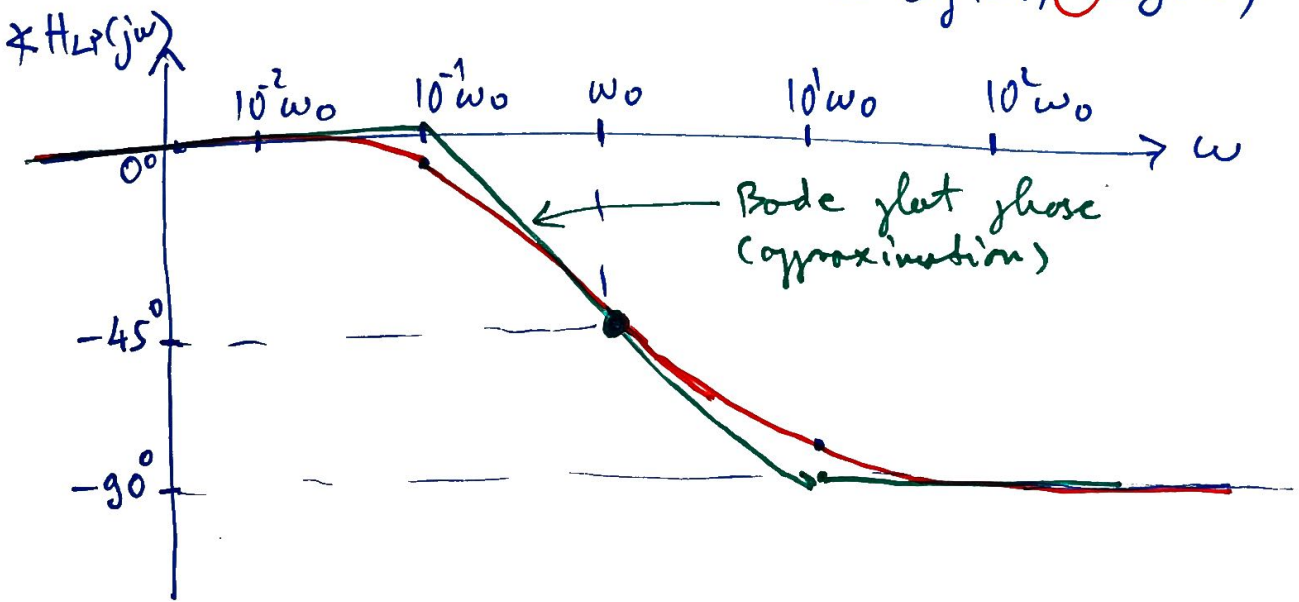



(25)

$$V_{out}(t) = \widetilde{V}_{out} e^{j\omega t} + \widetilde{V}_{out} e^{-j\omega t}$$

$$= 2 |\widetilde{V}_{out}| \cos(\omega t + \angle \widetilde{V}_{out}) \quad (1)$$

$$\widetilde{V}_{out} = H_{LP}(j\omega) \cdot \widetilde{V}_{in}$$

$$|\widetilde{V}_{out}| e^{j\angle \widetilde{V}_{out}} = |H_{LP}(j\omega)| \cdot e^{j\angle H_{LP}(j\omega)} \cdot |\widetilde{V}_{in}| \cdot e^{j\angle \widetilde{V}_{in}}$$

$$|\widetilde{V}_{out}| e^{j\angle \widetilde{V}_{out}} = |H_{LP}(j\omega)| \cdot |\widetilde{V}_{in}| e^{j(\angle H_{LP}(j\omega) + \angle \widetilde{V}_{in})}$$

$$|\widetilde{V}_{out}| = |H_{LP}(j\omega)| |\widetilde{V}_{in}| \quad @ \quad \omega = \omega_{in}$$


$$\angle \widetilde{V}_{out} = \angle \widetilde{V}_{in} + \angle H_{LP}(j\omega) \quad @ \quad \omega = \omega_{in}$$

$$V_{out}(t) = \left| 2 |H_{LP}(j\omega)| \cdot |\widetilde{V}_{in}| \cos(\omega t + \angle \widetilde{V}_{in} + \angle H_{LP}(j\omega)) \right|_{\omega = \omega_{in}}$$


for input  $V_{in}(t) = V_{in} \cos(\omega_{in} t + \phi)$

$$V_{out}(t) = 2 |H_{LP}(j\omega_{in})| |\widetilde{V}_{in}| \cos(\omega_{in} t + \phi + \angle H_{LP}(j\omega_{in}))$$

# Example 2: High-pass filter

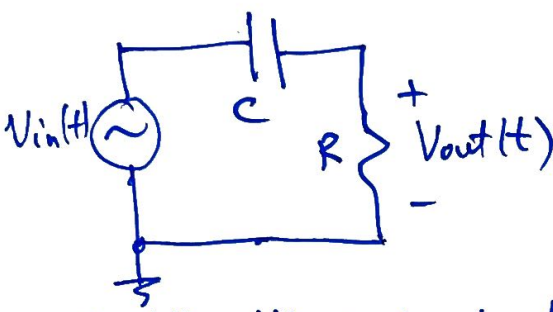

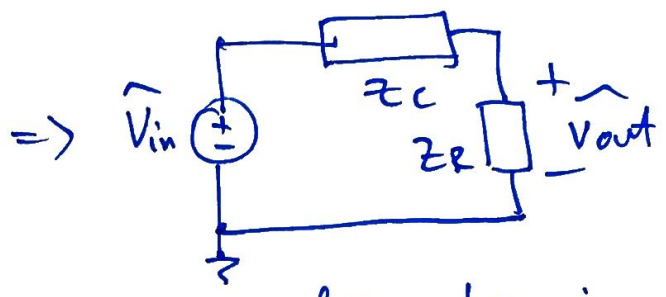$V_{in}(t) = V_{in} \cos(\omega t + \phi)$   
time-domain



phasor-domain


$$H_{HP}(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$H_{HP}(j\omega) = \frac{j\omega RC}{1 + j\omega RC}, \quad \omega_0 = \frac{1}{RC} \quad \text{"cut-off" frequency}$$


$$H_{HP}(j\omega) = \frac{j\frac{\omega}{\omega_0}}{1 + j\frac{\omega}{\omega_0}} = \frac{1}{1 - j\frac{\omega_0}{\omega}}$$

$$|H_{HP}(j\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega_0}{\omega})^2}}$$


$\xrightarrow{\omega \gg \omega_0} 1$   
 $\xrightarrow{\omega \ll \omega_0} 0 \left(\frac{\omega}{\omega_0}\right)$

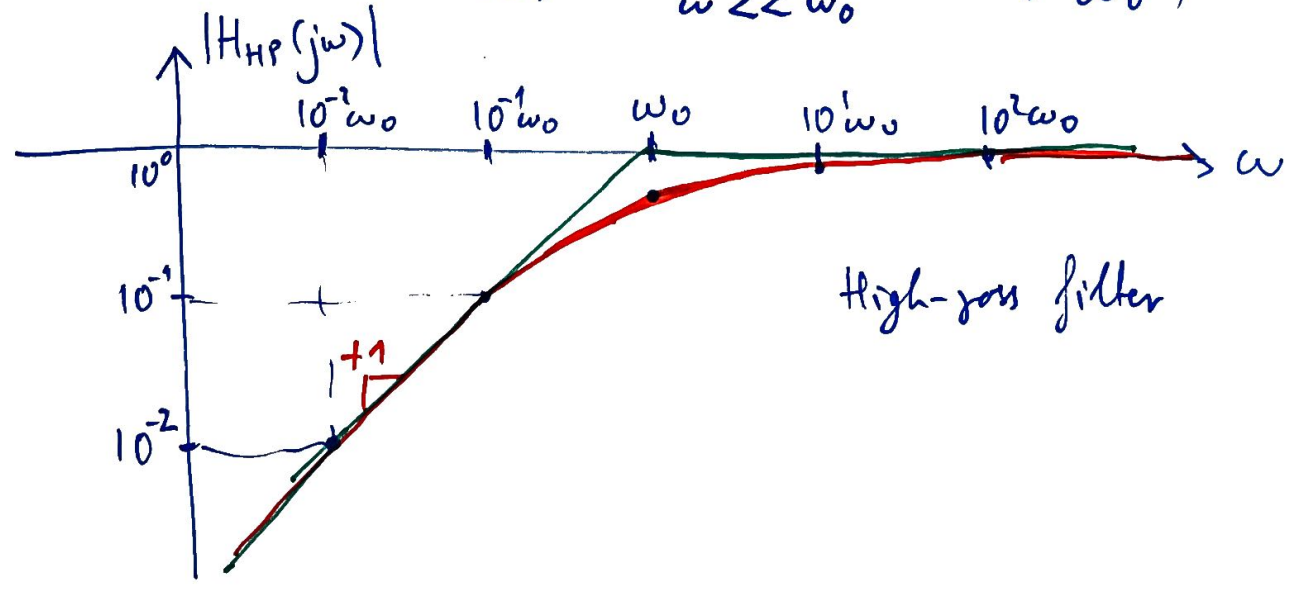

In 16A:

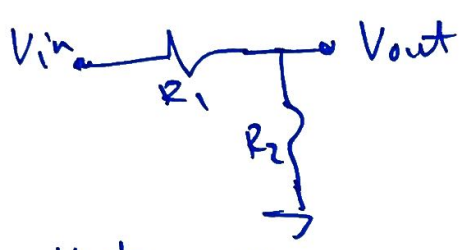


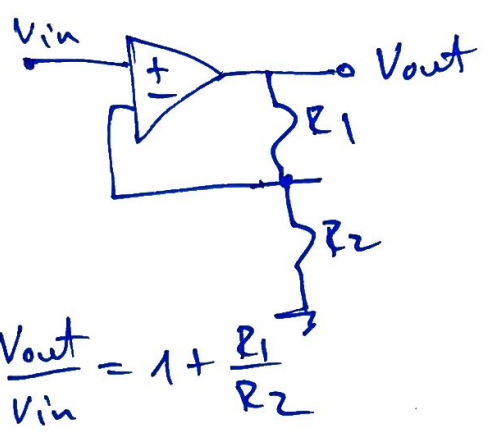
$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$



$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

"Operetas" : Transfer functions

16B:



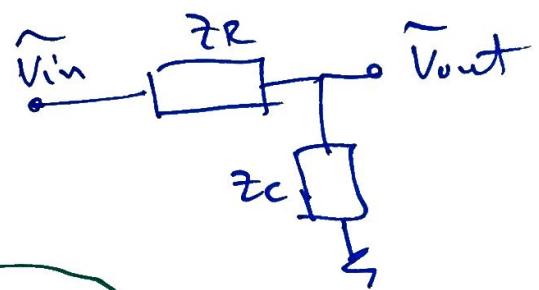
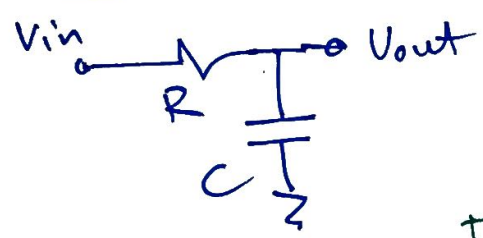


$$\frac{\tilde{V}_{out}}{\tilde{V}_{in}} = H(j\omega) = \frac{z_C}{z_C + z_R}$$

transfer function

How do we cascade circuits in a tractable way to build more complex transfer functions?

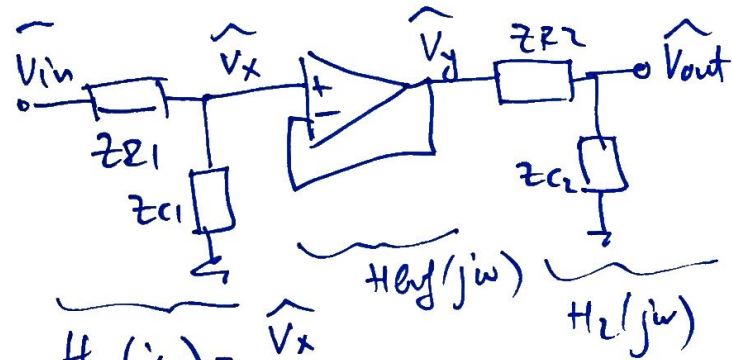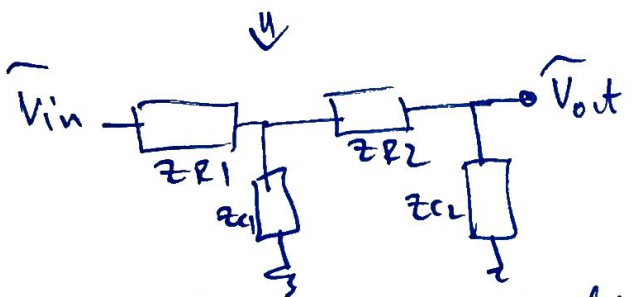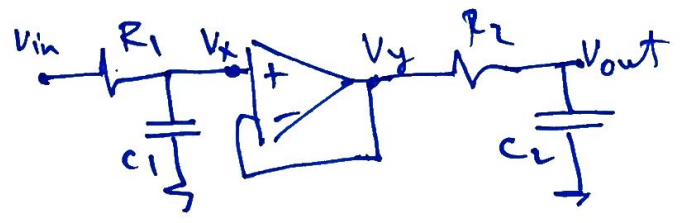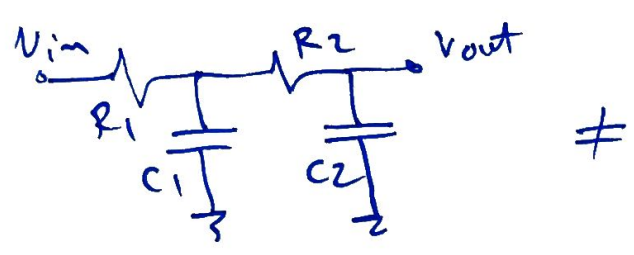Circuit blocks should not "load" (i.e. take current from) each other in order to preserve the transfer function.



Need to solve the full circuit to find  $\frac{\widehat{V}_{out}}{\widehat{V}_{in}} = H(j\omega)$

$$H_1(j\omega) = \frac{\widehat{V}_x}{\widehat{V}_{in}}$$

$$H_{buf}(j\omega) = \frac{\widehat{V}_y}{\widehat{V}_x} = 1$$

$$H_2(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_y}$$

$$H(j\omega) = \frac{\widehat{V}_{out}}{\widehat{V}_{in}} = \underbrace{\frac{\widehat{V}_{out}}{\widehat{V}_y}}_{H_2(j\omega)} \cdot \underbrace{\frac{\widehat{V}_y}{\widehat{V}_x}}_{H_{buf}(j\omega)} \cdot \underbrace{\frac{\widehat{V}_x}{\widehat{V}_{in}}}_{H_1(j\omega)}$$

$$H_1(j\omega) = \frac{Z_{C1}}{Z_{C1} + Z_{R1}}$$

$$H_2(j\omega) = \frac{Z_{C2}}{Z_{C2} + Z_{R2}}$$

$$H_1(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{01}}}$$

$$\omega_{01} = \frac{1}{R_1 C_1}$$

$$H_2(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_{02}}}$$


$$\omega_{02} = \frac{1}{R_2 C_2}$$



$$H(j\omega) = H_1(j\omega) \cancel{H_{\text{eff}}(j\omega)} H_2(j\omega)$$

$$= \frac{1}{1 + j\frac{\omega}{\omega_{01}}} \cdot \frac{1}{1 + j\frac{\omega}{\omega_{02}}}$$

In general:

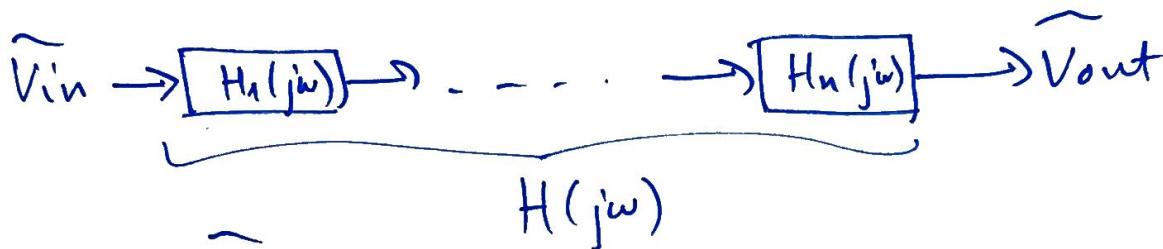

$$H(j\omega) = \frac{\widehat{V_{out}}}{\widehat{V_{in}}} = H_1(j\omega) \cdot \dots \cdot H_n(j\omega) \quad , \quad H_i(j\omega) = |H_i(j\omega)| e^{j\angle H_i(j\omega)}$$

$$H(j\omega) = \underbrace{|H_1(j\omega)| \cdot \dots \cdot |H_n(j\omega)|}_{|H(j\omega)|} e^{j(\angle H_1(j\omega) + \dots + \angle H_n(j\omega))} = |H(j\omega)| e^{j\angle H(j\omega)}$$

time domain :  $(V_{in}(t) = V_{in} \cos(\omega_{in}t + \phi))$

$$V_{out}(t) = |H(j\omega = \omega_{in})| \cdot 2 |\widehat{V_{in}}| \cos(\omega_{in}t + \angle \widehat{V_{in}} + \angle H(j\omega_{in}))$$

$$V_{out}(t) = |H(j\omega = \omega_{in})| V_{in} \cos(\omega_{in}t + \phi + \angle H(j\omega_{in}))$$