

EE 16B Midterm 1, February 15, 2017

Name: _____

SID #: _____

Discussion Section and TA: _____

Discussion Section and TA: _____

Lab Section and TA: _____

Name of left neighbor: _____

Name of right neighbor: _____

Important Instructions:

Show your work. An answer without explanation is not acceptable and does not guarantee any credit.

Only the front pages will be scanned and graded. Back pages won't be scanned; you can use them as scratch paper.

Do not remove pages, as this disrupts the scanning. Instead, cross the parts that you don't want us to grade.


| PROBLEM | MAX |
|----------------|------------|
| 1 | 20 |
| 2 | 20 |
| 3 | 15 |
| 4 | 30 |
| 5 | 15 |

“Well, Diotallevi and I are planning a reform in higher education. A School of Comparative Irrelevance, where useless or impossible courses are given. The school's aim is to turn out scholars capable of endlessly increasing the number of unnecessary subjects.”

– Umberto Eco, *Foucault's Pendulum*

Problem 1 Warm up (20 points)

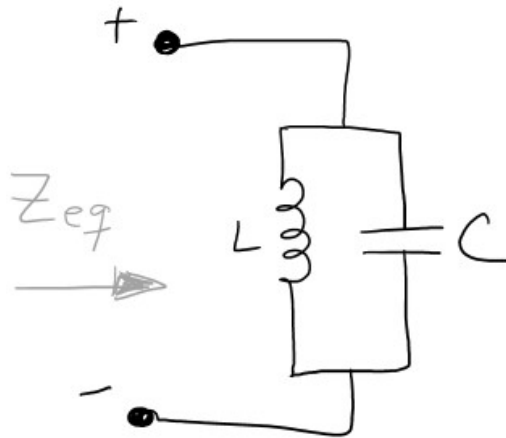a) Consider the following circuit. Z_{eq} is the impedance looking into the circuit from the left, as shown. Provide an expression for Z_{eq} .



$$Z_{eq} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$Z_{eq} = Z_L \parallel Z_C = j\omega L \parallel \frac{1}{j\omega C}$$

$$= \frac{j\omega L \left(\frac{1}{j\omega C}\right)}{j\omega L + \frac{1}{j\omega C}} = \frac{\frac{j\omega L}{j\omega C}}{\frac{j^2 \omega^2 LC + 1}{j\omega C}}$$

$$= \frac{j\omega L}{1 + j^2 \omega^2 LC} = \frac{j\omega L}{1 - \omega^2 LC}$$

b) If this impedance is driven by a sinusoidal source at frequency, ω [rad/s], for what ω is $Z_{eq} = \infty$?

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\frac{j\omega L}{1 - \omega^2 LC} \rightarrow \infty \quad \text{when the denominator} \rightarrow 0$$


$$1 - \omega^2 LC = 0$$

$$\omega^2 LC = 1$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega = \frac{1}{\sqrt{LC}}$$

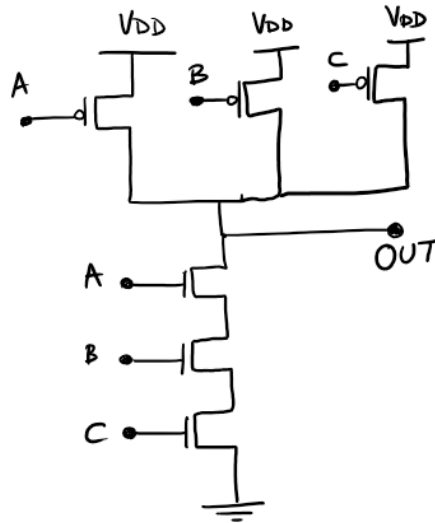c) What logic function does the following circuit perform?



$$OUT = (A \text{ and } B \text{ and } C)$$

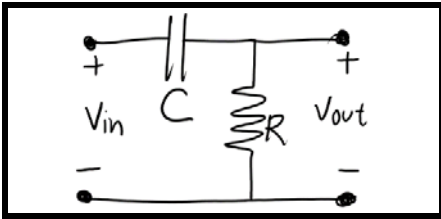d) Consider the following four circuits. For each, we define the voltage transfer function, $H_V(\omega) = V_{out}/V_{in}$. With respect to $H_V(\omega)$, circle what class of frequency response each circuit performs.



Lowpass filter

Highpass filter

Bandpass filter


Bandstop filter

$$Z_C \rightarrow \infty \text{ as } \omega \rightarrow 0$$

$$Z_C \rightarrow 0 \text{ as } \omega \rightarrow \infty$$

$$\omega \rightarrow 0$$

$$\omega \rightarrow \infty$$

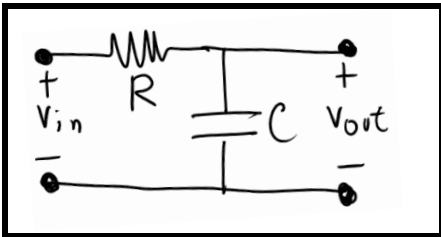


Lowpass filter

Highpass filter

Bandpass filter

Bandstop filter

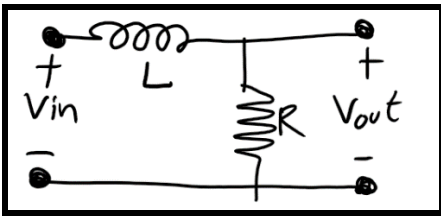

Lowpass filter

Highpass filter

Bandpass filter


Bandstop filter

$$Z_L \rightarrow \infty \text{ as } \omega \rightarrow \infty$$

$$Z_L \rightarrow 0 \text{ as } \omega \rightarrow 0$$

$$\omega \rightarrow \infty$$

$$\omega \rightarrow 0$$

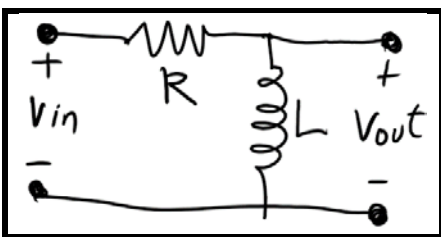

Lowpass filter

Highpass filter

Bandpass filter

Bandstop filter


(extra space)

"You can tell you've found a really interesting question when nobody wants you to answer it."

— James S.A. Corey, *Nemesis Games*

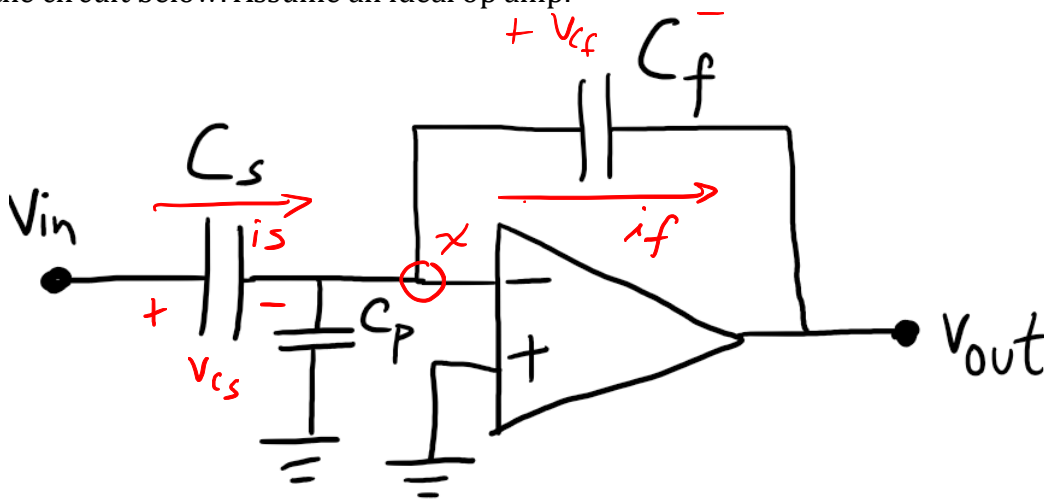Problem 2 (20 points)

Consider the circuit below. Assume an ideal op amp.



a) Find an expression that relates the derivative of v_{out} (dv_{out}/dt) to the input voltage (v_{in}) and/or its derivative (dv_{in}/dt).

$$\frac{dv_{out}}{dt} = -\frac{C_s}{C_f} \frac{dv_{in}}{dt} = -\frac{1}{5} \cdot 5 = -1$$

b) Now given that $C_s = 1 \text{ nF}$, $C_f = 5 \text{ nF}$, $C_p = 1 \text{ nF}$, $v_{cf}(t < 0) = v_{cs}(t < 0) = 0$ and $v_{in}(t \geq 0) = 5 \cdot t$ [volts], provide an expression for $V_{out}(t)$ for $t \geq 0$.

$$V_x = 0$$

$$i_s = i_f \quad i_s = C_s \frac{dv_s}{dt} = C_s \frac{dv_{in}}{dt}$$


$$i_f = -C_f \frac{dv_{out}}{dt}$$

$$C_s \frac{dv_{in}}{dt} = -C_f \frac{dv_{out}}{dt}$$

$$\frac{dv_{out}}{dt} = -\frac{C_s}{C_f} \frac{dv_{in}}{dt}$$

C_p does nothing as both terminals are at the same potential.

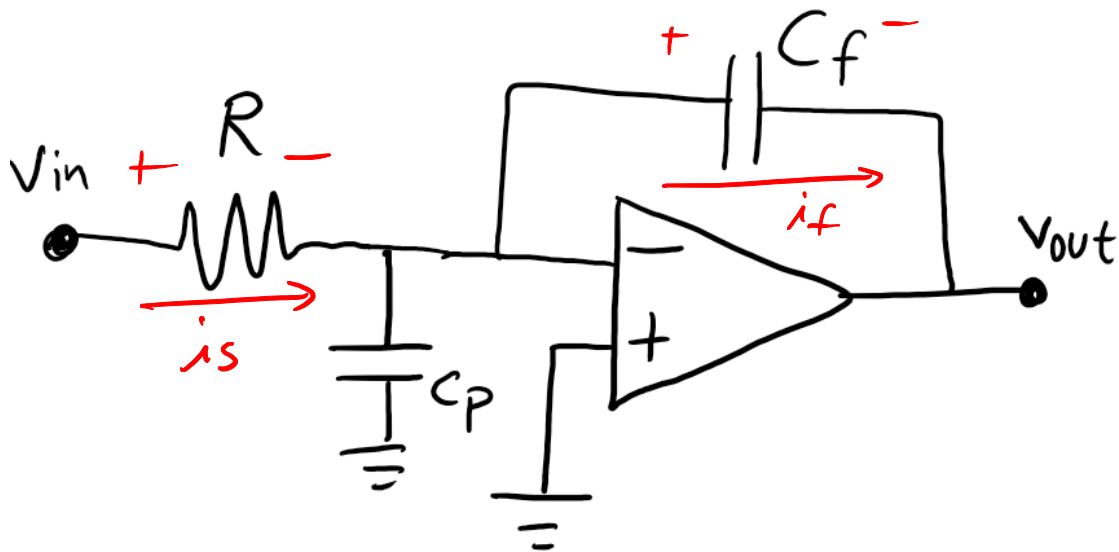Consider now the different circuit below. Assume an ideal op amp.



c) Provide a symbolic expression for $V_{out}(t)$ for $t \geq 0$.

$$V_{out}(t) = - \frac{\int v_{in} dt}{RC}$$

d) Assume $v_{in}(t \geq 0) = 5 \cdot t$ [volts] and $v_{cf}(t < 0) = 0$. What is the value of $V_{out}(t)$ at $t = 1$ s?

$$V_{out}(t) = - \frac{5}{2} \cdot \frac{1}{RC}$$

$$i_s = i_f$$

$$\frac{V_{in}}{R} = -C \frac{dv_{out}}{dt}$$

$$\frac{dv_{out}}{dt} = \left(-\frac{1}{RC} \right) v_{in}$$

$$V_{out} = \frac{-\int v_{in} dt}{RC}$$


(extra space)

$$\int_0^1 5t \, dt = \left. \frac{5t^2}{2} \right|_0^1 = \frac{5}{2}$$

“One should never mistake pattern for meaning.”
– Iain Banks, *The Hydrogen Sonata*

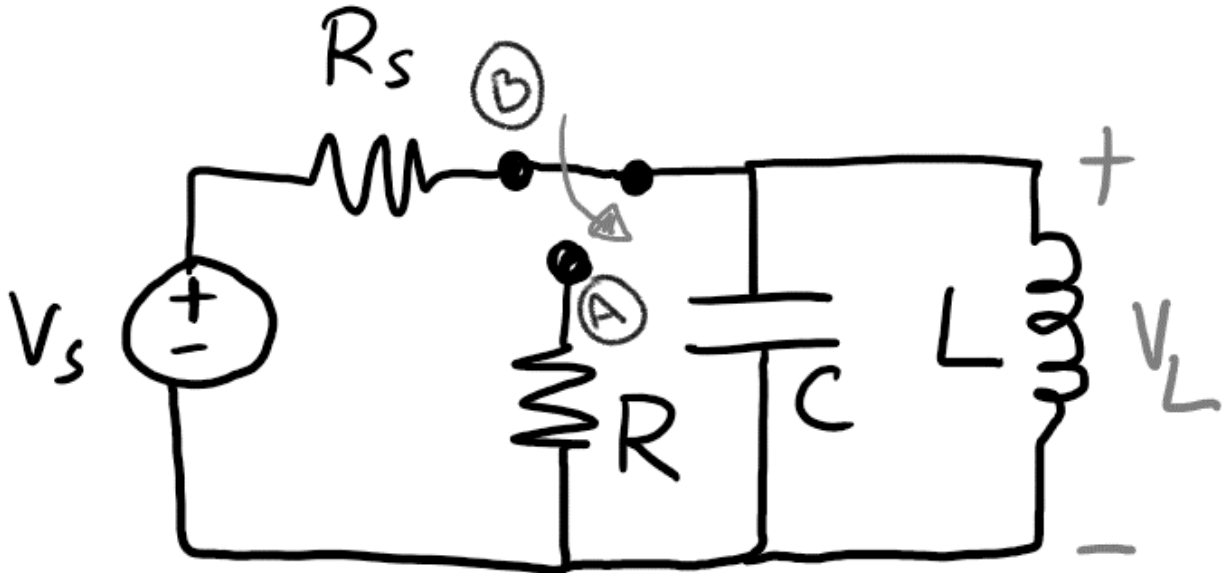
Problem 3 (15 points)

The following circuit is part of a near field communication system. A realistic voltage source (V_s , R_s) is connected through a switch onto a three component circuit. The inductor represents an antenna; the voltage across it modulates how much energy is radiated away from the system. The switch alternates continuously between position A and position B; it has been doing this since $t = -\infty$. It spends π microseconds at each position.



We want the voltage on the inductor, V_L , to follow the curve plotted below. Specifically, we want to fulfill the following condition.

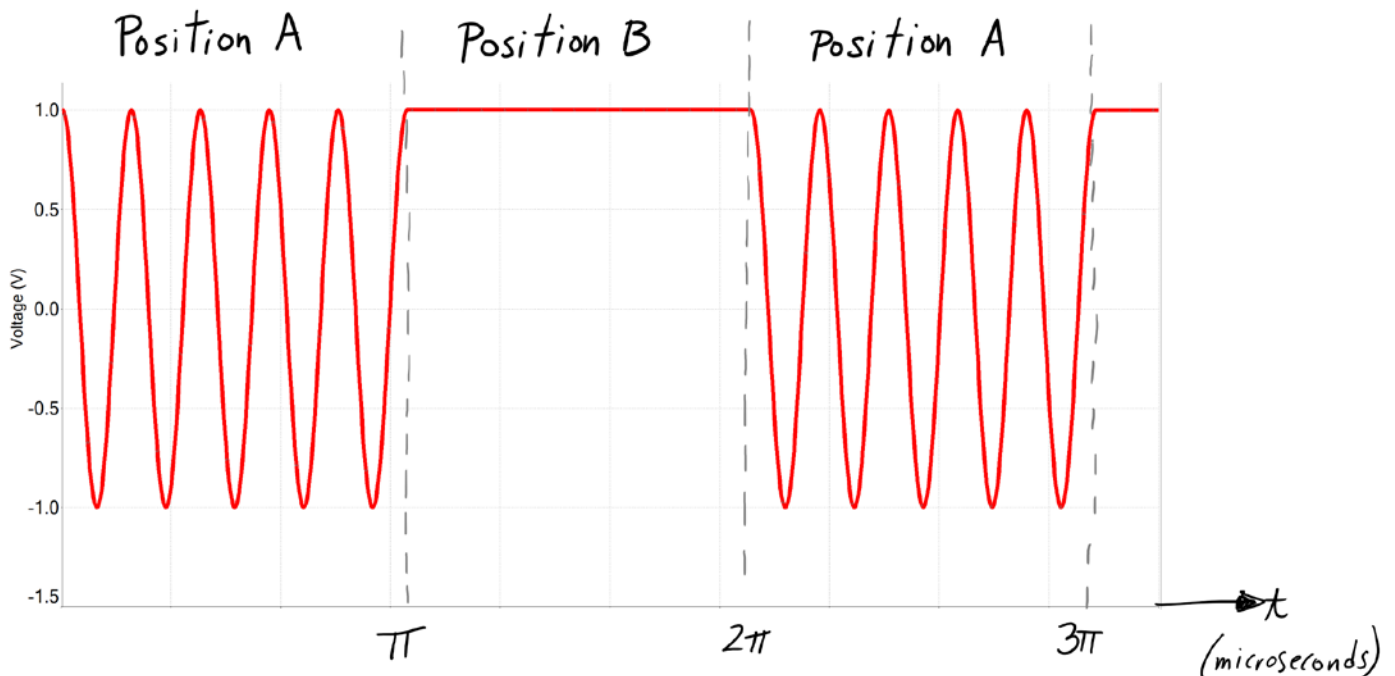Condition: The inductor voltage should oscillate 5 times during period when the switch is in position A.



Plot of V_L as a function of time with switch positions labeled. **Note the units of time (10^{-6} seconds)!**

a) If $R \rightarrow \infty$ and L is non-zero and known, provide an expression for C such that the above condition is met. (Reminder: the condition is that the inductor voltage should oscillate 5 times during period when the switch is in position A.)

$$C = \frac{1}{10^{14} L} \quad [F]$$

If $R \rightarrow \infty$, LC circuit will oscillate at

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \frac{1}{\sqrt{LC}} = 10^7; \quad \frac{1}{LC} = 10^{14}$$

$$C = \frac{1}{10^{14} L}$$

$$\omega_0 = 2\pi f_0 = \frac{(2\pi)5}{\pi 10^6} = 10^7 \text{ rad/s}$$

b) Unfortunately, a colleague tells you that $R \neq \infty$; if L and C are known, provide an expression for R such that the above condition is met. (Reminder: the condition is that the inductor voltage should oscillate 5 times during period when the switch is in position A.)

$$R = \left(\frac{L}{4C(1 - 10^{14} LC)} \right)^{1/2}$$

If $R \neq \infty$, then the circuit will oscillate

$$\text{at } \omega_D = \sqrt{\omega_0^2 - \alpha^2} \quad \text{where } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{and } \alpha = \frac{1}{2RC}$$

$$10^7 = \sqrt{\frac{1}{LC} - \frac{1}{4R^2 C^2}}$$

$$10^{14} = \frac{1}{LC} - \frac{1}{2R^2 C^2}$$



(extra space)

$$10^{14} = \frac{4R^2C^2 - LC}{(4R^2C^2)(LC)}$$

$$10^{14} = \frac{(4R^2C - L)C}{(4R^2C^2L)C}$$

$$= \frac{4R^2C - L}{4R^2C^2L}$$

$$4 \cdot 10^{14} R^2 C^2 L = 4R^2 C - L$$

$$(4 \cdot 10^{14} C^2 L - 4C) R^2 = -L$$

$$(4C - 4 \cdot 10^{14} C^2 L) R^2 = L$$

$$R^2 = \frac{L}{4(C - 10^{14} C^2 L)}$$


$$R = \left(\frac{L}{4C(1 - 10^{14} LC)} \right)^{1/2}$$

“Chang Tzu tells us of a persevering man who after three laborious years mastered the art of dragon-slaying. For the rest of his days, he had not a single opportunity to test his skills.”

— Jorge Luis Borges, *The Book of Imaginary Beings*

Problem 4 (30 points)

Consider the circuit below.

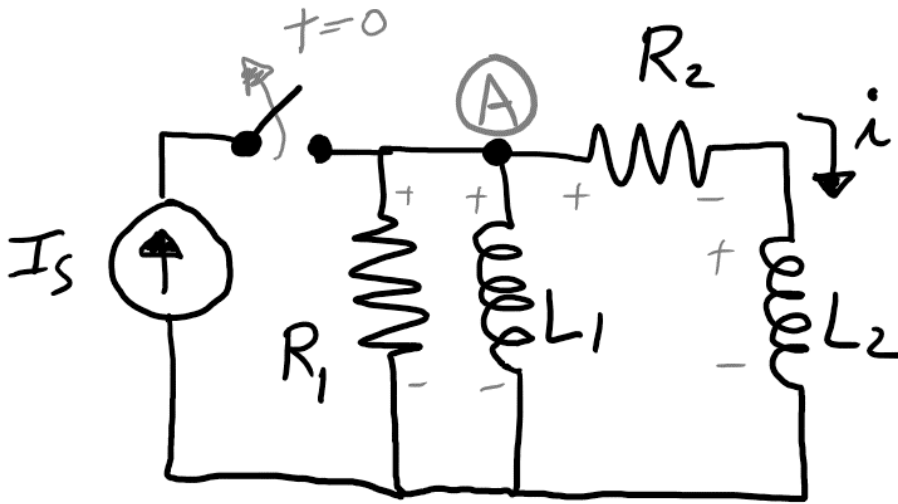

a) What is $i(0)$?

Hint. What is the current flowing through L_1 before the switch opens? Consequently, what is the current flowing through L_2 ?

Solution. Because inductors behave like shorts to direct current, the current flowing through L_1 is I_S . Since all the current is flowing through L_1 , it must mean that the current flowing through L_2 is 0 from KCL.

b) What is $di/dt(0)$?

$$\begin{aligned}
 i_{L_1}(0^-) &= I_S \\
 i_{L_2}(0^-) &= 0 \\
 V_{R_1} &= -I_S R_1 = V_{L_1} = V_{L_2} \\
 V &= L \frac{di}{dt} \quad \therefore \frac{di_{L_1}}{dt} = \frac{-I_S R_1}{L_1} \\
 & \quad \frac{di_{L_2}}{dt} = \frac{-I_S R_1}{L_2}
 \end{aligned}$$

c) What is the relationship between the voltages across L_1 and R_1 ?

Solution. They are the same.

d) Use KCL on Node A and the relationship derived above to arrive at a differential equation of the form,

$$\frac{d^2 i}{dt^2}(t) + a_1 \frac{di}{dt}(t) + a_0 i(t) = 0$$

where $i(t)$ is the current going through L_2 .

Solution. Let the current going through R_1 be i_0 and the current going through L_1 be i_1 . Then,

$$i_0 + i_1 + i = 0 \implies \frac{di_0}{dt} + \frac{di_1}{dt} + \frac{di}{dt} = 0$$

This means that,

$$\frac{di_0}{dt} = -\frac{di}{dt} - \frac{V_{L_1}}{L_1}$$

or,

$$\frac{di_0}{dt} = -\frac{di}{dt} - i \frac{R_2}{L_1} + \frac{L_2}{L_1} \frac{di}{dt}$$

Now, taking the derivative with respect to time of,

$$V_{L_1} = V_{R_2} + V_{L_2}$$

we get,

$$R_1 \frac{di_0}{dt} = R_2 \frac{di}{dt} + L_2 \frac{d^2 i}{dt^2}$$

Plugging in the expression for $\frac{di_0}{dt}$, we get,

$$a_1 = \frac{R_2}{L_2} + \frac{R_1}{L_2} + \frac{R_1}{L_1} \text{ and } a_0 = \frac{R_1 R_2}{L_1 L_2}$$

e) Let $R_1 = R_2 = R$ and $L_1 = L_2 = L$. Recall that the above differential equation can be reshaped into the following linear algebra problem:

$$\begin{bmatrix} \frac{di}{dt} \\ \frac{d^2 i}{dt^2} \end{bmatrix} = A \begin{bmatrix} i \\ \frac{di}{dt} \end{bmatrix}$$

What is the A matrix and what are its eigenvalues?

Solution. We have,

$$\begin{bmatrix} 0 & 1 \\ -a_0 & -a_1 \end{bmatrix}$$

with,

$$a_1 = \frac{3R}{L} \text{ and } a_0 = \frac{R^2}{L^2}$$

This tells us that the eigenvalues are,

$$\lambda = \frac{R}{2L} (-3 \pm \sqrt{5})$$

f) Will this circuit exhibit any oscillations?


Solution. The eigenvalues we calculated does not have any imaginary terms, so no.

(extra space)

"I am Groot."
 - Groot, *Guardians of the Galaxy*

Problem 5 (15 points)

Consider the circuit below.

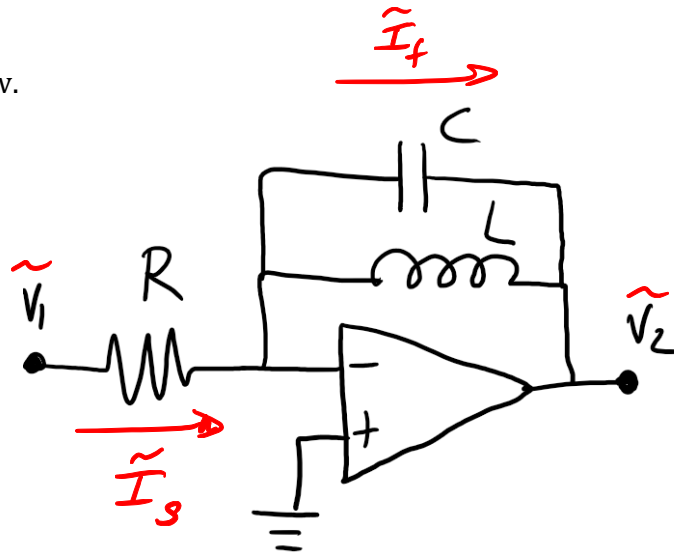

a) Given an input voltage, $v_1(t)$, which is a sinusoid at frequency ω , and phasors corresponding to the input and output voltages, V_1 and V_2 , find an expression for V_2/V_1 .

$$\frac{V_2}{V_1} = \frac{-j\omega L}{R - \omega^2 RLC}$$

$$\tilde{I}_s = \tilde{I}_f$$

$$Z_f = \frac{j\omega L}{1 - \omega^2 LC}$$

$$\frac{\tilde{V}_1}{R} = \frac{-\tilde{V}_2}{Z_f}$$

$$\frac{\tilde{V}_2}{\tilde{V}_1} = -\frac{Z_f}{R} = \boxed{\frac{-j\omega L}{R - \omega^2 RLC}}$$

b) If $v_1(t) = \cos(\omega t)$ where $\omega = 10^6$ rad/s and $L = 1 \mu\text{H}$, $R = 1 \Omega$, and $C = 0.5 \mu\text{F}$, solve for $v_2(t)$.

$$v_2(t) = -2 \cos\left(\omega t + \frac{\pi}{2}\right)$$

$$\tilde{V}_2 = \left(\frac{-j\omega L}{R - \omega^2 RLC} \right) \tilde{V}_1$$

$$\tilde{V}_1 = 1$$

$$= - \left(\frac{j 10^6 10^{-6}}{1 - 10^{12} (1) (10^{-6}) (0.5 \times 10^{-6})} \right)$$

$$= \frac{-j}{1 - (0.5)} = \textcircled{-2j}$$

$$\tilde{V}_2 = -2j = -2e^{j\pi/2}$$

$$v_2(t) = -2 \cos\left(\omega t + \frac{\pi}{2}\right)$$