

SID# _____

**EE 16B Midterm 1
Spring 2018**

Name: _____

SID #: _____

(after the exam begins add your SID# in the top right corner of each page)

Discussion Section and TA: _____

Discussion Section and TA: _____

Lab Section and TA: _____

Name of left neighbor: _____

Name of right neighbor: _____

Instructions:

Show your work. An answer without explanation is not acceptable and does not guarantee any credit.


Only the front pages will be scanned and graded. Back pages won't be scanned; you can use them as scratch paper.

Do not remove pages, as this disrupts the scanning. If needed, cross out any parts that you don't want us to grade.

PROBLEM	MAX
1	15
2	25
3	15
4	20
5	25

Problem 1 Warm up (15 points)


a) Consider the following circuit.

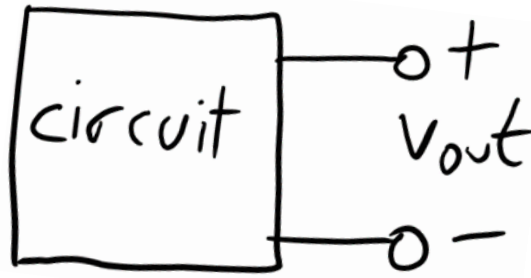a) For $t \geq 0$, the following equation applies to $v_{out}(t)$. In addition, $v_{out}(0) = V_0$ and $\frac{dv_{out}}{dt} = 0$ at $t=0$.

$$\frac{d^2 v_{out}}{dt^2} + A \frac{dv_{out}}{dt} + B v_{out} = 0$$

If $A < 2\sqrt{B}$, provide an expression for $v_{out}(t) \geq 0$. (5 points)**Solution:** $v_{out}(t) =$

b) Consider the circuit below.

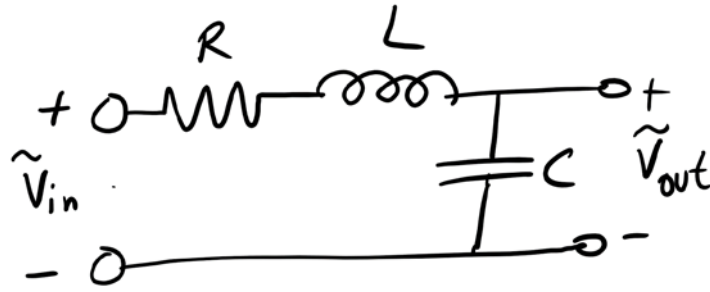


What is $\tilde{\mathbf{H}}_{\text{out}}(\omega) = \frac{\tilde{V}_{\text{out}}(\omega)}{\tilde{V}_{\text{in}}(\omega)}$ for $\omega \rightarrow \infty$? (5 points)

Solution:

$$\tilde{\mathbf{H}}_{\text{out}}(\omega \rightarrow \infty) =$$

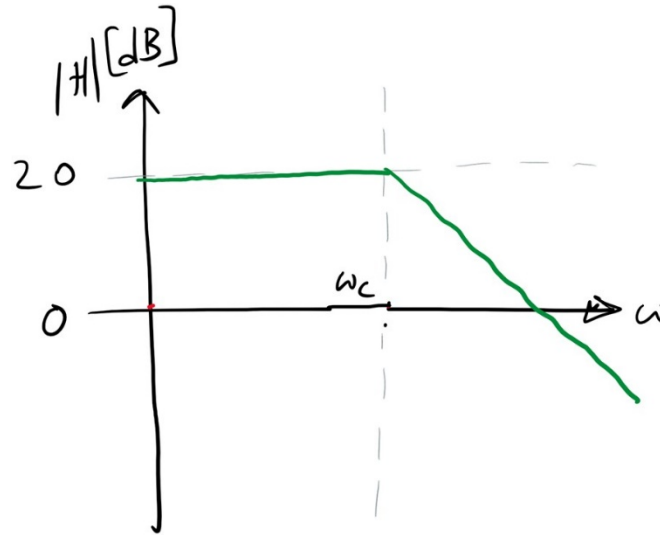c) Consider the Bode plot below. (5 points)



This is a Bode magnitude plot of the transfer function $\tilde{\mathbf{H}}(\omega)$. The expression for $\tilde{\mathbf{H}}(\omega)$ is shown below.

$$\tilde{\mathbf{H}}(\omega) = \frac{\tilde{\mathbf{H}}_x(\omega)}{1 + j\left(\frac{\omega}{\omega_c}\right)}$$


What is $\tilde{\mathbf{H}}_x(\omega)$?

Solution:

$$\tilde{\mathbf{H}}_x(\omega) =$$

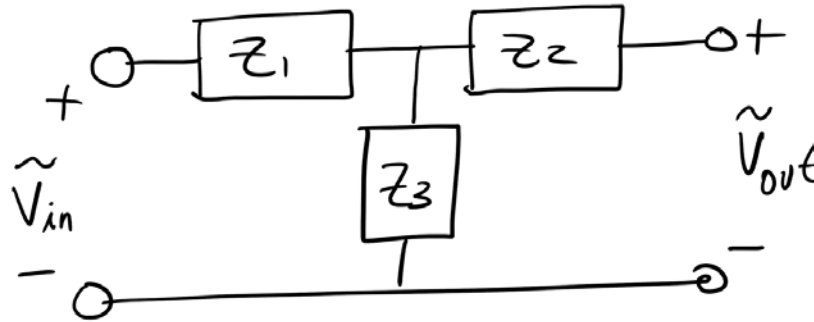Problem 2 *H's and Bodes...* (25 points)

Consider the circuit below. There is nothing connected to the V_{out} terminal. (5 points)



a) Provide an expression for $\tilde{\mathbf{H}}_{out}(\omega) = \frac{\tilde{V}_{out}(\omega)}{\tilde{V}_{in}(\omega)}$

Solution:

$$\tilde{\mathbf{H}}_{out}(\omega) =$$


b) For this part of the problem, assume you have ONE capacitor, ONE inductor and ONE resistor. If $\mathbf{Z}_2 = \mathbf{0}$ for all ω , which components would you choose for \mathbf{Z}_1 and \mathbf{Z}_3 such that the filter response is a passive low pass filter with a slope of -20 dB/decade for frequencies beyond a single cutoff frequency? **(5 points)**

Solution:

Circle ONE component to go into the \mathbf{Z}_1 box: **Capacitor** **Inductor** **Resistor**

Circle ONE component to go into the \mathbf{Z}_3 box: **Capacitor** **Inductor** **Resistor**

c) Consider the following circuit:

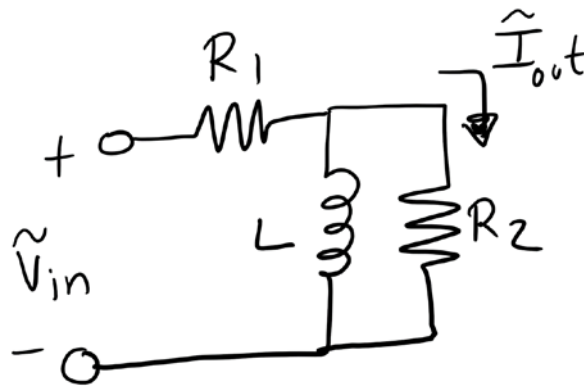

We define a transfer function $\tilde{\mathbf{H}}_{out}(\omega) = \frac{\tilde{\mathbf{I}}_{out}(\omega)}{\tilde{\mathbf{V}}_{in}(\omega)}$.

LOOK AT THE DEFINITION OF THE TRANSFER FUNCTION CAREFULLY.


Provide an expression in canonical form for $\tilde{\mathbf{H}}_{out}(\omega)$. (10 points)

Solution:


$$\tilde{\mathbf{H}}_{out}(\omega) =$$

d) If $L = 1 \text{ H}$ and $R_1 = R_2 = 1 \ \Omega$, provide below magnitude and phase Bode plots for $\tilde{\mathbf{H}}_{\text{out}}(\omega)$. (5 points)

Magnitude

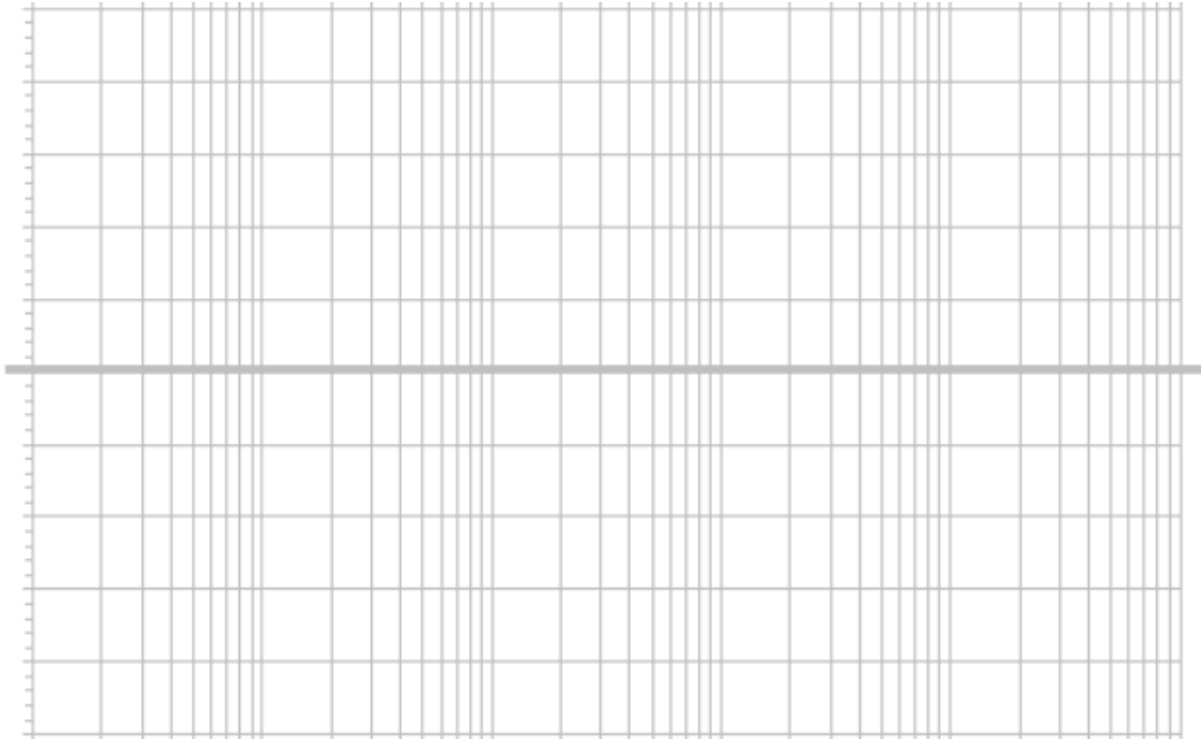


Phase

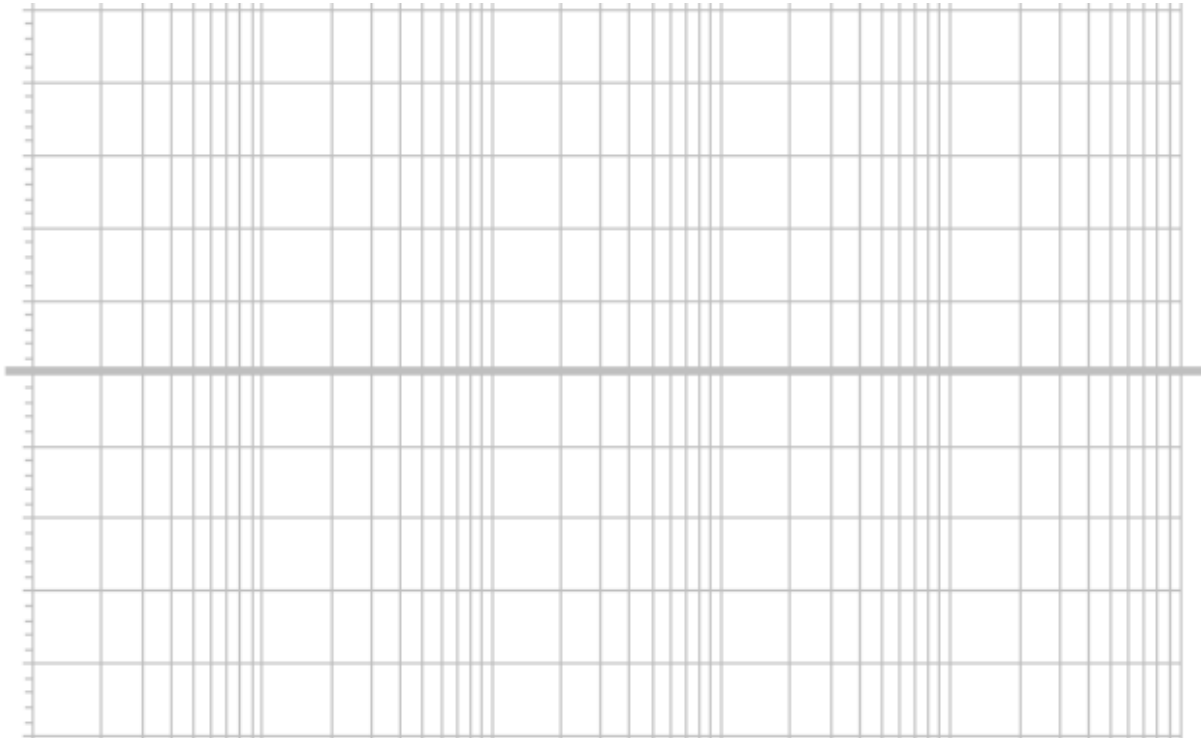

Problem 3 Transistors and RC's (15 points)

Consider the circuit below.

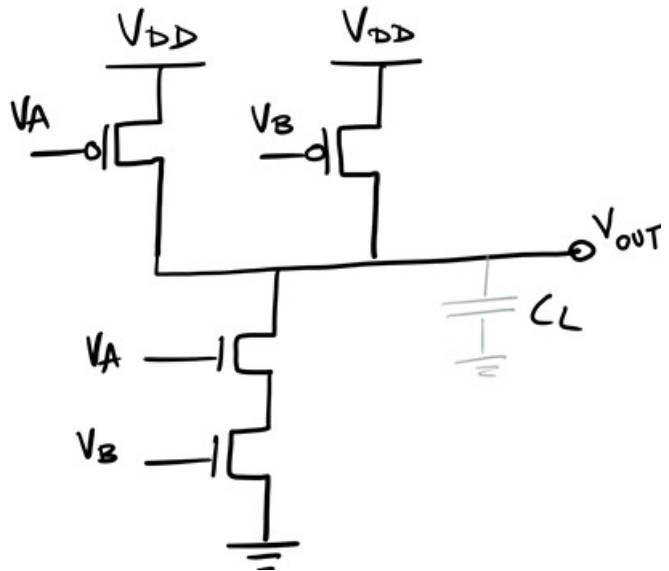

a) Fill in the truth table below for the circuit above. V_A , V_B and V_{out} are digital voltages that can only assume values of 0 or V_{DD} . (5 points)

V_A	V_B	V_{out}
0	0	
0	V_{DD}	
V_{DD}	0	
V_{DD}	V_{DD}	

For this part, assume that $V_A = V_B = V_{DD}$ for $-\infty < t < 0$. At $t=0$, V_A and V_B switch instantly from V_{DD} to 0. Assume all transistors behave as resistors with the same value, R , if in the ON state and that all capacitances are already accounted for in the circuit above.

b) Provide an expression for $V_{out}(t \geq 0)$. **(10 points)**

Solution:

b) Solve for $v_{OUT}(t)$ if $i_{IN}(t) = I_0 \cos(\omega t)$ and $V_{DD} = 0$ V. **(10 points)**


Solution:

c) Solve for $v_{OUT}(t)$ if $i_{IN}(t) = I_0 \cos(\omega t)$ and $V_{DD} =$ a non-zero constant. **(5 points)**

Solution:

Problem 5 (25 points)

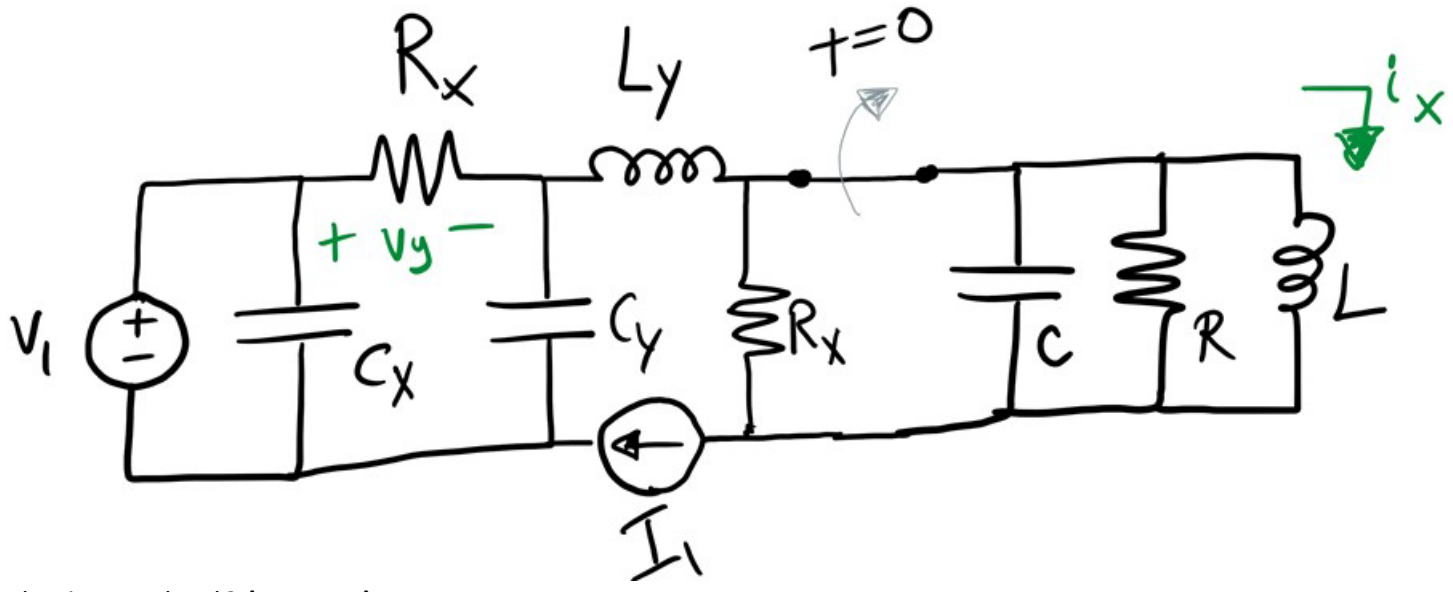a) Consider the following circuit. The switch is closed for $t < 0$, then opens at $t = 0$. Both of the independent sources have a DC value (i.e. they do not change with time).



a) What is $i_x(t < 0)$? (5 points)

Solution:

b) What is $v_y(t < 0)$? (5 points)

Solution:

c) Provide an equation in the variable $i_x(t)$ that, when solved, would provide an expression for $i_x(t)$ for $t \geq 0$.
DO NOT SOLVE THE EQUATION. (10 points)

Solution:

d) If $C_x = C_y = C = 1$ F and $R_x = R = 1$ Ω and $L_y = L = 1$ H, provide an expression for $i_x(t)$ for $t \geq 0$. (5 points)

Solution:

$i_x(t) =$

Extra Space

SID# _____

Factor	Bode Magnitude	Bode Phase
Constant K	$20 \log K$ 0 dB	$\pm 180^\circ$ if $K < 0$ 0° if $K > 0$
Zero @ Origin $(j\omega)^N$	slope = $20N$ dB/decade 0 dB	$(90N)^\circ$ 0°
Pole @ Origin $(j\omega)^{-N}$	slope = $-20N$ dB/decade 0 dB	$(-90N)^\circ$ 0°
Simple Zero $(1 + j\omega/\omega_c)^N$	slope = $20N$ dB/decade 0 dB	$(90N)^\circ$ 0°
Simple Pole $\left(\frac{1}{1 + j\omega/\omega_c}\right)^N$	slope = $-20N$ dB/decade 0 dB	$(-90N)^\circ$ 0°
Quadratic Zero $[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N$	slope = $40N$ dB/decade 0 dB	$(180N)^\circ$ 0°
Quadratic Pole $\frac{1}{[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N}$	slope = $-40N$ dB/decade 0 dB	$(-180N)^\circ$ 0°

Contributors:

- Murat Arcaç.
- Justin Yim.
- Kyoungtae Lee.
- Nikhil Shinde.