

EECS192 Lecture 4

Velocity and Line Sensor I

Feb. 11, 2020

Notes:

Check off-

- 2/14: Motor drive/stall, steering servo using LiPo
- Quiz 2: power MOSFET/motor drive Tues 2/18

Topics

- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Driving MOSFETs and motor (conclusion)
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor




Topics

- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor

Motor Electrical Model

 Motor Electrical Model
 Back EMF
 Motor electromechanical behavior




Also- see motor worksheet.....

$$i_m = \frac{V_{BAT} - k_e \dot{\theta}_m}{R_m}$$

Conclusion:
 $\langle i_m \rangle = ?$


Motor Resistance?
 Peak current?

 

Driving MOSFETs and motor

$R_m = 0.1 \text{ ohms}$, $V_{\text{batt}} = 7.2 \text{ V}$, $R_{\text{bat}} = 0$.
 $V_{\text{ds}} = 3.6\text{V} \rightarrow I_{\text{ds}} = (7.2-3.6\text{V})/(0.1 \text{ ohm}) = 36 \text{ amps}$

 - Key design points:
- 1) High V_{gs} better than low V_{gs}
 - 2) Switch quickly
 - 3) Make sure $V_{\text{s}}=0$ (big ground)




Topics




- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor

Battery Model- 3S

 

Battery Model- 3S

avoid weakly charged cell

 

Topics

- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor



Power supply wiring- BAD!


+11.1V



Voltage regulator




Voltage regulator

 

On board: what does this look like electrically (as a schematic)? 9

Power supply wiring- Star is better!

+11.1V

 

Voltage regulator

Voltage regulator

Low power ground

On board: what does this look like electrically (as a schematic)? ₁₀

Topics

- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor



1.4 Voltage and current operating ratings

Table 4. Voltage and current operating ratings

LATCHUP!

Symbol	Description	Min.	Max.	Unit
V_{DD}	Digital supply voltage	-0.3	3.8	V
I_{DD}	Digital supply current		100	mA
V_{IO}	IO pin input voltage	-0.3	$V_{DD} + 0.3$	V

Caution: input voltage from sensor may be greater than 0.3V when CPU is off
 $V_{DD} = 0!$

Latchup phenomena:
make sure V_{in} always less than V_{DD}


 
 



Figure 2. Cross-section of PMOS and NMOS devices, showing parasitic transistors Q1 and Q2.

Protection circuit

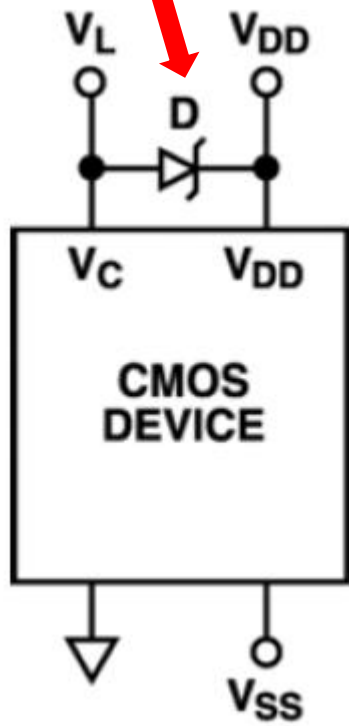

Schottky diode

Protection circuit

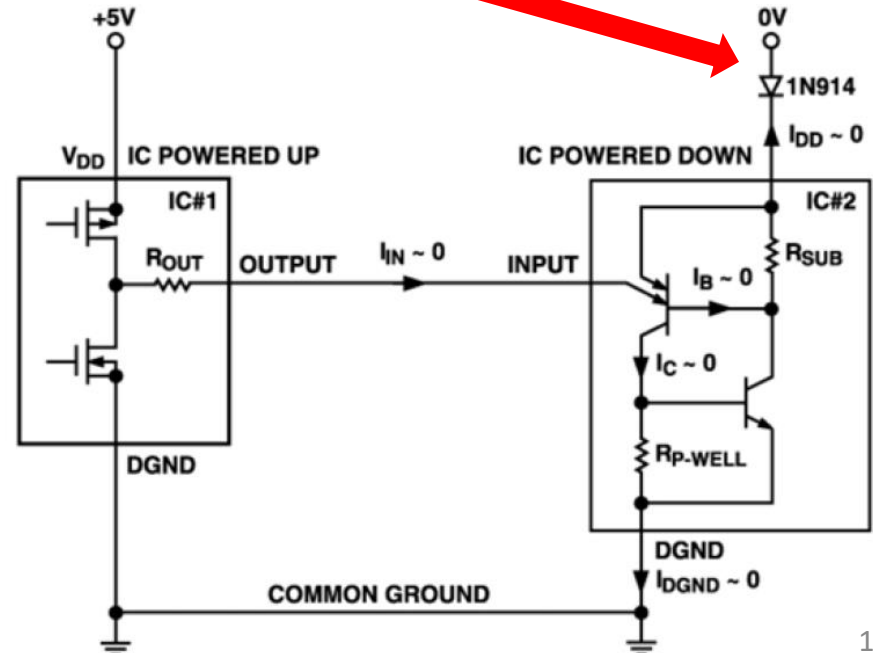


Topics


- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor




Quadrature Encoder

 

3.3 V DC
0 vdc

 

 
<https://www.sinotech.com/wp-content/uploads/quadrature-encoder.gif>



Fab suggestion: aluminum foil covered with black paper with slots. 4 slots probably enough. Note: sensors can be placed where convenient-don't need to look at same slot.

Beagle Bone Blue Quad Encoder

 

```
int rc_encoder_read (int ch)
```

Returns

The current position (signed 32-bit integer)
or -1 and prints an error message if there is a problem.

Ch 1-3 are available

Examples:

rc_test_encoders.c.

Sharp GPS260

Fig.9 Test Circuit for Response Time


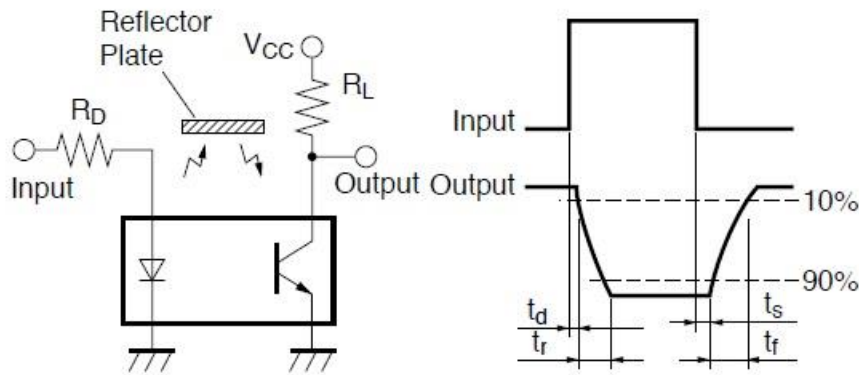


Fig.13 Detecting Position Characteristics (2)

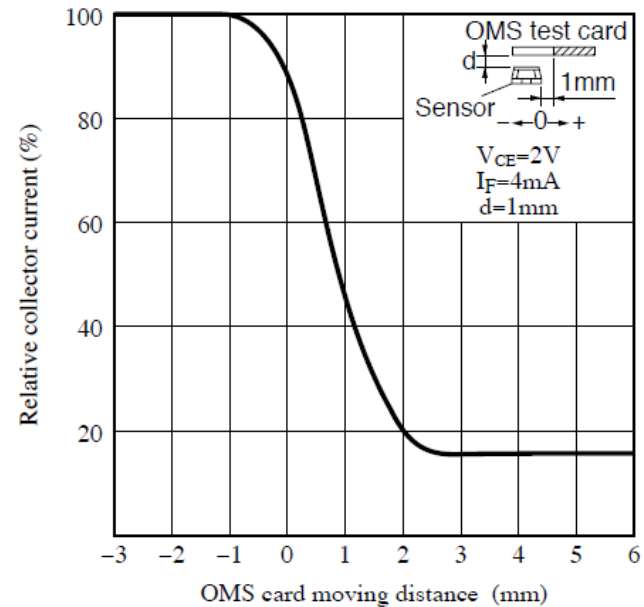


- Choose current 4 mA in LED
- $V_{cc} = 3.3 \text{ V}$
- May want regulated/clean voltage for V_{cc}



100 us
response
time

Velocity Sensing

 - On board: estimating $\Delta x/\Delta T$



Note: care about velocity sensing usually at cruise speed (also stopping)


Topics

- Driving MOSFETs and motor (conclusion)
- Battery Model
- Power wiring
- Quiz 1
- Latchup gotcha
- Speed sensing
- Line sensor



Example Line camera data

natcar2016_team1.csv

 


Start line

Steps


crossing

Old style finish line

 

TSL 1401 line sensor

Functional Block Diagram

 

TSL 1401 line sensor

PARAMETER MEASUREMENT INFORMATION

 


Figure 1. Timing Waveforms

 


Figure 2. Operational Waveforms


Possible algorithms for line detection

e.g. `scipy.signal.filter`


- Subtraction- to find left and right edge of line (ok if not noisy, somewhat lighting invariant)
- Difference of gaussians (idea is to smooth then differentiate)
- Correlation (best match position for known features)
 - `scipy.signal.correlate`

TSL 1401 line sensor NATCAR 8 bit


Frame 0

 


Frame 1

 


Frame 1-Frame 0

 


Frame 0

 


Frame 2

 

Frame 2-Frame 0

 

 
<type 'file'>
inner step cir1800-2300.csv



Programmable Real-time Unit (PRU)

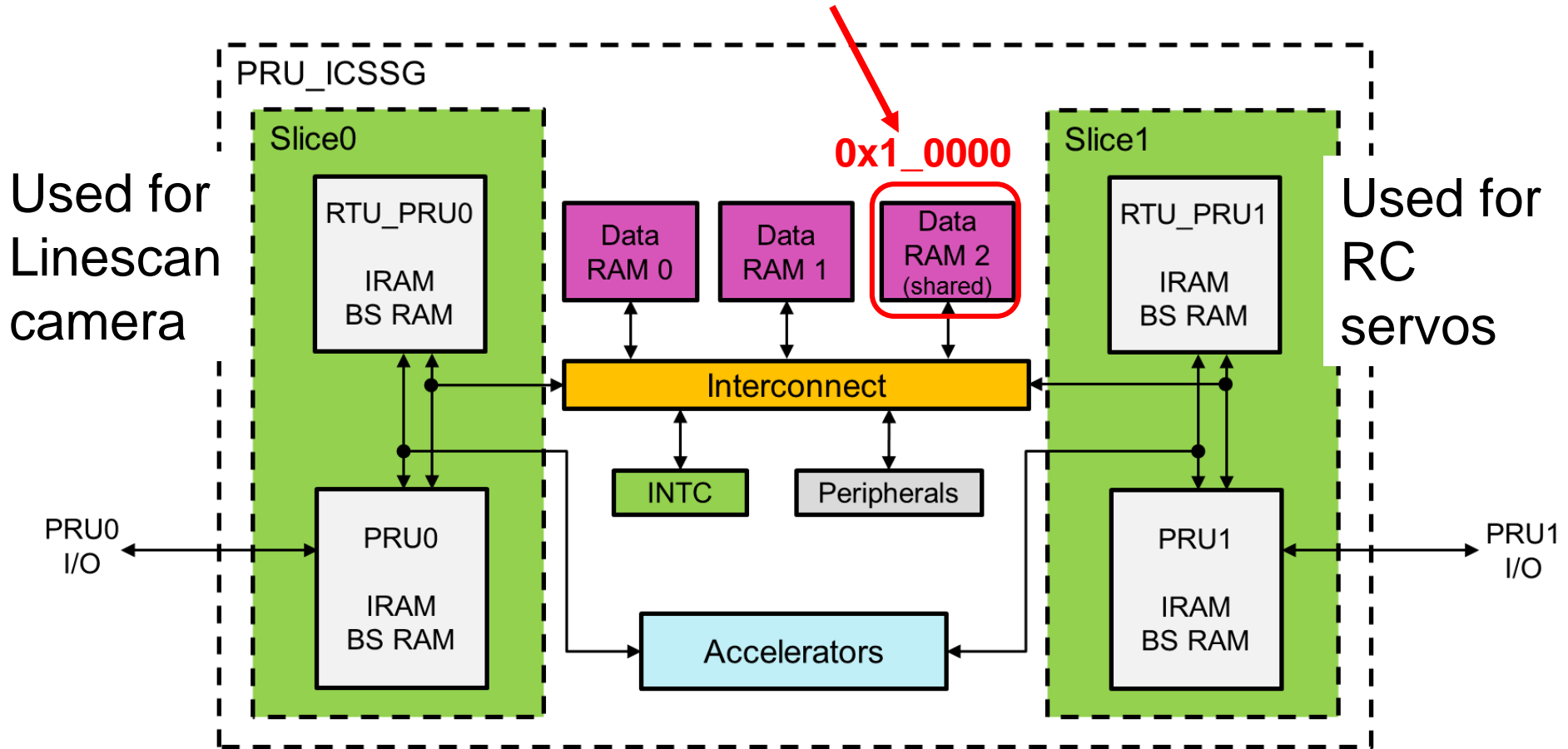Shared RAM used for communication with Linux process



Used on BeagleBone Blue

PRU1: RC servo

PRU0: real-time A/D for line camera (was originally used for quad encoder Ch4)

Shared 12 kb Address Space

PRU0

0x1_0000

For encoder
Flag = 1 to start conversion
Pixel 0
...
Pixel 127

LINUX

```
rc_pru_shared_mem_ptr();  
shared_mem_32bit_ptr[16+1]  
shared_mem_32bit_ptr[16+2]  
...  
shared_mem_32bit_ptr[16+2+127]
```

Linux LineCamera.c line 116:


```
shared_mem_32bit_ptr[ENCODER_MEM_OFFSET+1] = 1;  
// set flag to start conversion by PRU  
while(shared_mem_32bit_ptr[ENCODER_MEM_OFFSET+1] == 1);
```

PRU main_pru0.c line 117:

```
while(shared_mem_32bit_ptr[ENCODER_MEM_OFFSET+1] == 0);  
// loop until command  
//... read 128 pixels ...  
shared_mem_32bit_ptr[ENCODER_MEM_OFFSET+1] = 0;  
// reset to zero
```

Extra Slides

Velocity control overview

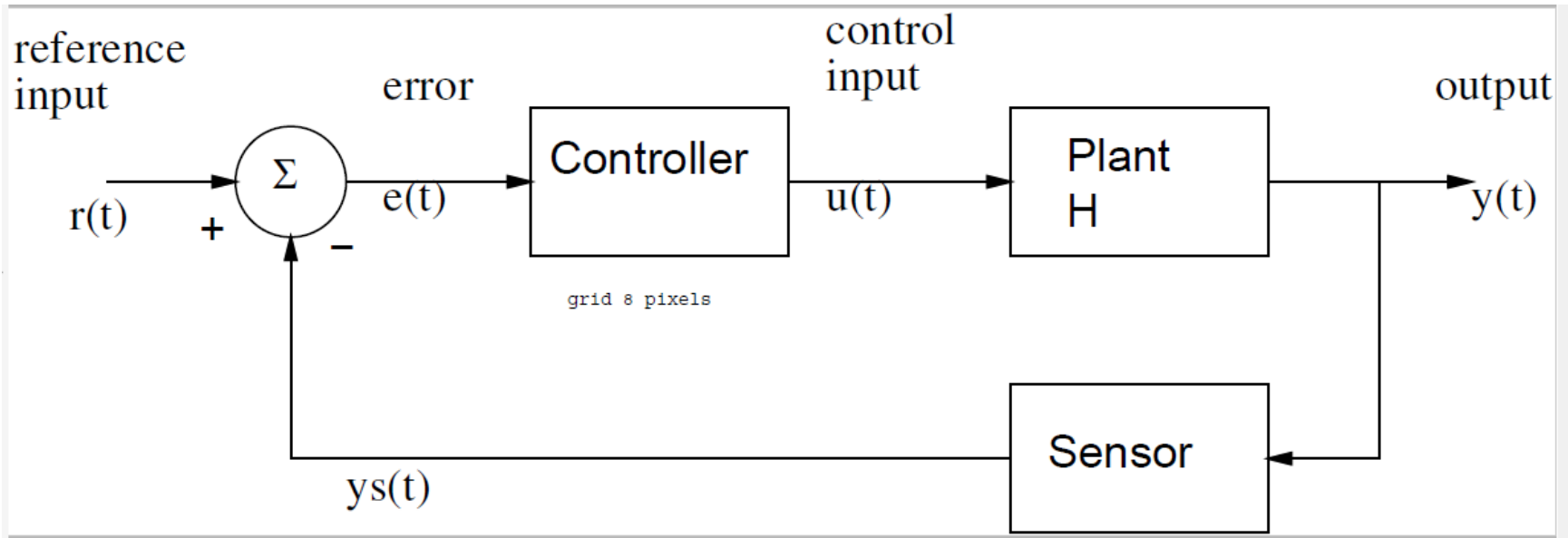

On board...

Proportional control:

$$U = k_p * e = k_p * (r - y);$$


Here: r is desired velocity, U is PWM %

Proportional + integral control

$$U = k_p * e + k_i * e_sum;$$

$$e_sum = e_sum + e;$$

Velocity sensing

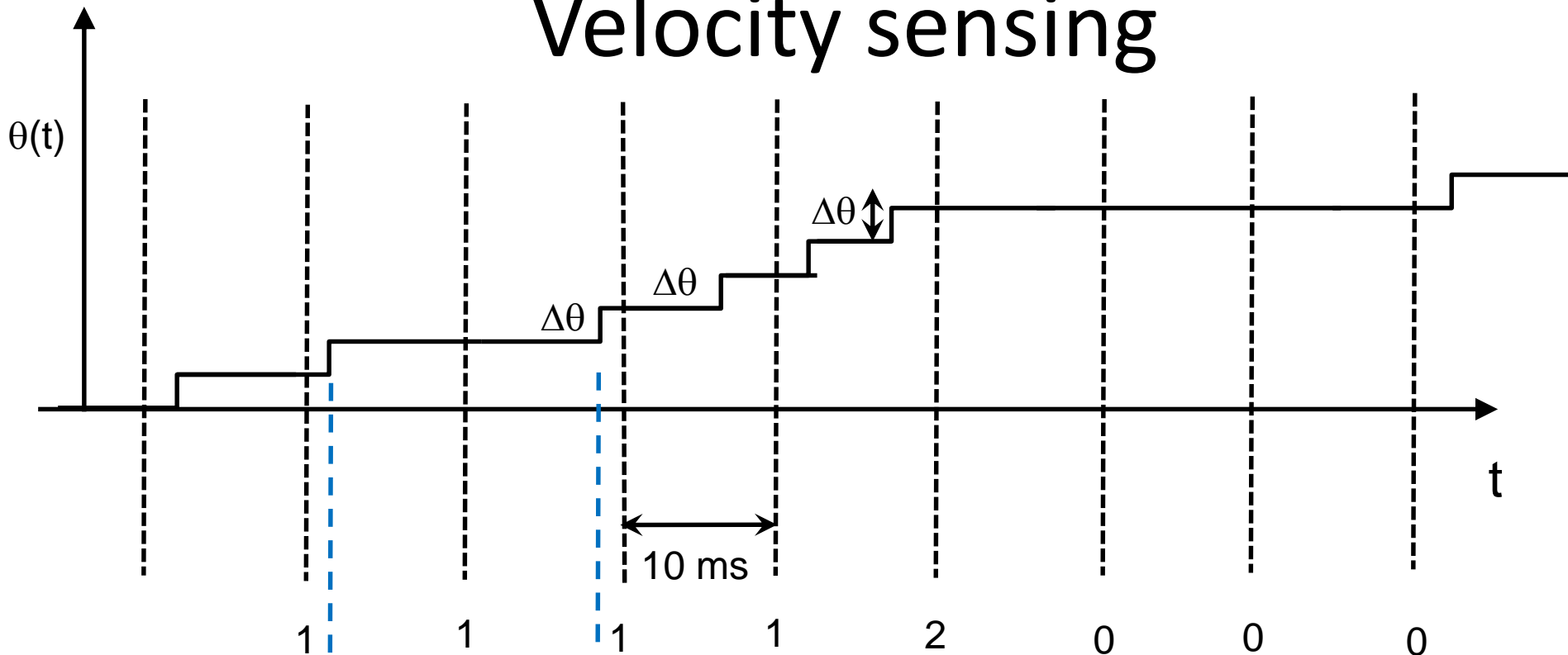

$$V_{\text{uniform}} = \frac{N\Delta\theta}{10 \text{ ms}}$$

Uniform
sampling


$$V_{\text{edge}} = \frac{\Delta\theta}{\Delta T_1}$$

Edge
timing


Velocity sensing (recap)

$V \sim (\text{change in angle}) / (\text{change in time})$

On board...

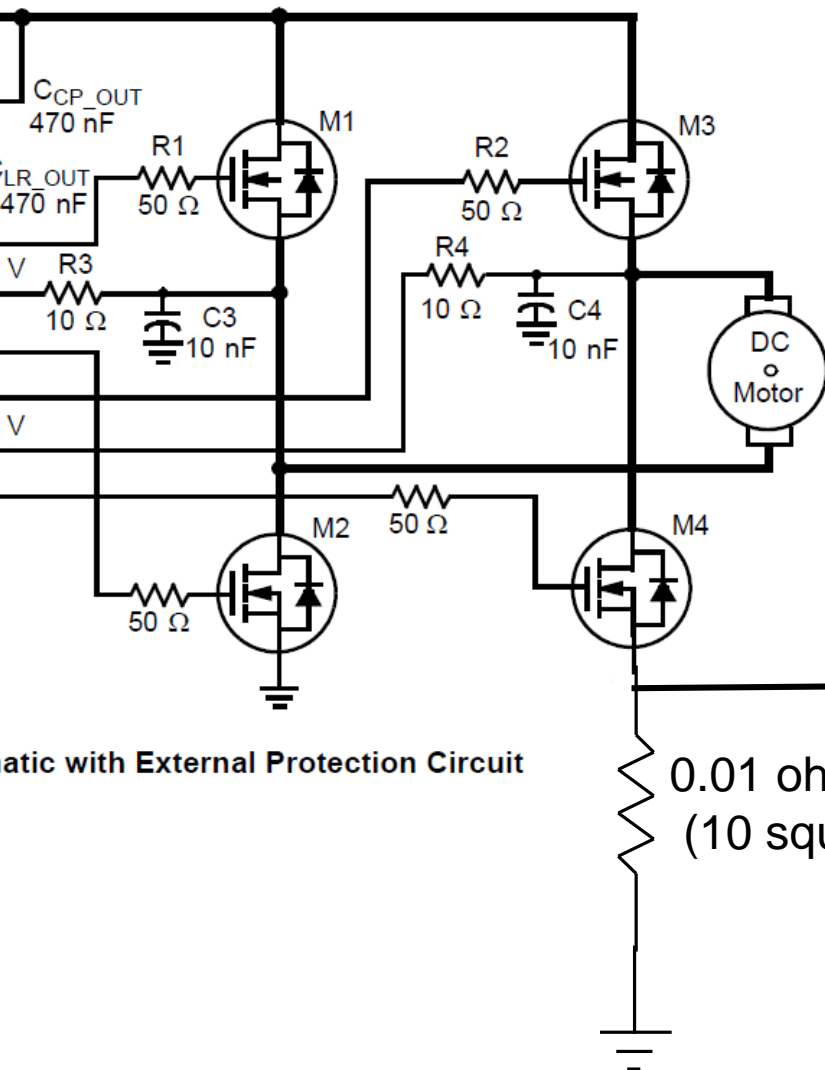

 Non-inverting amp to measure motor current.
 Back EMF can be estimated from battery voltage and motor resistance.




Cu Weight oz.	Thickness mm(mils)	mΩ/Square 25°C	mΩ/Square 100°C
1/2	.02 (0.7)	1.0	1.3
1	.04 (1.4)	0.5	0.65

Back EMF velocity sensing

Analog/Digital Overview

Figure 12-2. Functional Block Diagram

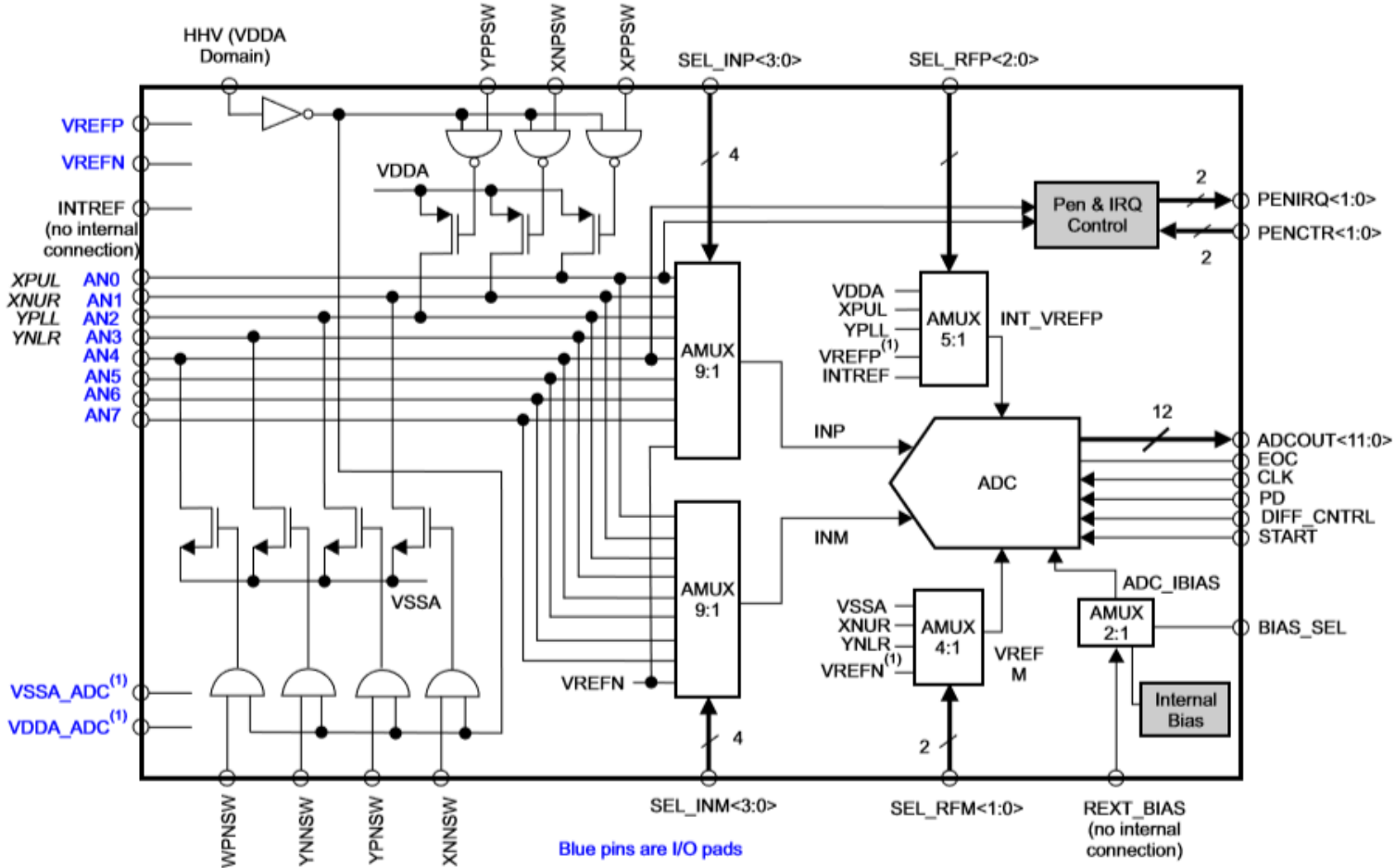

(1) In the device-specific datasheet:


- VDDA_ADC and VSSA_ADC are referred to as "Internal References"
- VREFP and VREFN are referred to as "External References"

Caution: 1.8V MAXIMUM


Note: lots of sequencing/delays.

Set up in PRU0 to read 128 elements at ~8 us/sample.

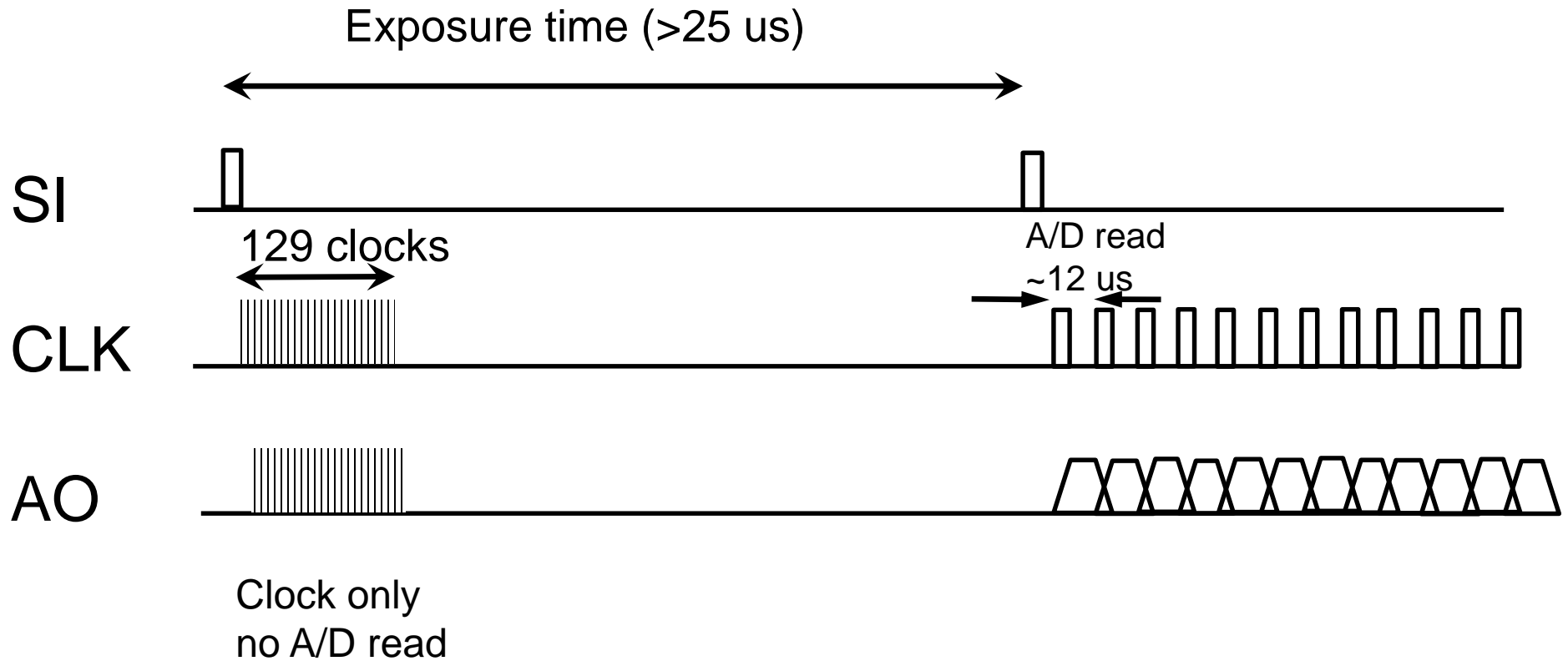TSL 1401 line sensor- option exposure control (would need to modify PRU code)



Automatic Gain Control

 

In all the discussion that follows, we will be using one-shot imaging.

